

Assignment 1
Solution

Q1

a) $i = \frac{dq}{dt}$

$$\frac{d}{dt} (5t \sin 4\pi t)$$

$$= 5 \sin 4\pi t + 20\pi t \cos 4\pi t \text{ mA}$$

→ At $t = 0.5$

$$i = 5 \sin 2\pi + 10\pi \cos 2\pi$$

$$= 0 + 10\pi$$

$$i = 31.42 \text{ mA}$$

b)

$$Q_1 = \int_0^1 2 dt = [2t]_0^1$$

$$= 2 - 0 = \underline{2}$$

$$Q_2 = \int_1^2 2t^2 dt = \left[\frac{2t^3}{3} \right]_1^2$$

$$Q_2 = \frac{16}{3} - \frac{2}{3} = \underline{\underline{\frac{14}{3}}}$$

$$Q_{\text{Total}} = Q_1 + Q_2$$

$$= 2 + \frac{14}{3} = \underline{\underline{6.667 \text{ C}}}$$

c)

$$Q = \int_1^2 i dt = \int_1^2 (3t^2 - t) dt$$

$$= \left[t^3 - \frac{t^2}{2} \right]_1^2 = (8 - 2) - \left(1 - \frac{1}{2}\right) = \underline{\underline{5.5 \text{ C}}}$$

(1d)

Total charge

$$\Delta q = i \Delta t = 2 \times 10 = \underline{20C}$$

Voltage drop:

$$V = \frac{\Delta w}{\Delta q} = \frac{2.3 \times 10^3}{20} = \boxed{115V}$$

(1e)

(i)

$$\frac{-30}{2} = \boxed{-15V}$$

(ii)

$$\frac{-30}{-6} = \boxed{5V}$$

(1f)

(i)

$$v = 3i = 15 \cos 60\pi t$$

$$P = vi$$

$$= 75 \cos^2 60\pi t \text{ W}$$

At $t = 3\text{ms}$.

$$P = 75 \cos^2 (60\pi \times 3 \times 10^{-3}) = 75 \cos^2 0.18\pi$$

$$= \boxed{53.48 \text{ W}}$$

(ii)

$$v = 3 \frac{di}{dt} = 3(-60\pi) 5 \sin 60\pi t$$

$$= -900\pi \sin 60\pi t \text{ V}$$

$$P = vi = -4500\pi \sin 60\pi t \cos 60\pi t \text{ W}$$

At $t = 3\text{ms}$.

$$P = -4500\pi \sin(0.18\pi) \cos(0.18\pi) \text{ W}$$

$$= \boxed{-6.396 \text{ kW}}$$

Q2

$$(a) \quad i = \frac{dq}{dt}$$

$$i = 40\pi \cos 4\pi t \text{ mA}$$

$$P = Vi$$

$$P = 80\pi \cos^2 4\pi t \text{ mW}$$

$$\text{At } t = 0.3 \text{ s.}$$

$$P = 80\pi \cos^2 (4\pi \times 0.3)$$

$$= 164.5 \text{ mW}$$

$$(b) \quad W = \int P dt$$

$$W = 80\pi \int_0^{0.6} \cos^2 4\pi t dt$$

$$= 40\pi \int_0^{0.6} (1 + \cos 8\pi t) dt \text{ mJ}$$

$$W = 40\pi \left[0.6 + \frac{1}{8\pi} \sin 8\pi t \right]_0^{0.6}$$

$$W = 78.34 \text{ mJ}$$

Q3

(a)

$$Q_2 = \int i dt$$

$$Q_2 = \int_0^2 3e^{-2t} dt$$

$$Q_2 = \left[\frac{-3}{2} e^{-2t} \right]_0^2$$

$$= \frac{-3}{2} e^{-4} + \frac{3}{2} \quad \boxed{= 1.473 \text{ C}}$$

(b)

$$P_2 = VI$$

$$V = 5 \frac{di}{dt} \Rightarrow \frac{di}{dt} = -6e^{-2t}$$

$$V = -30e^{-2t}$$

$$P_2 = -30e^{-2t} \times 3e^{-2t}$$

$$\boxed{P = -90e^{-4t} \text{ W}}$$

(c)

$$E = \int P dt$$

$$E = \int_0^3 -90e^{-4t}$$

$$\left[\frac{90}{4} e^{-4t} \right]_0^3$$


$$\frac{90}{4} e^{-12} - \frac{90}{4}$$

$$\boxed{= -22.5 \text{ J}}$$

Aus 4:

$$C = 1 \text{ F} \quad R = 1 \Omega$$

(a)

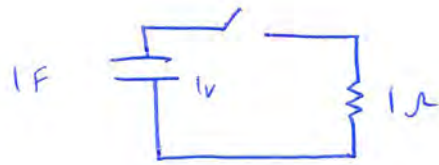

$$i = e^{-t}$$

$$e^{-t} = 0.37$$

$$\boxed{t = 1 \text{ s}}$$

→ we have to find $\frac{dv}{dt}$

$$i = C \frac{dv}{dt}$$

— (1) mark

$$0.37 = 1 \frac{dv}{dt}$$

→ (3) marks

$$\boxed{\frac{dv}{dt} = 0.37}$$

— (2) mark

(b)

$$Q_{\text{initial}} = CV = \boxed{1 \text{ C}}$$

— (1) mark

$$\text{charge flowing out} = \int_0^1 i \, dt$$

$$= \int_0^1 e^{-t} \, dt$$

$$= \boxed{0.632 \text{ C}} \quad \text{— (1) mark}$$

(3) marks

$$\boxed{Q_{\text{left}} = 0.368 \text{ C}}$$

— (1) mark

↔

Aus 5:

$$d_i = 5 \times 10^{-3} \text{ m}$$

$$C_i = 6 \times 10^{-13} \text{ F}$$

$$V = 8$$

$$A = ?$$

$$d_f = 0.2 \times 10^{-3} \text{ m}$$

$$V = 8 \text{ V}$$

$$C_f = ?$$

$$C_i = \frac{\epsilon_0 A}{d_i} \Rightarrow 6 \times 10^{-13} = \frac{8.85 \times 10^{-12} \cdot A}{5 \times 10^{-3}}$$

$$\therefore \epsilon_0 = 8.85 \times 10^{-12}$$

$$A = 3.39 \times 10^{-4} \text{ m} \quad 1$$

$$C_f = \frac{\epsilon_0 A}{d_f} = 1.5 \times 10^{-11} \text{ F} \quad 1$$

2

$$(b) \quad q_i = C_i V = 4.8 \times 10^{-12} \text{ C} \quad 1$$

$$q_f = C_f V = 1.2 \times 10^{-10} \text{ C} \quad 1$$

2

$$\text{change in charge} = 1.152 \times 10^{-10} \text{ C} \quad 1 \quad \leftarrow \text{Charge flowing out.}$$

$$(c) \quad E_i = \frac{1}{2} C_i V^2 = 1.92 \times 10^{-11} \text{ J}$$


$$E_f = \frac{1}{2} C_f V^2 = 4.8 \times 10^{-10} \text{ J} \Rightarrow \text{Energy increased}$$

2

Reason: Energy used to press the key is converted into electrical Energy which is used to send a pulse to computer.



Ans 6:

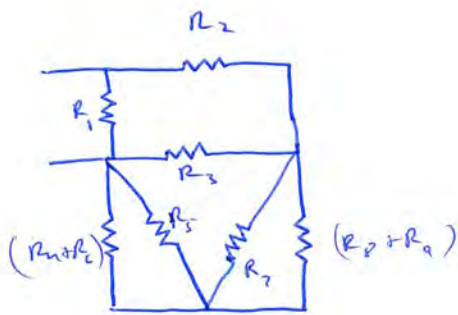


→ R_8 in series with $R_9 = 1100\Omega$

→ R_6 in series with $R_7 = 2k\Omega$

(2)

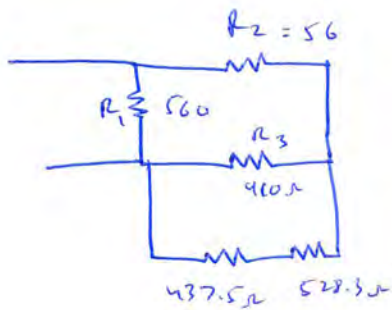(2)

$$\begin{aligned} \rightarrow (R_8 + R_9) // R_7 &= 528.3\Omega \\ \rightarrow (R_6 + R_7) // R_5 &= 437.5\Omega \end{aligned} \left. \vphantom{\begin{aligned} \rightarrow (R_8 + R_9) // R_7 \\ \rightarrow (R_6 + R_7) // R_5 \end{aligned}} \right\} \text{in series}$$



(2)

→ These two resultant are in series & parallel with R_3 . → 468.5Ω




(2)

→ 468.5Ω in series with R_2 & both are parallel to R_1

So $(R_2 + 468.5) // R_1$

Final

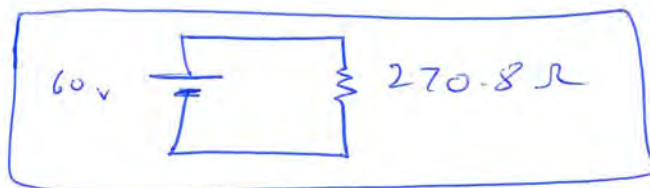


(2)

(→)

Aus 7:


(a)

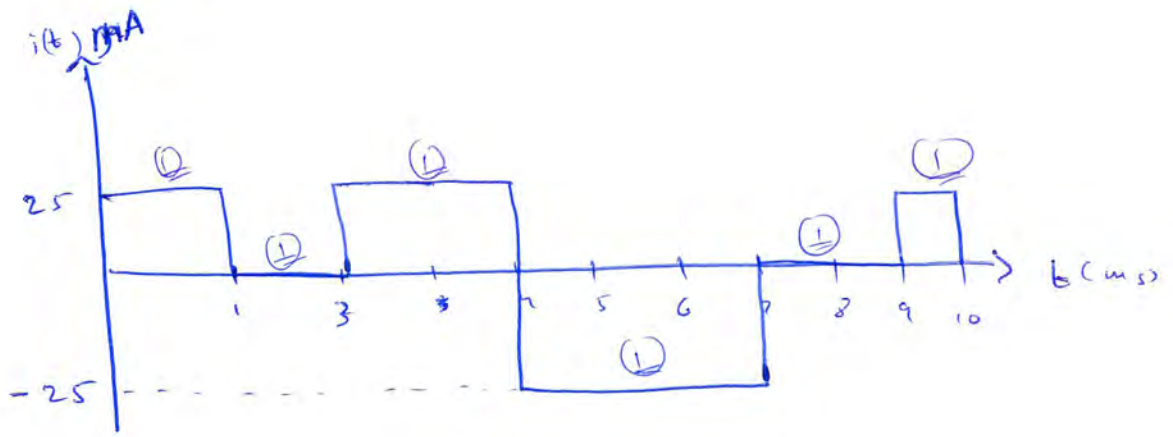

$$p(t) = i(t) v(t) = 25 \times 10^{-6} = 250 \mu\text{W}$$

$$\text{Energy} = 250 \mu\text{J} \quad (2)$$

(b)

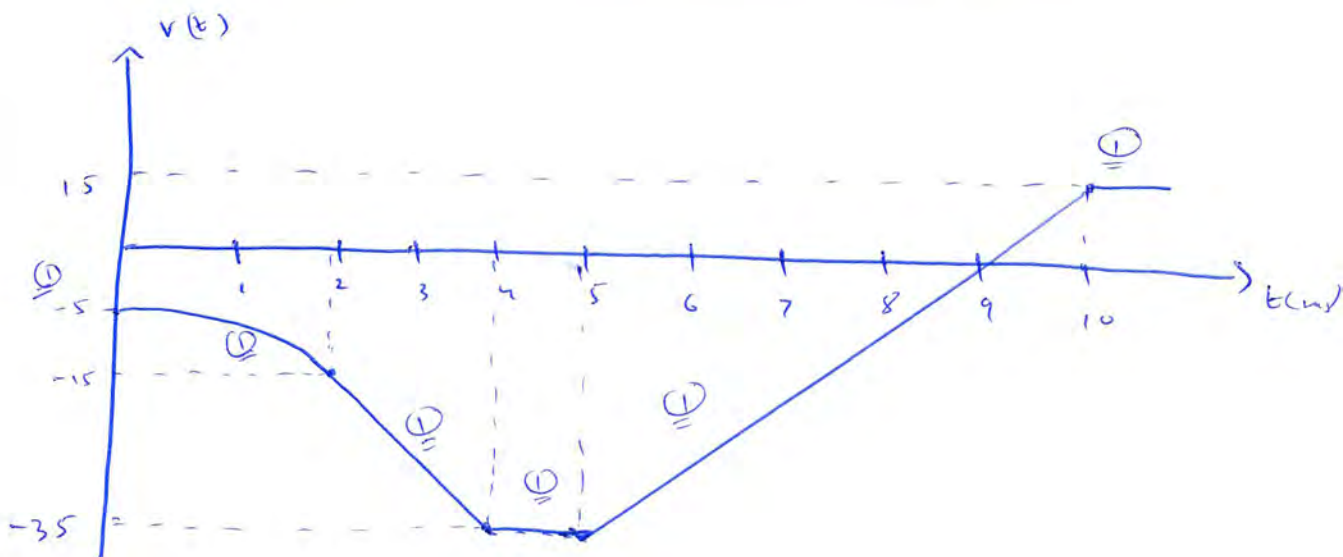

$$\text{Energy} = 312.5 \mu\text{J} \quad (2)$$



$$\textcircled{Q8} \quad Q = \int i \, dt$$

$$\underline{0 - 6 \text{ s.}}$$

$$Q = \frac{3t^2}{2}$$

$$Q = \left[\frac{3t^2}{2} \right]_0^6$$

$$\underline{Q = 54 \text{ C.}}$$

$$\underline{6 - 10 \text{ s.}}$$

$$Q = [18t]_6^{10}$$

$$Q = 180 - 108$$

$$= 72$$

$$\text{Total } Q \text{ at } 10 \text{ s} = 54 + 72 = \underline{126 \text{ C.}}$$

$$\underline{10 - 15 \text{ s.}}$$

$$Q = [-12t]_{10}^{15}$$

$$= -180 + 120$$


$$= -60$$

$$\text{Total } Q \text{ at } 15 \text{ s} = 126 - 60 = 66$$

$$\underline{t > 15 \text{ s.}}$$

$$\text{Final Answer} \\ = 66$$

Graph for Q8

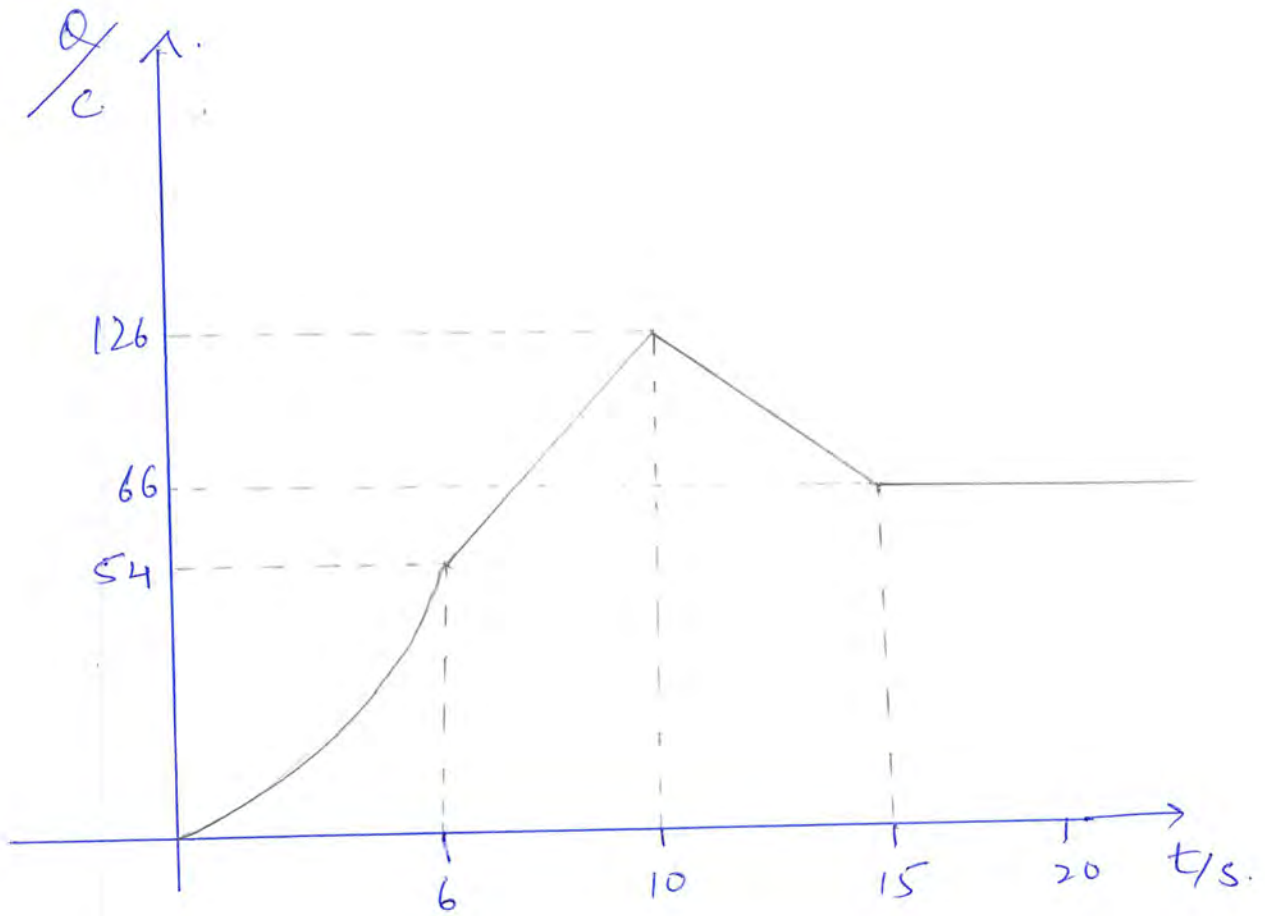

Ans 9:

$$v(t) = \begin{cases} (1-3t)e^{-3t} \text{ mV} & ; t \geq 0 \\ 0 & ; t < 0 \end{cases}$$

(a) $V = L \frac{di}{dt}$ (1)

$$i = \frac{1}{L} \int_0^t v \, dt = 5 \int_0^t (1-3t)e^{-3t} \, dt$$

$$i = 5 \left[\int_0^t e^{-3t} \, dt - 3 \int_0^t t e^{-3t} \, dt \right]$$

(2) ↓ integration by parts

$$i = 5 \left[\left. \frac{e^{-3t}}{-3} \right|_0^t - 3 \left. \frac{-e^{-3t}(3t+1)}{9} \right|_0^t \right]$$


$$i = 5 \left[\frac{-e^{-3t}}{3} + \frac{t}{3} + \frac{e^{-3t}(3t+1)}{3} - \frac{t}{3} \right]$$

$$i = 5 \left[\frac{e^{-3t}(3t+1)}{3} \right]$$

$$i(t) = \begin{cases} 5t e^{-3t} \text{ mA} & ; t \geq 0 \\ 0 & ; t < 0 \end{cases}$$

(2)




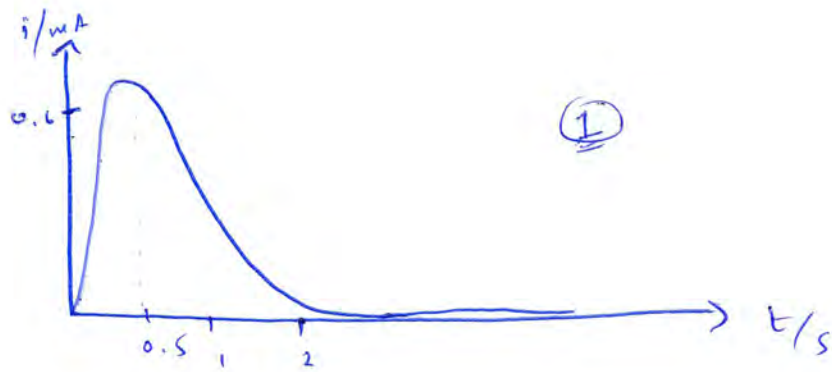

(b) $p(t) = v(t) i(t)$

$$p(t) = \begin{cases} 5t(1-3t)e^{-6t} \mu\text{W} & ; t \geq 0 \\ 0 & ; t < 0 \end{cases}$$


②

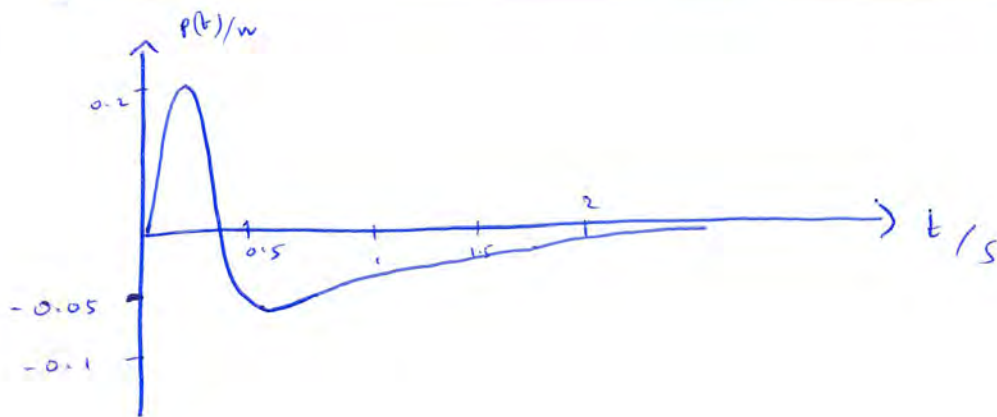

(c) $w(t) = \frac{1}{2} L i(t)^2$

$$w(t) = \begin{cases} 2.5t^2e^{-6t} \mu\text{J} & ; t \geq 0 \\ 0 & ; t < 0 \end{cases}$$

②

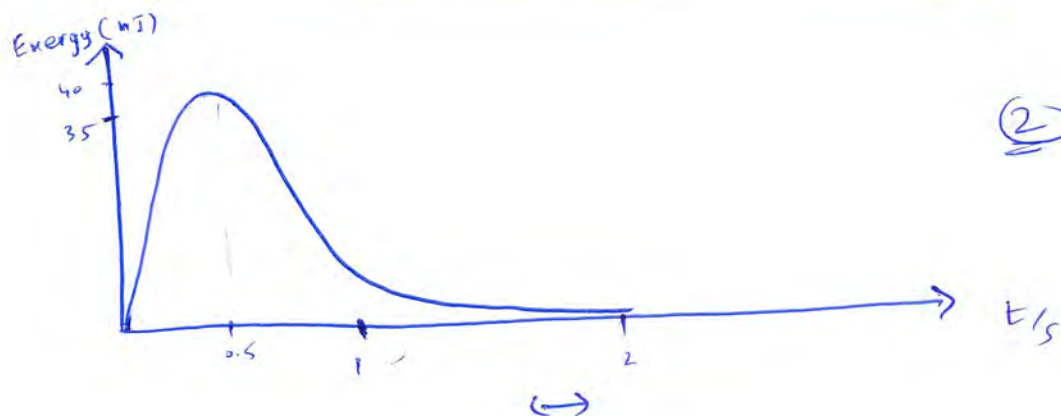

Ans 10:

$$L = 50 \times 10^{-3} \text{ H}$$

$$i(t) = \begin{cases} 0 & ; t < 0 \\ 2te^{-4t} & ; t > 0 \end{cases}$$

(a) $V = L \frac{di}{dt}$ ①

$$V = L [e^{-4t}(2-8t)]$$
 ①

$$\boxed{V(t) = 50 \times 10^{-3} (2-8t)e^{-4t}}$$
 ①

(b) $\frac{di(t)}{dt} = (2-8t)e^{-4t} = 0$ ②

① $\boxed{t = \frac{1}{4} \text{ s}}$ ①

(c) $\frac{dV(t)}{dt} = 0$

① $5 \times 10^{-2} [16e^{-4t}(2t-1)] = 0$ ②

$$2t-1 = 0$$

$$\boxed{t = \frac{1}{2} \text{ s}}$$
 ①

