

Fall 2018: EE-240 Circuits I
Assignment # 02
Due Date: 16 October 2018, Tuesday


Please read the following instructions:

- Submit the assignment on A-4 sheets bound together. Please note that assignments submitted from torn notebook pages will not be accepted.
- You are required to submit the assignment at the start of class on the due date. Late submissions will not be accepted.
- Please ensure that you have clearly written your name and roll numbers on the assignment.
- The assignment is long, so you are advised to start as soon as possible. Please note that no deadline extension requests will be entertained.
- You are aware of the LUMS honor code and therefore, any plagiarism attempts will be directly reported to the **Disciplinary Committee**. If you are facing any difficulties or have questions, ask the course staff (Instructor/TA), they are there to help you.

The total marks for the assignment are **100**.


Q1: Find V_o indicated in the circuit below using source transformation.

[10]

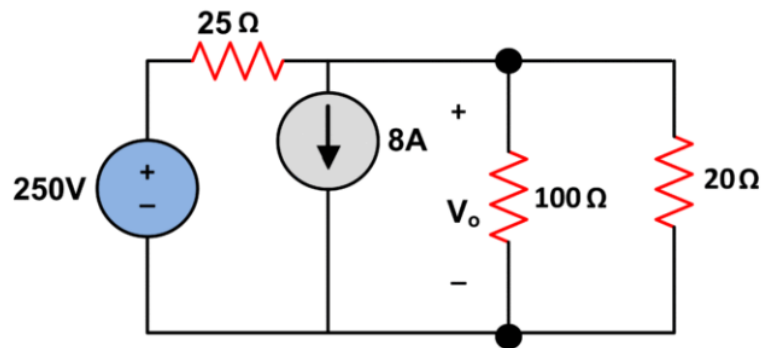

Q2: Use superposition principle to find i_o and v_o in the circuit given below.

[10]

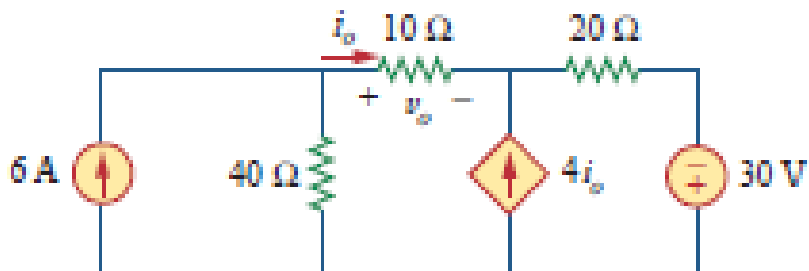

Q3: Two inductors with inductance L_1 and L_2 are connected in series in a circuit and are mutually coupled. Find the expression of combined voltage across both inductors and the equivalent inductance if:


- a) Both inductors have the dot on the same side [5]
- b) Both inductors have the dot on the opposite side [5]

(Drawing the separate diagrams and then applying analysis may help).


Q4: The figure below shows four windings on a magnetic flux-conducting core. Using different shapes, establish polarity markings for the windings.

Note: Do give the key (for each shape along with the coil number) to get marks!

[10]

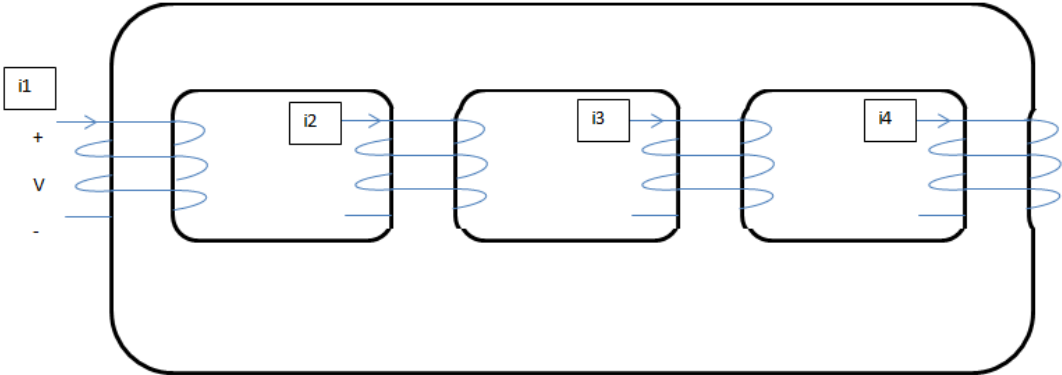


Q5: Consider the circuit given below.

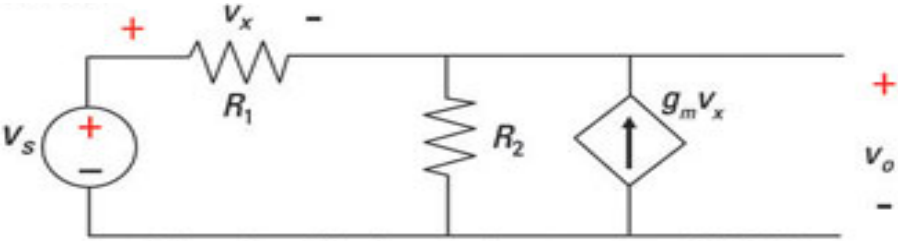

- a) Which of the two sources above can be simplified using source transformation? [2]
- b) Apply the source transformation to simplify the circuit. [3]


Q6: Calculate V_o for the circuit given below.

[10]

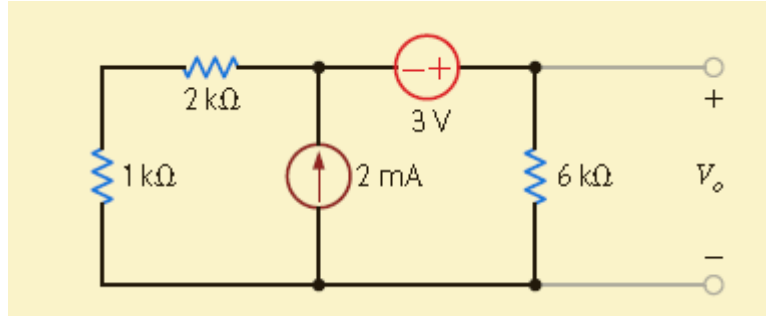


Q7: For the circuit given below, write the loop equations for I_1 and I_2 .


[10]

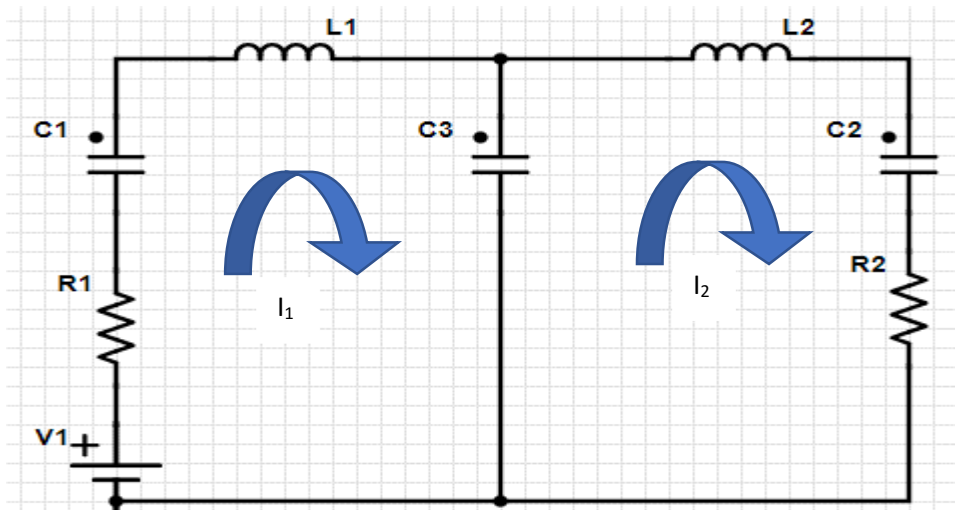

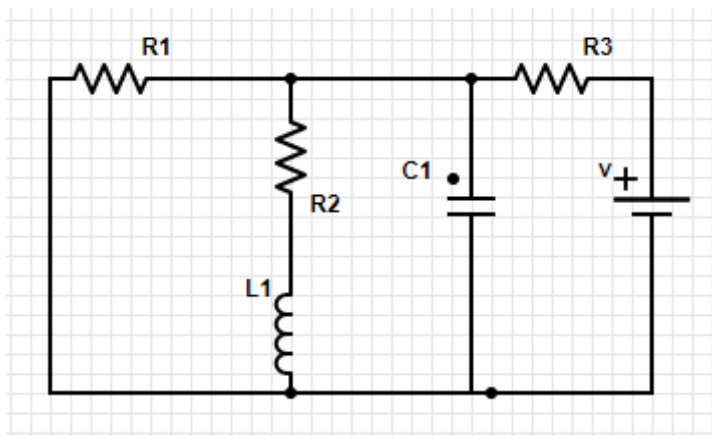
Q8: For the circuit given below, identify the number of nodes and write the set of nodal equations. [10]



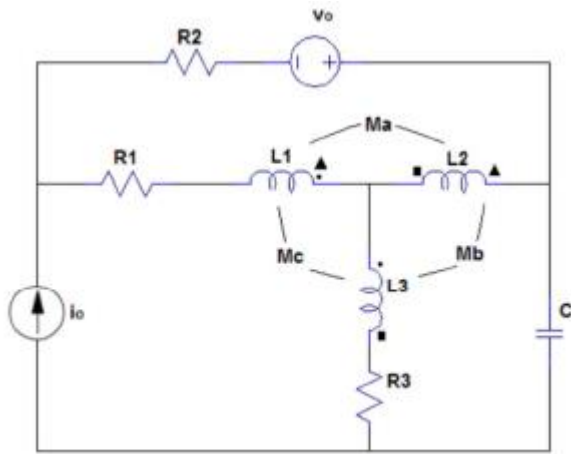Q9: Write independent KVL equations for the circuit given below (choose appropriate loops and loop current variables yourself). [15]



Q10: Consider the circuit given below.

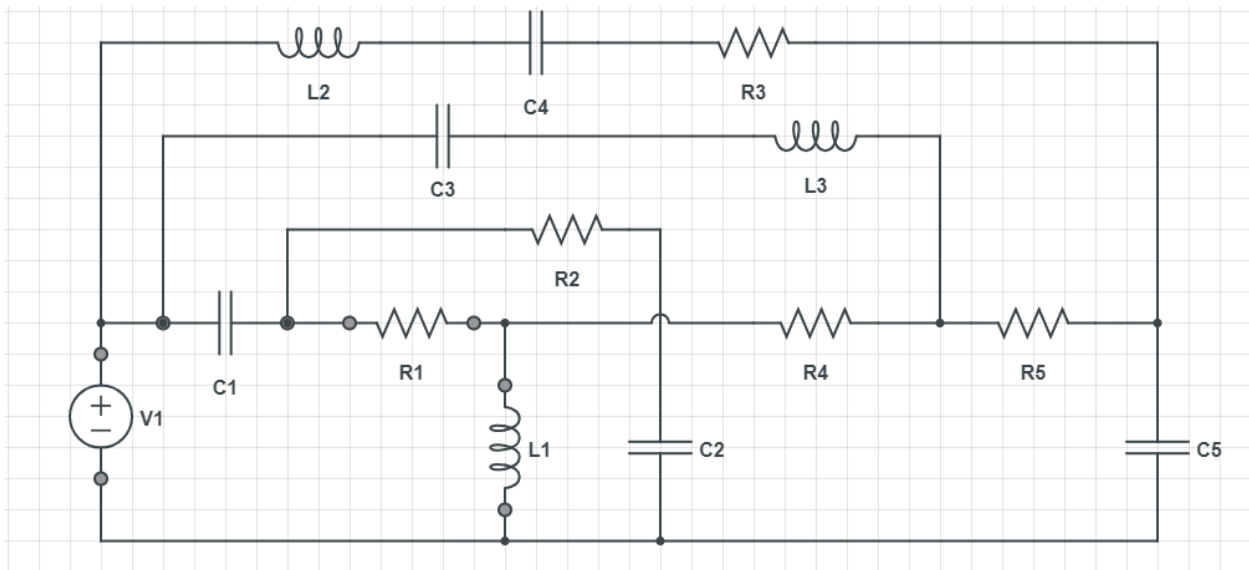

- Identify the number of nodes and mark them on the circuit [1]
- Identify the number of equations that will be obtained in performing Nodal analysis [1]
- Identify the number of equations that will be obtained in performing Loop analysis [1]
- Draw the graph [5]
- Draw a tree [2]