
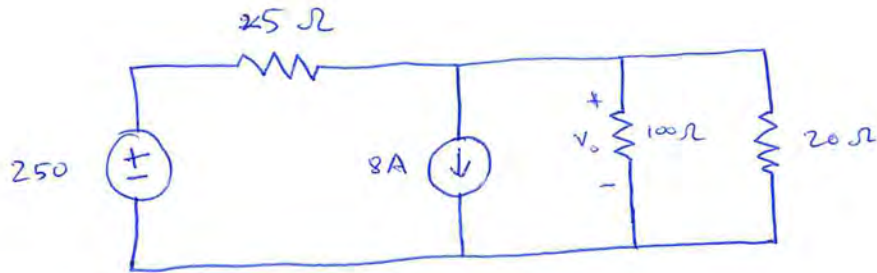


Assignment #2 solutionAns 1:


Convert  
voltage to  
current source
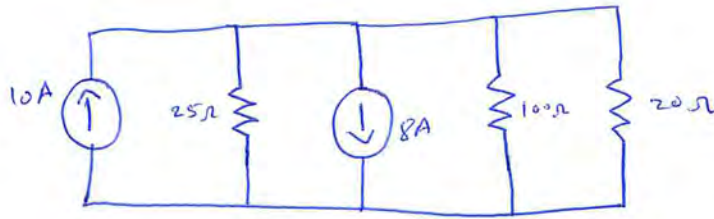
$$i = \frac{V}{R} = \frac{250}{25} = 10$$




→ Fake resultant of parallel current sources.

$$10 - 8 = 2A$$

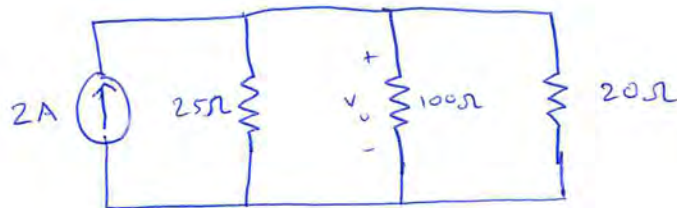

$$100 // 20 // 25 = 10\Omega$$

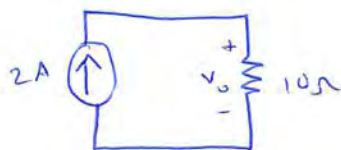

$$V_o = IR$$

$$V_o = 20V$$




Q2

Let  $V_0 = V_1 + V_2$ .

$V_1 \Rightarrow$  due to 6A source.

$V_2$  due to 80A source.

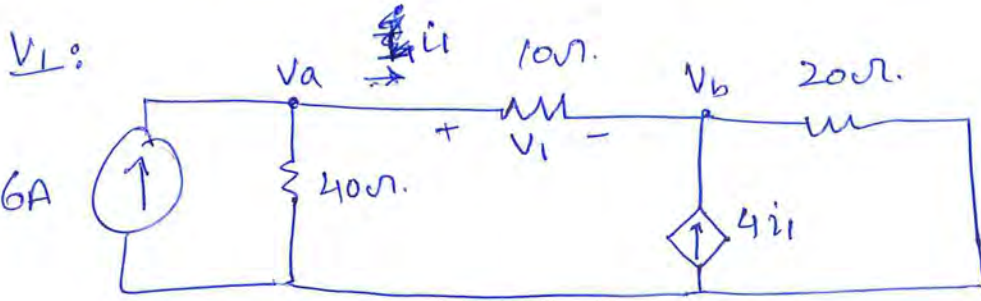

Node a :

$$6 = \frac{V_a}{40} + \frac{V_a - V_b}{10}$$

$$240 = 5V_a - 4V_b \quad \text{--- (1)}$$

Node b

$$-i_1 + 4i_1 + \frac{(V_b - 0)}{20} = 0$$

$$V_b = 100i_1$$

$$i_1 = \frac{V_a - V_b}{10}$$


$$V_b = 10(V_a - V_b) \Rightarrow V_b = 0.9091V_a \quad \text{--- (2)}$$

Substituting (2) into (1)

$$V_a = 175.95 \quad \text{and} \quad V_b = 159.96$$

$$V_1 = V_a - V_b = 15.99V$$

③ Now considering voltage source only:

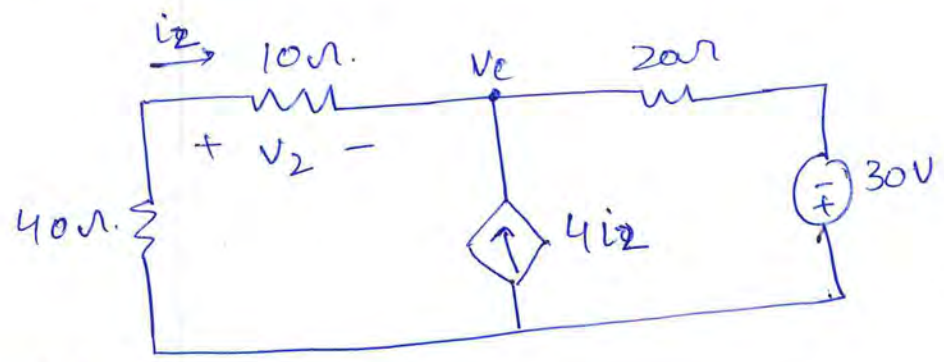

Nodal

$$4i_2 = \frac{V_c}{50} + \frac{V_c + 30}{20}$$

$$i_2 = \frac{0 - V_c}{50}$$

$$-\frac{4V_c}{50} = \frac{V_c}{50} + \frac{V_c + 30}{20}$$

$$V_c = -10V$$

$$i_2 = \frac{0 - V_c}{50} = \frac{0 + 10}{50} = \frac{1}{5}$$

$$V_2 = 10i_2 = 2V$$


$$V_0 = V_1 + V_2 = 15.99 + 2 = \boxed{17.99V}$$

$$I_0 = \frac{V_0}{10} = \boxed{1.799A}$$

Ans 3:

(4)

a)

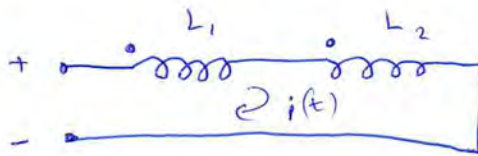


$$V_1 = L_1 \frac{di}{dt} + M \frac{di}{dt}$$

$$V_2 = L_2 \frac{di}{dt} + M \frac{di}{dt}$$

$$V_T = (L_1 + L_2 + 2M) \frac{di}{dt} \Rightarrow \text{hence } L_{eq} = L_1 + L_2 + 2M$$

b)

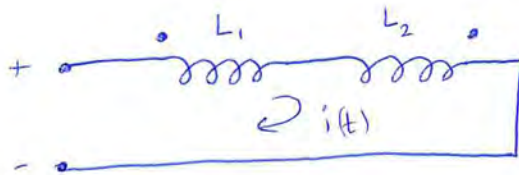


$$V_1 = L_1 \frac{di}{dt} - M \frac{di}{dt}$$

$$V_2 = L_2 \frac{di}{dt} - M \frac{di}{dt}$$

$$V_T = (L_1 + L_2 - 2M) \frac{di}{dt} \Rightarrow \text{hence } L_{eq} = L_1 + L_2 - 2M$$




Q4

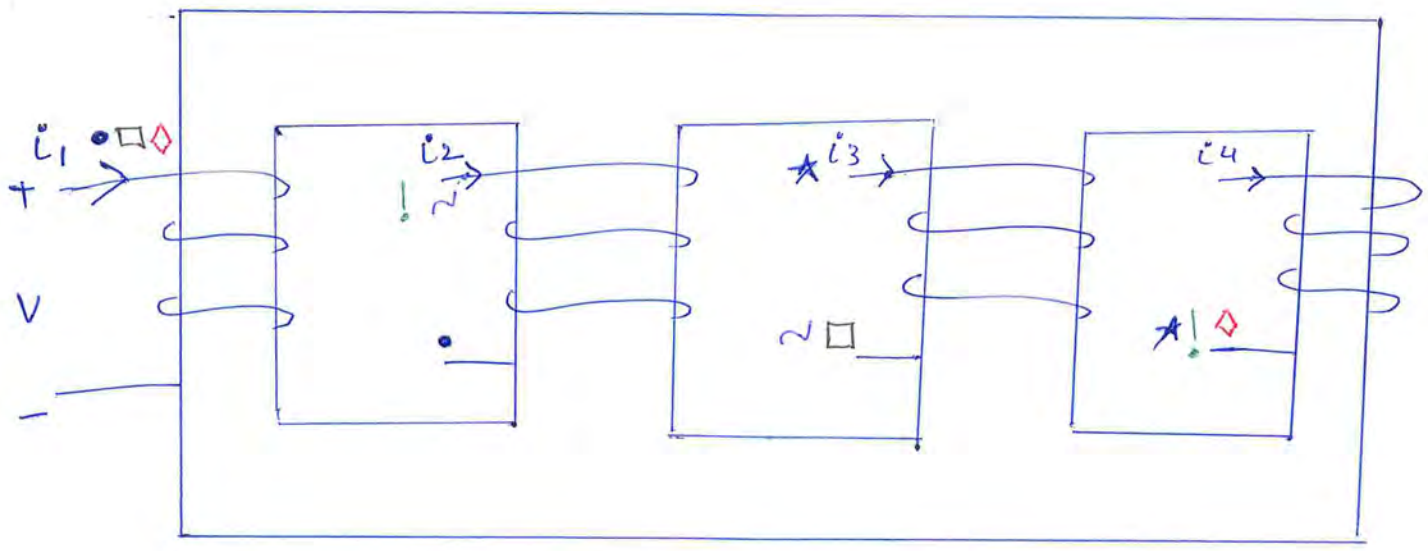

Key


1-2	•
1-3	□
1-4	◇
2-3	~
2-4	!
3-4	*

Ans 5.

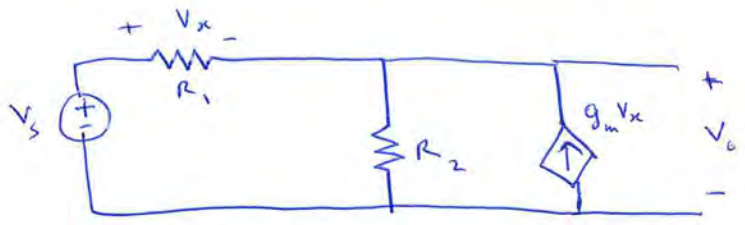

a) Both sources can be simplified


b)

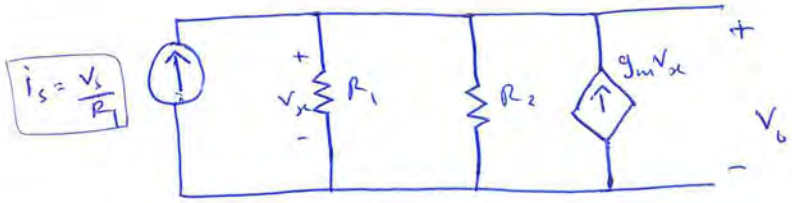


$$R_{eq} = R_1 // R_2$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

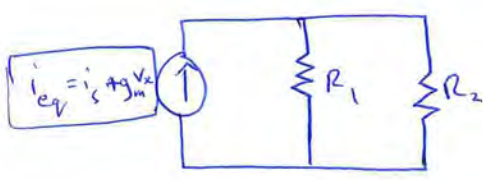→ current sources in parallel so → simplify



→ replace  $R_1$  &  $R_2$  by  $R_{eq}$

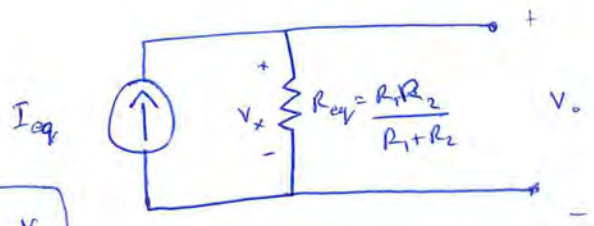


$$I_{eq} = \frac{V_s}{R_1} + g_m V_x$$




7

Ans 6:

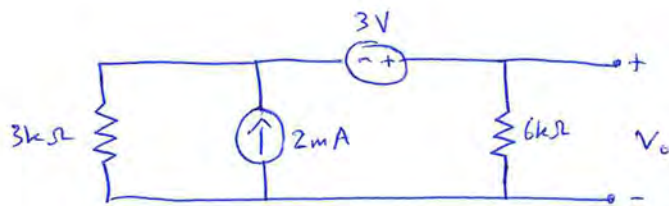

use Superposition Principle

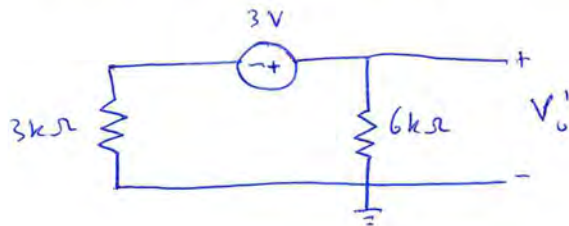→ Use voltage source only & treat current source as open circuit




$V_o'$  → voltage due to voltage source

voltage divided b/w  $3k\Omega$  and  $6k\Omega$ .

$$V_o' = \frac{6k\Omega}{9k\Omega} \times 3$$

$$\boxed{V_o' = 2V}$$

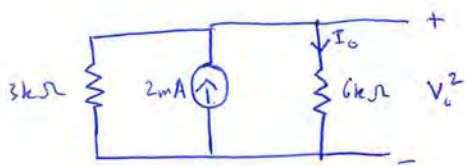→ Now use current source only & treat voltage source as short circuit




$V_o''$  → voltage due to current source

$$I_o = \frac{3k\Omega}{9k\Omega} \times (2 \times 10^{-3}) = \boxed{\frac{2}{3} \text{ mA}}$$

$$V_o'' = \left(\frac{2}{3} \times 10^{-3}\right) \times (6 \times 10^3) = \boxed{4V}$$

$$V_o = V_o' + V_o'' = \boxed{6V}$$

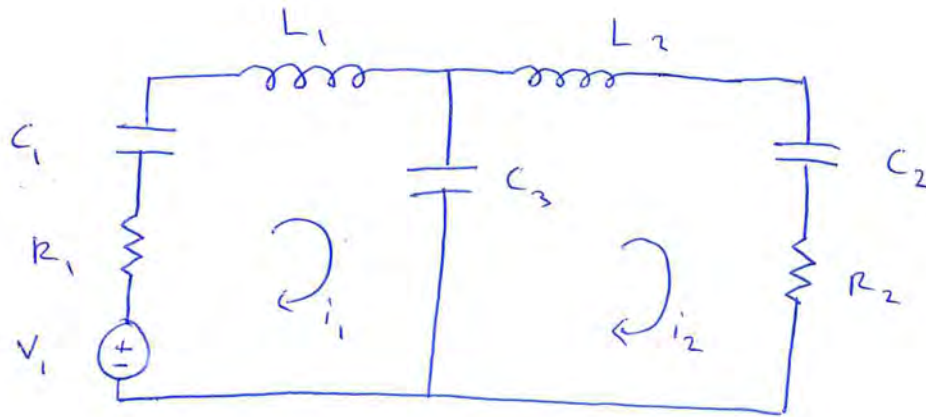

Ans 7:

→ Inductors are not coupled and the only common element is  $C_3$

KVL analysisLoop 1:

$$L_1 \frac{di_1}{dt} + \frac{1}{C_3} \int (i_1 - i_2) dt + i_1 R_1 + \frac{1}{C_1} \int i_1 dt = V_1$$

Loop 2:


$$L_2 \frac{di_2}{dt} + \frac{1}{C_2} \int i_2 dt + i_2 R_2 + \frac{1}{C_3} \int (i_2 - i_1) dt = 0$$





9

Ans 8:

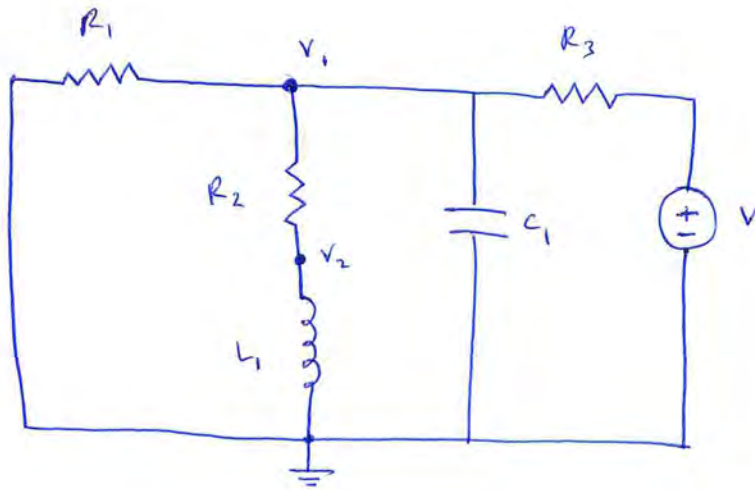

→ 4 nodes, but 1 is at ground & other between R3 & V so its voltage is known.

↳ so unknown voltage nodes = 2

i.e.  $V_1$  and  $V_2$

KCL Analysis

node 1:

$$\frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2} + \frac{V_1 - V_3}{R_3} + C_1 \frac{dV_1}{dt} = 0$$


node 2:

$$\frac{V_2 - V_1}{R_2} + \frac{1}{L_1} \int V_2 dt = 0$$

↔

Q9

10

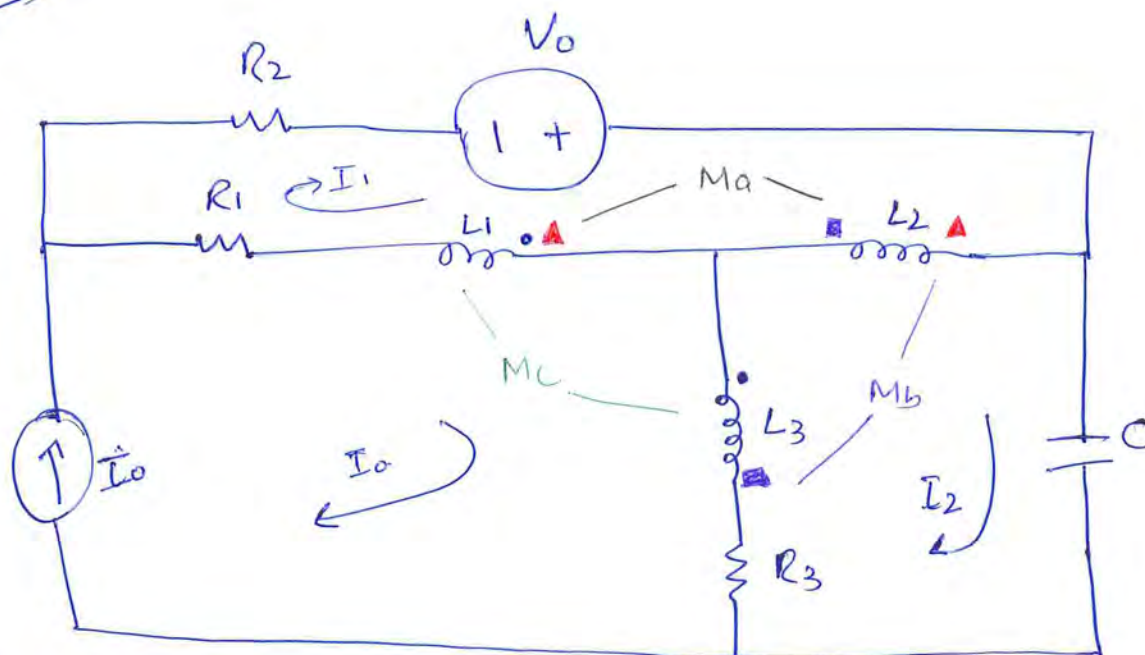Loop I<sub>0</sub>

$$R_1(I_0 - I_1) + L_1 \frac{d}{dt}(I_0 - I_1) + L_3 \frac{d}{dt}(I_0 - I_2) + R_3(I_0 - I_2) - M_c \frac{d}{dt}(I_0 - I_1) + M_c \frac{d}{dt}(I_0 - I_2) + M_a \frac{d}{dt}(I_2 - I_1) - M_b \frac{d}{dt}(I_2 - I_1) = 0$$


Loop 1

$$V_0 = R_2 I_2 + L_2 \frac{d}{dt}(I_1 - I_2) + L_1 \frac{d}{dt}(I_1 - I_0) + R_1(I_1 - I_0) + M_a \frac{d}{dt}(I_1 - I_0) - M_a \frac{d}{dt}(I_2 - I_1) - M_b \frac{d}{dt}(I_2 - I_0) - M_c \frac{d}{dt}(I_2 - I_0)$$

Loop 2

$$0 = \frac{1}{C} \int I_2 dt + R_3(I_2 - I_0) + L_3 \frac{d}{dt}(I_2 - I_0) + L_2 \frac{d}{dt}(I_2 - I_1) + M_b \frac{d}{dt}(I_2 - I_0) + M_b \frac{d}{dt}(I_2 - I_1) + M_c \frac{d}{dt}(I_0 - I_1) + M_a \frac{d}{dt}(I_0 - I_1)$$

10

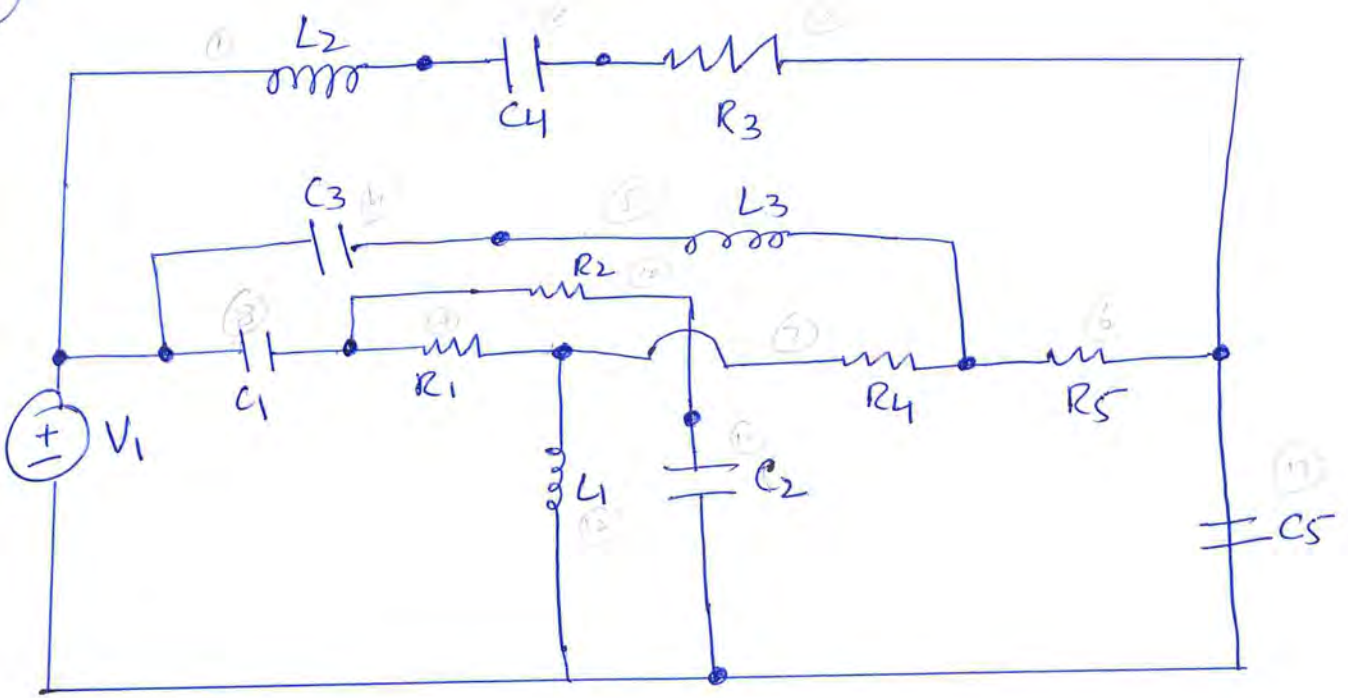

(a) 11 nodes

(b) 9  $(n-1) - 1$   $\rightarrow$  as voltage source is present

(c) 4  $b - (n-1)$   
 $b = 14$