


**Fall 2018: EE-240 Circuits I**  
**Assignment # 04**  
**Due Date: 22 November 2018, Thursday**

**Please read the following instructions:**

- Submit the assignment on A-4 sheets bound together. Please note that assignments submitted from torn notebook pages will not be accepted.
- You are required to submit the assignment at the start of class on the due date. Late submissions will not be accepted.
- Please ensure that you have clearly written your name and roll numbers on the assignment.
- The assignment is long, so you are advised to start as soon as possible. Please note that no deadline extension requests will be entertained.
- You are aware of the LUMS honor code and therefore, any plagiarism attempts will be directly reported to the **Disciplinary Committee**. If you are facing any difficulties or have questions, ask the course staff (Instructor/TA), they are there to help you.


The total marks for the assignment are **100**.

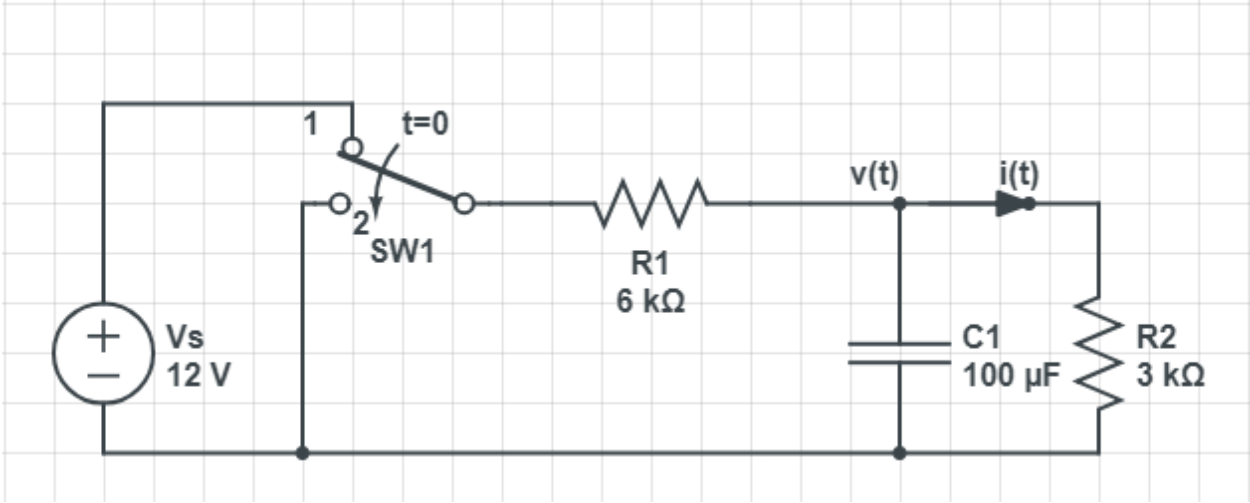Q1: The switch SW1 has been in position 1 for a long time. At  $t=0$ , the switch moves to position 2. Calculate  $i(t)$  for  $t>0$ . [10]




Q2: Switch S1 is closed at  $t=0$ . Find:

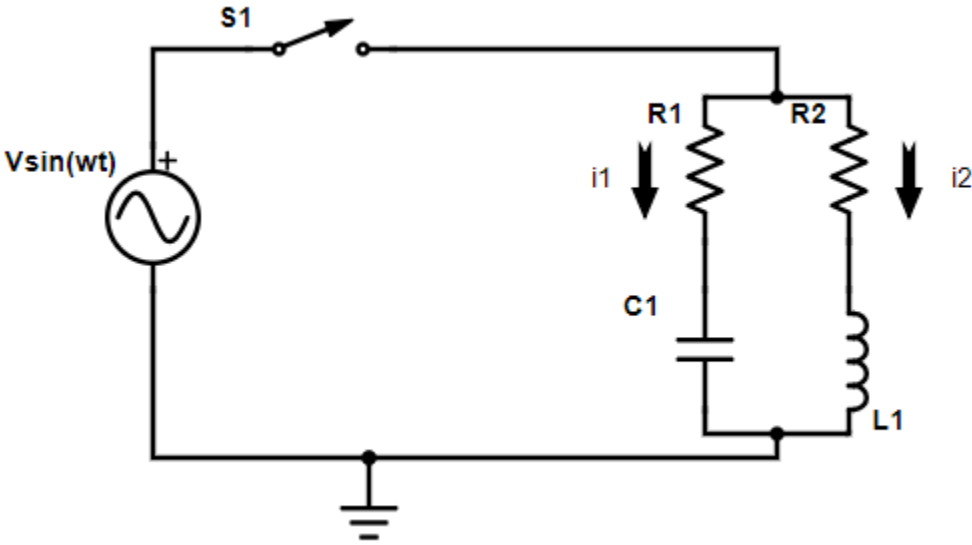
- a)  $di_1/dt$  at  $t=0^+$  [5]
- b)  $di_2/dt$  at  $t=0^+$  [5]



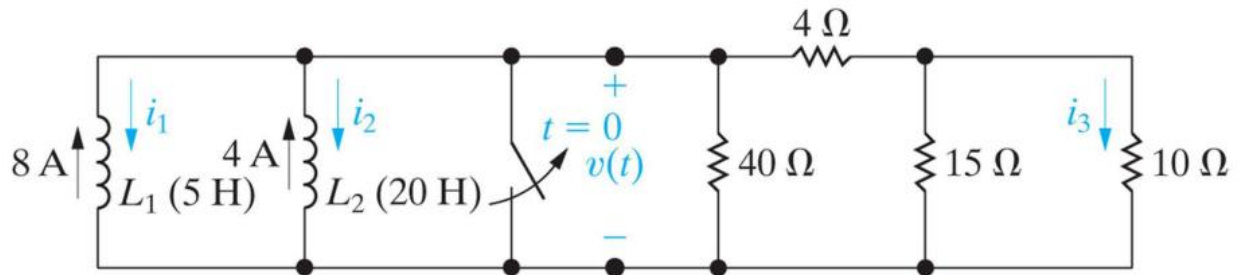
Q3: The switch is closed for  $t < 0$ . The initial currents and their directions through each inductor are shown in the diagram below. At  $t = 0$ , the switch is opened. Calculate  $i_1(t)$ ,  $i_2(t)$  and  $i_3(t)$  for  $t > 0$ . Also describe, both quantitatively and qualitatively, what happens as when  $t \rightarrow \infty$ . [20]



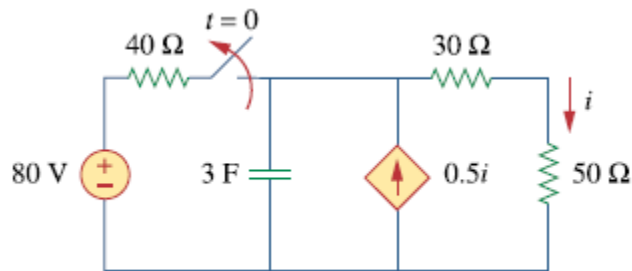Q4: The switch is closed for long time and opened at  $t = 0$ . Find  $i(0^-)$  and  $i(t)$  and for  $t > 0$ . [10]



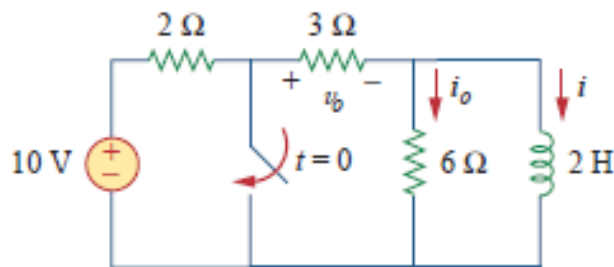
Q5: In the circuit shown below, find  $i_o$ ,  $v_o$  and  $i(t)$  for all time, assuming the switch was open for a long time. Also sketch  $i(t)$  and  $i_o$  on a same graph. [10]



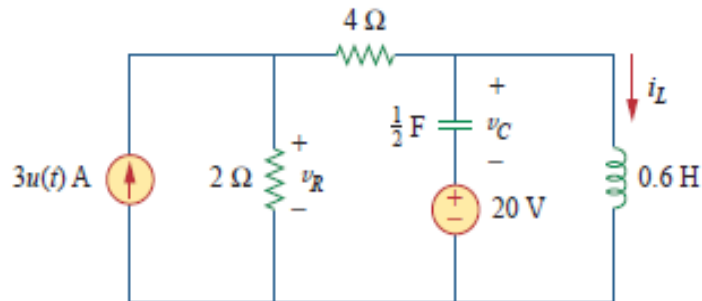Q6: In the circuit given below, calculate:


[15]

- $i_L(0^+)$ ,  $v_C(0^+)$ ,  $v_R(0^+)$
- $di_L(0^+)/dt$ ,  $dv_C(0^+)/dt$ ,  $dv_R(0^+)/dt$
- $i_L(\infty)$ ,  $v_C(\infty)$ ,  $v_R(\infty)$



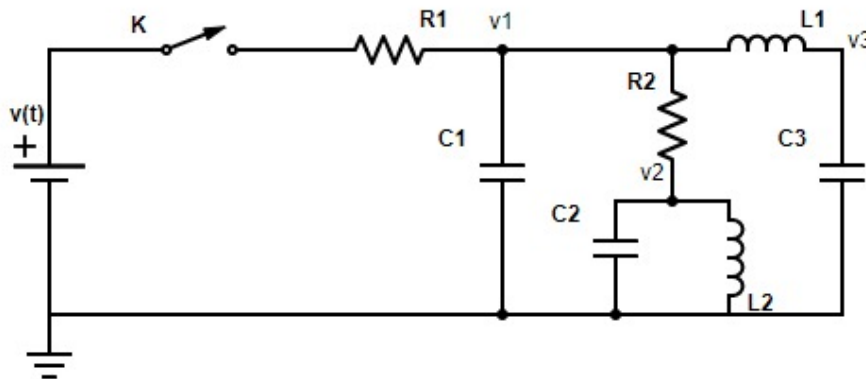Q7: In the network given below, the switch K is closed at  $t = 0$ . At  $t = 0^-$ , all capacitor voltages and inductor currents are zero. Three node-to-datum voltages are identified as  $v_1$ ,  $v_2$  and  $v_3$ . Find:

- $v_1$  and  $dv_1/dt$  at  $t = 0^+$  [5]
- $v_2$  and  $dv_2/dt$  at  $t = 0^+$  [5]
- $v_3$  and  $dv_3/dt$  at  $t = 0^+$  [5]



Q8: The network below reaches a steady state with the switch K open. At  $t = 0$ , switch K is closed. Find  $i(t)$  for the numerical values given, sketch the current waveform, and indicate the value of the time constant. [10]

