

EE 240 - Circuits 1


Assignment 4 Solution

Ans 1:


Switch is at '1' for long time, so capacitor charged.

↳ open circuit.
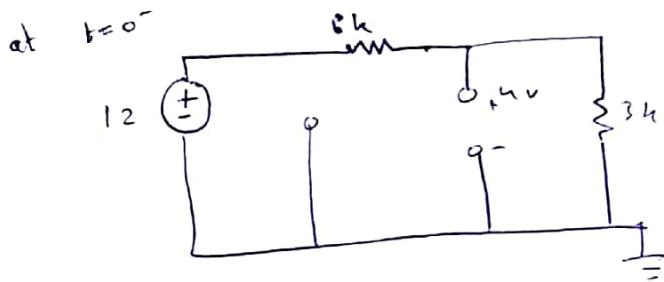
$$V_c(0^-) = 12 \left(\frac{3k}{9k} \right) = \boxed{4V}$$



then, for $t > 0$:

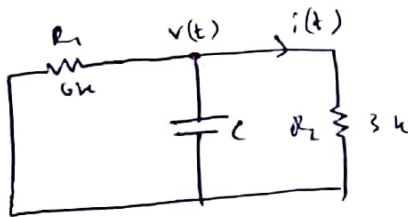

$$\frac{v(t)}{R_1} + C \frac{dv(t)}{dt} + \frac{v(t)}{R_2} = 0$$

$$\frac{v(t)}{2000} + (1 \times 10^{-4}) \frac{dv(t)}{dt} = 0$$

$$\boxed{\frac{dv(t)}{dt} + 5v(t) = 0} \rightarrow (1)$$

using homogeneous equations:

$$v(t) = K_2 e^{-t/\tau}$$

$$-\frac{1}{\tau} K_2 e^{-t/\tau} + 5 K_2 e^{-t/\tau} = 0$$

$$\frac{1}{\tau} = 5$$

$$\boxed{\tau = 0.2}$$

so,

$$v(t) = K_2 e^{-t/0.2}$$

$$v_c(0^-) = v_c(0^+) = \boxed{4V}$$

$$K_2 e^0 = 4$$

$$\boxed{K_2 = 4}$$

$$\boxed{v(t) = 4 e^{-t/0.2} \quad V}$$

now for $i(t)$;


$$i(t) = \frac{v(t)}{R_2}$$

$$i(t) = \frac{4 e^{-t/0.2}}{3000} \quad A$$

$$\boxed{i(t) = \frac{4}{3} e^{-t/0.2} \quad mA}$$



Ans 2:

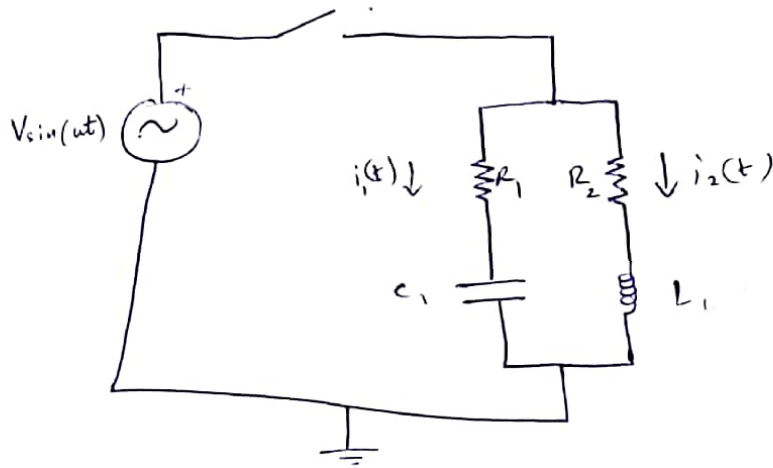

(a) KVL on inner loop:

$$R_1 i_1 + \frac{1}{C_1} \int i_1 dt = V \sin(\omega t)$$

derivate:

$$R_1 \frac{di_1}{dt} + \frac{1}{C_1} i_1 = V \omega \cos(\omega t)$$

at $t=0^+$:

[capacitor is s.c]

$$i_1 = \frac{V \sin(\omega t)}{R_1}$$

$$i_1 = \frac{V \sin(\omega 0^-)}{R_1}$$

$$i_1(0^+) = 0 \text{ A}$$

so,

$$R_1 \frac{di_1(0^+)}{dt} + \frac{1}{C} i_1(0^+) = V \omega \cos(0^+)$$

$$R_1 \frac{di_1(0^+)}{dt} + 0 = V \omega$$

$$\frac{di_1(0^+)}{dt} = \frac{V \omega}{R_1}$$

(b)

$$\left. \begin{aligned} i_L(0^+) &= i_L(0^-) = i_2(0^+) = 0 \text{ A} \\ v_C(0^+) &= v_C(0^-) = 0 \end{aligned} \right\} \text{initial conditions}$$

$$i_2 = i_L$$

$$\boxed{i_2(0^+) = 0 \text{ A}}$$

Take KVL outer loop:

$$R_2 i_2 + L \frac{di_2}{dt} = V \sin(\omega t)$$

$$R_2 i_2(0^+) + L \frac{di_2(0^+)}{dt} = V \sin(\omega t)$$

$$0 + L \frac{di_2(0^+)}{dt} = 0$$

$$\boxed{\frac{di_2(0^+)}{dt} = 0}$$



Ans 3:

for $t < 0$, L_1 & L_2 are s.c so no current in resistors.


$$i_3(0^-) = 0$$

$$i_2(0^-) = i_2(0^+) = -4A$$

$$i_1(0^+) = i_1(0^-) = -8A$$

→ These are initial conditions.

for $t > 0$; circuit becomes:

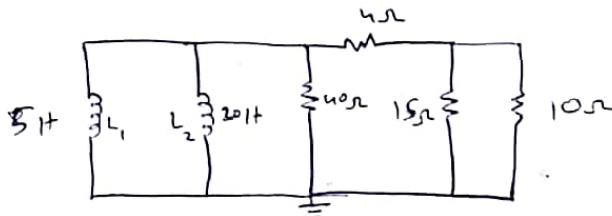


This can be simplified

$$L_{eq} = 5 // 20 = 4H$$

$$R_{eq} = \left[\left[(15 // 10) + 4 \right] // 40 \right] = 8\Omega$$

combined current is $12A$ upwards

Redraw:

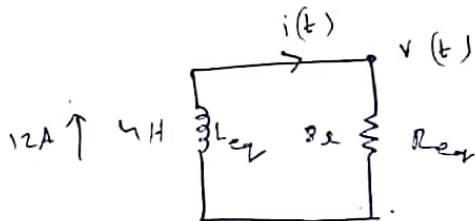

$$\tau = \frac{L_{eq}}{R_{eq}} = \frac{4}{8} = \frac{1}{2}$$

$$i(t) = I_0 e^{-t/\tau}$$

$$i(t) = 12 e^{-2t} A$$

$$v(t) = i(t) R_{eq}$$

$$v(t) = 96 e^{-2t} V$$

Now we know the node voltage, this node is common to all, so now we can find currents.

$$i_1(t) = i_1(0^+) + \frac{1}{L_1} \int_0^t v(t') dt'$$

$$i_1(t) = -8 + \frac{1}{5} \int_0^t 96 e^{-2t'} dt'$$

$$i_1(t) = 1.6 - 9.6 e^{-2t} \text{ A}$$


similarly:

$$i_2(t) = i_2(0^+) + \frac{1}{L_2} \int_0^t v(t') dt'$$

$$i_2(t) = -4 + \frac{1}{20} \int_0^t 96 e^{-2t'} dt'$$

$$i_2(t) = -1.6 - 2.4 e^{-2t} \text{ A}$$

for resistor network:

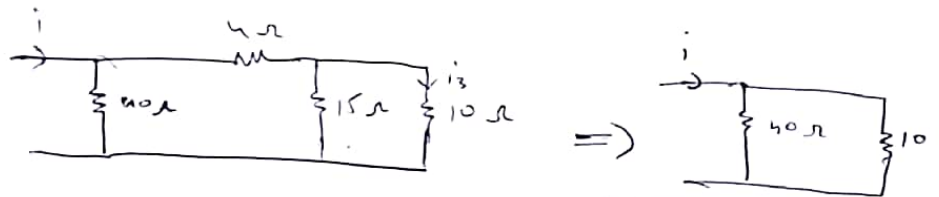

current through equivalent $10 \Omega = \frac{v(t)}{10} = 9.6 e^{-2t} \text{ A}$


$$\left(\frac{15}{10}\right) + 4 = 10$$

so, analyzing that part

current divider

$$i_3(t) = \frac{15}{25} i = \frac{3}{5} (9.6 e^{-2t})$$

$$i_3(t) = 5.76 e^{-2t} \text{ A}$$

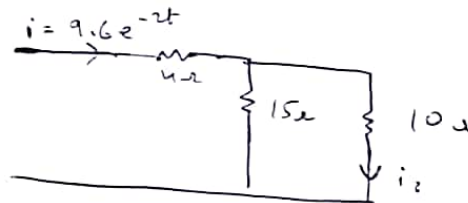

now for $t \rightarrow \infty$:

L_1 & L_2 :

$$i_1(t) = 1.6 - 9.6 e^{-2t} \rightarrow \text{transient dies, } i_1(t) = 1.6 \text{ A}$$


$$i_2(t) = -1.6 - 9.6 e^{-2t} \rightarrow \text{ // // , } i_2(t) = -1.6 \text{ A}$$

$i_3(t) = 5.76 e^{-2t}$; $t \rightarrow \infty$, $i_3(t) = 0 \text{ A}$. Inductors form a closed loop between themselves, & current flows between them, hence no current through resistors.



Ans 4: For $t < 0$, capacitor charged so O.C

redraw

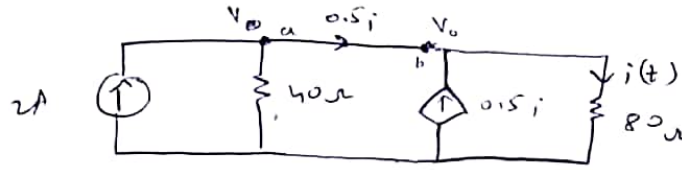

node voltage $V_a = V_b$

for V_a , node equation, current entering = current leaving

so $0.5i$ entering from $a \rightarrow b$, so $0.5i + 0.5i = i$


node a:

$$0.5i = 2 - \frac{V_a}{40}$$

$$\therefore i = \frac{V_a}{80} \rightarrow \text{so } \frac{V_a}{160} = 2 - \frac{V_a}{40} \quad \boxed{V_a = 64 \text{ V}}$$

hence, $i = \frac{V_a}{80} \rightarrow \boxed{i = 0.8 \text{ A}}$ for $\boxed{t < 0}$

for $t > 0$; redraw

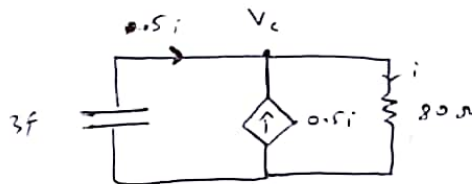

using OPE


$$V_c = V_a e^{-t/\tau}$$

$$\tau = 160 \text{ s}$$

$$\boxed{V_a = 64 \text{ V}}$$

Find I_{test} :

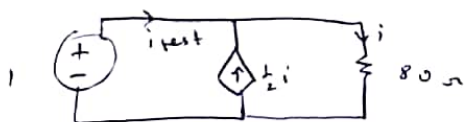attach test source of 1V in place of capacitor



$$\boxed{I_{test} = 0.5i}$$

$$i = \frac{V_c}{80} \quad \therefore \quad V_c = 1 \text{ v}$$

$$\boxed{i = \frac{1}{80}} \rightarrow \text{so} \quad \boxed{I_{\text{test}} = \frac{1}{160}}$$

$$R_{\text{th}} = \frac{1}{I_{\text{test}}} = \boxed{160 \Omega}$$

$$\text{so} \quad \tau = 160(3)$$

$$\boxed{\tau = 480}$$

$$\text{so,} \quad \boxed{V_c(t) = 64 e^{-t/480} \text{ v}}$$

now, current through capacitor = -0.5 i [opposite direction]

$$C \frac{dV_c(t)}{dt} = -0.5 i(t)$$


$$i(t) = -2C \frac{dV_c(t)}{dt}$$

$$i(t) = -6 \times \frac{64 e^{-t/480}}{480}$$

$$\boxed{i(t) = 0.8 e^{-t/480} \text{ A}; t > 0}$$

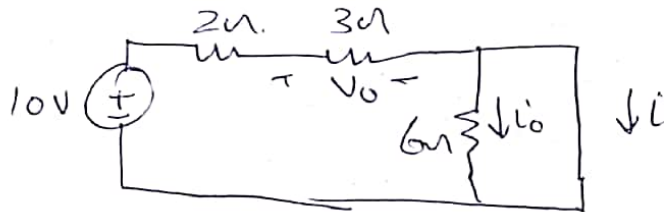Q5

For $t < 0$, The switch is open. Since Inductor acts like a short circuit to dc, the 6Ω resistor is also short circuited




Hence $i_0 = 0$

$$i(t) = \frac{10}{2+3} = 2A \quad t < 0$$

$$V_0(t) = 3i(t) = 6V \quad t < 0$$

$$i(0) = 2$$

For $t > 0$ now voltage source is S.C

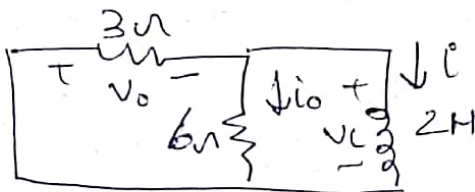

$$R_{TH} = 3 \parallel 6 = 2\Omega$$

Time constant:

$$\tau = \frac{L}{R_{TH}} = 1s$$

Hence


$$i(t) = i(0)e^{-t/\tau} = 2e^{-t}A \quad t > 0$$

Since Inductor is parallel with 6Ω and 3Ω resistors, !

$$V_o(t) = -V_L = -L \frac{di}{dt} = -2(-2e^{-t}) = 4e^{-t} \text{ V}, \quad t > 0$$

and

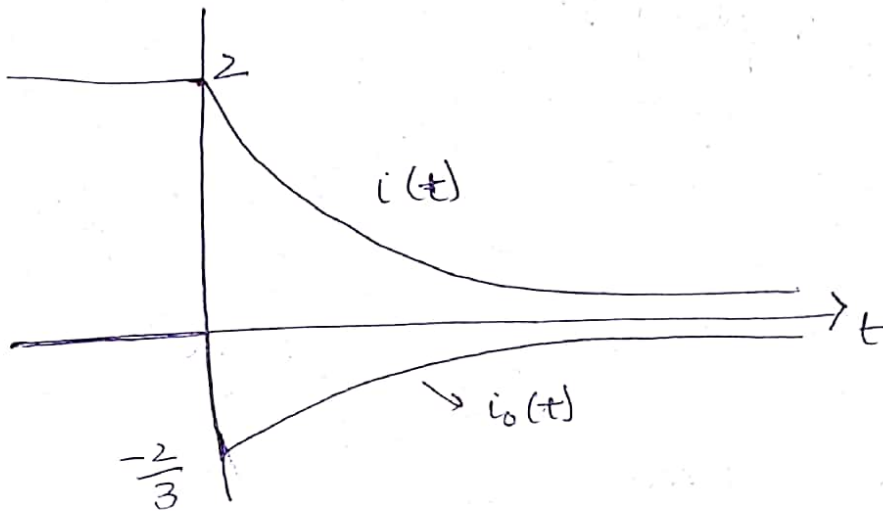
$$i_o(t) = \frac{V_L}{6} = -\frac{2}{3}e^{-t} \text{ A} \quad t > 0$$



Q6

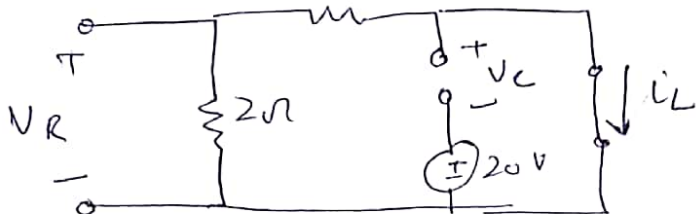a) For $t < 0$, $3u(t) = 0$; Inductor \Rightarrow S.C,
Capacitor \Rightarrow O.C

$$i_L(0^-) = 0, \quad V_R(0^-) = 0, \quad V_C(0^-) = -20V$$




For $t > 0$, $3u(t) = 3$, \Rightarrow so source is of 3A

Since Inductor current and Capacitor voltage cannot abruptly change hence:

$$i_L(0^+) = i_L(0^-) = 0$$

$$V_C(0^+) = V_C(0^-) = -20$$

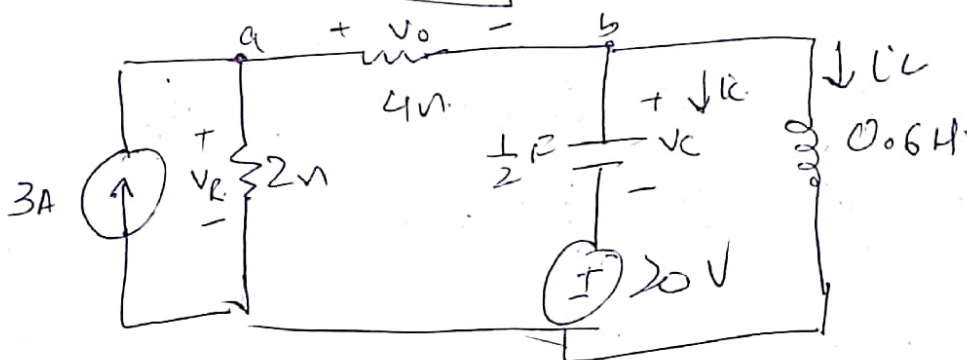

KCL at node a:

$$3 = \frac{V_R(0^+)}{2} + \frac{V_0(0^+)}{4}$$

Applying KVL to the middle mesh:

$$-V_R(0^+) + V_0(0^+) + V_C(0^+) + 20 = 0$$

Since $V_C(0^+) = -20V$ so $V_R(0^+) = V_0(0^+)$

$$V_R(0^+) = V_0(0^+) = 4V$$

(b) We know $L \frac{di_L}{dt} = V_L$

hence.

$$\frac{dV_L(0^+)}{dt} = \frac{V_L(0^+)}{L}$$

KVL in Right Most Mesh:

$$V_L(0^+) = V_C(0^+) + 20 = 0$$

$$\therefore \boxed{\frac{di_L(0^+)}{dt} = 0}$$

$$C \frac{dV_C}{dt} = i_C \Rightarrow \frac{dV_C}{dt} = \frac{i_C}{C}$$

KVL at node b

$$\frac{V_0(0^+)}{4} = i_C(0^+) + i_L(0^+)$$

Since $V_0(0^+) = 4$, $i_L(0^+) = 0$, $i_C(0^+) = \frac{4}{4} = 1$ Then:

$$\frac{dV_C(0^+)}{dt} = \frac{i_C(0^+)}{C} = \frac{1}{0.5} = \boxed{2 = \frac{dV_C(0^+)}{dt}}$$

$\frac{dV_R(0^+)}{dt} \Rightarrow$ apply KCL at node a.

$$3 = \frac{V_R}{2} + \frac{V_0}{4}$$

Take its derivative and setting $t=0^+$

$$0 = 2 \frac{dV_R(0^+)}{dt} + \frac{dV_0(0^+)}{dt}$$

KVL to middle mesh

$$-V_R + V_C + 20 + V_0 = 0$$

$$\frac{dV_R(0^+)}{dt} + \frac{dV_C(0^+)}{dt} + \frac{dV_0(0^+)}{dt} = 0$$

Substitute $\frac{dv_c(0^+)}{dt} = 2$

$$\frac{dv_R(0^+)}{dt} = 2 + \frac{dv_o(0^+)}{dt}$$

$$\text{hence } \boxed{\frac{dv_R(0^+)}{dt} = \frac{2}{3} \text{ V/s}}$$

Q7

Using KCL at node 'V₁'

For $t \geq 0$

$$\frac{v_1 - v(t)}{R_1} + C_1 \frac{dv_1}{dt} + \frac{(v_1 - v_2)}{R_2} + \frac{1}{L} \int (v_1 - v_3) dt = 0 \text{ (i)}$$

Using KCL at node 'V₂'

$$\frac{v_2 - v_1}{R_2} + C_2 \frac{dv_2}{dt} + \frac{1}{L_2} \int v_2 dt = 0 \text{ (ii)}$$

Using KCL at node 'V₃'

$$\frac{1}{L_3} \int (v_3 - v_1) dt + C_3 \frac{dv_3}{dt} = 0 \text{ (iii)}$$

At $t = 0^+$ C_1 becomes short circuit as a result of which:

$$v_1(0^+) = 0V; \quad v_2(0^+) = 0V; \quad v_3(0^+) = 0V.$$

At $t = 0^+$

$$\frac{1}{L_1} \int (v_3 - v_1) dt + C_3 \frac{dv_3}{dt} = 0.$$

$$i_{L_1}(0^+) + C_3 \frac{dv_3(0^+)}{dt} = 0.$$

After simplification:

$$\boxed{\frac{dv_3(0^+)}{dt} = 0}$$

Here $i_{L1}(0^-) = i_{L1}(0^+) = 0A$

At $t = 0^+$

$$\frac{v_2(0^+) - v_1(0^+)}{R_2} + C_2 \frac{dv_2(0^+)}{dt} + i_{L2}(0^+) = 0 \quad (ii)$$

$i_{L2}(0^-) = i_{L2}(0^+) = 0A$

after simplification

$$\boxed{\frac{dv_2(0^+)}{dt} = 0}$$

At $t = 0^+$ eq (i) :

$$\frac{v_1(0^+) - v(0^+)}{R_1} + C_1 \frac{dv_1(0^+)}{dt} + \frac{(v_1(0^+) - v_2(0^+))}{R_2} + \frac{1}{L} \int (v_1(0^+) - v_3(0^+)) dt = 0$$

$\underbrace{\hspace{10em}}_{i_3(0^+)}$

hence :

$$\boxed{\frac{dv_1(0^+)}{dt} = 0}$$


Q8

For $t < 0$;

$$-10 - 20 + 30i(0^-) + 2i(0^-) + 0 = 0$$

$$-30 + 50i(0^-) = 0$$

$$i(0^-) = \frac{3}{5} = 0.6$$

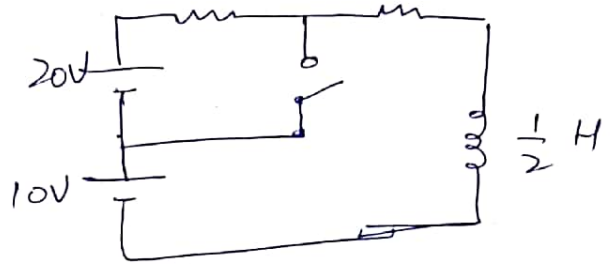

For $t > 0$;

$$-10 + 20i(t) + \frac{1}{2} \frac{di(t)}{dt} = 0$$

$$\frac{di(t)}{dt} + 40i(t) = 20$$

$$I.F = e^{40t}$$

$$\therefore i(t) e^{40t} = \int 20e^{40t} dt + K$$

$$i(t) e^{40t} = \frac{20e^{40t}}{40} + K$$

$$\frac{1}{T} = 40 \quad T = \frac{1}{40} \text{ s}$$

$$i(t) = 0.5 + K e^{-40t}$$

$$i(0) = 0.5 + K = 0.6$$

$$K = 0.1$$

$$i(t) = 0.5 + 0.1 e^{-40t}$$

