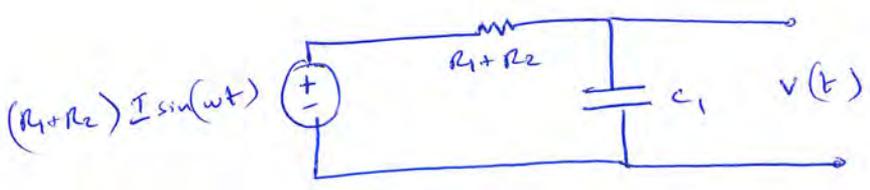


EE 240 - Circuits 1
Assignment 5 solution


Ans 1: at $t < 0$



when capacitor charged \rightarrow OC

$$V(0^-) = I \sin(\omega t) (R_1 + R_2) = \boxed{0}$$

for $t > 0$

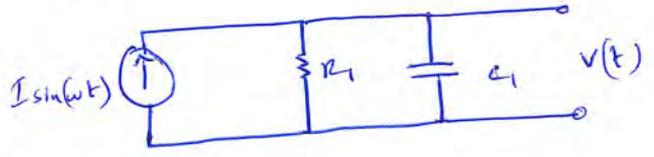

KCL

$$C_1 \frac{dv(t)}{dt} + \frac{v(t)}{R_1} = I \sin(\omega t)$$

$$\frac{dv(t)}{dt} + \frac{v(t)}{R_1 C_1} = \frac{I \sin(\omega t)}{C_1}$$

non-homogeneous

complementary solution:

$$\frac{dv(t)}{dt} = -\frac{1}{R_1 C_1} v(t)$$

$$v(t) = k e^{-t/R_1 C_1}$$

particular

$$v_p(t) = k_1 \sin(\omega t) + k_2 \cos(\omega t) \quad \text{--- (1)}$$

substitute (1) in KCL:

$$\omega k_1 \cos(\omega t) - \omega k_2 \sin(\omega t) + \frac{1}{R_1 C_1} [k_1 \sin(\omega t) + k_2 \cos(\omega t)] = \frac{I \sin(\omega t)}{C}$$

equating coefficients:

$$\cos(\omega t) \quad \omega k_1 + \frac{k_2}{R_1 C_1} = 0$$

$$k_1 = -\frac{k_2}{\omega R_1 C_1} \quad (2)$$

$\sin(\omega t)$

$$-\omega k_2 + \frac{k_1}{R_1 C_1} = \frac{I}{C_1}$$

$$k_2 = \frac{k_1}{\omega R_1 C_1} - \frac{I}{\omega C_1} \quad (3)$$

substitute (3) in (2):

$$k_1 = -\frac{1}{\omega R_1 C_1} \left[\frac{k_1}{\omega R_1 C_1} - \frac{I}{\omega C_1} \right]$$

$$k_1 = \frac{I R_1}{\omega^2 R_1^2 C_1^2 + 1} \quad (4)$$

substitute (4) in (3)

$$k_2 = -\frac{\omega R_1^2 C_1 I}{\omega^2 R_1^2 C_1^2 + 1}$$

$$v(t) = k e^{-\frac{t}{R_1 C_1}} + \left(\frac{I R_1}{\omega^2 R_1^2 C_1^2 + 1} \right) \sin(\omega t) - \left(\frac{\omega R_1^2 C_1 I}{\omega^2 R_1^2 C_1^2 + 1} \right) \cos(\omega t)$$

find k :

$$\text{at } t=0^+ \quad v(0^+) = I \sin(\omega t) [R_1 + R_2]$$

$$k - \frac{\omega R_1^2 C_1 I}{\omega^2 R_1^2 C_1^2 + 1} = I \sin(\omega t) [R_1 + R_2] = 0$$

$$k = I \sin(\omega t) [R_1 + R_2] + \frac{\omega R_1^2 C_1 I}{\omega^2 R_1^2 C_1^2 + 1}$$


$$k = \frac{\omega R_1^2 C_1 I}{\omega^2 R_1^2 C_1^2 + 1}$$

so,

$$v(t) = \left[\frac{\omega R_1^2 C_1 I}{\omega^2 R_1^2 C_1^2 + 1} \right] e^{-\frac{t}{R_1 C_1}} + \left(\frac{I R_1}{\omega^2 R_1^2 C_1^2 + 1} \right) \sin(\omega t) - \left(\frac{\omega R_1^2 C_1 I}{\omega^2 R_1^2 C_1^2 + 1} \right) \cos(\omega t)$$



Ans 2:

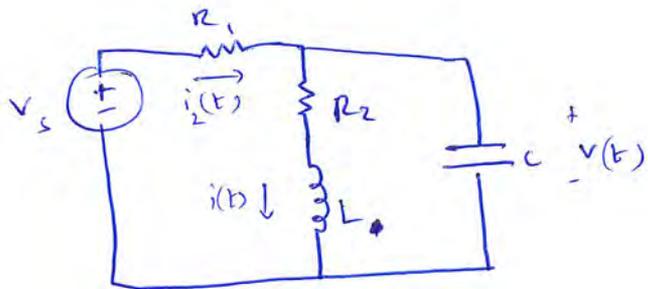

→ let $i_2(t)$ pass through R_1

KVL:

$$R_2 i(t) + L \frac{di(t)}{dt} = v(t) \quad (1)$$

KCL:

$$i(t) + C \frac{dv(t)}{dt} = i_2(t) \quad (2)$$

KVL on left loop:

$$v_s = R_1 i_2(t) + v(t)$$

$$v_s = R_1 \left[i(t) + C \frac{dv(t)}{dt} \right] + v(t) \quad (3)$$

substitute (1) in (3)

$$v_s = R_1 i(t) + R_1 C \left[R_2 \frac{di(t)}{dt} + L \frac{d^2 i(t)}{dt^2} \right] + R_2 i(t) + L \frac{di(t)}{dt}$$

$$v_s = R_1 C L \frac{d^2 i(t)}{dt^2} + (R_1 R_2 C + L) \frac{di(t)}{dt} + (R_1 + R_2) i(t)$$

$$\frac{d^2 i(t)}{dt^2} + \left(\frac{R_2}{L} + \frac{1}{R_1 C} \right) \frac{di(t)}{dt} + \left(\frac{R_1 + R_2}{R_1 C L} \right) i(t) = \frac{v_s}{R_1 C L}$$

(a) any value for which:

$$\left(\frac{R_2}{L} + \frac{1}{R_1 C} \right)^2 < 4 \left(\frac{R_1 + R_2}{R_1 C L} \right)$$

simplifies to

$$L^2 > (\text{or } <) R_1^2 R_2^2 C^2 (4L^2 - 1) + R_1 R_2 C L (4R_1 R_2 C L - 2)$$

(b) any value for which:

$$\left(\frac{R_2}{L} + \frac{1}{R_1 C} \right)^2 > 4 \left(\frac{R_1 + R_2}{R_1 C L} \right)$$

(—)

Aus 3:

(a)


$$s^2 + 4s + 10 = 0$$

(b)

$$\begin{aligned} b^2 - 4ac &= 16 - 40 \\ &= -24 \\ &< 0 \end{aligned}$$

Since $b^2 - 4ac < 0 \rightarrow$ under-damped

or
roots are complex conjugates

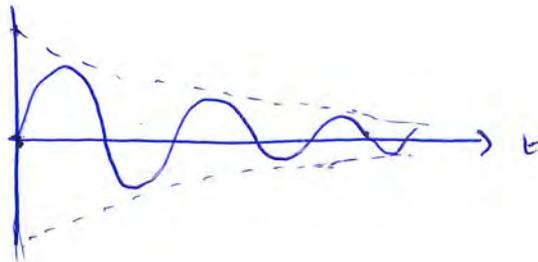

(c)

$$s^2 + 4s + 10 = 0$$

$$s = \frac{-4 \pm \sqrt{-24}}{2}$$

$$s = -2 \pm 2.45j$$

$$i(t) = e^{-2t} [k_1 \sin(2.45t) + k_2 \cos(2.45t)]$$

$$i(0) = k_2 = 1$$

$$\frac{di(t)}{dt} = [-2k_1 \sin(2.45t) - 2k_2 \cos(2.45t) + 2.45k_1 \cos(2.45t) - 2.45k_2 \sin(2.45t)] e^{-2t}$$

$$\frac{di(0)}{dt} = -2k_2 + 2.45k_1 = 2 \quad \therefore k_2 = 1$$

$$2.45k_1 = 4$$

$$k_1 = 1.63$$

$$i(t) = e^{-2t} [1.63 \sin(2.45t) + \cos(2.45t)]$$



Ans u.


$t < 0$, capacitor oc

$i(0^-) = 0$


$V(0^-) = \frac{5}{30} \times 100$

$V(0^-) = \frac{50}{3}$

for $t > 0$

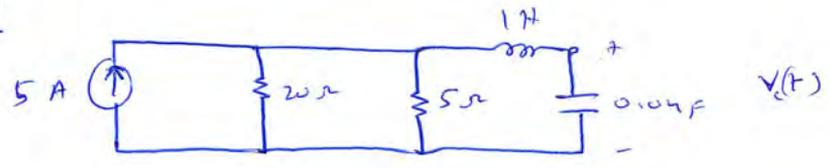

$20 // 5 = 4 \Omega$

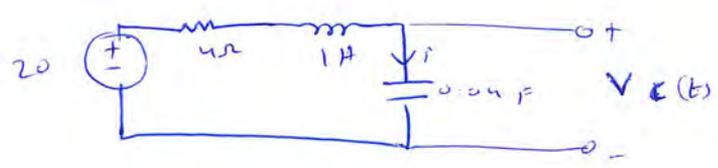

RLC series circuit

KVL

$4i(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt = 0$

take derivative:

$\frac{d^2 i(t)}{dt^2} + 4 \frac{di(t)}{dt} + 25 i(t) = 0$

$s^2 + 4s + 25 = 0$

$s = -2 \pm 5j$ → under-damped

$i(t) = e^{-2t} [k_1 \sin(5t) + k_2 \cos(5t)]$

$i(0) = k_2 = 0$

$v(t) = \frac{1}{C} \int i(t) dt$ → do cyclic integration

$v(t) = \frac{20}{3} + \frac{1}{C} \int i(t) dt$
at $t = \infty$
 $v(t) = 20$ → so this term covers for it.

$v(t) = 20 + e^{-2t} [(\sqrt{25} k_2 - 2k_1) \sin(5t) + (-2k_2 - \sqrt{25} k_1) \cos(5t)]$

$v(0^-) = 20 - 2k_2 - 5k_1 = \frac{50}{3} \therefore k_2 = 0$

$k_1 = 0.727$

$\dot{i}(t) = 0.727 e^{-2t} \sin(5t)$

Q: 5

$$(a) \quad 2 \frac{d^3 i}{dt^3} + 9 \frac{d^2 i}{dt^2} + 13 \frac{di}{dt} + 6i = 0$$

Substituting $\frac{di}{dt} = s$.

$$\Rightarrow 2s^3 + 9s^2 + 13s + 6 = 0$$

By either solving through long division / synthetic division / calculator.

$$s = -2, -1, -3/2$$

$$\therefore i(t) = k_1 e^{-2t} + k_2 e^{-t} + k_3 e^{-\frac{3}{2}t}$$

Now solving for k_1, k_2 and k_3 .

At $t = 0^+$:

$$i(0^+) = k_1 e^{-2(0^+)} + k_2 e^{-1(0^+)} + k_3 e^{-\frac{3}{2}(0^+)}$$

$$\boxed{0 = k_1 + k_2 + k_3} \quad - (1)$$

$$\frac{di(t)}{dt} = -2k_1 e^{-2t} - k_2 e^{-t} - \frac{3}{2}k_3 e^{-\frac{3}{2}t}$$

At $t = 0^+$:

$$\frac{di(0^+)}{dt} = -k_1 (e)^{-1(0^+)} - k_2 (e)^{-1(0^+)} - 6k_3 (e)^{-\frac{3}{2}(0^+)}$$

$$\boxed{1 = -2k_1 - k_2 - \frac{3}{2}k_3} \quad - (2)$$

$$\frac{d^2 i(t)}{dt} = 4k_1 e^{-t} + k_2 e^{-t} + \frac{9}{4} k_3 e^{-6t}$$

At $t = 0^+$:

$$\frac{d^2 i(0^+)}{dt} = 4k_1 e^{-0^+} + k_2 (e)^{-0^+} + \frac{9}{4} k_3 e^{-6(0^+)}$$

$$\boxed{-1 = 4k_1 + k_2 + \frac{9}{4} k_3} \quad \text{--- (3)}$$

Solving 1, 2 and 3 simultaneously.

$$k_1 = 3$$

$$k_2 = 5$$

$$k_3 = -8$$

$$\Rightarrow \boxed{i(t) = 3e^{-2t} + 5e^{-t} - 8e^{-3/2t}}$$

$$(b) \frac{d^2 i}{dt^2} + 3 \frac{di}{dt} + 2i = 10 \sin 10t \quad - (1)$$

Non homogeneous differential equation:

$$\Rightarrow s^2 + 3s + 2 = 0$$

$$s = -1, -2$$

$$i_c(t) = k_1 e^{-t} + k_2 e^{-2t}$$

$$i_p(t) = A \sin 10t + B \cos 10t$$

Substituting i_p in (1):

$$-100A \sin 10t - 100B \cos 10t + 30A \cos 10t - 30B \sin 10t + 2A \sin 10t + 2B \cos 10t = 10 \sin 10t$$

Equating coefficients:

for \sin :

$$-100A - 30B + 2A = 10$$

$$\boxed{-98A - 30B = 10} \quad - (x)$$

for \cos :

$$-100B + 30A + 2B = 0$$

$$\boxed{-98B + 30A = 0} \quad - (y)$$

Solving for (x) and (y):

$$A = -0.094 \quad \rightarrow B = 0.306A$$

$$\Rightarrow i_p(t) = -0.094 \sin 10t + (-0.029) \cos 10t$$

Solving for k_1 and k_2 :

At $t = 0^+$:

$$i(0^+) = k_1 e^{0^+} + k_2 e^{0^+} - 0.0094 \sin(0^+) - 0.029 \cos(0^+)$$

$$\boxed{1.029 = k_1 + k_2} -$$


$$\frac{di(0^+)}{dt} = -k_1 e^{0^+} - 2k_2 e^{0^+} - 0.094(10) \cos(0^+) + 0.029(10) \sin 10(0^+)$$

$$\boxed{k_1 + k_2 = 0.06}$$



Solving for k_1 and k_2 further:

$$k_1 = 1.998 \quad ; \quad k_2 = -0.969.$$
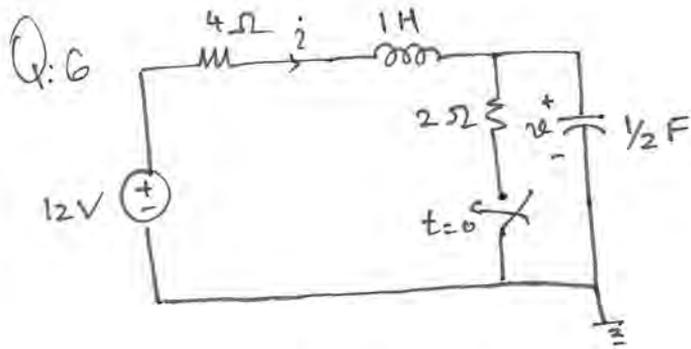
$$\Rightarrow i(t) = 1.998 e^{-t} - 0.969 e^{-2t} - 0.094 \sin 10t - 0.029 \cos 10t$$


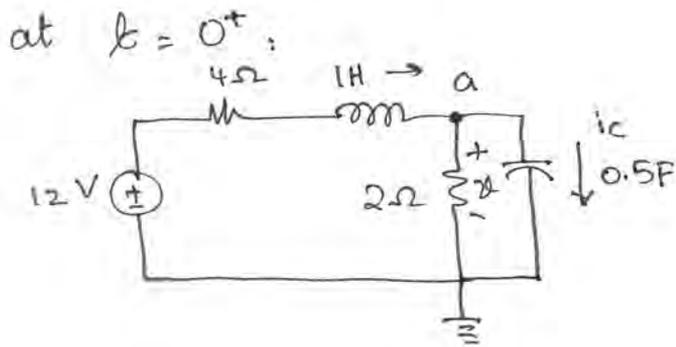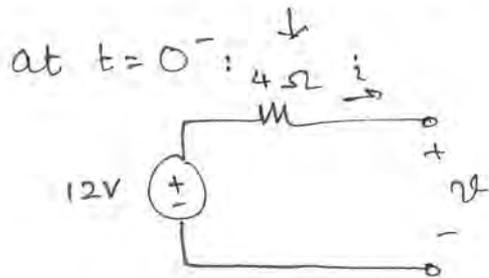
$$v_c(0^-) = 12V \quad ; \quad i(0^-) = 0A$$



$$\therefore v(0^+) = v(0^-) = 12V$$

$$i(0^+) = i(0^-) = 0A$$

$$i_c = C \frac{dv_c}{dt} \quad ; \quad \text{Nodal at } a \text{ for } t = 0^+ :$$

$$i(0^+) = i_c(0^+) + \frac{v_c(0^+)}{2}$$


$$0 = i_c(0^+) + \frac{12}{2} \Rightarrow i_c(0^+) = -6A$$

$$\therefore \frac{dv(0^+)}{dt} = \frac{-6}{0.5} = -12V/s$$

At $t = \infty$, capacitor will be open circuit and inductor short circuit.

$$i(\infty) = \frac{12}{4+2} = 2A \quad \Rightarrow \quad v(\infty) = 2i(\infty) = 4V$$

For $t > 0$:

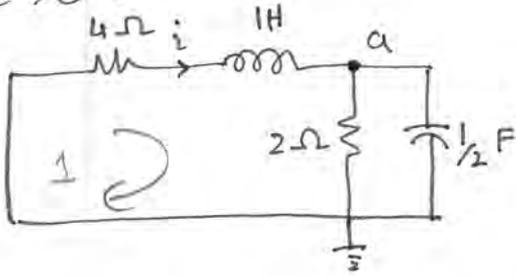

$$i(t) = \frac{v(t)}{2} + \frac{1}{2} \frac{dv}{dt} \quad \text{--- (2)}$$

Applying KVL to the left mesh results in
(loop 1)

$$4i + 1 \frac{di}{dt} + v = 0 \quad \text{--- (1)}$$

Substituting (2) in (1):

$$2v + 2 \frac{dv}{dt} + \frac{1}{2} \frac{dv}{dt} + \frac{1}{2} \frac{d^2v}{dt^2} + v = 0$$

or

$$\frac{d^2v}{dt^2} + 5 \frac{dv}{dt} + 6v = 0$$

Substituting $\frac{dv}{dt} = s$

$$\Rightarrow s^2 + 5s + 6s = 0$$

$$s = -2, -3$$

$$\Rightarrow v(t) = K_1 e^{-2t} + K_2 e^{-3t}$$

At steady state: $v(\infty) = 4$.

$$\Rightarrow v(t) = v(\infty) + v(t) = 4 + K_1 e^{-2t} + K_2 e^{-3t}$$

at $t = 0^+$: ~~12 = 4 + K_1 + K_2~~ $12 = 4 + K_1 + K_2 \Rightarrow K_1 + K_2 = 8$ --- (X)

$$\frac{dv}{dt} = -2K_1 e^{-2t} - 3K_2 e^{-3t}$$

at $t=0^+$:

$$-12 = -2K_1 - 3K_2$$

$$\Rightarrow 2K_1 + 3K_2 = 12 \quad \text{--- (Y)}$$

Solving (X) & (Y) simultaneously yields:

$$K_1 = 12 \quad ; \quad K_2 = -4.$$


$$\Rightarrow v(t) = 4 + 12e^{-2t} - 4e^{-3t}$$

Now Solving for i for $t > 0$:

$$i = \frac{v}{2} + \frac{1}{2} \frac{dv}{dt} = 2 + 6e^{-2t} - 2e^{-3t} - 12e^{-2t} + 6e^{-3t}$$

$$= 2 - 6e^{-2t} + 4e^{-3t} \quad A$$

Q:7

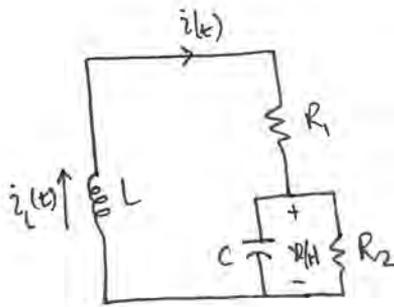

$$R_1 = 10\Omega ; R_2 = 8\Omega ; C = \frac{1}{8}F ;$$

$$L = 2H , v_c(0) = 1V ; i_L(0^+) = 0.5A$$

$$(a) L \frac{di}{dt} + R_1 i(t) + v(t) = 0$$

$$(b) C \frac{dv}{dt} + \frac{v(t)}{R_2} = i(t)$$

Substituting b into a :

$$\frac{d^2 v}{dt^2} + \left[\frac{1}{R_2 C} + \frac{R_1}{L} \right] \frac{dv}{dt} + \frac{R_1 + R_2}{R_2 L C} v = 0$$

Substituting the given values , yields :

$$\frac{d^2 v}{dt^2} + 6 \frac{dv}{dt} + 9v = 0$$

Substituting $\frac{dv}{dt} = s$

$$\Rightarrow s^2 + 6s + 9 = 0$$

$$s = -3, -3.$$

This becomes the critically damped case , hence :

$$\boxed{v(t) = k_1 e^{-3t} + k_2 t e^{-3t}} \quad \text{--- (1)}$$

At $t=0$:

$$\boxed{v(0) = v_c(0) = 1 = k_1}$$

Differentiating (1) :

$$\frac{dv}{dt} = -3k_1 e^{-3t} + k_2 e^{-3t} - 3k_2 t e^{-3t} \quad \text{--- (2)}$$

$$i_2(t) = C \frac{dv_c}{dt}$$

$$\Rightarrow \frac{dv_c}{dt} = \frac{i(t)}{C} - \frac{v(t)}{R_2 C} \quad \text{--- (3)}$$

Putting (2) = (3):

At $t=0$:

$$\boxed{3 = -3k_1 + k_2}$$

Substituting $k_1 = 1$, yields:

$$\boxed{k_2 = 6}$$

$$\Rightarrow \boxed{v(t) = e^{-3t} + 6te^{-3t}} \quad \checkmark$$


Now we'll put (b) $v(t)$ into $i(t)$ (b):

$$i(t) = C \frac{dv_c(t)}{dt} + \frac{v(t)}{R_2}$$

$$i(t) = \frac{1}{8} \left[-3e^{-3t} + 6e^{-3t} - 18te^{-3t} \right] + \frac{1}{8} \left[e^{-3t} + 6te^{-3t} \right]$$

$$\Rightarrow \boxed{i(t) = \frac{1}{2} e^{-3t} - \frac{3}{2} t e^{-3t}} \quad \text{A}$$


Q.8

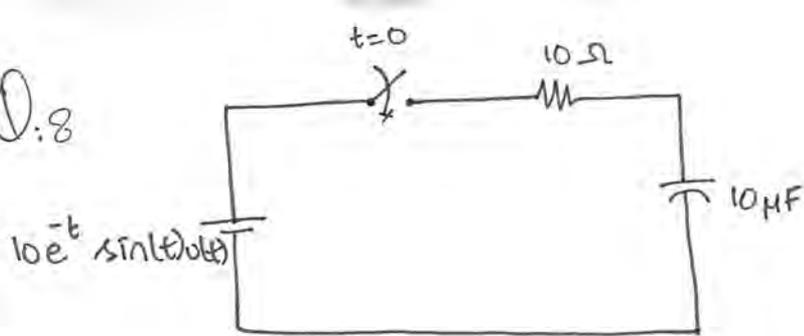

$$v_C(0^-) = v_C(0^+) = 0V$$

$$i(0^+) = \frac{10e^{-(0^+)} \sin(0^+)}{10}$$

$$i(0^+) = 0 \text{ A}$$

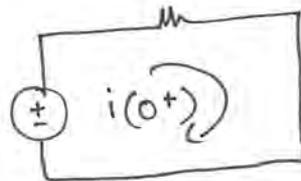

For $t \geq 0$;

Applying loop analysis:

$$10i(t) + \frac{1}{C} \int i(t) dt = 10e^{-t} \sin(t) V$$

$$i(t) + 10000 \int i(t) dt = e^{-t} \sin(t)$$

Differentiating w.r.t t :

$$\frac{di(t)}{dt} + 10000i = e^{-t} \cos(t) - e^{-t} \sin(t) \quad \text{--- (1)}$$

This is a non-homogeneous equation, hence:

$$si + 10^4 i = 0$$

$$\Rightarrow s = -10^4$$

$$i_c = k e^{-10,000t}$$

The particular solution will be:

$$i_p(t) = [A \cos t + B \sin t] e^{-t}$$

Putting the particular integral into the equation (1):

$$-A e^{-t} \sin t - A e^{-t} \cos t + B e^{-t} \cos t - B e^{-t} \sin t \\ + 10,000 e^{-t} A \cos t + 10,000 B e^{-t} \sin t = e^{-t} \cos t - e^{-t} \sin t$$

Equating coefficients of $e^{-t} \sin t$:

$$-A - B + 10,000 B = -1$$

$$\boxed{-A + 9999B = -1} \quad \text{--- (a)}$$

Equating coefficients of $e^{-t} \cos t$:

$$-A + B + 10,000A = 1$$

$$\boxed{B + 9999A = 1} \quad \text{--- (b)}$$

Solving (a) and (b) simultaneously; yields:

$$A = 10^{-4}, \quad B = -10^{-4}$$

$$\Rightarrow i(t) = i_c(t) + i_p(t)$$

$$= k e^{-10,000t} + 10^{-4} e^{-t} \cos t - 10^{-4} e^{-t} \sin t$$

Now solving for k :


At $t=0^+$:

$$i(0^+) = k e^{-10,000(0^+)} + \left[10^{-4} \cos(0^+) - 10^{-4} \sin(0^+) \right] e^{-10,000(0^+)}$$

$$\boxed{k = -10^{-4}}$$

$$\Rightarrow \boxed{i(t) = -10^{-4} e^{-10,000t} + 10^{-4} e^{-t} \cos t - 10^{-4} e^{-t} \sin t}$$

Q: 9

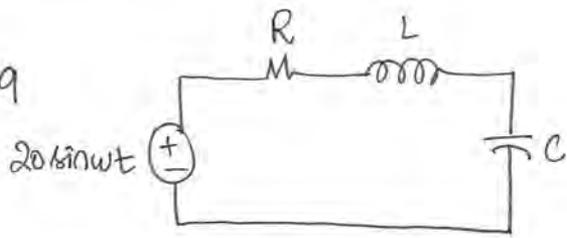

$$R = 2 \Omega$$

$$L = 1 \times 10^{-3} \text{ H}$$

$$C = 0.4 \times 10^{-6} \text{ F}$$

(a) The resonant frequency:

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \times 10^{-3} \times 0.4 \times 10^{-6}}} = 50 \times 10^3 \text{ rad/s}$$

(b) The bandwidth will be:

$$B = \frac{R}{L} = \frac{2}{1 \times 10^{-3}} = 2 \times 10^3 \text{ rad/s}$$

(c) The quality factor will be:

$$Q = \frac{\omega_0}{B} = \frac{50 \times 10^3}{2 \times 10^3} = 25$$