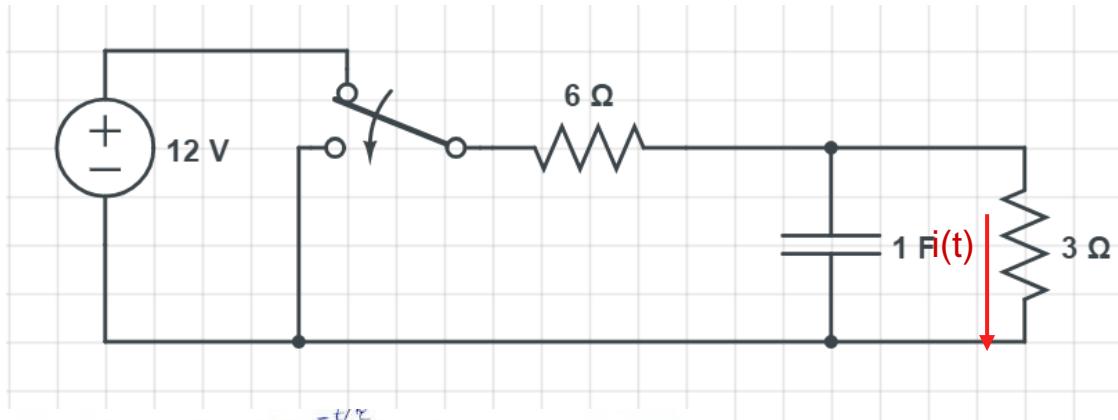


# First Order Circuits

## Problems – In class

**Problem 1:** In the following circuit, the switch is operated at  $t=0$ . Determine the current  $i(t)$  through  $3\Omega$  resistor for all times.



$$i(t) = K_1 + K_2 e^{-t/\tau}$$

$$v_c(0^-) = v_c(0^+) = \frac{3}{9} \times 12 = 4V$$

$$i(0^-) = \frac{12}{9} = 1.33A$$

$$i(0^+) = \frac{v_c(0^+)}{3} = \frac{1.33}{3}A$$

$$i(\infty) = 0$$

$$\begin{cases} K_1 = i(\infty) = 0 \\ K_2 = i(0) - i(\infty) \end{cases} \Rightarrow K_2 = 1.33$$

$$\Rightarrow i(t) = 1.33 e^{-t/\tau}$$

$$\boxed{i(t) = 1.33 e^{-t/2} A}$$

$\tau = ?$   
 only one time constant.  
 At position 2  
 3Ω and 6Ω  
 are in parallel  
 $\Rightarrow R_{eq} = 3/6$   
 $= \frac{18}{9} = 2\Omega$   
 $\tau = R_{eq} C = 2 \text{ sec.}$

Alternatively: If you couldn't figure out  $\tau$ ,

write down differential equation:

$$\frac{v_c}{3} + \frac{v_c}{6} + \frac{dv_c}{dt} = 0 \Rightarrow \frac{dv_c}{dt} + \frac{1}{2} v_c = 0$$

$$\downarrow \frac{1}{\tau} = \boxed{\tau = 2}$$

Homogeneous equation:

$$v_c(t) = K_1 e^{-t/2}$$


$$K_1 = v_c(0^+) = 4V \Rightarrow \boxed{v_c(t) = 4 e^{-t/2}}$$

$$\begin{cases} i_c(t) = \frac{4}{3} e^{-t/2} & t \geq 0 \\ i_c(t) = 1.33A & t < 0 \end{cases}$$

# First Order Circuits

## Problems – In class

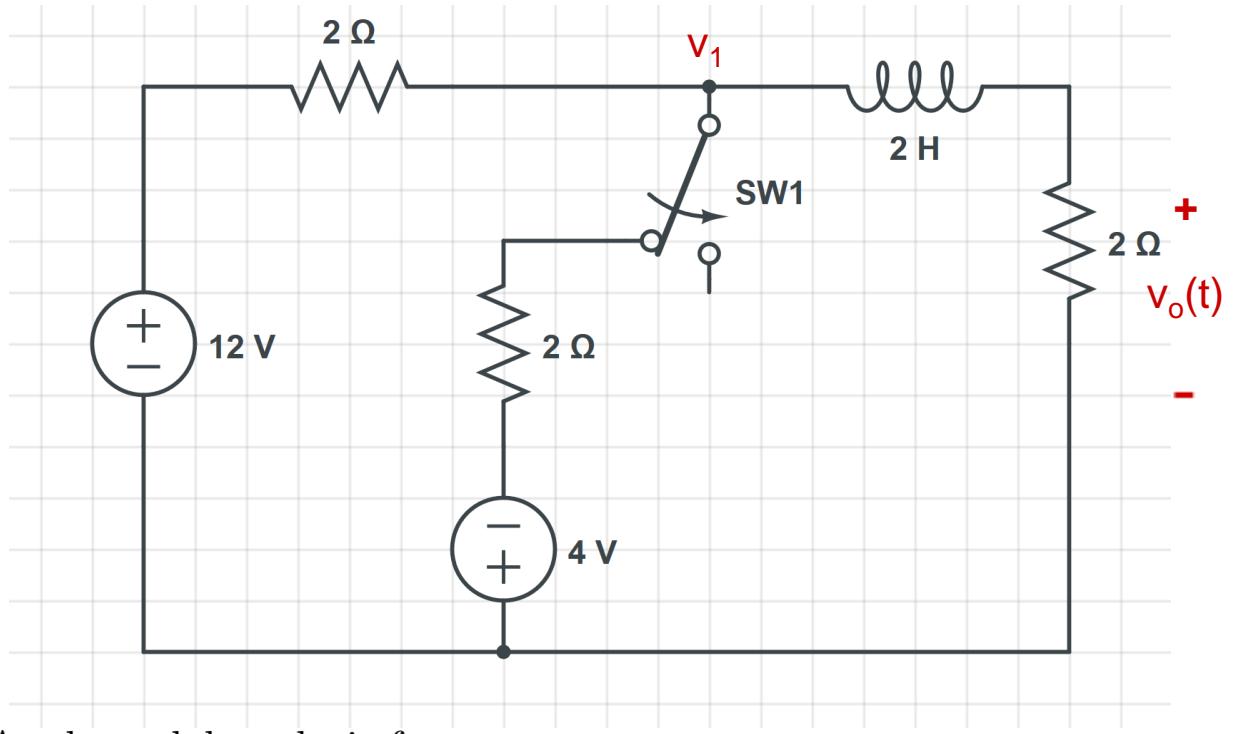**Problem 2:** In the following circuit, the switch is operated at  $t=0$ . Determine the voltage  $v_o(t)$  for all times.





Apply nodal analysis for  $v_1$ :

$$\frac{v_1 - 12}{2} + \frac{v_1 + 4}{2} + \frac{v_1}{2} = 0 \Rightarrow v_1 = \frac{8}{3}V.$$

Current through inductor:  $i_L(0^-) = i_L(0^+) = \frac{4}{3}A, \Rightarrow v_o(0^+) = \frac{8}{3}V$

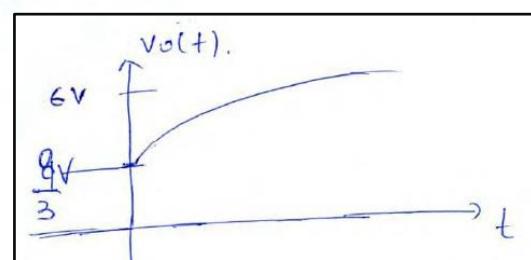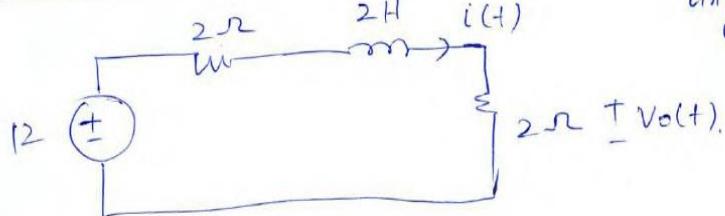At  $t=0^+$ ;  $4V$  and  $2\Omega$  (do not have any contribution)




$$v_o(t) = K_1 + K_2 e^{-t/\tau}, \quad K_1 = v_o(\infty) = 6V, \quad K_2 = v_o(0^+) - v_o(\infty) = \frac{10}{3}V$$

$$\tau = \frac{L}{R}, \quad L = 2H, \quad R = 4\Omega \Rightarrow \tau = 0.5 \text{ seconds.}$$

# First Order Circuits

## Problems – In class

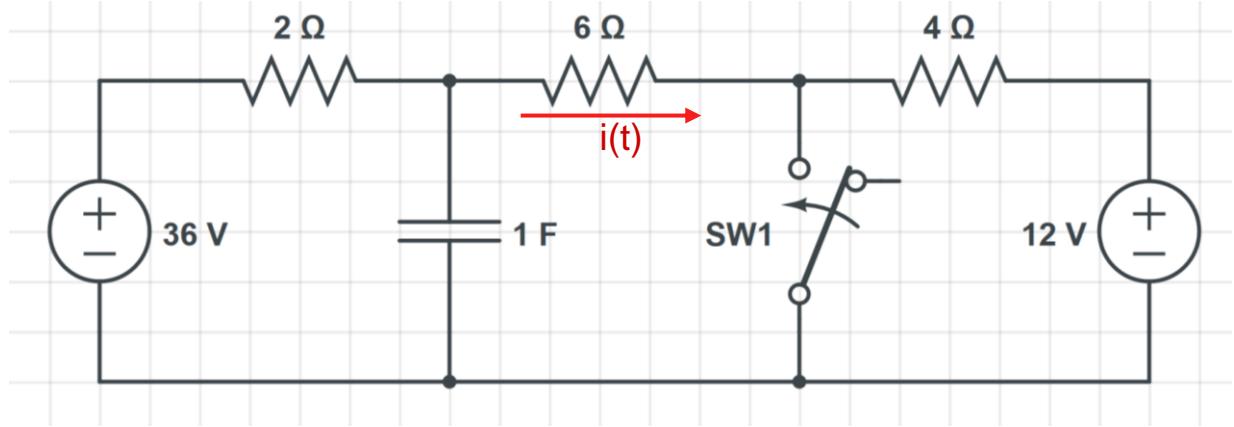**Problem 3:** In the following circuit, the switch is operated at  $t=0$ . Determine the current  $i(t)$  for all times.



$$v_c(0^-) = v_c(0^+) = 32V$$

$$i(0+) = \frac{32}{6} = \frac{16}{3}A$$

$$i(\infty) = \frac{36}{8} = 4.5A$$


$$i(t) = K_1 + K_2 e^{-t/\tau}, \quad K_1 = i(\infty) = 4.5A, \quad K_2 = i(0^+) - i(\infty) = 5/6A$$

$\tau = R_{eq}C$ ,  $c = 1F$ ,  $R_{eq} = \frac{4}{3}\Omega \Rightarrow \tau = 1.33$  seconds. Here  $R_{eq}$  is the equivalent resistance that appears across capacitor, that is, the parallel combination of 6 and 2 Ohms.

# First Order Circuits

## Problems – In class

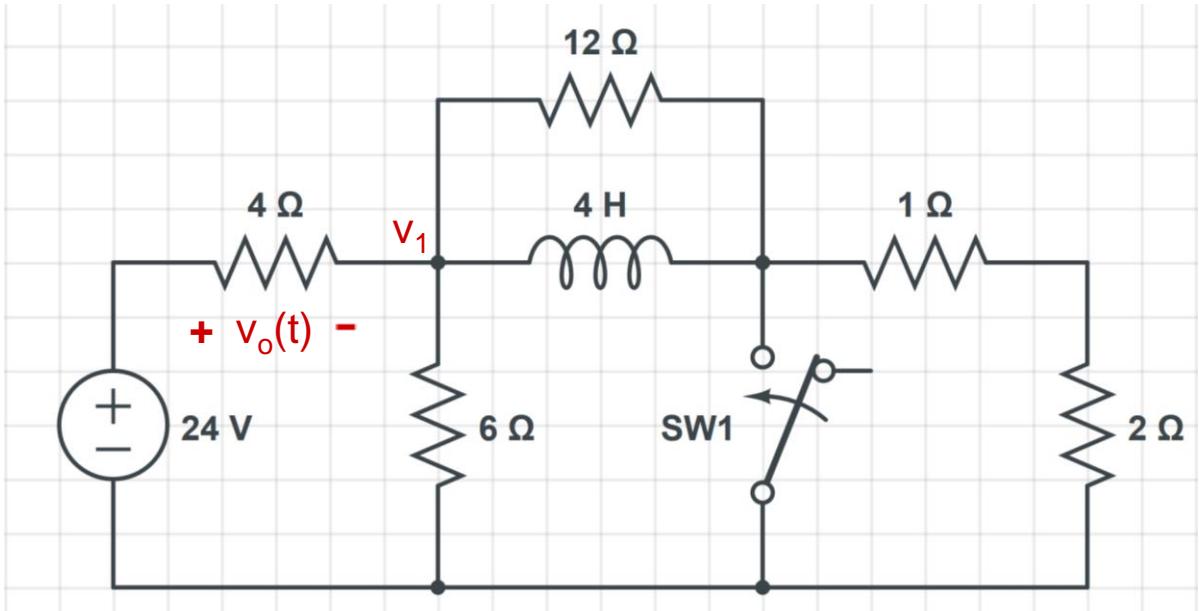**Problem 4:** In the following circuit, the switch is operated at  $t=0$ . Determine the voltage  $v_o(t)$  for all times.



$$i_L(0^-) = i_L(0^+) = \frac{8}{3}A$$

$$v_o(\infty) = 24V$$

To find out  $i(0+)$ , we use KCL to find  $v_1$  considering the bottom node as ground: (equation of the circuit at  $t = 0^+$ )

$$\frac{v_1 - 24}{4} + \frac{v_1}{6} + \frac{v_1}{12} + \frac{8}{3} = 0, \quad \Rightarrow v_1 = \frac{20}{3}V$$

$$v_o(0^+) = 24 - v_1 = \frac{52}{3}V$$

$$v_o(t) = K_1 + K_2 e^{-t/\tau}, \quad K_1 = v_o(\infty) = 24V, \quad K_2 = v_o(0^+) - v_o(\infty) = -\frac{20}{3}V$$

$\tau = \frac{L}{R_{eq}}$ ,  $L = 4H$ ,  $R_{eq} = 2\Omega \Rightarrow \tau = 2$  seconds. Here  $R_{eq}$  is the equivalent resistance that appears across inductor, that is, the parallel combination of 12, 6 and 4 Ohms.