

Second-Order Circuits

SOLUTIONS

Problem 01


* First analyze circuit at $t=0^-$

- Inductor; SC
- Capacitor; OC

$$V_C(0^-) = 0V = V_C(0)$$

$$i_L(0^-) = \frac{12}{6} = 2A = i_L(0)$$

$$\Rightarrow \boxed{i(0) = 2A}$$

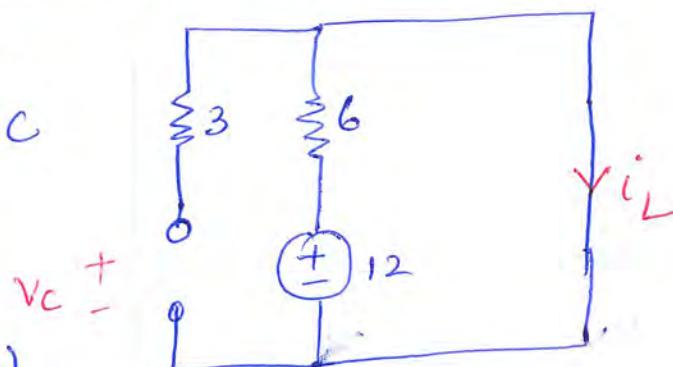

$$i(0) = i_L = 2A$$

Circuit is simple RLC series at $t=0^+$.

$$L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt = 0 \quad - \textcircled{01}$$

At $t=0^+$

$$L \frac{di}{dt}(0) + R i(0) + 0 = 0$$

$$\Rightarrow \frac{di}{dt}(0) = -\frac{(2)(3)}{2} = \underline{-3 \text{ A/sec}}$$

* Solve for $i(t)$

Take derivative of $\textcircled{01}$

$$\Rightarrow L \frac{d^2i}{dt^2} + R \frac{di}{dt} + \frac{i(t)}{C} = 0$$

$$\Rightarrow \frac{d^2i}{dt^2} + \frac{3}{2} \frac{di}{dt} + \frac{i(t)}{2} = 0$$

Characteristic Equation :-

$$s^2 + \frac{3}{2}s + \frac{1}{2} = 0 \Rightarrow s = -1, -\frac{1}{2}$$


$$\Rightarrow i(t) = K_1 e^{-t} + K_2 e^{-t/2}$$

$$i(0) = 2 = K_1 + K_2$$

$$\frac{di}{dt}(0) = -3 = -K_1 - \frac{K_2}{2}$$

$$\Rightarrow \boxed{K_2 = -2} \Rightarrow \boxed{K_1 = 4}$$

$$i(t) = \begin{cases} 0 \text{ A} & t < 0 \\ 2 \text{ A} & t = 0 \\ 4e^{-t} - 2e^{-t/2} \text{ A} & t \geq 0 \end{cases}$$

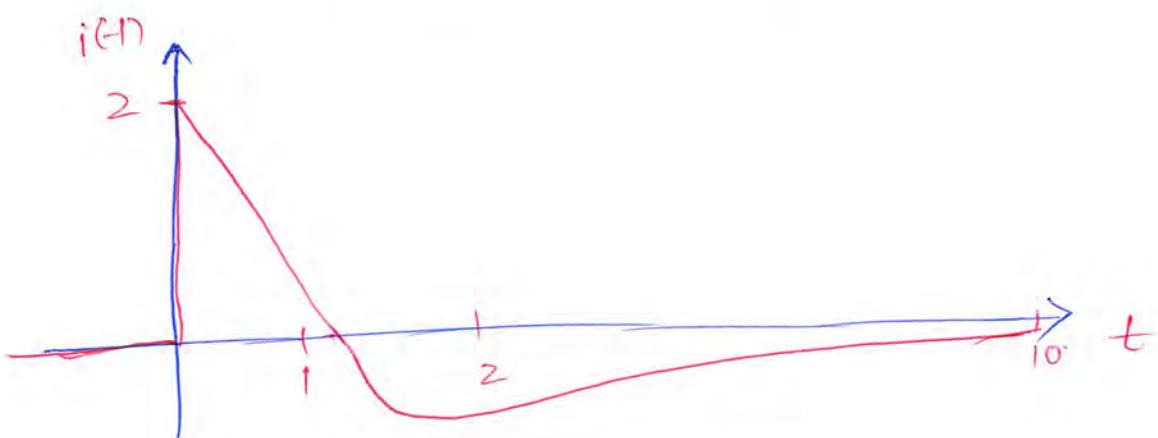

Problem 02

* Analyze circuit at $t=0^-$

Inductor: $\propto C$


Capacitor: $\propto C$

$$v_C(0^-) = 0 = v_C(0^+)$$

$$i_L(0^-) = 2 = \underline{i_L(0^+)}$$

$$V_o(0) = (-2)(2) = \underline{-4V}$$

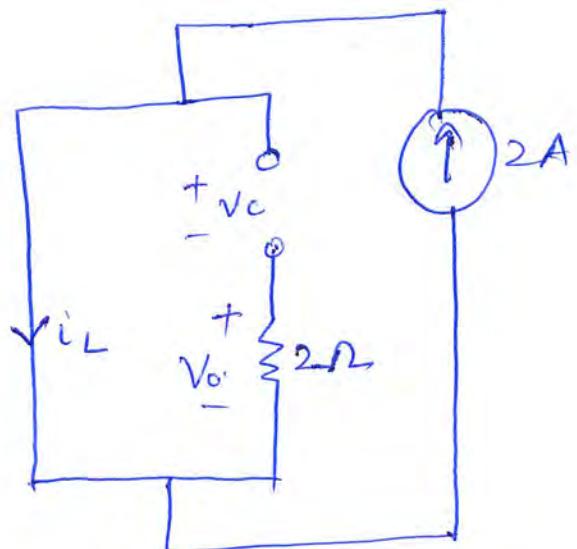\Rightarrow we have series RLC
at $t=0^-$




$$\Rightarrow L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt = 0$$

$t=0^+$

$$\Rightarrow \frac{di(0^+)}{dt} = -\frac{R}{L} i(0^+)$$

$$= -(4)(2) = -8 \text{ A/sec}$$

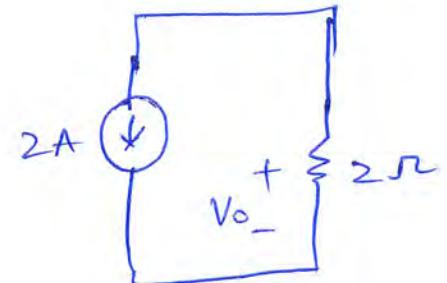

* Here $i(+)$ is taken as

the current in the counter-clockwise

direction, that is, $i = i_L$

$$\therefore V_o = -iR$$

$$\frac{dV_o}{dt}(0^+) = -\frac{di(0^+)}{dt}(R) = \underline{+16 \text{ V/sec}}$$

* Solve for $i(+)$ or $\underline{V_o(+) = -\frac{i(+)}{R} R}$

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i(+) = 0$$

$$\Rightarrow -\frac{1}{R} \frac{d^2 v_o(t)}{dt^2} \cancel{\oplus} \frac{1}{L} \frac{dv_o}{dt} + \frac{1}{RLC} v_o(t) = 0$$

$$\Rightarrow \frac{d^2 v_o(t)}{dt^2} + \frac{R}{L} \frac{dv_o}{dt} + \frac{1}{LC} v_o(t) = 0$$

$$\Rightarrow \frac{d^2 v_o}{dt^2} + 4 \frac{dv_o}{dt} + 3 v_o(t) = 0$$

$$\Rightarrow s^2 + 4s + 3 = 0 \Rightarrow s_1 = -1, s_2 = -3$$


$$\Rightarrow v_o(t) = K_1 e^{-t} + K_2 e^{-3t}$$

$$v_o(0) = -4 = K_1 + K_2$$

$$\frac{dv_o(0)}{dt} = 16 = -K_1 - 3K_2$$

$$\Rightarrow \boxed{K_2 = 6}, \boxed{K_1 = -14/2}$$

$$\Rightarrow \boxed{v_o(t) = 2e^{-t} - 6e^{-3t} V}$$

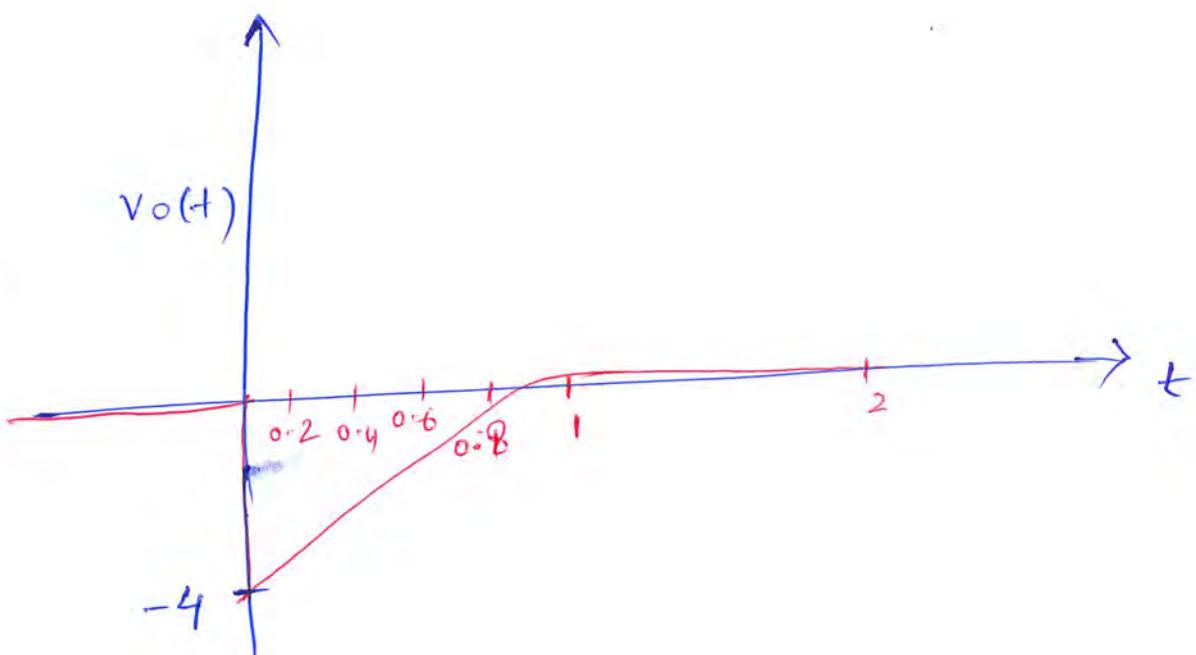


Problem 03.

* Analyse Circuit at $t=0^-$

$$i_L(0^-) = \boxed{2 \text{ A}}$$
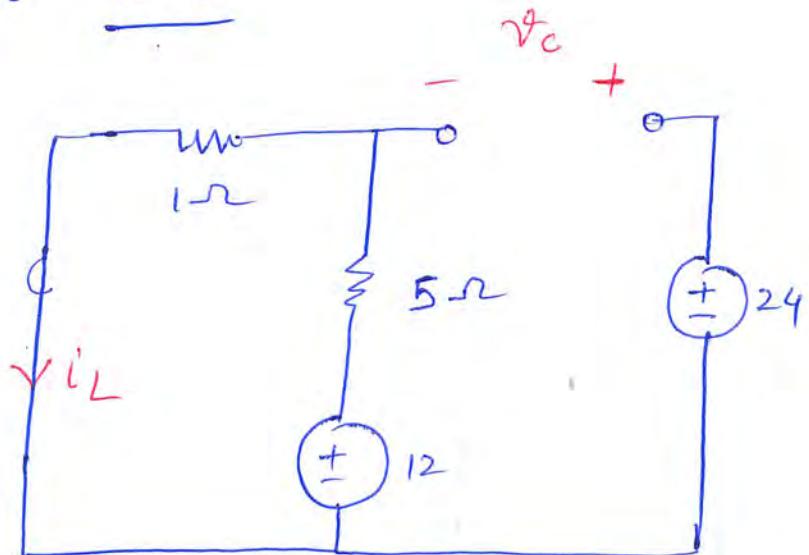
$$\begin{aligned} v_C(0^-) &= 24 - 2 \\ &= \boxed{22 \text{ V}} \\ &= v_C(0^+). \end{aligned}$$




At $t=0^+$,

current through capacitor

is i_L

$$\Rightarrow i_L(0^+) = C \frac{dv_C(0^+)}{dt}$$

$t=0^+$

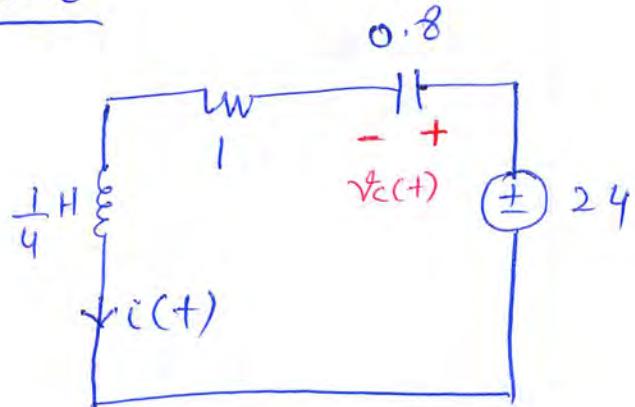

$$\Rightarrow \frac{dv_C(0^+)}{dt} = \frac{i_L(0^+)}{C} = 2.5 \text{ V/sec.}$$

Solve for $i(t)$

$$\frac{1}{4} \frac{di}{dt} + i + \frac{1}{0.8} \int i = 24$$

$$\Rightarrow \frac{d^2i}{dt^2} + 4 \frac{di}{dt} + 5i = 0$$

$$s^2 + 4s + 5 = 0 \Rightarrow s_1, s_2 = -2 \pm 1i$$

$$i(t) = e^{-2t} (K_1 \cos t + K_2 \sin t).$$

$$i(0) = \boxed{K_1 = 2}.$$

To find $\frac{di(0^+)}{dt}$,

$$\frac{1}{4} \frac{di}{dt}(0^+) + i(0^+) + \frac{1}{6\pi} v_c(0^+) = 24$$

$$\frac{di}{dt}(0^+) = 4(24 - 24) = 0$$

Use to find K_2

$$\Rightarrow \frac{di(0)}{dt} = e^{-2t} (-K_1 \sin t + K_2 \cos t) \Big|_{t=0} = 0,$$

$$\quad \quad \quad + 2e^{-2t} (K_1 \cos t + K_2 \sin t) \Big|_{t=0}$$

$$= K_2 - 2K_1 = 0 \Rightarrow \boxed{K_2 = 4}$$

$$i(t) = e^{-2t} (2 \cos t + 4 \sin t)$$

$$\text{Now } v_c(t) = 24 - i(t) - \frac{1}{4} \frac{di}{dt}$$

$$= 24 - e^{-2t} (2 \cos t + 1.5 \sin t)$$

Problem 04

$t = 0^-$

$$i_L(0^-) = i_o(0^-) = \frac{12}{24} = 0.5A$$


$$v_C(0^-) = v_C(0^+) = 0V$$

$t = 0^+$

$$i_o(0^+) = 0.5A$$

$$18\dot{i}_o + L \frac{di_o}{dt} + 36 \int i_o dt = 8$$

$\checkmark v_C(0^+) = 0$

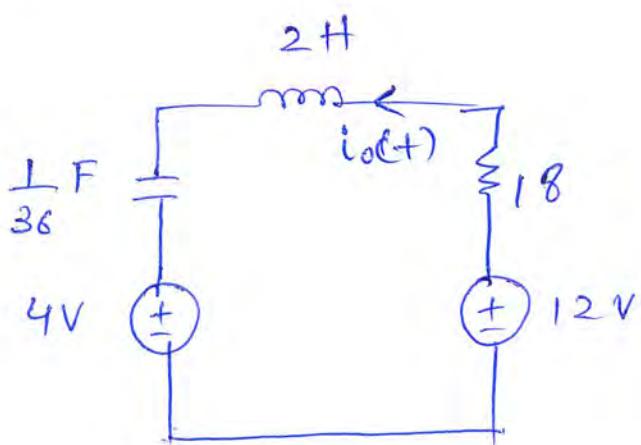

$$\Rightarrow \frac{di_o}{dt}(0^+) = \frac{(8 - 9)}{2} = -0.5 A/\text{sec.}$$

Solve for i_o :

$$2 \frac{d^2 i_o}{dt^2} + 18 \frac{di_o}{dt} + 36 i_o = 0$$

$$\Rightarrow s^2 + 9s + 18 = 0$$

$$s_1 = -6, s_2 = -3$$

$$\Rightarrow i_o(t) = K_1 e^{-3t} + K_2 e^{-6t}$$

$$K_1 + K_2 = 0.5$$

$$-3K_1 - 6K_2 = -0.5$$

$K_1 = \frac{5}{6}$
$K_2 = -\frac{1}{3}$

Problem 05

6-25

* We first analyze circuit at $t = 0^-$

* Find $i(t)$ at $t = 0^-$

* Circuit is in steady state; $i(t) = i_p(t)$

Equation for $i(t)$: $\boxed{R \frac{di}{dt} + Ri + \frac{1}{C} \int i = 100 \sin 377t}$ —(01)

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = (100)(377) \cos 377t$$

$$\Rightarrow \frac{d^2i}{dt^2} + 10^3 \frac{di}{dt} + (2 \times 10^6)i = (37700) \cos 377t \quad \text{---(02)}$$

$$i_p(t) = A \cos 377t + B \sin 377t$$

$$\Rightarrow \boxed{A = 0.0195} \quad \boxed{B = 0.0040} \quad \text{After substituting } i_p(t) \text{ in (02)}$$

$$i(t) = (0.0195 \cos 377t + 0.0040 \sin 377t) \text{ Ampes } t < 0$$

* Inductor ensures $i(0^+) = i(0^-) = \underline{0.0195} \text{ Ampes}$

$$* V_C(0^-) = -R i(0) - L \frac{di}{dt} \Big|_{t=0^-}$$

$$= -10^3(0.0195) - (1)(377)(0.0040)$$

$$= -21.0080 \text{ Volts}$$

Now analyze at $t = 0^+$

$$\frac{di}{dt} + \frac{1}{LC} \int i = 100 \sin 377t$$

$$\frac{d^2i}{dt^2} + \frac{i}{LC} = (100) (377) \cos 377t$$

(03)

$$\frac{d^2i}{dt^2} + (2 \times 10^6) = (37700) \cos 377t$$

$$i(t) = i_c(t) + i_p(t)$$

$$i_p(t) = A \cos 377t + B \sin 377t$$

$$A = 0.0203, \quad B = 0$$

$$\underline{i_c(t) = ?}$$

$$s^2 + 2 \times 10^6 s = 0 \Rightarrow s_1, s_2 = j1414.2, -j1414.2$$

$$\Rightarrow i_c(t) = K_1 \cos 1414.2t + K_2 \sin 1414.2t$$

Find K_1 and K_2 ?

$$i(0) = 0.0195 = K_1 + 0.0203 \Rightarrow K_1 = -8 \times 10^{-4}$$

* To find K_2 ; we first find $\frac{di}{dt}(0^+)$ using (03)

$$\frac{di}{dt}(0^+) = -\sqrt{c} = 21.0080 \text{ A/sec}$$

$$377(B) + (1414.2)(K_2) = 21.0080 \Rightarrow K_2 = 149 \times 10^{-4}$$

$$\Rightarrow i(t) = 0.0203 \cos 377t + 10^{-4} \left[-8 \cos 1414.2t + 149 \sin 1414.2t \right] A$$