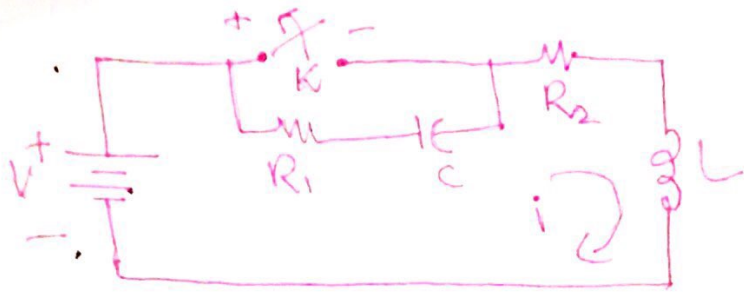


QUIZ 07 SEC 02 SOLUTION



at time $t = 0^-$:




$$v_K(0^-) = 0 \quad (1)$$

$$v_C(0^-) = v_{R2}(0^-) = 0 = v_C(0^+) \quad (1)$$

$$i(0^-) = \frac{V}{R_2} = i(0^+) \quad (1)$$

at time t :

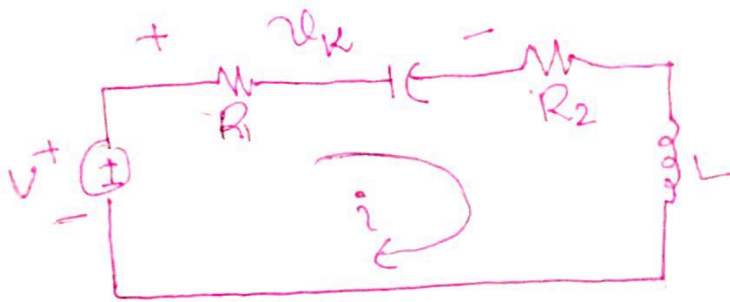

Loop equation:

$$v_K + iR_2 + L \frac{di}{dt} = V \quad \text{--- (1) (2)}$$

at time $t = 0^+$:

$$v_K(0^+) = iR_1 + v_C(0^+)$$

$$v_K(0^+) = \frac{VR_1}{R_2} \quad \text{--- (2) (2)}$$

putting (2) in (1):

$$\frac{VR_1}{R_2} + \frac{VR_2}{R_2} + L \frac{di}{dt} = V$$

$$\frac{di}{dt} = - \frac{VR_1}{R_2 L} \text{ A/S} \quad (3)$$