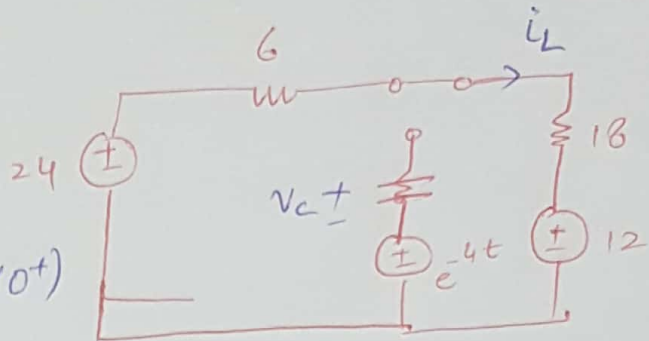


Quiz - 09

Section 01

Solution




At $t = 0^-$

Inductor sc

$$i_L(0^-) = \frac{24 - 12}{24} = 0.5A = i_L(0^+)$$

$$v_c(0^-) = v_c(0^+) = 0$$

At $t = 0^+$ (Series RLC network)

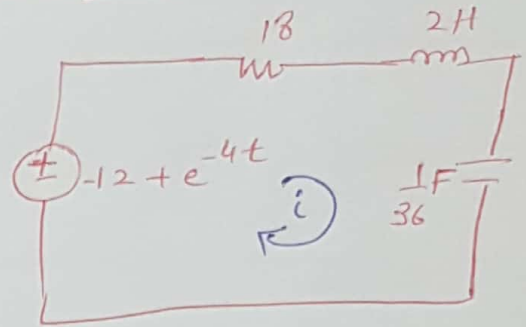

$$2 \frac{di}{dt} + 18i + \frac{1}{C} \int i dt = e^{-4t} - 12 \quad (1)$$

$$\Rightarrow \boxed{\frac{d^2 i}{dt^2} + 9 \frac{di}{dt} + 18i = -2e^{-4t}} \quad (2)$$

$$i_p(t) = A e^{-4t}$$

$$16Ae^{-4t} - 9Ae^{-4t} + 18Ae^{-4t} = -2e^{-4t}$$

$$\Rightarrow \boxed{A = \frac{-2}{25}}$$

$i_c(t)$; Auxiliary equation

$$s^2 + 9s + 18 = 0 \Rightarrow s_1 = -3, s_2 = -6$$

$$\boxed{i_c(t) = K_1 e^{-3t} + K_2 e^{-6t}}$$

$$\boxed{i(t) = K_1 e^{-3t} + K_2 e^{-6t} - \frac{2}{25} e^{-4t}}$$

* Use initial conditions to find K_1 and K_2

$$i(0) = i_L(0^+) = 0.5A = K_1 + K_2 - \frac{2}{25}$$

$$\frac{di}{dt}(0^+) = \frac{1 - 12 - 18i(0^+)}{2} = -10A/sec = -3K_1 - 6K_2 - \frac{8}{25}$$

$$\Rightarrow \boxed{K_1 = -2.28, K_2 = 2.86}$$

$$\boxed{v_o(t) = 18 i(t) = -2.28e^{-3t} + 2.86e^{-6t} - \frac{2}{25} e^{-4t}, t \geq 0}$$