

EE240: Circuits I

ASSIGNMENT 1

Due Date: 24 Sep 2019

- Submissions will only be accepted on A4 sized papers.
 - Write your name and roll number clearly at the top of the assignment.
 - You are required to show working where necessary; answers will not be graded if working is not shown.
 - The assignment is worth **100** marks, you are advised to start early as it is long.
 - Feel free to contact the instructor or teaching assistants if you have any questions.
 - Any instance of plagiarism will be **severely** dealt with; such cases would be subjected to **disciplinary action** in accordance with the university rules and regulations.
-

Course Learning Outcomes Covered:

CLO1: Derive and apply working principle of passive components R, L,C and independent and controlled energy sources for device and circuit modeling and analysis

Problem 1 (11 marks)

- (a) [3 marks] A 24V battery is connected to a motor. The battery provides a current of 250mA. The motor is switched on, calculate the energy it consumed in 2 hours.
- (b) [4 marks] The current through an element is given by $i(t) = (5 - 2t)^2$ A for $t \geq 0$. Give an expression for the charge in the element.
- (c) [4 marks] The charge entering a terminal is given by the equation:

$$q(t) = 4\sin\left(2\pi t + \frac{\pi}{3}\right) - \cos\left(\frac{5\pi t}{2}\right) \text{mC}$$

Calculate the current flowing through it at $t = 1$ s.

Problem 2 (10 marks)

- (a) [3 marks] A simple circuit consists of a 12V battery connected in series with a light bulb.
- (i) If the battery supplies a current of 1.3 A for 2 minutes to the bulb, calculate the energy dissipated across the bulb.
- (ii) If 3.7kJ of energy was dissipated across the bulb in 8 seconds, calculate the current flowing through the circuit.
- (b) [1 mark] How much energy does a charge of -45 mC require to move across a potential difference of 5V? Recall that charges can be negative too.
- (c) [6 marks] The following current flows from the positive to the negative terminal of a device. Calculate the total charge that enters the positive terminal.

$$i(t) = \begin{cases} 4t & ; & 0 < t \leq 3 \\ 3t^2 + 2 & ; & 3 < t \leq 7 \\ -7t + 1 & ; & 7 < t \leq 9 \\ 5 & ; & 9 < t \leq 13 \\ 0 & ; & \text{otherwise} \end{cases}$$

Problem 3 (10 marks)

The charge entering a positive terminal of a device is given by $q(t) = -12e^{-2t}$ mC, and the power is given by $p(t) = 3e^{-8t}$ W. In the time interval $0 \leq t \leq 500$ ms, compute the following:

- (a) [3 marks] The current across the device.
- (b) [3 marks] The voltage across the device.
- (c) [4 marks] The energy delivered to the device.

Problem 4 (10 marks)

(a) [5 marks] Find the equivalent capacitance across points A and B

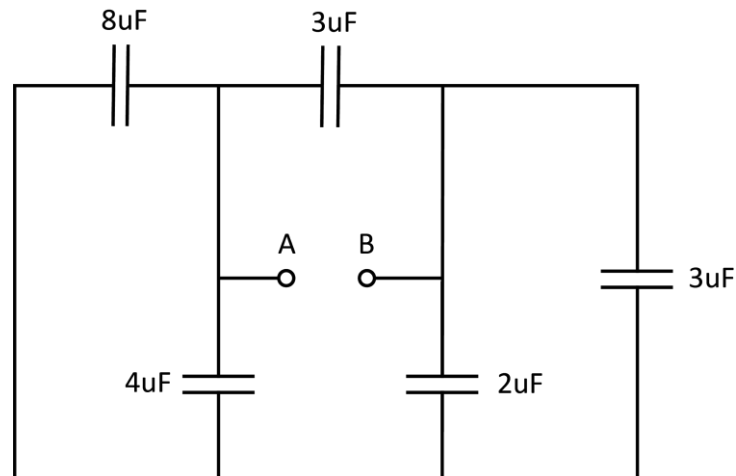


Figure 1

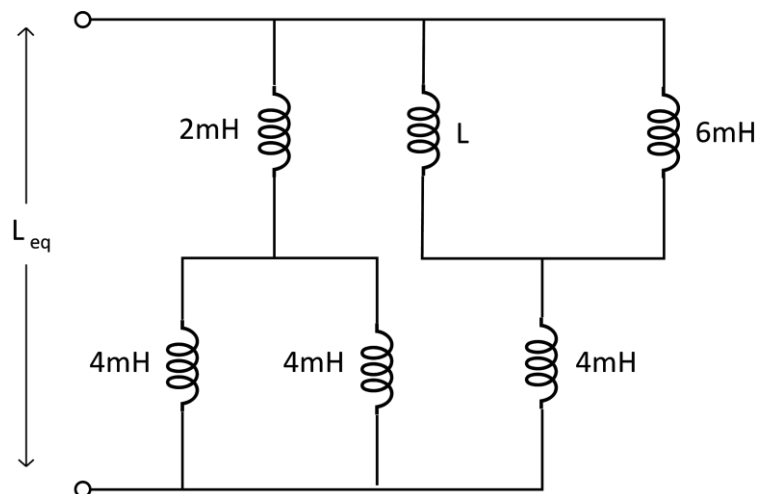
(b) [5marks] Given that L_{eq} is 2.4mH, calculate the value of L.

Figure 2

Problem 5 (10 marks)

(a) [5 marks]

(i) Find R_{eq} for the following circuit.

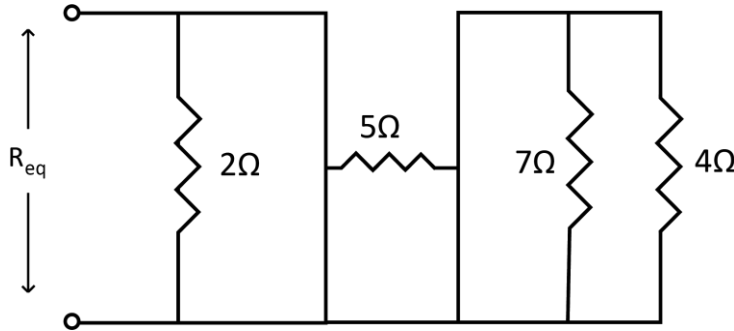


Figure 3

(ii) You are provided with 4 resistors, each rated at 1Ω . Design a circuit using **all** resistors provided, connecting in series and parallel combinations; the circuit should have an equivalent resistance of 1.33Ω . There may be more than 1 configurations, but you are only required to make one.

(b) [5 marks] Each resistor in the following figure is rated at 4Ω . Find the equivalent resistance across terminals A and B.

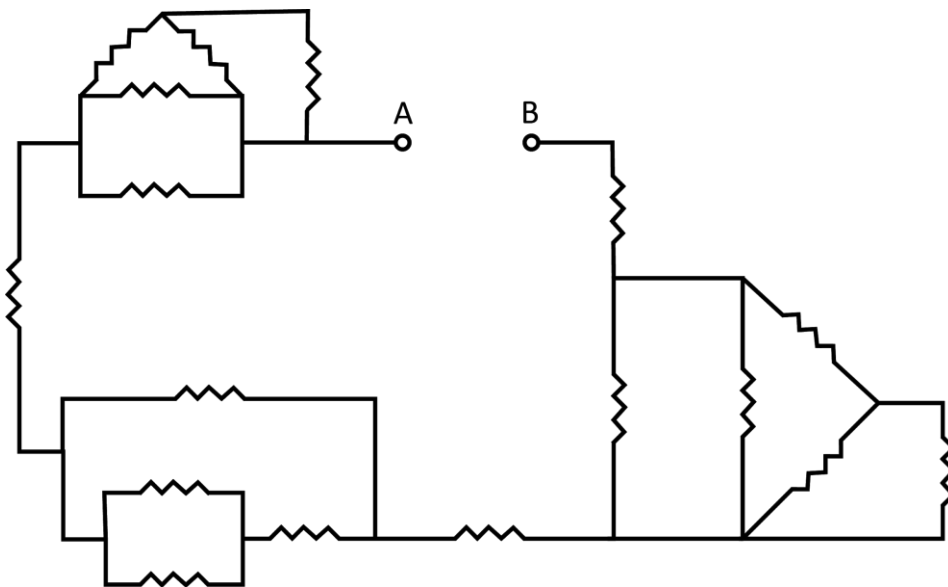


Figure 4

Problem 6 (8 marks)

A parallel-plate capacitor with capacitance $10\mu\text{F}$ is connected to a 24V DC voltage source.

- [2 marks] What is the charge on each of its plates?
- [3 marks] Calculate the charge if the area of the plates is doubled but the separation is kept constant.
- [3 marks] Calculate the charge if the separation is quadrupled and the area is halved.

Problem 7 (6 marks)

(a) [2 marks] A solenoid has a radius of 10 mm and an average length of 0.5 m. If the number of turns is 200, calculate the self-inductance of the coil.

(b) [4 marks] A 50mH inductor is connected with a 12V battery and a 2Ω resistor in series.

Sketch waveforms (with appropriate labels) for:

- the current in the circuit.
- potential difference across the inductor.
- potential difference across the resistor.

Problem 8 (10 marks)

The waveform given below shows the current through a $1\mu\text{F}$ capacitor. Initial voltage across the capacitor is 0V, i.e. $v(0) = 0\text{V}$.

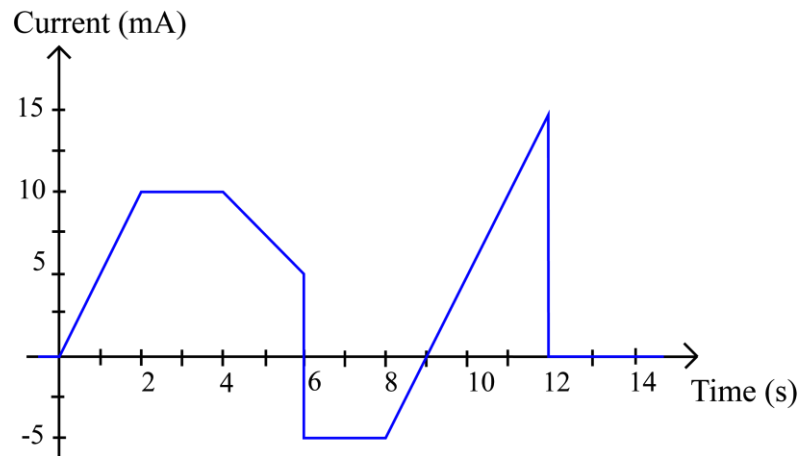


Figure 5

- [5 marks] Sketch the voltage waveform, all relevant points should be **labelled**.
- [2 marks] Calculate the instantaneous power at $t = 4\text{s}$.
- [3 marks] Compute the energy delivered to the capacitor at $t = 3\text{s}$.

Problem 9 (8 marks)

The waveform below shows the current across a 2mH inductor over time.

- (a) [5 marks] Plot the waveform for the voltage over the same time period
 (b) [3 marks] Find the energy stored in the inductor at $t = 5\text{ms}$.

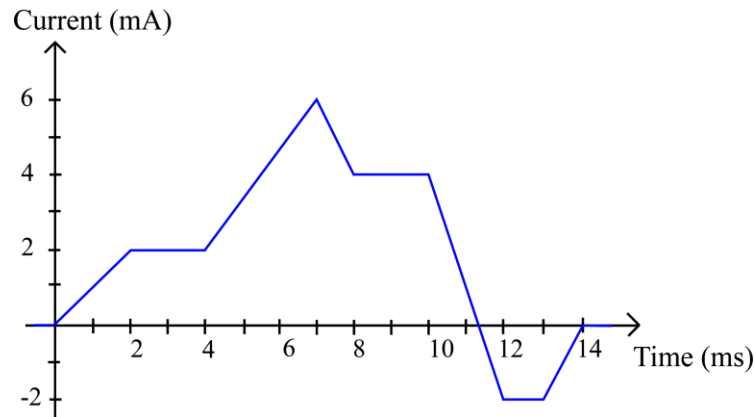


Figure 6

Problem 10 (8 marks)

The voltage and current across an element are given by:

$$v(t) = 30 - 30e^{-15t}\text{V}$$

$$i(t) = 75e^{-15t}\text{mA}$$

for $t \geq 0$, and they are zero otherwise.

- (a) [2 marks] Give an expression for the instantaneous power across the element.
 (b) [3 marks] At what time is maximum power delivered to the element?
 (c) [3 marks] Calculate the total energy supplied to the element.

Problem 11 (9 marks)

The independent current source in the circuit shown generates the following current:

$$\begin{cases} i(t) = 0 & ; & t \leq 0 \\ 14te^{-2t}\text{A} & ; & t > 0. \end{cases}$$

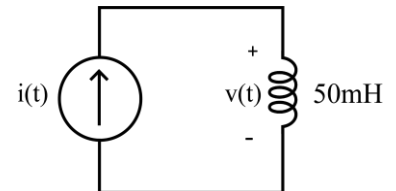


Figure 7

- (a) [2 marks] Sketch the waveform for the current through the inductor.
 (b) [2 marks] At what instant is the current maximum?
 (c) [3 marks] Express the voltage across the inductor as a function of time.
 (d) [2 marks] Plot the voltage waveform.