
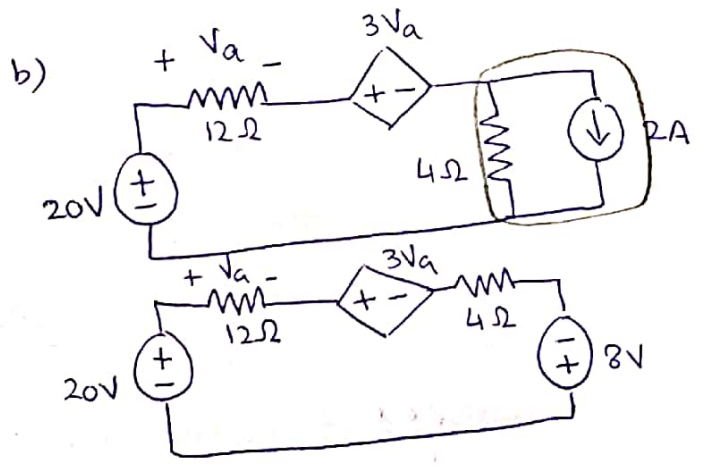


$$i_o = \frac{2.71}{(8 + 1.43) \times 10^3}$$

$i_o = 0.287 \text{ mA}$ ANS

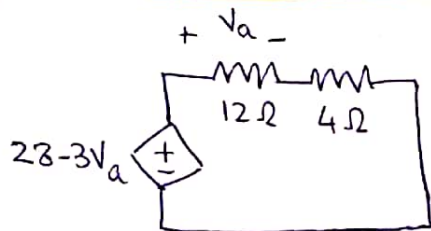



$$V_a = \frac{12}{16} \times (28 - 3V_a)$$


$$V_a = 21 - 2.25V_a$$

$$3.25V_a = 21$$



$$V_a = 6.46V$$

$$i_o = \frac{6.46}{12}$$

$$i_o = 0.538A$$

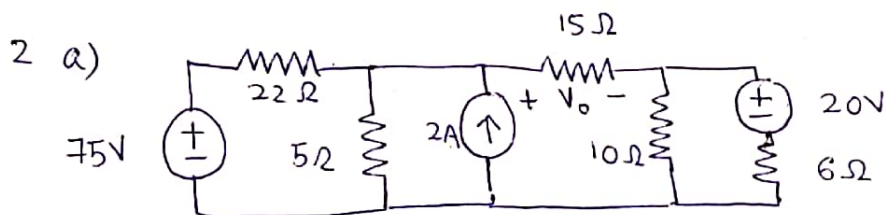

using 75V source: 15Ω

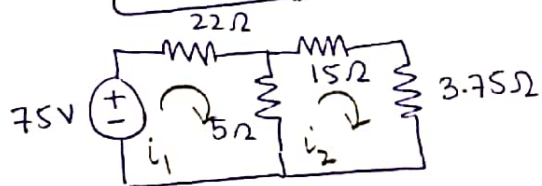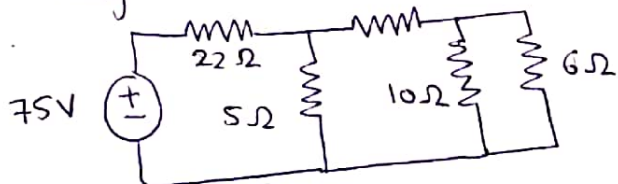

$$75 = 22i_1 + 5i_1 - 5i_2$$

$$27i_1 - 5i_2 = 75 \quad (1)$$

$$5i_2 - 5i_2 + 15$$

$$5i_2 - 5i_1 + 15i_2 + 3.75i_2 = 0$$

$$23.75i_2 - 5i_1 = 0 \quad (2)$$

* solving (1) & (2) simultaneously




$$i_1 = 2.89A$$

$$i_2 = 0.609A$$

$$V_{o(75V)} = 15 \times 0.609$$

$$V_{o(75V)} = 9.13V$$



using 2A source:

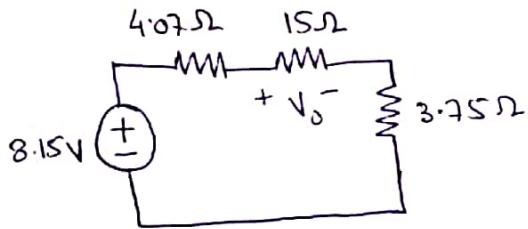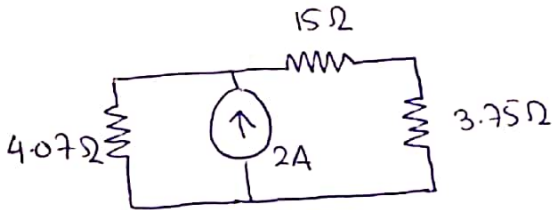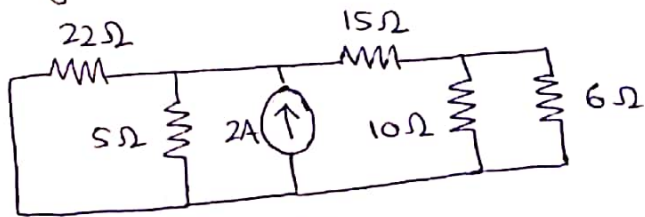

$$V_o(2A) = \frac{15}{15 + 3.75 + 4.07} \times 8.15$$

$$V_o(2A) = 5.36 \text{ V}$$

using 20V source:

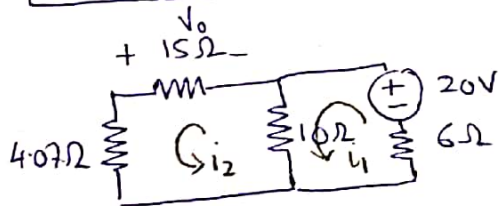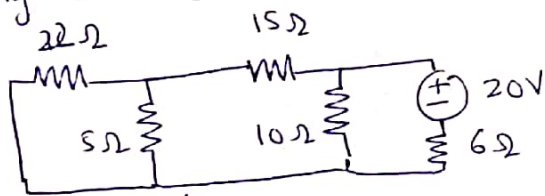

$$20 = 6i_1 + 10i_1 - 10i_2$$

$$16i_1 - 10i_2 = 20 \quad (1)$$

$$10i_2 - 10i_1 + 15i_2 + 4.07i_2 = 0$$

$$29.07i_2 - 10i_1 = 0 \quad (2)$$

solving (1) & (2) simultaneously

$$i_2 = 0.548 \text{ A}$$


since i_2 is flowing from - to +, V_o will be negative

$$V_o(20V) = -0.548 \times 15$$



$$V_o(20V) = -8.22 \text{ V}$$

$$V_o = 9.13 + 5.36 - 8.22$$
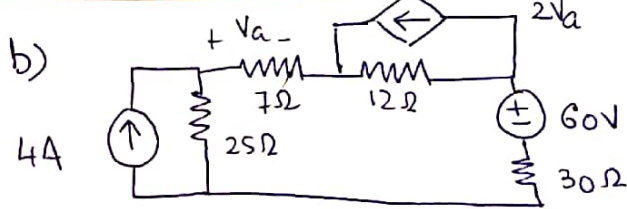
$$V_o = 6.27 \text{ V} \quad \text{ANS}$$



using 4A source:

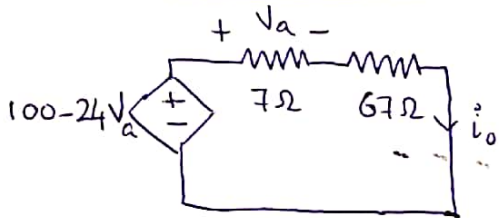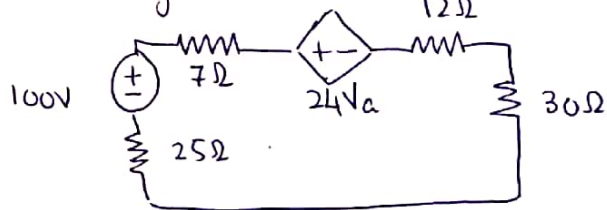

$$V_a = \frac{7}{74} \times (100 - 24V_a)$$

$$74V_a = 700 - 168V_a$$

$$242V_a = 700$$

$$V_a = 2.89V$$



$$i_o(4A) = \frac{2.89}{7}$$

$$i_o(4A) = 0.413A$$

$$i_o = 0.413 - 0.248$$

$$i_o = 0.165A \quad \text{ANS}$$

using 60V source:

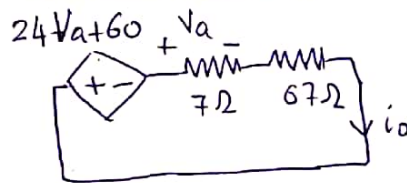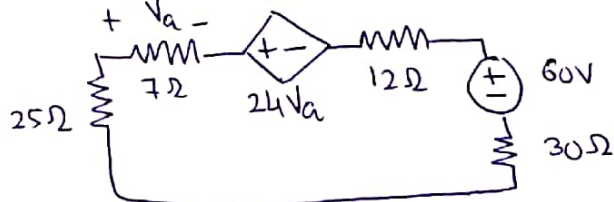

* since flow of current is from negative to positive in the 7Ω resistor, V_a will be negative

$$V_a = -\frac{7}{74} \times (24V_a + 60)$$

$$74V_a = -168V_a - 420$$


$$242V_a = -420$$

$$V_a = -1.735V$$


$$i_o(60V) = \frac{-1.735}{7}$$

$$i_o(60V) = -0.248A$$

Q3-

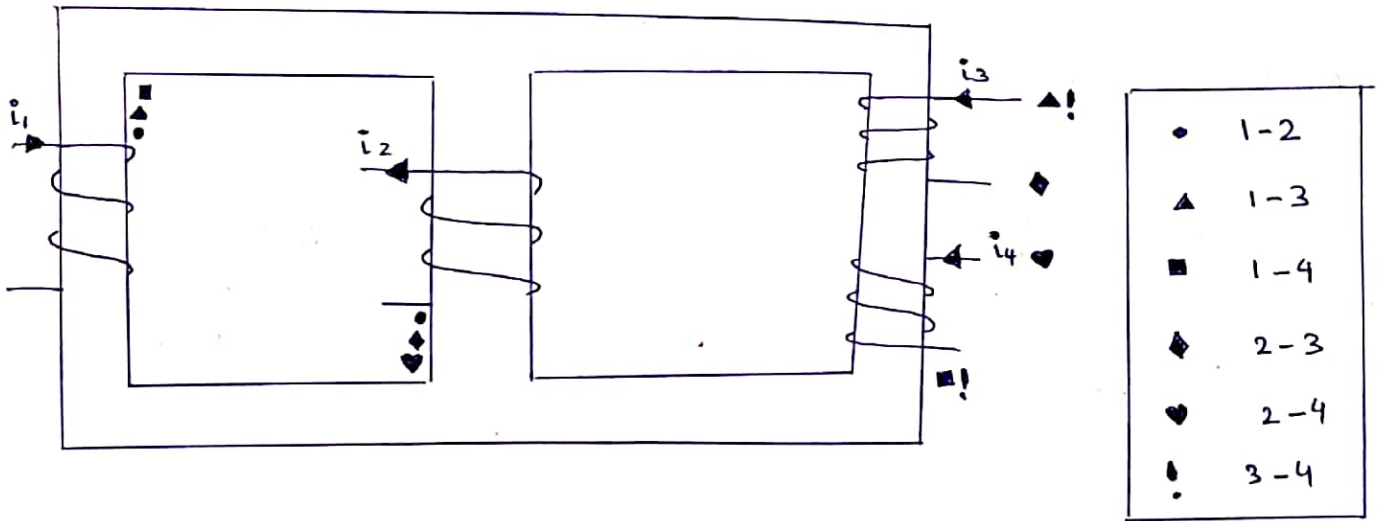


Q4-

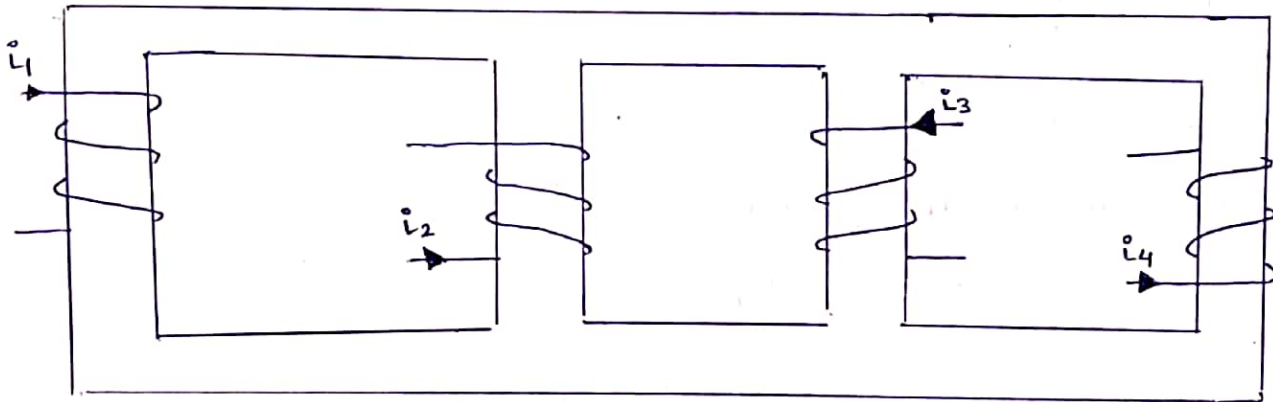


Q5-

① Using source transformation :

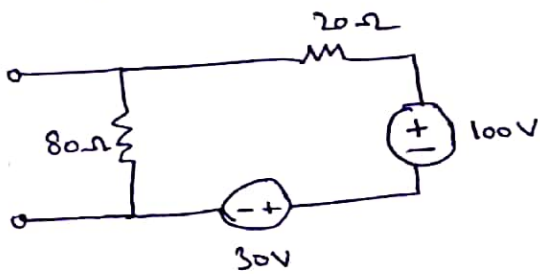

\Rightarrow

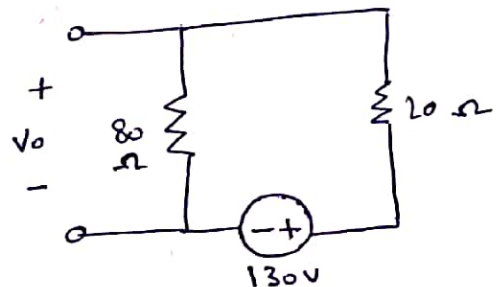


$$V_0 = \frac{80}{80+20} \times 130 = 104 \text{ V} \quad \underline{\underline{\text{Ans.}}}$$

(voltage division rule)

② Using principle of superposition


1) 5A off \rightarrow open circuit

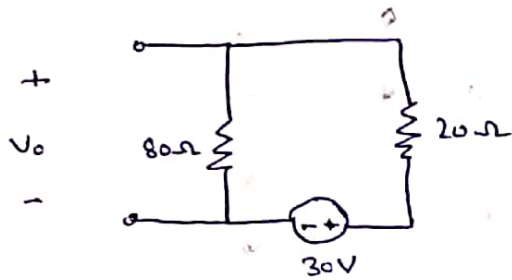

V_o using potential divider :

$$V_o = \frac{80}{80+20} \times 30 = 24 \text{ V}$$

2) 30V off \rightarrow short circuit

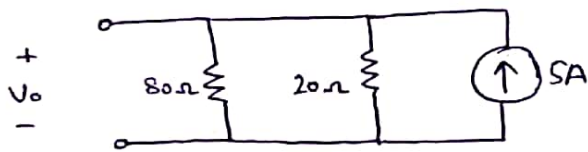

Let current through 80Ω resistor = i_o

i_o (using current division rule)

$$= \frac{20}{80+20} \times 5 = 1 \text{ A}$$

$$\therefore V_o = iR = 80 \text{ V}$$

$$\Rightarrow \text{Total } V_o = 24 + 80$$

$$= 104 \text{ V } \underline{\underline{\text{Ans.}}}$$

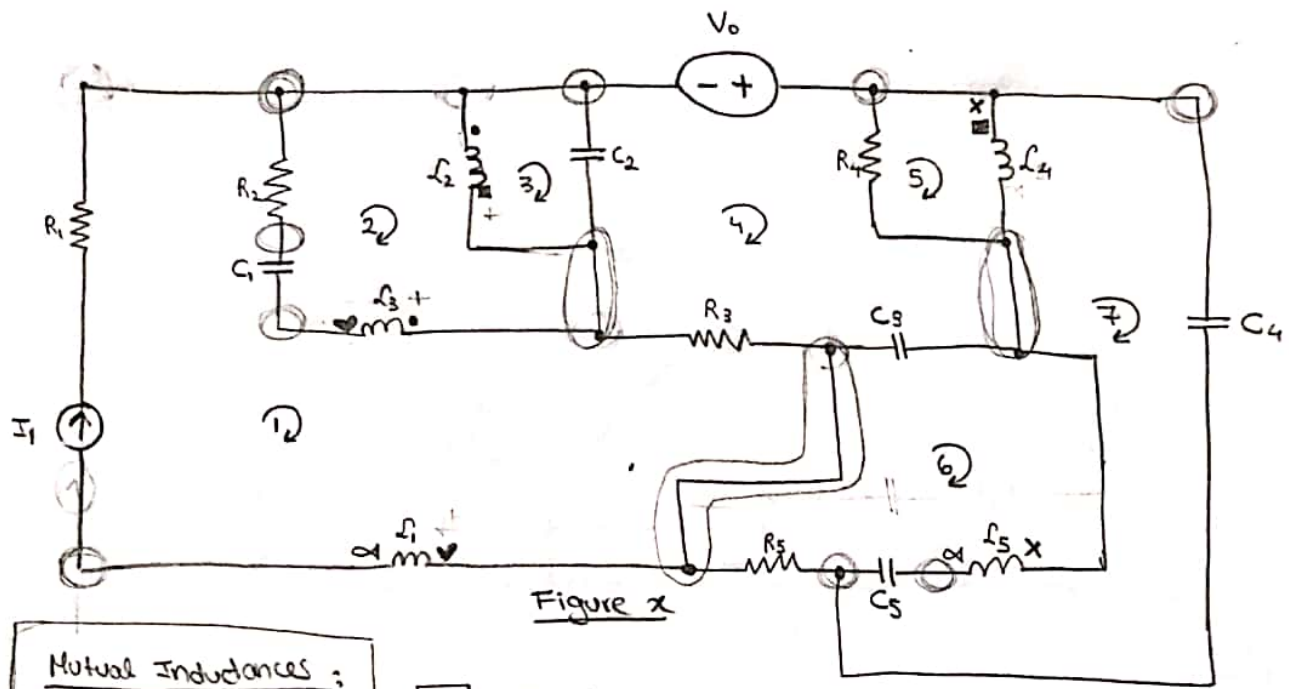


Figure X

Mutual Inductances :
 $L_1 \& L_3 = M_a$
 $L_1 \& L_5 = M_b$
 $L_2 \& L_3 = M_c$
 $L_2 \& L_4 = M_d$
 $L_4 \& L_5 = M_e$

Q: For the circuit given below with the stipulated mutual inductances, apply Mesh Analysis to write the complete set of loop equations. You may define your own loops & loop currents. (Hint: Pay attention to dot convention)

b) For the same circuit, identify the # of nodes & label them on the diagram. How many nodal equations will this circuit yield?

c) GRAPHS & TREES :
 1pt i) Calculate the # of branches in this circuit
 2pt ii) Draw the graph of the circuit
 2pt iii) Draw a tree.

1 $R_1(I_1) + R_2(I_1 - I_2) + \frac{1}{C_1} \int (I_1 - I_2) dt + L_3 \frac{d(I_1 - I_2)}{dt} + R_3(I_1 - I_4) + L_1 \frac{d(I_1)}{dt} + M_a \frac{d(I_1)}{dt} + M_a \frac{d(I_1 - I_2)}{dt} - M_c \frac{d(I_2 - I_3)}{dt} = 0$

2 $\frac{1}{C_1} \int (I_2 - I_1) dt + R_2(I_2 - I_1) + L_2 \frac{d(I_2 - I_3)}{dt} + L_3 \frac{d(I_2 - I_1)}{dt} - M_d \frac{d(I_5 - I_2)}{dt} + M_c \frac{d(I_2 - I_1)}{dt} + M_c \frac{d(I_2 - I_3)}{dt} - M_b \frac{d(I_1)}{dt} = 0$

3 $L_2 \frac{d(I_3 - I_2)}{dt} + \frac{1}{C_2} \int (I_3 - I_4) dt - M_c \frac{d(I_2 - I_1)}{dt} + M_d \frac{d(I_5 - I_2)}{dt} = 0$

4 $R_4(I_4 - I_5) + \frac{1}{C_3} \int (I_4 - I_6) dt + R_3(I_4 - I_1) + \frac{1}{C_2} \int (I_4 - I_3) dt = V_0$

5 $R_4(I_5 - I_4) + L_4 \frac{d(I_5 - I_2)}{dt} + M_e \frac{d(I_6 - I_7)}{dt} + M_c \frac{d(I_3 - I_2)}{dt} = 0$


6 $\frac{1}{C_3} \int (I_6 - I_4) dt + L_5 \frac{d(I_6 - I_7)}{dt} + \frac{1}{C_5} \int (I_6 - I_7) dt + R_5(I_6) + M_e \frac{d(I_5 - I_2)}{dt} + M_c \frac{d(I_1)}{dt} = 0$

7 $\frac{1}{C_5} \int (I_7 - I_6) dt + L_5 \frac{d(I_7 - I_6)}{dt} + L_4 \frac{d(I_7 - I_5)}{dt} + \frac{1}{C_4} \int I_7 dt - M_d \frac{d(I_3 - I_2)}{dt} + M_e \frac{d(I_7 - I_6)}{dt} + M_e \frac{d(I_7 - I_5)}{dt} - M_b \frac{d(I_1)}{dt} = 0$

b) \rightarrow labeled \rightarrow Nodes = 12
 Nodal Eqs = $(n-1) - 1 = 10$
due to V_s

E Branches:
 Graph:
 Tree:

10 PTS
Nodal Analysis

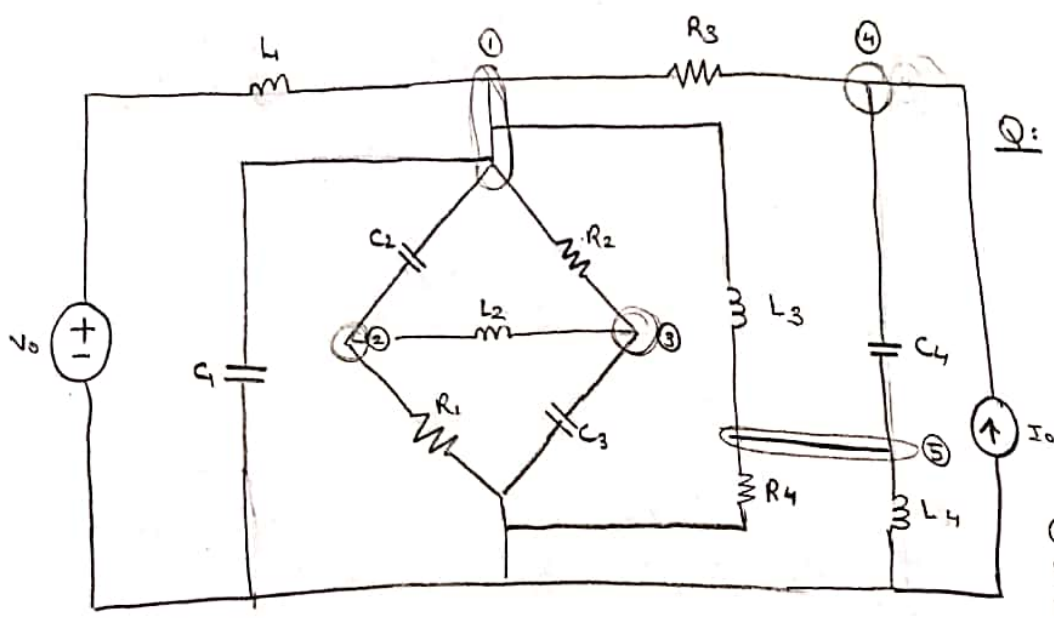

Q: For the circuit given below, apply Kirchhoff's Current Law (KCL) to write the complete set of Nodal Equations

Goal: to test whether students can correctly visualize nodes / connections AND correctly formulate Nodal Equations

Solution:

- 1 $\frac{1}{L_1} \int (V_1 - V_0) dt + C_1 \frac{dV_1}{dt} + \frac{1}{L_4} \int V_1 - V_5 dt + C_2 \frac{d(V_1 - V_2)}{dt} + \frac{V_1 - V_3}{R_1} = 0$
- 2 $C_2 \frac{d(V_2 - V_1)}{dt} + \frac{V_2}{R_1} + \frac{1}{L_2} \int V_2 - V_3 dt = 0$
- 3 $\frac{V_3 - V_1}{R_2} + C_3 \frac{d(V_3)}{dt} + \frac{1}{L_2} \int V_3 - V_2 dt = 0$
- 4 $\frac{V_4 - V_1}{R_3} + C_4 \frac{d(V_4 - V_5)}{dt} = I_0$
- 5 $\frac{V_5}{R_4} + \frac{1}{L_4} \int V_5 dt = 0$

2pts p/Nodal Equation