
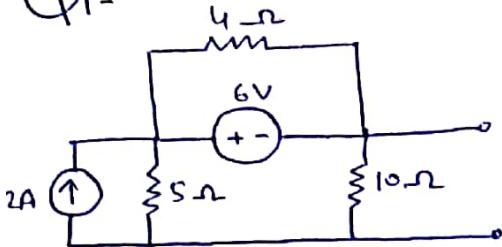



Q1-

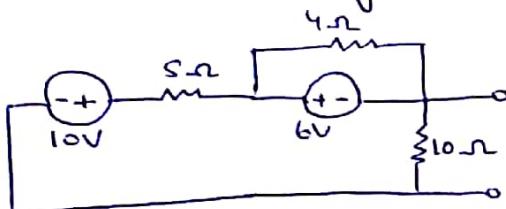


Source transforming:




Shifting sources:

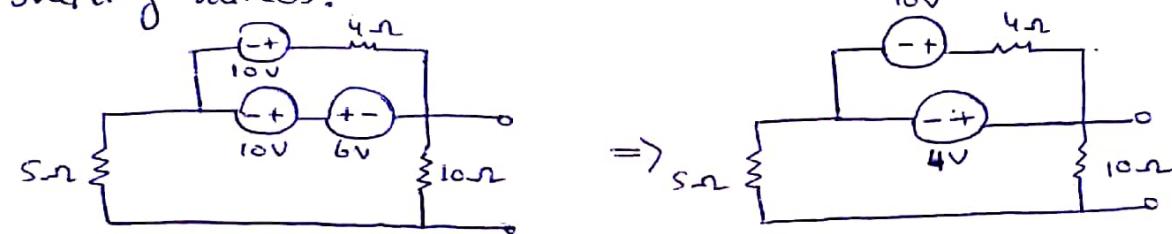

Source transformation:

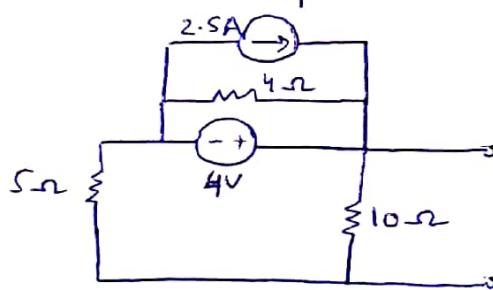


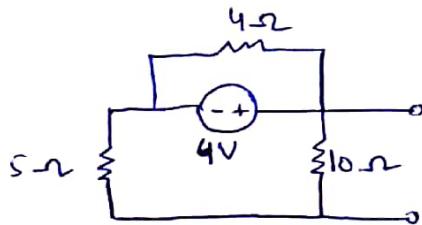
The current source is redundant. Simplifying:



$$\therefore V_o = 4V$$

2.



a)

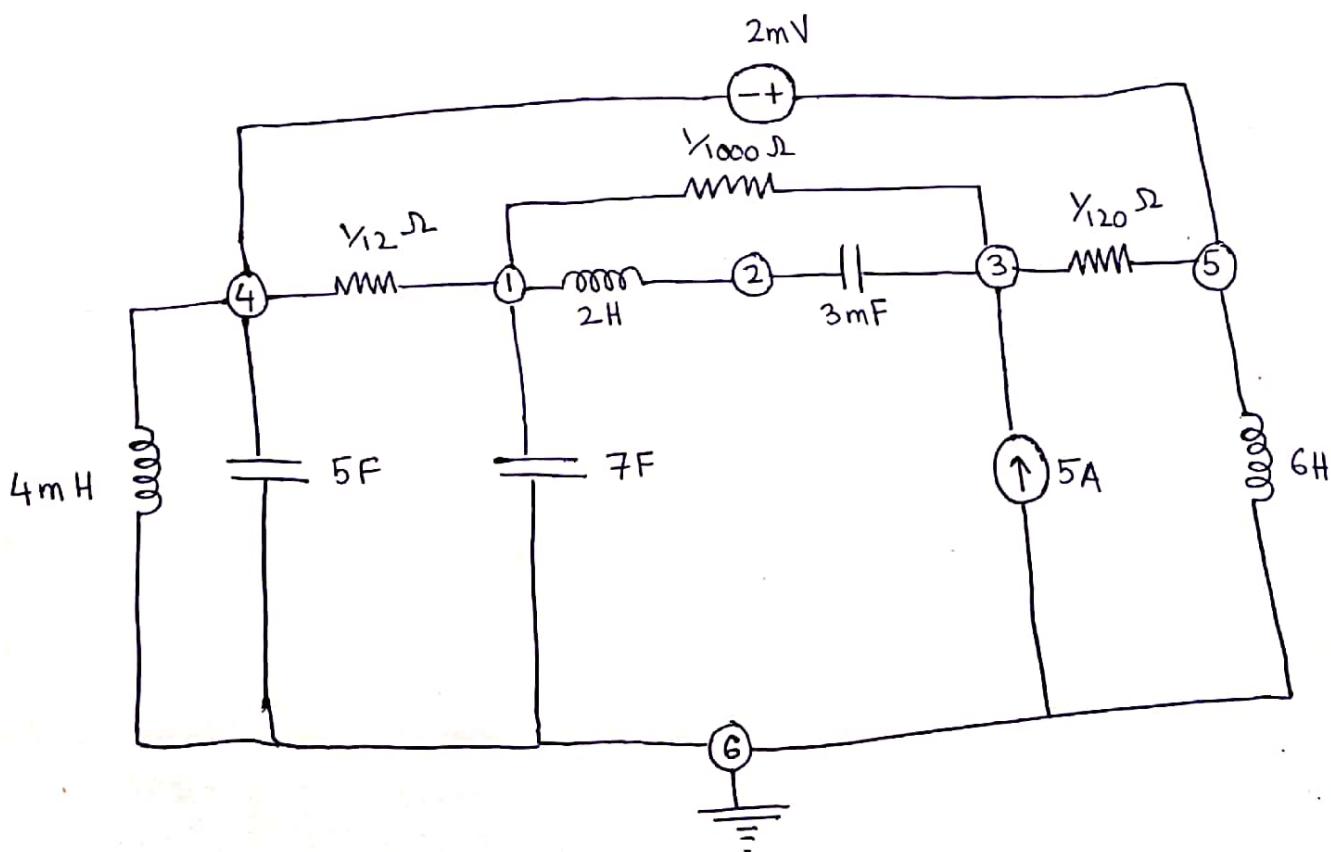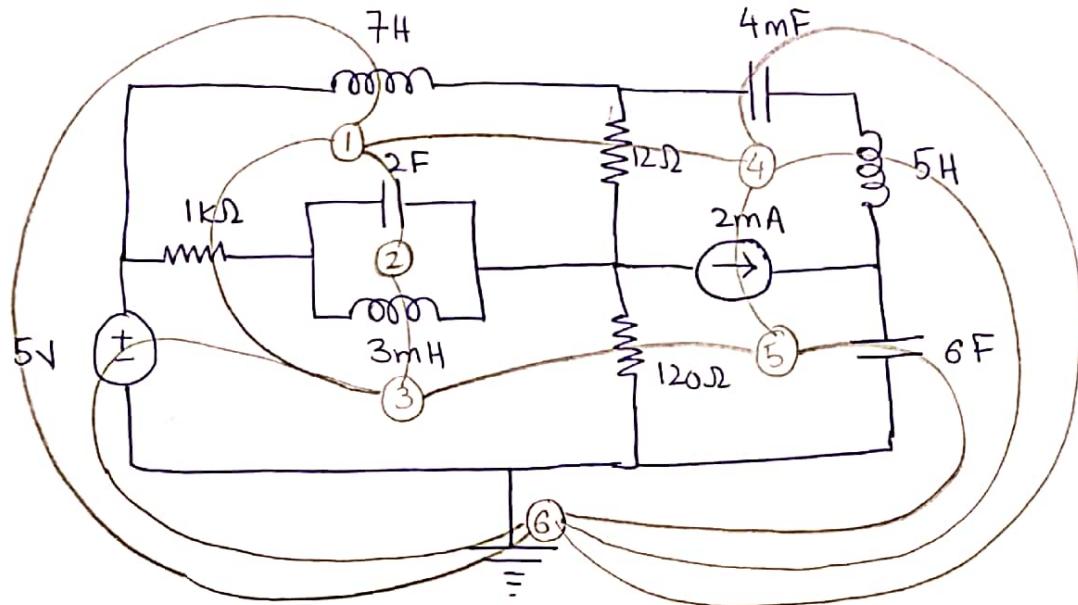

QUESTION # 2


PART BSOLUTION

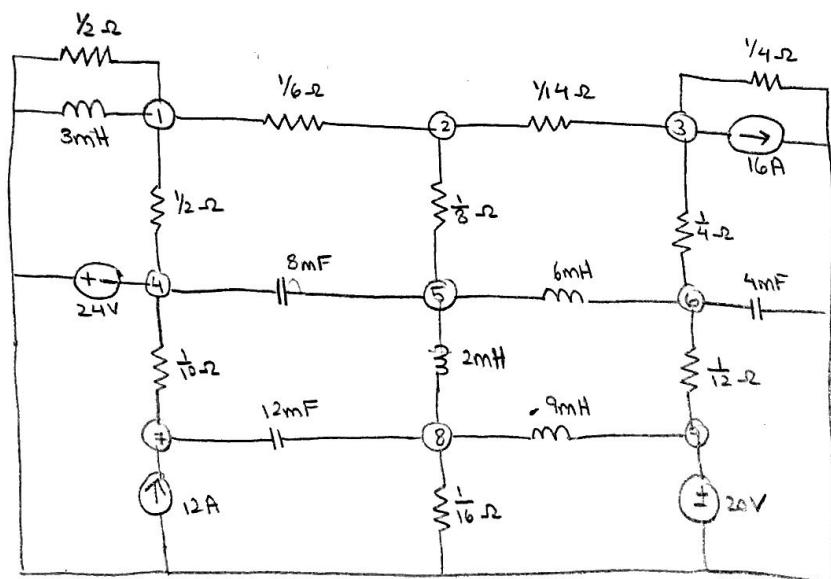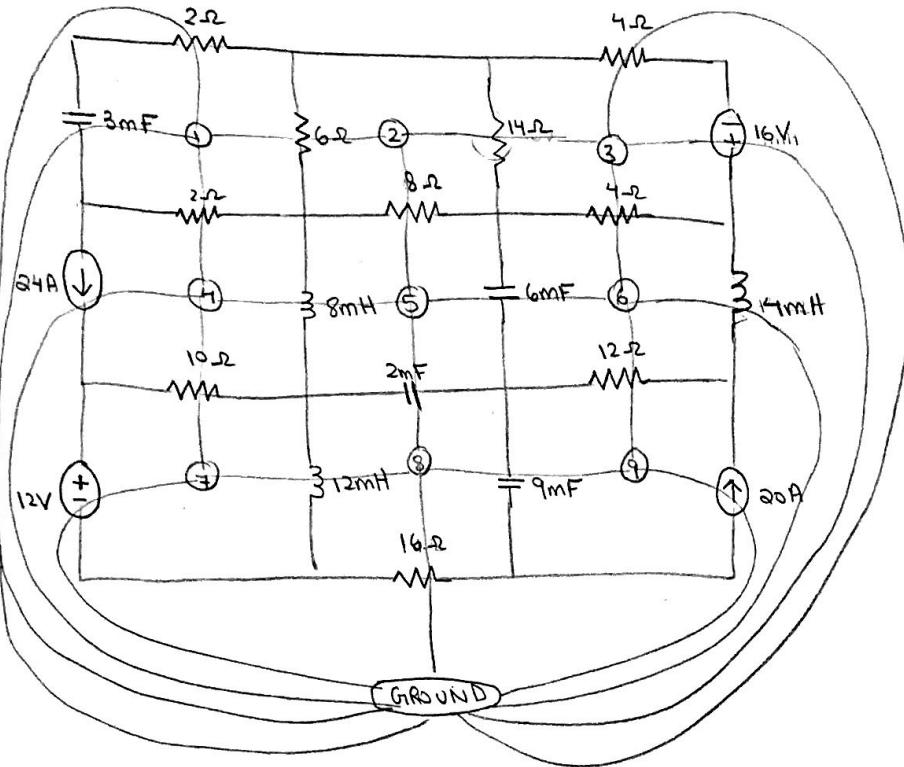- 1) Create a node inside each mesh
- 2) Create connections from node to node or node to ground that pass through each element.
- 3) Redraw Nodes & connections, taking the dual of each element



Q3-

Finding V_{th} :

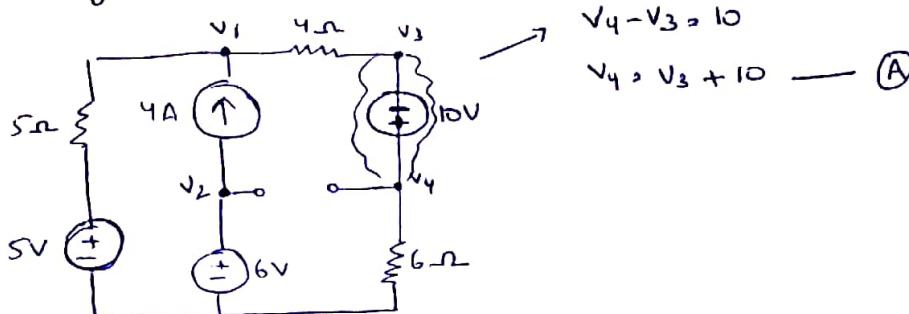

$$(1) \frac{v_1 - 5}{5} + \frac{v_1 - v_3}{4} = 4 \Rightarrow 9v_1 - 5v_3 = 100 \quad \text{--- (1)}$$

$$(2) \frac{v_2 - 6}{3} + 4 = 0 \Rightarrow v_2 = -6 \text{ V}$$

$$(3) \frac{v_3 - v_1}{4} + \frac{v_4}{6} = 0 \quad (\text{Supernode eq.})$$

$$\Rightarrow 6v_3 - 6v_1 + 4v_4 = 0$$

Using (A):

$$6v_3 - 6v_1 + 4(v_3 + 10) = 0 \Rightarrow -6v_1 + 10v_3 = -40 \quad \text{--- (3)}$$


Solving (1) and (3) simultaneously:

$$v_1 = \frac{40}{3}, \quad v_3 = 4$$

$$v_4 = v_3 + 10 \\ = 14 \text{ V}$$


$$\therefore V_{th} = 14 - (-6) = 20 \text{ V}$$

Finding R_{th} , switching off sources:

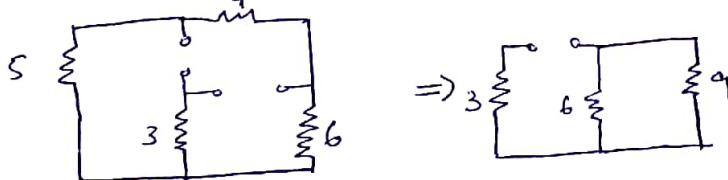

$$R_{th} = 3 + (6 \parallel 9) \\ = \frac{33}{5}$$

Norton eq:

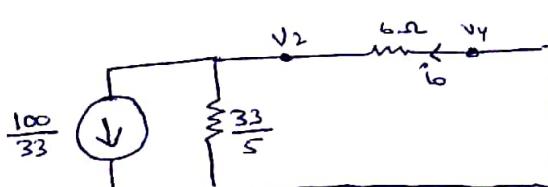


$$i_o = \frac{100}{33} \left(\frac{\frac{33}{5}}{\frac{33}{5} + 6} \right)$$

(using current division rule)

$$i_o = 1.587 \text{ A}$$

4. a)

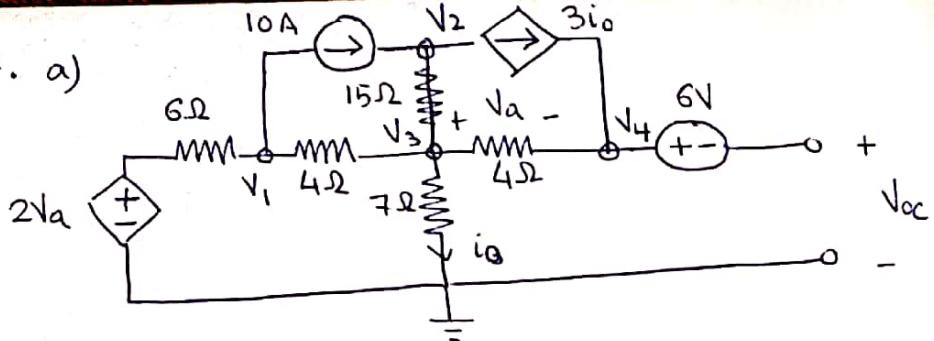

$$\boxed{V_{oc} = V_4 - 6}$$

$$V_a = V_3 - V_4$$

$$i_0 = V_3 / 7$$

$$\frac{V_1 - 2V_a}{6} + \frac{V_1 - V_3}{4} + 10 = 0$$

$$\frac{V_1 - 2(V_3 - V_4)}{6} + \frac{V_1 - V_3}{4} + 10 = 0$$

$$\frac{\frac{V_1 + V_1}{6}}{4} - \frac{\frac{V_3 - V_3}{3}}{4} + \frac{\frac{V_4}{3}}{4} = -10$$

$$\boxed{\frac{5V_1}{12} - \frac{7V_3}{12} + \frac{V_4}{3} = -10} \quad (1)$$

$$\frac{V_2 - V_3}{15} + 3i_0 = 10$$

$$\frac{V_2}{15} - \frac{V_3}{15} + \frac{3V_3}{7} = 10$$

$$\boxed{\frac{V_2}{15} + \frac{38V_3}{105} = 10} \quad (2)$$

$$\frac{V_3 - V_4}{4} + \frac{V_3}{7} + \frac{V_3 - V_1}{4} + \frac{V_3 - V_2}{15} = 0$$

$$\frac{V_3}{4} + \frac{V_3}{4} + \frac{V_3}{7} + \frac{V_3}{15} - \frac{V_1}{4} - \frac{V_2}{15} - \frac{V_4}{4} = 0$$

$$\boxed{-\frac{V_1}{4} - \frac{V_2}{15} + \frac{149}{210}V_3 - \frac{V_4}{4} = 0} \quad (3)$$

$$\frac{V_4 - V_3}{4} = \frac{3V_3}{7}$$

$$-\frac{V_3}{4} - \frac{3V_3}{7} + \frac{V_4}{4} = 0$$

$$\boxed{-\frac{19V_3}{28} + \frac{V_4}{4} = 0} \quad (4)$$

solving for V_4 :

$$V_1 = -29.3V$$


$$V_2 = 112.9V$$

$$V_3 = 6.83V$$

$$\Rightarrow \boxed{V_4 = 18.5V}$$

$$V_{oc} = 18.5 - 6$$

$$\boxed{V_{oc} = 12.5V} \text{ ANS}$$

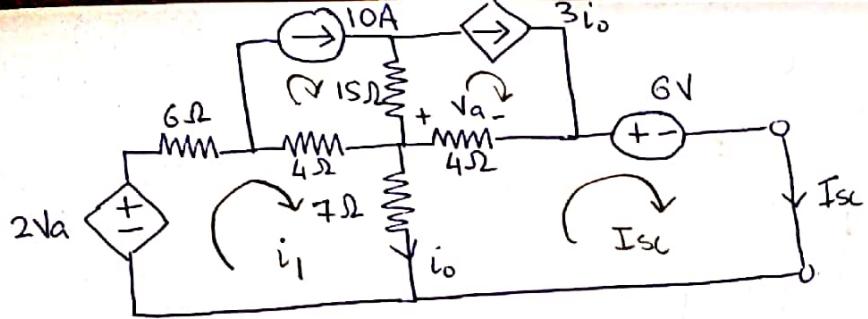

$$i_0 = i_1 - Isc$$

$$v_a = 4(Isc - 3i_0)$$

$$= 4Isc - 12i_0$$

$$= 4Isc - 12i_1 + 12Isc$$

$$v_a = 16Isc - 12i_1$$

$$2v_a = 6i_1 + 4i_1 + 7i_1 - 4(10) - 7Isc$$

$$32Isc - 24i_1 = 17i_1 - 40 - 7Isc$$

$$\boxed{41i_1 - 39Isc = 40} \quad (1)$$

$$4Isc + 7Isc - 4(3i_0) = -6$$

$$11Isc - 12i_1 + 12Isc = -6$$

$$\boxed{23Isc - 12i_1 = -6} \quad (2)$$


$$i_1 = 1.44A$$

$$\boxed{Isc = 0.493A} \quad \underline{\text{ANS}}$$

$$R_{th} = \frac{V_{oc}}{Isc} = \frac{12.5}{0.493}$$

$$\boxed{R_{th} = 25.4\Omega} \quad \underline{\text{ANS}}$$

$$\boxed{R_L = 25.4\Omega}$$

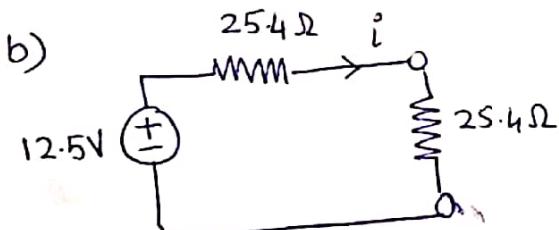


$$i = \frac{12.5}{2(25.4)}$$

$$i = 0.246A$$

power dissipated across $R_L \Rightarrow P = i^2 R$

$$\begin{aligned} &= (0.246)^2 \times 25.4 \\ \boxed{P_{max} = 1.54W} \quad &\underline{\text{ANS}} \end{aligned}$$

5.

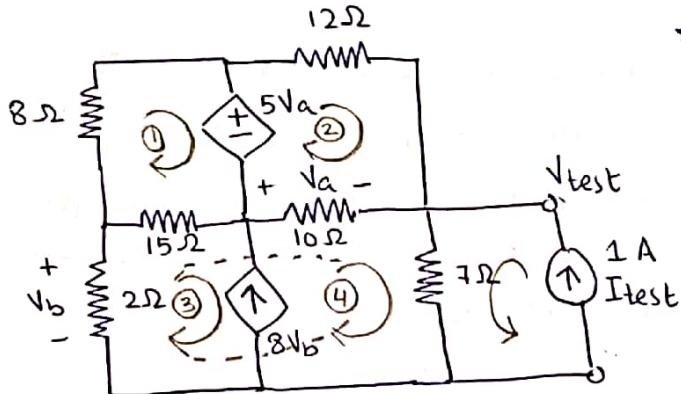

+ apply test source and calculate corresponding current or voltage

note that: since there are no independent sources we can only use test source method
 $(V_{th} = 0)$

use any value for I_{test} , e.g. $I_{\text{test}} = 1 \text{ A}$ here

$$\text{V}_{\text{test}} = 7(I_{\text{test}} + i_4)$$

$$\text{V}_{\text{test}} = 7(1 + i_4)$$

$$8i_1 + 15i_1 - 15i_3 = -5V_a$$

$$V_a = 10(i_4 - i_2)$$

$$23i_1 - 15i_3 = -50i_4 + 50i_2$$

$$V_b = -2i_3$$

$$23i_1 - 50i_2 - 15i_3 + 50i_4 = 0 \quad (1)$$

$$12i_2 + 10i_2 - 10i_4 = 50(i_4 - i_2)$$

$$22i_2 + 50i_2 - 10i_4 - 50i_4 = 0$$

$$72i_2 - 60i_4 = 0 \quad (2)$$

* ③ ④ form supermesh

$$i_4 - i_3 = 8V_b$$

$$i_4 - i_3 = 8(-2i_3)$$

$$i_4 - i_3 = -16i_3$$

$$15i_3 + i_4 = 0 \quad (3)$$

$$2i_3 + 15i_3 - 15i_1 + 10i_4 + 7i_4 - 10i_2 + 7(1) = 0$$

$$-15i_1 - 10i_2 + 17i_3 + 17i_4 = -7 \quad (4)$$

solving equations for i_4 :

$$i_1 = 0.208 \text{ A}$$

$$i_2 = -0.428 \text{ A}$$

$$i_3 = 0.0343 \text{ A}$$


$$i_4 = -0.514 \text{ A} \Rightarrow \text{V}_{\text{test}} = 7(1 - 0.514)$$

$$\text{V}_{\text{test}} = 3.40 \text{ V}$$

$$R_{th} = \frac{\text{V}_{\text{test}}}{I_{\text{test}}}$$

$$R_{th} = 3.40 \Omega$$

ANS

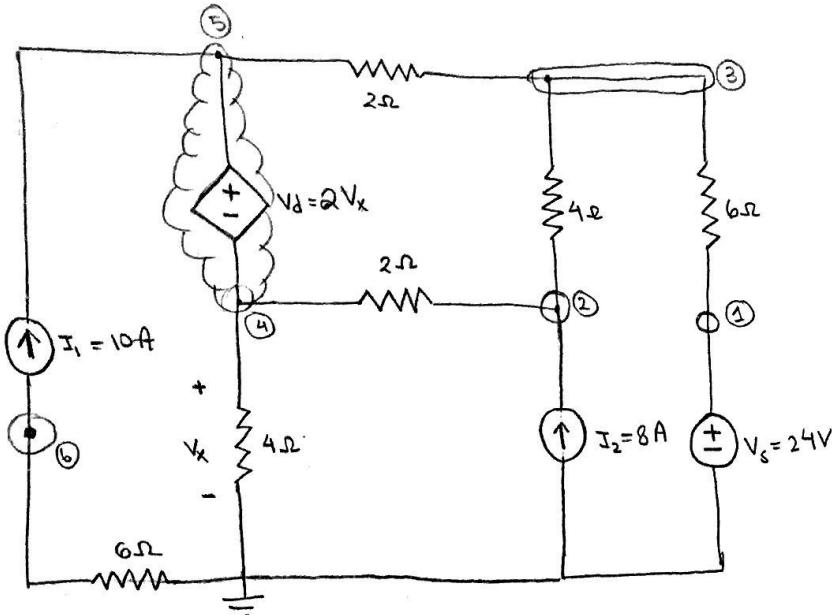

STEP 1: Identify Nodes & Any Super Nodes

STEP 2: Formulate Nodal Equations

$$\textcircled{1} \quad V_1 = V_s = 24V$$

$$\textcircled{2} \quad \frac{V_2 - V_3}{4} + \frac{V_2 - V_4}{2} = I_2$$

$$\textcircled{3} \quad \frac{V_3 - V_1}{6} + \frac{V_3 - V_2}{4} + \frac{V_3 - V_5}{2} = 0$$

Super Node

$$V_5 - V_4 = V_d = 2V_x$$

$$\textcircled{4} \& \textcircled{5} \quad \frac{V_5 - V_3}{2} + \frac{V_4 - V_2}{2} + \frac{V_4}{4} = I_1$$

$$\textcircled{6} \quad I_1 + \frac{V_6}{6} = 0$$

STEP 3: Simplify Equations

- * Substitute Knowns
- * Apply Super Node

$$\textcircled{1} \quad V_1 = 24$$

$$\textcircled{2} \quad \frac{V_2 - V_3}{4} + \frac{V_2 - V_4}{2} = 8$$

$$V_2 - V_3 + 2V_2 - 2V_4 = 32$$

$$3V_2 - V_3 - 2V_4 = 32$$

$$\textcircled{3} \quad \frac{V_3 - V_1}{6} + \frac{V_3 - V_2}{4} + \frac{V_3 - V_5}{2} = 0$$

$$2V_3 - 2V_1 + 3V_3 - 3V_2 + 6V_3 - 6V_5 = 0$$

$$-2V_1 - 3V_2 + 11V_3 - 6V_5 = 0$$

$$-2(24) - 3V_2 + 11V_3 - 6V_5 = 0$$

$$-3V_2 + 11V_3 - 6(3V_4) = 48$$

$$-3V_2 + 11V_3 - 18V_4 = 48$$

$$\textcircled{4} \& \textcircled{5} \quad \frac{V_5 - V_3}{2} + \frac{V_4 - V_2}{2} + \frac{V_4}{4} = 10$$

$$2V_5 - 2V_3 + 2V_4 - 2V_2 + V_4 = 40$$

$$-2V_2 - 2V_3 + 3V_4 + 2(3V_4) = 40$$

$$-2V_2 - 2V_3 + 9V_4 = 40$$

$$\textcircled{6} \quad 10 + \frac{V_6}{6} = 0$$

$$\frac{V_6}{6} = -10$$

$$V_6 = -60$$

Super Node :

$$V_5 - V_4 = 2V_x$$

$$V_5 - V_4 = 2(V_4)$$

$$V_5 = 3V_4$$

STEP 4: FORMULATE MATRIX & SOLVE

$$\begin{bmatrix} 3 & -1 & -2 \\ -3 & 11 & -18 \\ -2 & -2 & 9 \end{bmatrix} \begin{bmatrix} V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 32 \\ 48 \\ 40 \end{bmatrix}$$

$$V_1 = 24V$$

$$V_2 = 424/7 \approx 60.571V$$


$$V_3 = 552/7 \approx 78.857V$$

$$V_4 = 248/7 \approx 35.429V \quad = V_K$$

$$V_5 = 3V_4 = 3(248/7) = 744/7 \approx 106.286V$$


$$V_6 = -60V$$

QUESTION # 7

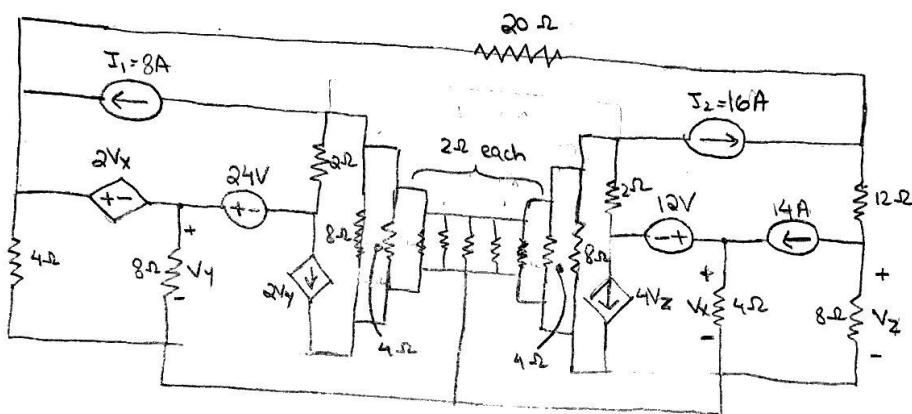

STEP 1: Simplify the circuit

* combine resistors

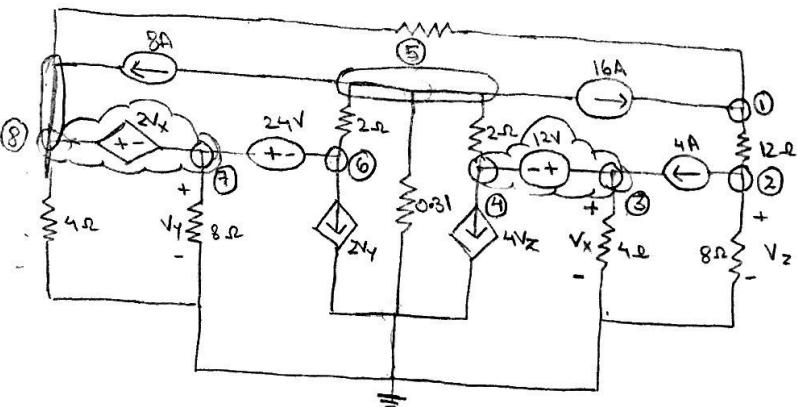

STEP 2: Identify Node & Super Nodes
(marked on circuit above)

STEP 3: Formulate Nodal Equations

$$① \frac{V_1 - V_2}{5} + \frac{V_1 - V_2}{12} = 16$$

$$② \frac{V_2 - V_1}{12} + \frac{V_2 - V_3}{8} + 4 = 0$$

$$③ \frac{V_3 - V_4}{4} + \frac{V_4 - V_5}{2} + 4V_Z = 4$$

Super Node: $V_3 - V_4 = 12$
 $V_3 = 12 + V_4$

$$\textcircled{5} \quad \frac{V_5 - V_4}{2} + \frac{V_5}{0.31} + \frac{V_5 - V_6}{2} + 8 + 16 = 0$$

$$\textcircled{6} \quad \frac{V_6 - V_5}{2} + 2V_7 + \frac{V_7}{8} + \frac{V_8}{4} + \frac{V_8 - V_1}{5} = 8$$

Super Node: $V_7 - V_6 = 24$
 $V_7 = 24 + V_6$

Super Node: $V_8 - V_7 = 2V_x$
 $V_8 = 2V_x + V_7 \rightarrow (V_x = V_3) \rightarrow 2V_3 + 24 + V_6 \rightarrow 2(12 + V_4) + 24 + V_6 = 48 + 2V_4 + V_6$

STEP 4: Simplify Nodal Equations
* Apply Super Nodes

$$\textcircled{1} \quad \frac{V_1 - V_8}{5} + \frac{V_1 - V_2}{12} = 16$$

$$12V_1 - 12V_8 + 5V_1 - 5V_2 = 960$$

$$12V_1 - 12(48 + 2V_4 + V_6) + 5V_1 - 5V_2 = 960 \rightarrow 17V_1 - 5V_2 - 24V_4 - 12V_6 = 1536$$

$$\textcircled{2} \quad \frac{V_2 - V_1}{12} + \frac{V_2}{8} + 4 = 0$$

$$2V_2 - 2V_1 + 3V_2 + 96 = 0$$

$$-2V_1 + 5V_2 = -96$$

$$\textcircled{3} \quad \frac{V_3}{4} + \frac{V_4 - V_5}{2} + 4V_2 = 4$$

$$V_3 + 2V_4 - 2V_5 + 16V_2 = 16$$

$$(12 + V_4) + 2V_4 - 2V_5 + 16V_2 = 16 \rightarrow V_2 = V_4$$

$$16V_2 + 3V_4 - 2V_5 = 4$$

$$\textcircled{5} \quad \frac{V_5 - V_4}{2} + \frac{V_5}{0.31} + \frac{V_5 - V_6}{2} + 8 + 16 = 0$$

$$0.31V_5 - 0.31V_4 + 2V_5 + 0.31V_5 - 0.31V_6 = -24$$

$$-0.31V_4 + 2.62V_5 - 0.31V_6 = -24$$

$$\textcircled{6} \quad \frac{V_6 - V_5}{2} + 2V_4 + \frac{V_7}{8} + \frac{V_8}{4} + \frac{V_8 - V_1}{5} = 8$$

$$20V_6 - 20V_5 + 80V_4 + 5V_7 + 10V_8 + 8V_8 - 8V_1 = 320 \rightarrow V_4 = V_7$$

$$-8V_1 - 20V_5 + 20V_6 + 85V_7 + 18V_8 = 320$$

$$V_7 = 24 + V_6 \quad \& \quad V_8 = 418 + 2V_4 + V_6$$

$$-8V_1 - 20V_5 + 20V_6 + 85(24 + V_6) + 18(48 + 2V_4 + V_6) = 320$$

$$-8V_1 + 36V_4 - 20V_5 + 123V_6 = -2584$$

STEP 5: FORMULATE MATRIX & SOLVE

$$\left[\begin{array}{cccccc} 0 & 0 & 0 & 0 & 0 & 0 \\ 17 & -5 & -24 & 0 & -12 & 0 \\ -2 & 5 & 0 & 0 & 0 & 0 \\ 0 & 16 & 3 & -2 & 0 & 0 \\ 0 & 0 & -0.31 & 2.62 & -0.31 & 0 \\ -8 & 0 & 36 & -20 & 123 & 0 \end{array} \right] \left[\begin{array}{c} V_1 \\ V_2 \\ V_4 \\ V_5 \\ V_6 \end{array} \right] = \left[\begin{array}{c} 1536 \\ -96 \\ 4 \\ -24 \\ -2584 \end{array} \right]$$

$$V_1 = 53.661$$

$$V_2 = 2.265 \quad \boxed{= V_4}$$

$$V_3 = 12 + V_4 = 12 + (-19.488) = -7.488 \quad \boxed{= V_x}$$

$$V_4 = -19.488$$


$$V_5 = -13.116$$

$$V_6 = -13.947$$

$$V_7 = 24 + V_6 = 24 - 13.947 = 10.053 \quad \boxed{= V_2}$$


$$V_8 = 48 + 2V_4 + V_6 = -4.923$$

Given the following circuit, produce the complete set of loop equations, formulate the equation matrix, and calculate all loop currents by performing Gaussian Elimination.

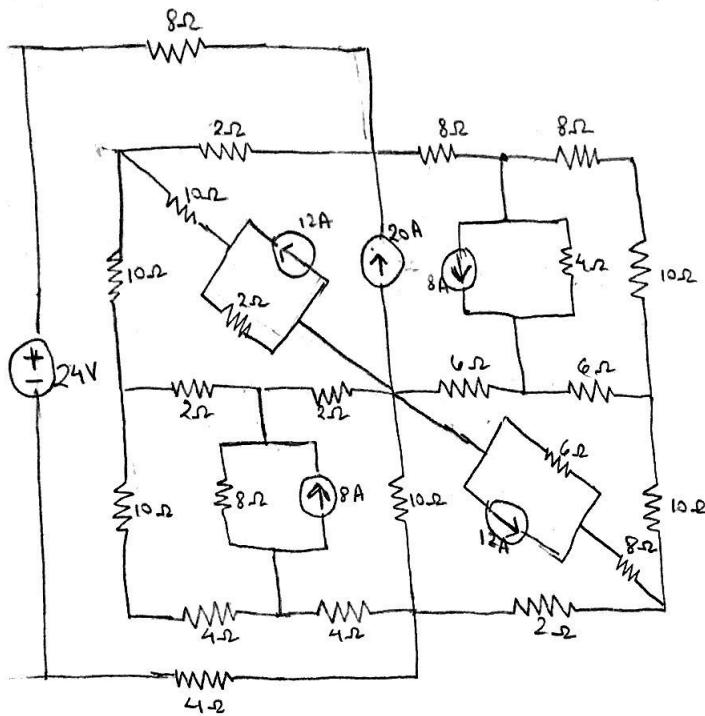STEP 1: Simplify the circuit.

- * Apply source transformation to current sources || to resistors
- * Combine resistances where possible

STEP 2: Identify & label loops. Identify any super loops. All loop currents are taken as clockwise.

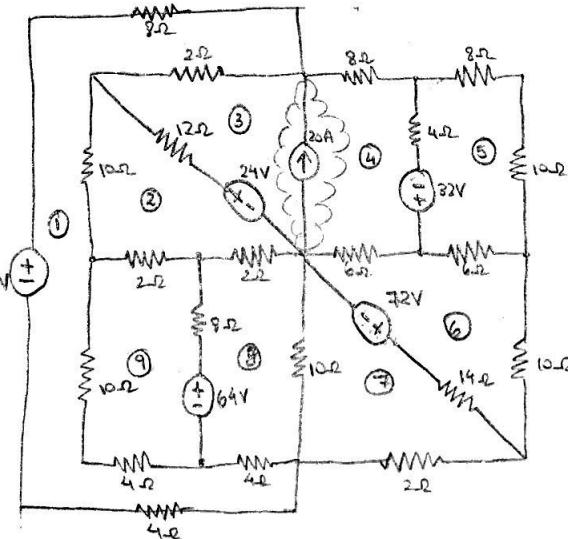STEP 3: Formulate Loop Equations

- ① $3i_1 + 2(i_1 - i_3) + 10(i_1 - i_2) + 10(i_1 - i_9) + 4(i_1 - i_7) + 4i_4 = 24'$
- ② $10(i_2 - i_4) + 12(i_2 - i_3) + 2(i_2 - i_8) + 2(i_2 - i_9) = -24$
- ③/④ $12(i_3 - i_2) + 2(i_3 - i_1) + 8i_4 + 4(i_4 - i_5) + 6(i_4 - i_6) = 24 + 32$
- (Super Loop): $i_3 + 20 = i_4$
- ⑤ $4(i_5 - i_4) + 8i_5 + 10i_5 + 6(i_5 - i_6) = -32$
- ⑥ $6(i_6 - i_4) + 6(i_6 - i_5) + 10i_6 + 14(i_6 - i_7) = -72$
- ⑦ $10(i_7 - i_8) + 14(i_7 - i_6) + 2i_7 = 72$
- ⑧ $8(i_8 - i_9) + 2(i_8 - i_2) + 10(i_8 - i_7) + 4(i_8 - i_1) = 64$
- ⑨ $10(i_9 - i_1) + 2(i_9 - i_2) + 8(i_9 - i_8) + 4(i_9 - i_5) = -64$

STEP 4: Simplify Loop Equations & Substitute Super loop

- ① $3i_1 + 2i_4 - 2i_3 + 10i_4 - 10i_2 + 10i_4 - 10i_9 + 4i_1 - 4i_9 + 4i_1 - 4i_8 + 4i_1 = 24$
 $32i_1 - 10i_2 - 2i_3 - 4i_8 - 14i_9 = 24$
- ② $10i_2 - 10i_1 + 12i_2 - 12i_3 + 2i_2 - 2i_8 + 2i_2 - 2i_9 = -24$
 $= 10i_1 + 26i_2 - 12i_3 - 2i_8 - 2i_9 = -24$
- ③/④ $12i_3 - 12i_2 + 2i_3 - 2i_4 + 8i_4 + 4i_4 - 4i_5 + 6i_4 - 6i_6 = 24 + 32$
 $-2i_4 - 12i_2 + 14i_3 + 18i_4 - 4i_5 - 6i_6 = 56$
 $-2i_4 - 12i_2 + 14i_3 + 18(i_3+20) - 4i_5 - 6i_6 = 56$
 $-2i_4 - 12i_2 + 14i_3 + 18i_3 + 360 - 4i_5 - 6i_6 = 56$
 $-2i_4 - 12i_2 + 32i_3 - 4i_5 - 6i_6 = -304$
- ⑤ $4i_5 - 4i_4 + 8i_5 + 10i_5 + 6i_5 - 6i_6 = -32$
 $-4(i_3+20) + 28i_5 - 6i_6 = -32$
 $-4i_3 - 80 + 28i_5 - 6i_6 = -32$
 $-4i_3 + 28i_5 - 6i_6 = 48$
- ⑥ $6i_6 - 6i_4 + 6i_6 - 6i_5 + 10i_6 + 14i_6 - 14i_7 = -72$
 $-6i_4 - 6i_5 + 36i_6 - 14i_7 = -72$
 $-6(i_3+20) - 6i_5 + 36i_6 - 14i_7 = -72$
 $-6i_3 - 120 - 6i_5 + 36i_6 - 14i_7 = 48$
 $-6i_3 - 6i_5 + 36i_6 - 14i_7 = -72$
- ⑦ $10i_7 - 10i_8 + 14i_7 - 14i_6 + 2i_7 = -72$
 $-14i_6 + 26i_7 - 10i_8$
- ⑧ $8i_8 - 8i_9 + 2i_8 - 2i_2 + 10i_8 - 10i_7 + 4i_8 - 4i_1 = 64$
 $-4i_1 - 2i_2 - 10i_7 + 80i_8 - 8i_9 = 64$
 $-4i_1 - 2i_2 - 8i_8 + 8i_9 - 8i_8 + 4i_9 - 4i_1 = -64$
 $-14i_1 - 2i_2 - 8i_8 + 24i_9 = -64$

STEP 5: Formulate Matrix

$$\left[\begin{array}{ccccccccc|c} i_1 & i_2 & i_3 & i_4 & i_5 & i_6 & i_7 & i_8 & i_9 & \\ \hline 32 & -10 & -2 & 0 & 0 & 0 & -4 & -14 & & i_1 \\ -10 & 26 & -12 & 0 & 0 & 0 & -2 & -8 & & i_2 \\ -2 & -12 & 32 & -4 & -6 & 0 & 0 & 0 & & i_3 \\ 0 & 0 & -4 & 28 & -6 & 0 & 0 & 0 & & i_4 \\ 0 & 0 & -6 & -6 & 36 & -14 & 0 & 0 & & i_5 \\ 0 & 0 & 0 & 0 & -14 & 26 & -10 & 0 & & i_6 \\ -4 & -2 & 0 & 0 & 0 & -10 & 20 & -8 & & i_7 \\ -14 & -2 & 0 & 0 & 0 & 0 & -8 & 24 & & i_8 \\ -14 & & & & & & & & & i_9 \end{array} \right] \left[\begin{array}{c} 24 \\ -24 \\ -804 \\ 48 \\ 48 \\ 72 \\ 64 \\ -64 \end{array} \right]$$

STEP 6: Solve

$$\begin{aligned} i_1 &= \frac{-884015336}{101599551} \approx -8.701 \\ i_2 &= \frac{-199386552}{101599551} \approx -11.805 \\ i_3 &= \frac{-1486866500}{101599551} \approx -14.635 \\ i_4 &= \frac{-52608336}{101599551} \approx -0.518 \\ i_5 &= \frac{-425375267549783}{6453187736343199} \approx -0.600 \\ i_6 &= \frac{46331296}{33366517} \approx 1.368 \\ i_7 &= \frac{-876248692}{101599551} \approx -8.719 \\ i_8 &= \frac{-955306192}{101599551} \approx -9.403 \end{aligned}$$

$$i_4 = i_3 + 20 \approx 5.365$$