

EE240: Circuits I

ASSIGNMENT 4

Due Date: 04 Nov 2019

- Submissions will only be accepted on A4 sized papers.
 - Write your name and roll number clearly at the top of the assignment.
 - You are required to show working where necessary; answers will not be graded if working is not shown.
 - The assignment is worth **100** marks, you are advised to start early as it is long.
 - Feel free to contact the instructor or teaching assistants if you have any questions.
 - Any instance of plagiarism will be **severely** dealt with; such cases would be subjected to **disciplinary action** in accordance with university rules and regulations.
-

In all of the following questions, assume that the circuit was in steady state before the switch is moved.

Problem 1 (10 marks)

For the figure shown below, calculate $v(0^-)$ and derive an expression for $v(t)$ for $t < 0$.

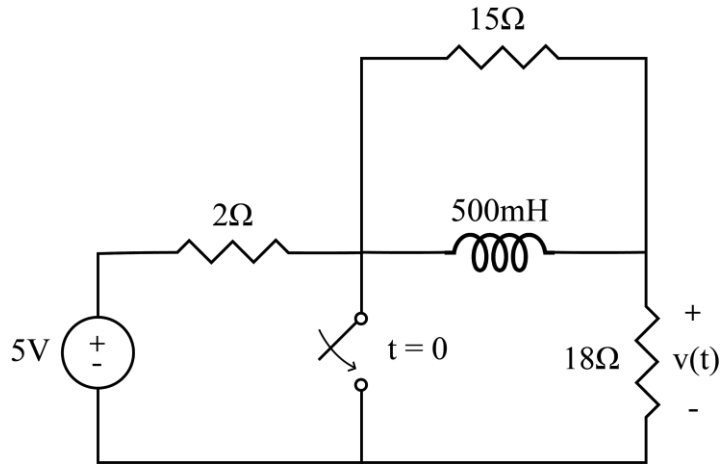


Figure 1

Problem 2 (20 marks)

- (a) [15 marks] In the circuit shown in Fig. 2, the switch is closed at $t = 0$, determine $i(t)$ for all time.
- (b) [5 marks] Sketch $i(t)$ for $t > 0$ on an appropriate scale.

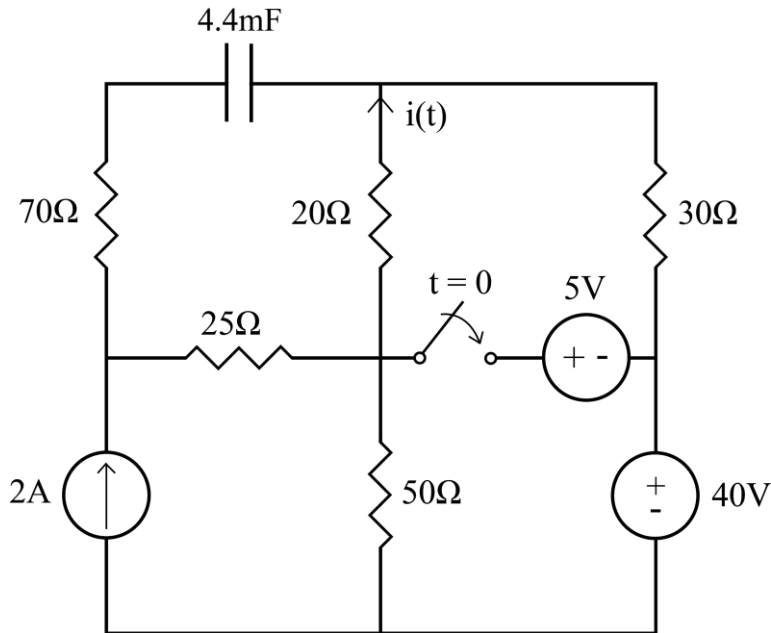


Figure 2

Problem 3 (15 marks)

For the circuit given below, determine $v(t)$ for $t > 0$ and sketch its waveform.

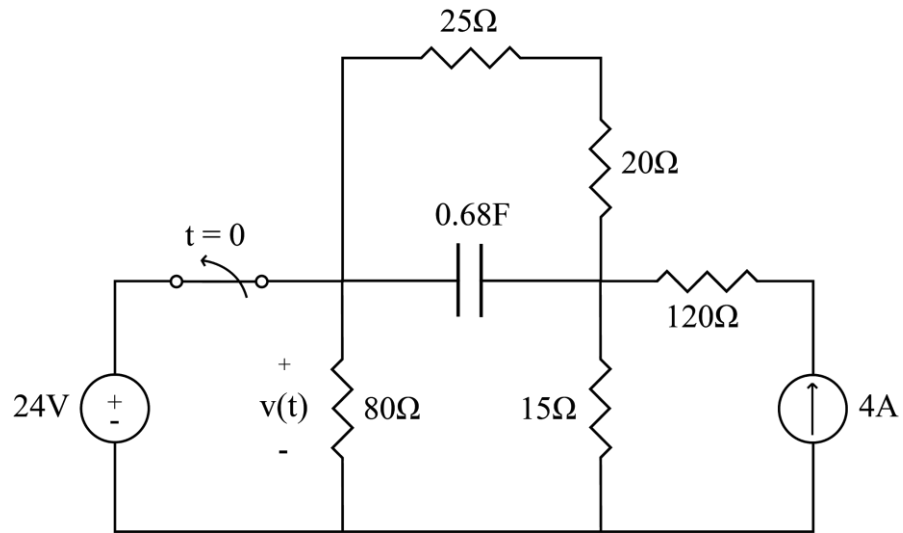


Figure 3

Problem 4 (10 marks)

For the circuit given below, calculate:

- (a) i_0 and v_0 for times $t = 0^-$ and $t = 0^+$.
- (b) dv_0/dt at $t = 0^+$.

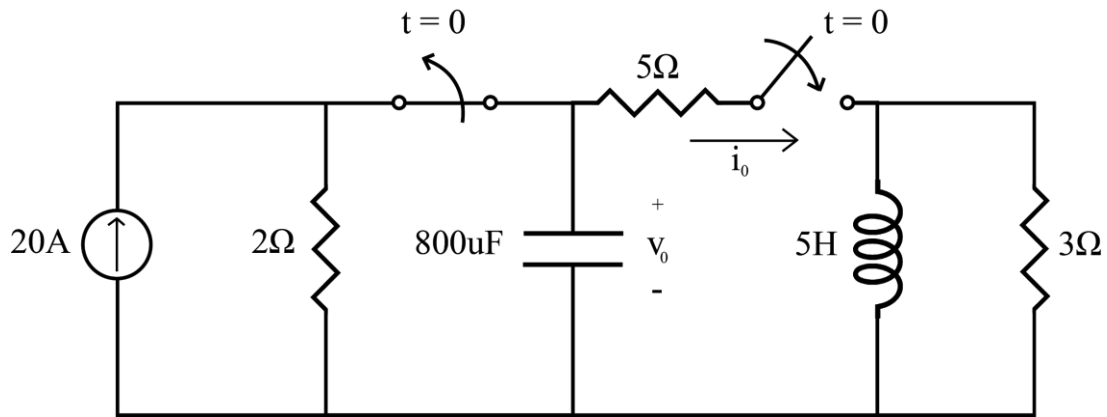


Figure 4

Problem 5 (15 marks)

In *figure 5* shown below, the switch is initially open and steady state is achieved. At time $t=0$, the switch is closed.

- (a) [4 marks] Produce the first order differential equations that govern the circuit.
- (b) [2 marks] Determine $V_c(0^-)$, the voltage across the capacitor before the switch is closed. Indicate its polarity.
- (c) [8 marks] Calculate $i_1(0^+)$, $i_2(0^+)$, $di_1(0^+)/dt$, and $di_2(0^+)/dt$.
- (d) [1 mark] Determine $di_1(\infty)/dt$.

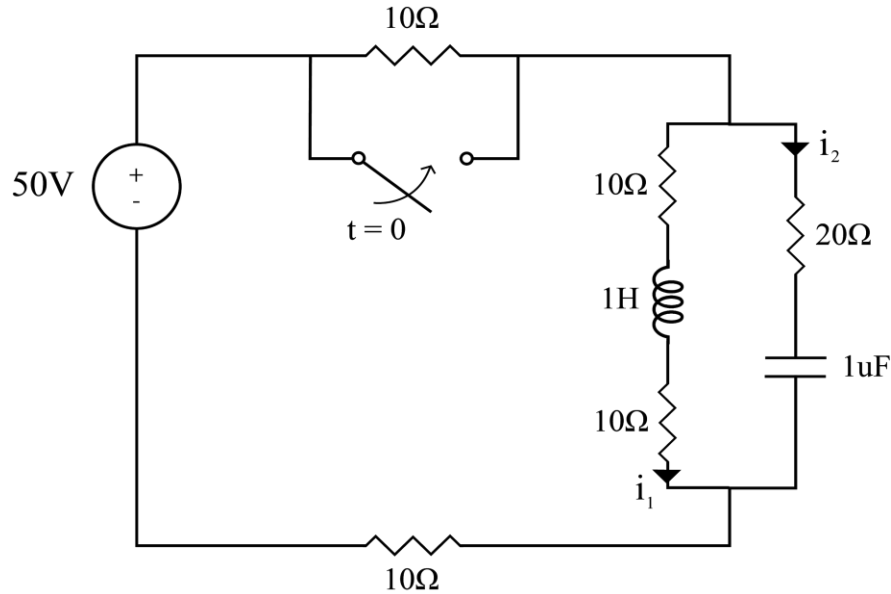


Figure 5

Problem 6 (15 marks)

For the circuit given below, calculate the following at time $t = 0^+$.

- (a) [5 marks] di_1/dt
- (b) [5 marks] di_2/dt
- (c) [5 marks] d^2i_2/dt^2

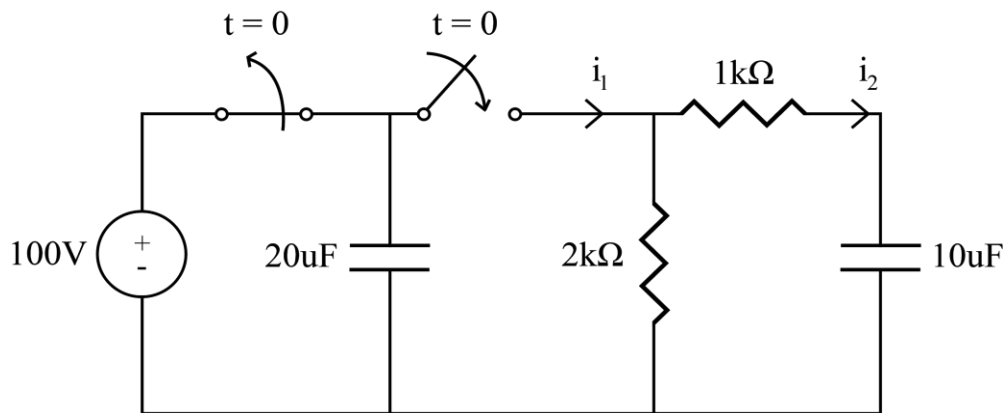


Figure 6

Problem 7 (15 marks)

In *figure 7* shown below, the switch is initially open and steady state is achieved. At time $t = 0$, the switch is closed.

- (a) [8 marks] Derive the equation for the current through the inductor for $t > 0$.
 (b) [2 marks] Sketch the current through the inductor for all time.
 (c) [5 marks] Find the time constant.

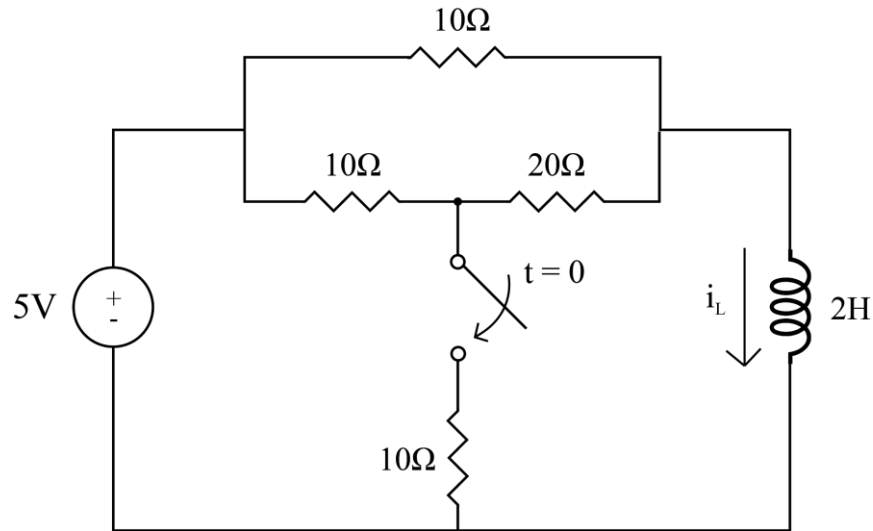


Figure 7