
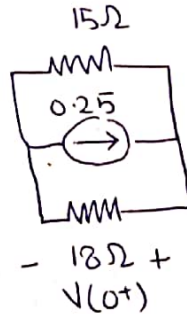


$$i_L(0^-) = i_L(0^+) = \frac{5}{20} = 0.25 \text{ A}$$

$$v(0^-) = \frac{18}{20} \times 5 = 4.5 \text{ V}$$


$$v(0^-) = 4.5 \text{ V}$$

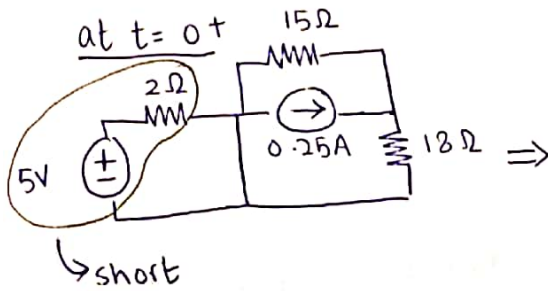

$$v(0^+) = \frac{15}{15+18} \times 0.25 \times 18 = \frac{45}{22}$$


$$v(0^+) = 2.04 \text{ V}$$

at $t=\infty$

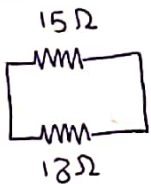

$$v(\infty) = 0 \text{ V}$$

R_{th} :

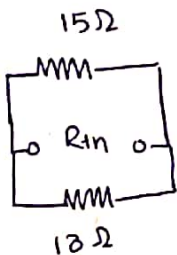

$$R_{th} = \frac{15 \times 18}{15+18} = \frac{90}{11}$$

$$R_{th} = 8.18 \Omega$$

$$\tau = L/R = \frac{500 \times 10^{-3}}{8.18} = 0.0611 \text{ s}$$

$$1/\tau = 16.4 \text{ s}^{-1}$$

$$K_1 = 0$$

$$K_2 = v(0^+) = 2.04$$


$$v(0^-) = 4.5 \text{ V}$$

$$v(t) = 2.04 e^{-16.4t} \quad t > 0$$

ANS

2) a) $t=0^-$

note: no current flows here

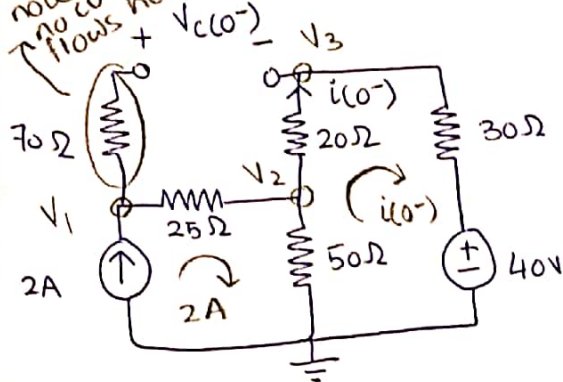

$$\frac{V_1 - V_2}{25} = 2 \Rightarrow V_1 - V_2 = 50 \quad (1)$$

$$\frac{V_2 - V_1}{25} + \frac{V_2}{50} + \frac{V_2 - V_3}{20} = 0 \quad (2)$$

substituting (1) in (2)

$$\frac{-50}{25} + \frac{V_2}{50} + \frac{V_2 - V_3}{20} = 0$$

$$\frac{V_2}{50} + \frac{V_2}{20} - \frac{V_3}{20} = 2$$

$$\frac{V_3 - V_2}{20} + \frac{V_3 - 40}{30} = 0 \quad (3) \Rightarrow$$

$$\frac{-V_2}{20} + \frac{V_3}{20} + \frac{V_3}{30} = \frac{4}{3}$$

solving simultaneously


$$\begin{aligned} V_2 &= 70 \text{ V} \\ V_3 &= 58 \text{ V} \end{aligned}$$

$$\begin{aligned} V_1 &= 50 + V_2 \\ &= 120 \text{ V} \end{aligned}$$

$$V_C(0^-) = V_1 - V_3 = 120 - 58$$

$$V_C(0^-) = 62 \text{ V}$$

at $t=0^+$

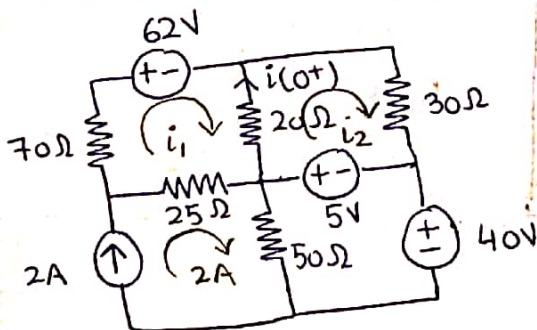

$$70i_1 + 25i_1 - 25(2) + 20i_1 - 20i_2 = -62$$

$$115i_1 - 20i_2 = -62 + 50$$

$$115i_1 - 20i_2 = -12 \quad (1)$$

$$20i_2 - 20i_1 + 30i_2 = 5$$

$$50i_2 - 20i_1 = 5 \quad (2)$$


solving
① & ②
simultaneously

$$\begin{aligned} i_1 &= \frac{-10}{107} \\ &= -0.0934 \text{ A} \\ i_2 &= \frac{67}{1070} \\ &= 0.0626 \text{ A} \end{aligned}$$

$$i(0^+) = i_2 - i_1$$

$$= 0.0626 + 0.0934$$

$$i(0^+) = 0.156 \text{ A}$$


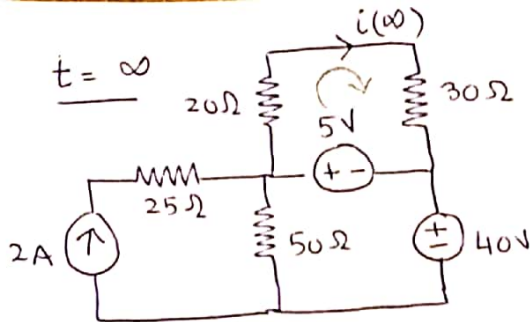


$$20i(\infty) + 30i(\infty) = 5$$

$$i(\infty) = 5/50$$

$$i(\infty) = 0.1 \text{ A}$$

R_{th} :

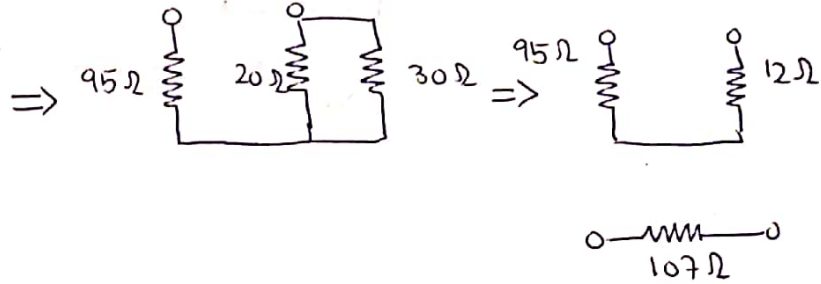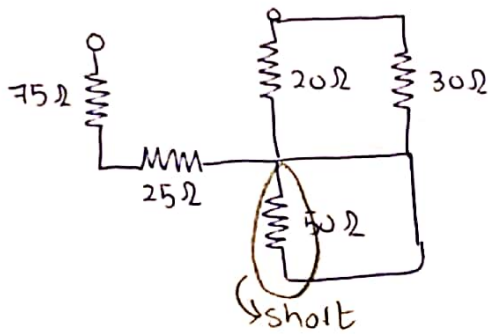

$$R_{th} = 107 \Omega$$

$$\tau = RC$$

$$= 107 \times 4.4 \times 10^{-3}$$

$$= 0.47 \text{ s}$$

$$K_1 + K_2 = 0.156$$

$$K_1 = 0.1$$


$$K_2 = 0.056$$


$$1/\tau = 2.12 \text{ s}^{-1}$$

$$i(t) = \begin{cases} 0.6 \text{ A} & t < 0 \\ 0.1 + 0.056e^{-2.12t} \text{ A} & t > 0 \end{cases}$$

ANS

b)

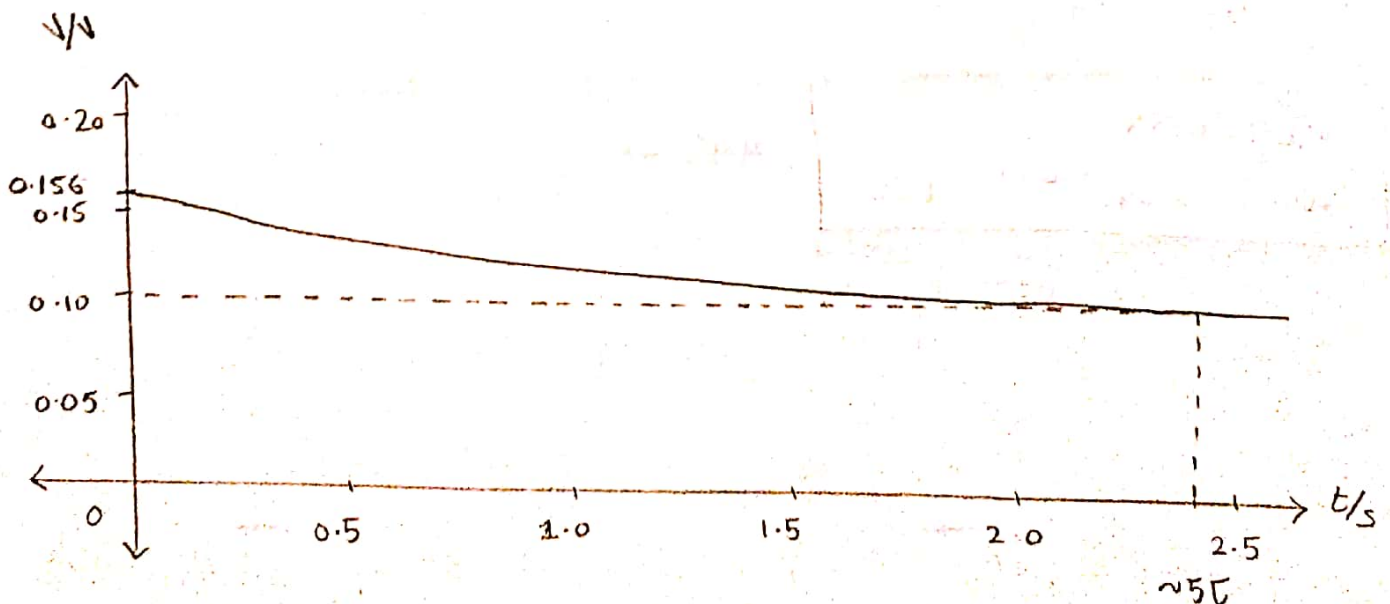

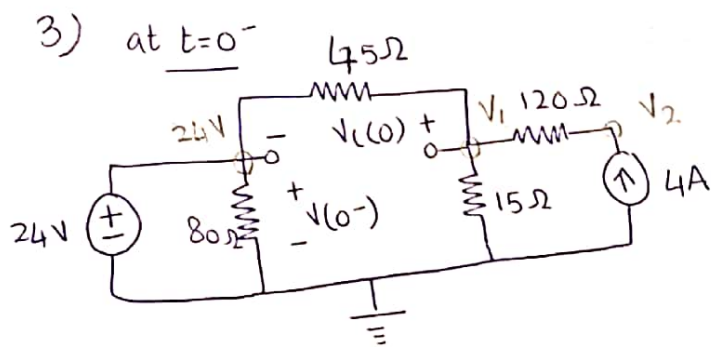

$$\frac{V_1 - V_2}{120} + \frac{V_1}{15} + \frac{V_1 - 24}{45} = 0 \quad (1)$$

$$\frac{V_2 - V_1}{120} = 4 \quad (2) \text{ substituting (2) in (1)}$$

$$\frac{V_1}{15} + \frac{V_1 - 24}{45} = 4$$

$$3V_1 + V_1 - 24 = 4 \times 45$$


$$4V_1 = 180 + 24$$

$$V_1 = 51 \text{ V}$$

$$V_c(0) = 51 - 24$$

$$V_c(0) = 27 \text{ V}$$

at $t=0^+$

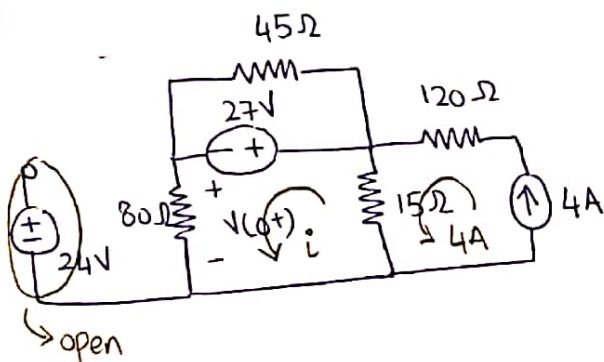

$$15i - 15(4) + 80i = -27$$

$$95i = -27 + 60$$


$$i = 33/95$$

$$i = 0.347 \text{ A}$$

$$V(0^+) = 0.347 \times 80$$

$$V(0^+) = 27.8 \text{ V}$$

$t = \infty$

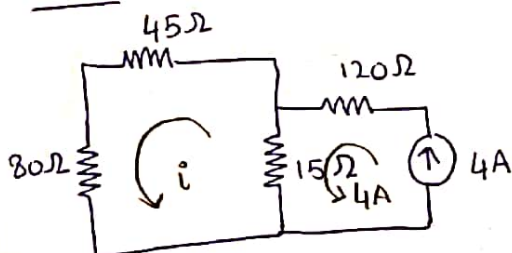


$$15i - 15(4) + 45i + 80i = 0$$

$$140i = 60$$


$$i = 3/7 \text{ A}$$

$$V(\infty) = 80 \times i$$

$$V(\infty) = 34.3 \text{ V}$$

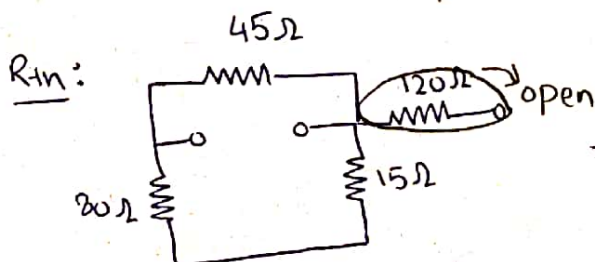

\Rightarrow

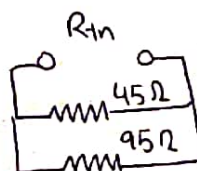

$$R_{th} = \frac{45 \times 95}{45 + 95}$$

$$R_{th} = 30.5$$

$$\tau = RC$$

$$= 20.8 \text{ s}$$


$$K_1 = 34.3$$

$$K_1 + K_2 = 27.8$$

$$K_2 = -6.5$$

$$1/\tau = 0.048 \text{ s}^{-1}$$

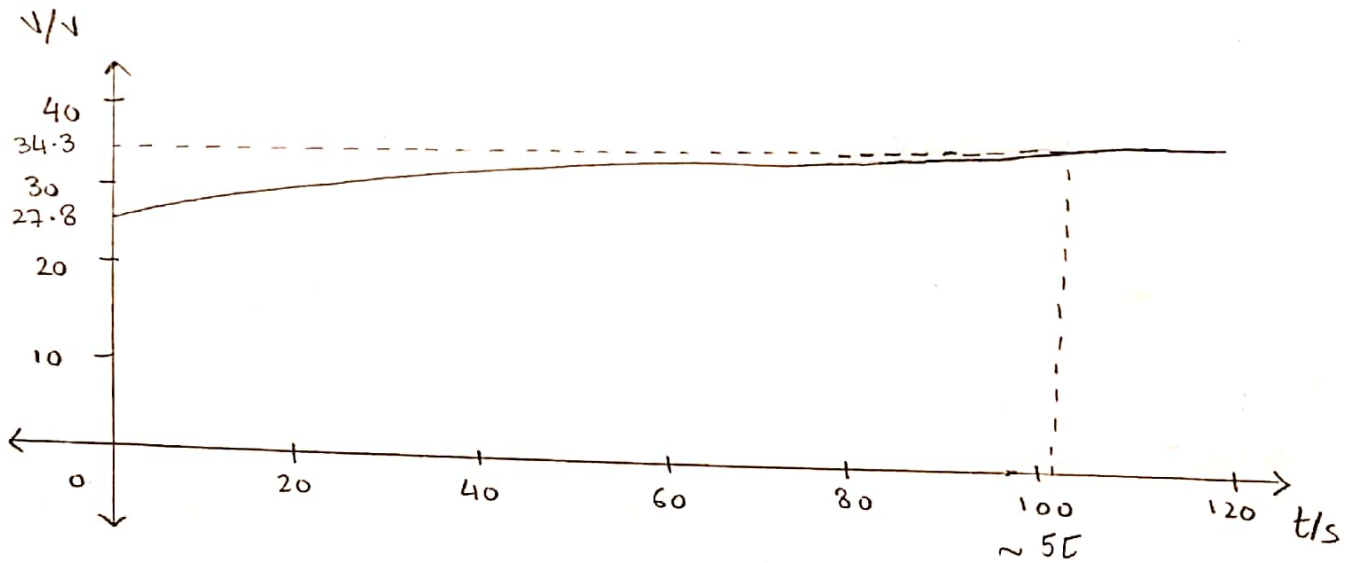
$$v(t) = 34.3 - 6.5e^{-0.048t} \quad t \geq 0 \quad t > 0$$



Q4.

a)

$t = 0^-$

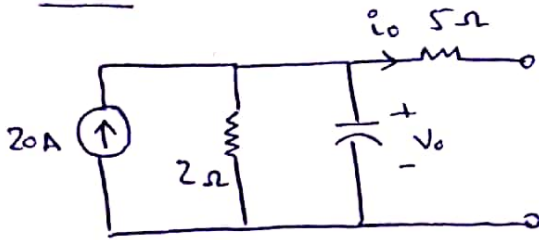


$$v_o(0^-) = v_c(0^-) = 40 \text{ V}$$

$$i_o = 0 \text{ A (since open circuit)}$$

$$i_L = 0 \text{ A}$$

$t = 0^+$

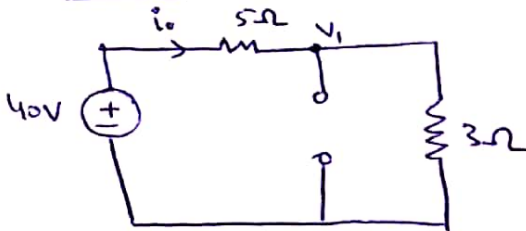


$$v_c(0^+) = v_o(0^+) = v_o(0^-) = 40 \text{ V}$$

$$i_o = 40/8 = 5 \text{ A}$$

$$v_1(0^+) = 5 \times 3 = 15 \text{ V}$$

$$i_L(0^+) = 0 \text{ A} = i_L(0^-)$$

b) $t \geq 0$

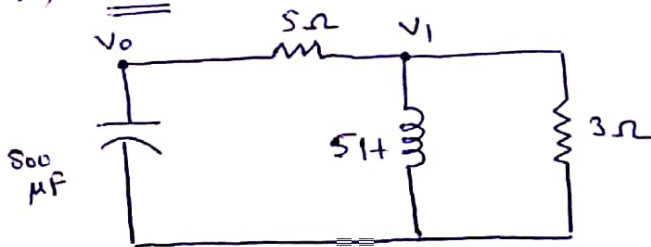

Node equations:

$$\textcircled{v_o} \quad C \frac{dv_o}{dt} + \frac{v_o - v_1}{5} = 0$$

$$\textcircled{v_1} \quad \frac{v_1 - v_o}{5} + \underbrace{\frac{1}{L} \int v_L dt}_{\hookrightarrow i_L(0^+) = 0} + \frac{v_1}{3} = 0$$

$$\Rightarrow \frac{v_1 - v_o}{5} + \frac{v_1}{3} = 0 \Rightarrow 8v_1 - 5v_o = 0 \Rightarrow v_o = \frac{8}{5}v_1$$

$$\textcircled{V_o} : C \frac{dv_o}{dt} + \frac{\left(\frac{8}{5} v_1\right) - v_1}{5} = 0$$

$$5C \frac{dv_o}{dt} + \frac{3}{5} v_1 = 0$$

$$\frac{dv_o}{dt}(0^+) = -\frac{3}{5} v_1 \times \frac{1}{5C}$$

$$v_1(0^+) = 15V \quad \text{and} \quad C = 800\mu F$$


$$\therefore \frac{dv_o}{dt}(0^+) = -2250 \text{ V/sec}$$

PROBLEM # 5

- * Steady State Achieved w/ Switch "S" initially open
- * Switch "S" is closed at time $t = 0$

- Produce the first order differential equations that govern the circuit
- Determine $V_c(0^-)$, the voltage across the capacitor before the switch is closed. Also find its polarity.
- Find $i_1(0^+)$ & $i_2(0^+)$
- Find $di_1/dt(0^+)$ & $di_2/dt(0^+)$
- Find $di_1/dt(\infty)$

STEP 1: Analyze the circuit at $t = 0^-$

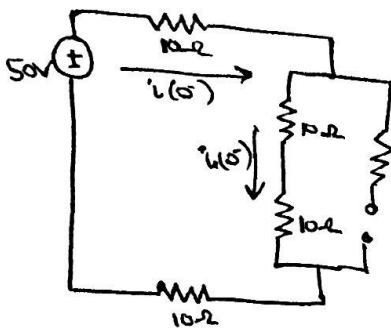

All of $i(0^-)$ is passed through the route of $i_1(0^-)$, hence $i(0^-) = i_1(0^-) = i_2(0^-)$ because inductor doesn't permit instantaneous change in current.

Because $V = IR$, $i_1(0^-) = \frac{V}{40\Omega} = \frac{50V}{40\Omega} = \frac{5}{4}$ Amps

$i_2(0^-) = 0$ Amps due to open circuit

$V_c(0^-) = V_c(0^+)$ because capacitor doesn't permit instantaneous change in voltage

$$\frac{50V(20\Omega)}{40\Omega} = \frac{1000}{40} = \frac{100}{4} = 25V \rightarrow \text{Polarity: } \begin{array}{c} \text{+} \\ | \\ \text{+} \end{array}$$

i) At $t > 0$: circuit Equations

$$\textcircled{1} - V = 20i_1 + L \frac{di_1(t)}{dt} = 20i_1 + \frac{di_1(t)}{dt} + 10$$

$$\textcircled{2} - V = 20i_2(t) + \frac{1}{C} \int_{-\infty}^t i_2(t) dt = 20i_2(t) + 1000000 \int_{-\infty}^t i_2(t) dt + 10$$

ii) $V_c(0^+) = 25V$ as determined above in $t = 0^-$ analysis. Polarity $\rightarrow \begin{array}{c} \text{+} \\ | \\ \text{+} \end{array}$

iii) $i_1(0^+) = i_1(0^-)$ because capacitor prohibits instantaneous change in current $= \frac{5}{4}$ Amps

$i_2(0^+) \rightarrow \dots$

$$\text{iv) Eq 1: } - V = i_1(t)(20) + L \frac{di_1}{dt} \rightarrow -50 = 20i_1(0^+) + \frac{di_1(0^+)}{dt} + 10$$

$$V = 20i_2(0^+) + V_c(0^+) + 10$$

$$50 = 20i_2(0^+) + 35 \rightarrow i_2(0^+) = \frac{15}{20} \text{ Amps} = 0.75A$$


$$\frac{di_1}{dt}(0^+) = 25 \text{ Amp/s}$$

$$\text{Eq 2: } - V = 20i_2(t) + \frac{1}{C} \int_{-\infty}^t i_2(t) dt + 10$$

\hookrightarrow differentiate

$$0 = 20 \frac{di_2(t)}{dt} + 1 \times 10^6 i_2(t) \rightarrow \frac{di_2(0^+)}{dt} = \frac{-10^6 \left[\frac{V - V_c(0^+)}{20} \right]}{20} = -6.25 \times 10^4 \text{ Amp/s}$$

v) $t = \infty$

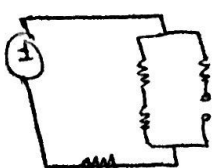

$$V_L(t) = L \frac{di_1(t)}{dt}$$

$$V_L(\infty) = L \frac{di_1(\infty)}{dt}$$


$V_L(\infty) = 0$ due to short circuit

Hence, $\frac{di_1}{dt}(\infty) = 0$

Q6.


Let $20\mu F \rightarrow C_1$
 $10\mu F \rightarrow C_2$

$t = 0^-$

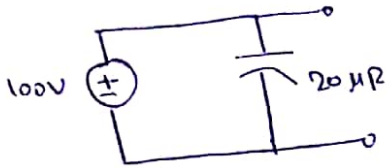

$$V_{C1} = 100V, V_{C2} = 0V, i_1 = i_2 = 0A$$

$t = 0^+$

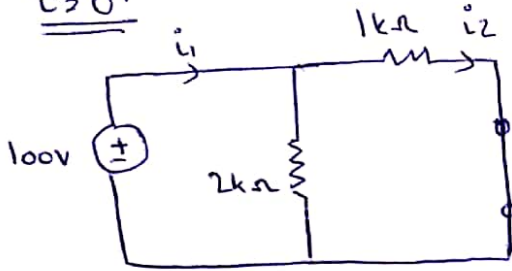


$$V_{C1}(0^+) = V_{C1}(0^-) = 100V$$

$$V_{C2}(0^+) = V_{C2}(0^-) = 0V$$

$$i_2 = \frac{100}{1000} = 0.1A$$

$$i_1 = 0.1 + \left(\frac{100}{2000}\right) = 0.15A$$

$t \geq 0$

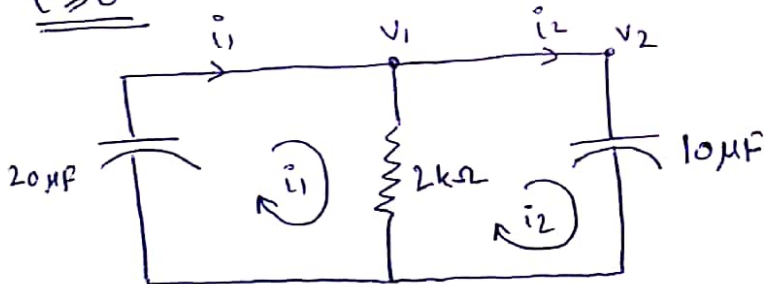

Loop eq.s :

$$\textcircled{i_1} \quad \frac{1}{C_1} \int i_1 dt + 2000(i_1 - i_2) = 0$$

$$\Rightarrow 2000(i_2 - i_1) = \frac{1}{C_1} \int i_1 dt \quad \text{--- ①}$$

$$\textcircled{i_2} \quad \frac{1}{C_2} \int i_2 dt + 1000i_2 + 2000(i_2 - i_1) = 0$$

Substitute ① in $\textcircled{i_2}$

$$\frac{1}{C_2} \int i_2 dt + 1000 i_2 + \frac{1}{C_1} \int i_1 dt = 0$$

Derivate wrt 't':

$$\frac{\dot{i}_2}{C_2} + 1000 \frac{di_2}{dt} + \frac{\dot{i}_1}{C_1} = 0 \quad \text{--- (2)}$$

$$\frac{di_2}{dt} = \frac{1}{1000} \left(-\frac{\dot{i}_1}{C_1} - \frac{\dot{i}_2}{C_2} \right)$$

Putting in values $\rightarrow \boxed{\frac{di_2}{dt} = -17.5 \text{ A/sec}}$

$$\textcircled{1}: \frac{1}{C_1} \int i_1 dt + 2000 (i_1 - i_2) = 0$$

Derivate wrt 't':

$$\frac{\dot{i}_1}{C_1} + 2000 \left(\frac{di_1}{dt} - \frac{di_2}{dt} \right) = 0$$

$$\frac{di_1}{dt} = \frac{-\dot{i}_1}{2000 C_1} + \frac{di_2}{dt}$$

Putting in values of $i_1, C_1, \frac{di_2}{dt}$

$$\Rightarrow \boxed{\frac{di_1}{dt} = -21.25 \text{ A/sec}}$$


Derivate $\textcircled{2}$ wrt 't':

$$\frac{1}{C_2} \cdot \frac{di_2}{dt} + 1000 \frac{d^2 i_2}{dt^2} + \frac{di_1}{dt} \cdot \frac{1}{C_1} = 0$$

$$\frac{d^2 i_2}{dt^2} = -\frac{1}{1000} \left(\frac{1}{C_1} \cdot \frac{di_1}{dt} + \frac{1}{C_2} \cdot \frac{di_2}{dt} \right)$$

Putting in values:

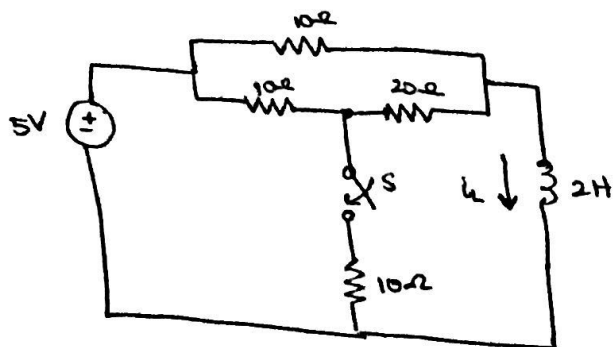
$$\boxed{\frac{d^2 i_2}{dt^2} = 2812.5 \text{ A/sec}^2}$$



PROBLEM #7

- * steady state Achieved w/ switch "S" open
- * Switch "S" is closed at time $t = 0s$.
- i) Derive & sketch the current i_L through the inductor for $t > 0$
- ii) Find the time constant

At $t = 0^-$

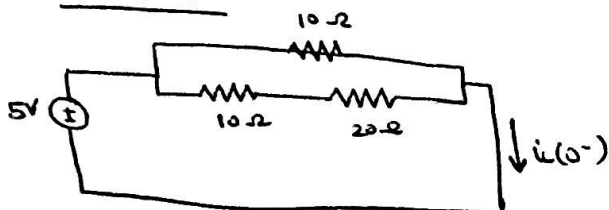

$$V = i_L(0^-) R_{eq}$$


$$5 = i_L(0^-) \left[\frac{(20)(10)}{20+10} \right] = i_L(0^-) \left(\frac{200}{30} \right)$$

$$i_L(0^-) = \frac{2}{3} \text{ Amps} = 0.667 \text{ Amps}$$

* Saturated Inductor = short circuit

* $i_L(0^-)$ represents total current in circuit

At $t = 0^+$

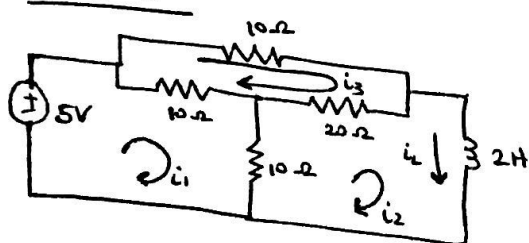

Loop Equations

$$-5 + 10(i_1 - i_3) + 10(i_1 - i_2) = 0$$

$$20i_1 - 10i_2 - 10i_3 = 5 \quad \text{--- [1]}$$

$$10i_3 + 20(i_3 - i_2) + 10(i_3 - i_1) = 0$$

$$i_1 + 2i_2 - 4i_3 = 0 \quad \text{--- [3]}$$

Substituting [3] in [1]

$$[3] \text{ becomes } \rightarrow i_3 = \frac{i_1 + 2i_2}{4} \rightarrow \text{substitute into [1]}$$

$$[1] \text{ becomes: } 20i_1 - 10i_2 - 10 \left[\frac{i_1 + 2i_2}{4} \right] = 5$$

$$7i_1 - 6i_2 = 2$$

$$i_1 = \frac{2 + 6i_2}{7}$$

Loop 2: $20(i_2 - i_3) + 2 \frac{di_2}{dt} + 10(i_2 - i_1) = 0$

$$20i_2 - 20 \left[\frac{i_1 + 2i_2}{4} \right] + 2 \frac{di_2}{dt} + 10i_2 - 10i_1 = 0$$

$$2 \frac{di_2}{dt} + 20i_2 = 15i_1 = 15 \left[\frac{2 + 6i_2}{7} \right]$$

$$\frac{di_2}{dt} + 3.5714 i_2 = 2.1429$$

$$\rightarrow i_2(t) = \frac{2.1429}{3.5714} + K e^{-3.5714t}$$

$$i_2(t) = 0.6 + K e^{-3.5714t}$$

$$i_2(0) = 0.6 + K = 0.667$$

$$K = 0.067$$

$$i_2(t) = 0.6 + 0.067 e^{-3.57t}$$

