
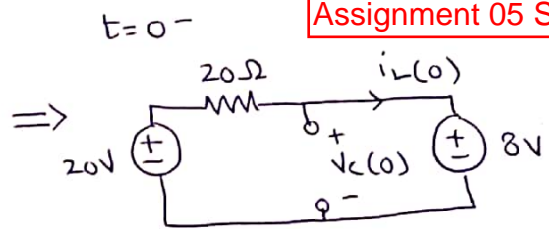



1.

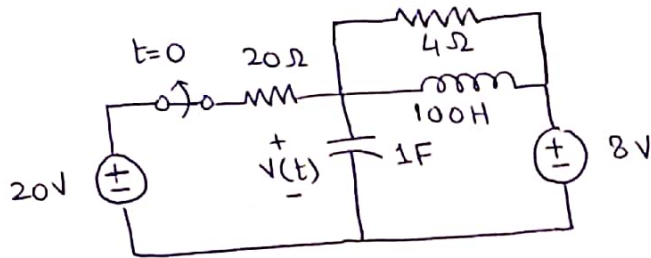

$$v_C(0) = 8V$$

$$i_L(0) = \frac{20-8}{20} = 0.6A$$

t=0+

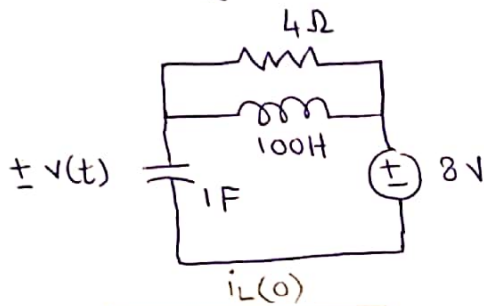

$$\frac{dv(t)}{dt} + \frac{1}{100} \int (v(t)-8) dt + \frac{v(t)-8}{4} = 0 \Rightarrow \frac{dv(t)}{dt} = -0.6A$$

$$\frac{d^2v(t)}{dt^2} + 0.01(v(t)-8) + \frac{1}{4} \frac{dv(t)}{dt} = 0$$

$$\frac{d^2v(t)}{dt^2} + 0.25 \frac{dv(t)}{dt} + 0.01v(t) = 0.08$$

char eq: $s^2 + 0.25s + 0.01 = 0$

$$s_1 = -0.05, -0.2$$

$$v_C(t) = K_1 e^{-0.05t} + K_2 e^{-0.2t}$$

$$v_p(t) = A$$

$$v_p'(t) = v_p''(t) = 0$$

$$\Rightarrow 0.01A = 0.08$$

$$\boxed{A=8}$$

$$v_p(t) = 8V$$

$$v(t) = K_1 e^{-0.05t} + K_2 e^{-0.2t} + 8$$

$$v(0) = K_1 + K_2 + 8 = 8$$

$$K_1 + K_2 = 0 \quad (1)$$



$$\frac{dv(0)}{dt} = -0.05K_1 - 0.2K_2 = -0.6 \quad (2)$$

solving (1) & (2) $\Rightarrow K_1 = -4$

$$K_2 = 4$$

$$v(t) = -4e^{-0.05t} + 4e^{-0.2t} + 8 \quad \checkmark \quad t > 0 \quad \text{ANS}$$

2.

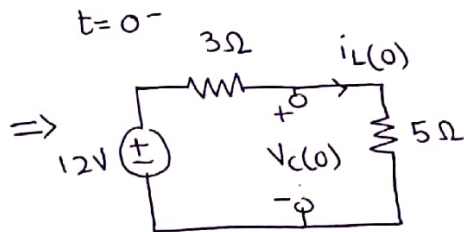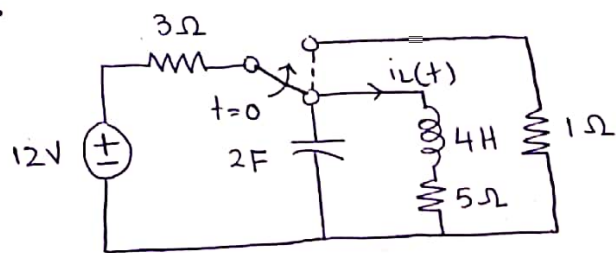


$$i_L(0) = \frac{12}{8} = 1.5 \text{ A}$$

$$V_C(0) = \frac{5}{8} \times 12 = 7.5 \text{ V}$$

↓

$t=0^+$

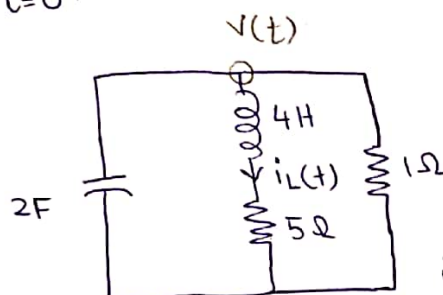

7.5

$$V_C(t) = \frac{4 \frac{di(t)}{dt}}{dt} + 5i(t)$$

5(1.5)

$$\frac{dV(t)}{dt} = 4 \frac{d^2 i(t)}{dt^2} + 5 \frac{di(t)}{dt}$$

$$i(t) + \frac{V(t)}{1} + \frac{2 \frac{dV(t)}{dt}}{dt} = 0$$

$$i(t) + \frac{4 \frac{di(t)}{dt}}{dt} + 5i(t) + \frac{8 \frac{d^2 i(t)}{dt^2}}{dt^2} + \frac{10 \frac{di(t)}{dt}}{dt} = 0$$

$$4 \frac{di(t)}{dt} = 7.5 - 5(1.5)$$

$$\frac{di(0)}{dt} = 0 \text{ A s}^{-1}$$

$$\frac{8 \frac{d^2 i(t)}{dt^2}}{dt^2} + \frac{14 \frac{di(t)}{dt}}{dt} + 6i(t) = 0$$

$$8s^2 + 14s + 6 = 0$$

$$s_1 = -0.75$$

$$s_2 = -1$$

$$i(t) = K_1 e^{-0.75t} + K_2 e^{-t}$$

$$\frac{di(t)}{dt} = -0.75 K_1 e^{-0.75t} - K_2 e^{-t}$$

$$i(0) = K_1 + K_2 = 1.5 \quad (1)$$

$$\frac{di(0)}{dt} = -0.75 K_1 - K_2 = 0 \quad (2)$$


solving (1) & (2)

$$K_1 = 6$$


$$K_2 = -4.5$$

$$i(t) = 6e^{-0.75t} - 4.5e^{-t} \text{ A} \quad t > 0 \quad \text{ANS}$$

3.

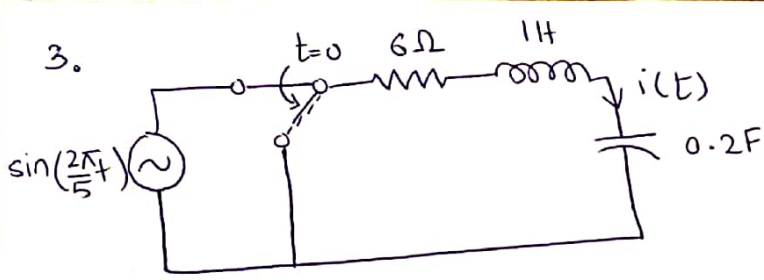

$t=0^-$

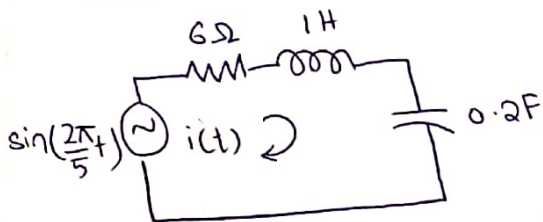

$$6i(t) + \frac{di(t)}{dt} + 5 \int i(t) dt = \sin\left(\frac{2\pi}{5} t\right)$$

$$6 \frac{di(t)}{dt} + \frac{d^2 i(t)}{dt^2} + 5i(t) = \frac{2\pi}{5} \cos\left(\frac{2\pi}{5} t\right)$$

$$i_p(t) = A \cos\left(\frac{2\pi}{5} t\right) + B \sin\left(\frac{2\pi}{5} t\right)$$

$$i_p'(t) = -\frac{2\pi}{5} A \sin\left(\frac{2\pi}{5} t\right) + \frac{2\pi}{5} B \cos\left(\frac{2\pi}{5} t\right)$$

$$i_p''(t) = -\frac{4\pi^2}{25} A \cos\left(\frac{2\pi}{5} t\right) - \frac{4\pi^2}{25} B \sin\left(\frac{2\pi}{5} t\right)$$

$$-\frac{12\pi}{5} A \sin\left(\frac{2\pi}{5} t\right) + \frac{12\pi}{5} B \cos\left(\frac{2\pi}{5} t\right) - \frac{4\pi^2}{25} A \cos\left(\frac{2\pi}{5} t\right) - \frac{4\pi^2}{25} B \sin\left(\frac{2\pi}{5} t\right) + 5A \cos\left(\frac{2\pi}{5} t\right)$$

$$+ 5B \sin\left(\frac{2\pi}{5} t\right) = \frac{2\pi}{5} \cos\left(\frac{2\pi}{5} t\right)$$

$$-\frac{12\pi}{5} A - \frac{4\pi^2}{25} B + 5B = 0$$

$$-\frac{12\pi}{5} A = \left(\frac{4\pi^2}{25} - 5\right) B$$

$$B = 2.204 A$$

$$\frac{12\pi}{5} B - \frac{4\pi^2}{25} A + 5A = \frac{2\pi}{5}$$

$$16.628 A - \frac{4\pi^2}{25} A + 5A = \frac{2\pi}{5}$$

$$A = 0.0627$$

$$B = 0.138$$

$$i_p(t) = 0.0627 \cos\left(\frac{2\pi}{5} t\right) + 0.138 \sin\left(\frac{2\pi}{5} t\right)$$

$$i(0) = i_p(0) = 0.0627 A$$


$$\frac{di(0)}{dt} = \frac{di_p(0)}{dt} = 0.138 \times \frac{2\pi}{5} = 0.174 \text{ As}^{-1}$$

$$6i(t) + \frac{di(t)}{dt} + 5 \int i(t) dt = \sin\left(\frac{2\pi}{5} t\right)$$

$$-(6(0.0627) + 0.174) = v_c(0)$$

$$v_c(0) = -0.550 \text{ V}$$

$$t = 0^+$$

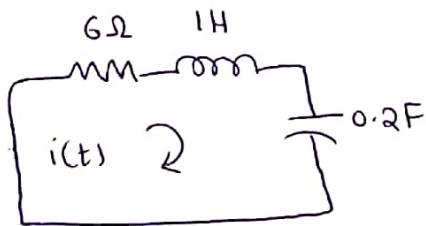

$$6i(t) + \frac{di(t)}{dt} + 5 \int i(t) dt = 0 \Rightarrow \frac{di(0)}{dt} = 0.550 - 6(0.0627)$$

$$\frac{d^2i(t)}{dt^2} + 6\frac{di(t)}{dt} + 5i(t) = 0 \quad \frac{di(0)}{dt} = 0.174 \text{ As}^{-1}$$

$$s^2 + 6s + 5 = 0$$

$$s_1 = -1$$

$$s_2 = -5$$

$$i(t) = K_1 e^{-t} + K_2 e^{-5t}$$

$$i(0) = K_1 + K_2 = 0.0627$$

$$\frac{di(t)}{dt} = \cancel{-K_1 e^{-t} - 5K_2 e^{-5t}} - K_1 e^{-t} - 5K_2 e^{-5t}$$

$$\frac{di(0)}{dt} = -K_1 - 5K_2 = 0.174$$

solving simultaneously:

$$K_1 = 0.122$$

$$K_2 = -0.060$$

$$i(t) = 0.122e^{-t} - 0.060e^{-5t} \text{ A} \quad t > 0 \quad \text{ANS}$$

Q4-

$$\underline{t > 0^-}$$


$$i(0^-) = 0 \text{ A}$$

$$\underline{t > 0^+}$$

$$i(0^+) = i(0^-) = 0 \text{ A}$$

(inductor prevents instantaneous change in current)

For $t > 0$:

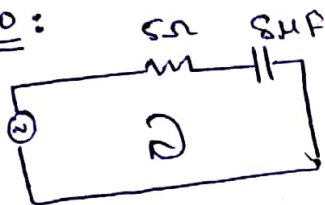

Loop eq:

$$5i(t) + \frac{1}{8\mu\text{F}} \int i(t) dt = 40e^{-2t} \cos(t)$$

Taking derivative and simplifying:

$$\frac{di(t)}{dt} + 25000 i(t) = -8e^{-2t} \sin(t) - 16e^{-2t} \cos(t) \quad \text{--- ①}$$

$$\text{Now, } i(t) = i_c(t) + i_p(t)$$

1) for $i_c(t)$, characteristic eq. from ①:

$$s + 25000 = 0$$

$$s = -25000$$

$$i_c(t) = Ke^{-25000t}$$

2) For $i_p(t)$:

Solution will be in the form:

$$i_p(t) = [A \cos(t) + B \sin(t)] e^{-2t}$$

$$\frac{di_p}{dt} = [A \cos(t) + B \sin(t)] (-2e^{-2t}) + [-A \sin(t) + B \cos(t)] e^{-2t}$$

Putting these in ①:

$$[A \cos(t) + B \sin(t)] (-2e^{-2t}) + [-A \sin(t) + B \cos(t)] e^{-2t}$$

$$+ 25000 [(A \cos(t) + B \sin(t)) e^{-2t}] = -8e^{-2t} \sin(t) - 16e^{-2t} \cos(t)$$

$$e^{-2t} \cos(t) [-2A + B + 25000 A] + e^{-2t} \sin(t) [-2B - A + 25000 B] \\ = -8e^{-2t} \sin(t) - 16e^{-2t} \cos(t)$$

By comparison :

$$24998 A + B = -16$$

$$-A + 24998 B = -8$$

Solving simultaneously :

$$A = -6.4 \times 10^{-4}$$

$$B = -3.2 \times 10^{-4}$$

$$\Rightarrow i_p = [(-6.4 \times 10^{-4}) \cos(t) + (-3.2 \times 10^{-4}) \sin(t)] e^{-2t}$$

$$\therefore i(t) = K e^{-25000t} + [(-6.4 \times 10^{-4}) \cos(t) + (-3.2 \times 10^{-4}) \sin(t)] e^{-2t}$$

For K, using $i(0^+) = 0$

$$i(0^+) = K e^{-25000(0)} + [(-6.4 \times 10^{-4}) \cos(0) + (-3.2 \times 10^{-4}) \sin(0)] e^{-2(0)} = 0$$

$$K - 6.4 \times 10^{-4} = 0$$

$$K = 6.4 \times 10^{-4}$$

$$\Rightarrow \boxed{i(t) = (6.4 \times 10^{-4}) e^{-15000t} + [(-6.4 \times 10^{-4}) \cos(t) + (-3.2 \times 10^{-4}) \sin(t)] e^{-2t}}$$

Parallel RLC circuit

QUESTION #5

$$R = 2 \text{ k}\Omega$$

$$L = 250 \text{ mH}$$

$$C = 10 \text{ nF}$$

a) Voltage Response Characteristic Equation + roots.

$$\text{neper frequency } \alpha = \frac{1}{2RC} = \frac{1}{(2)(2000)(10 \times 10^{-9})} = 25,000 \text{ rad/s}$$

$$\text{resonant radian frequency } \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(0.25)(10 \times 10^{-9})}} = 20,000 \text{ rad/s}$$

$$\begin{aligned} \text{Roots: } s_1 &= -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -25,000 + \sqrt{(25,000)^2 - (20,000)^2} = -10,000 \text{ rad/s} \\ s_2 &= -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -25,000 - \sqrt{(25,000)^2 - (20,000)^2} = -40,000 \text{ rad/s} \end{aligned}$$

b) $\omega_0^2 < \alpha^2$, therefore voltage response is over-damped.

$$\text{c) } \omega_d = \sqrt{\omega_0^2 - \alpha^2} \rightarrow \alpha = \sqrt{\omega_0^2 - \omega_d^2} = \sqrt{20,000^2 - 12,000^2} = 16,000 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} \rightarrow R = \frac{1}{2\alpha C} = \frac{1}{(2)(16,000)(10 \times 10^{-9})} = 3.125 \text{ k}\Omega = 3125 \Omega$$

d) $\omega_0^2 > \alpha^2$, therefore voltage response is under damped

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{20,000^2 - 16,000^2} = 12,000 \text{ rad/s}$$

$$s = -\alpha \pm j\omega_d$$


$$s_1 = -\alpha + j\omega_d = -16,000 + j12,000 \text{ rad/s}$$

$$s_2 = -\alpha - j\omega_d = -16,000 - j12,000 \text{ rad/s}$$

e) critically damped occurs when $\omega_0^2 = \alpha^2 = 20,000 \text{ rad/s}$

$$R = \frac{1}{2\alpha C} = \frac{1}{(2)(20,000)(10 \times 10^{-9})} = 2500 \Omega = 2.5 \text{ k}\Omega$$

QUESTION #6

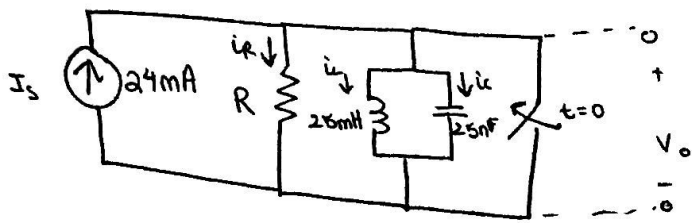

a) $R = 400 \Omega$

- Initial value i_L
- Initial value di/dt
- Char Eq & Roots
- expression $i_L(t)$ for $t \geq 0$. Plot 0-20 μs

b) $R = 625 \Omega$. Expression + plot

c) $R = 800 \Omega$. Expression + plot

d) compare graphs. Time for 90% output, which R-system = fastest

a) i) No energy stored $t < 0$. Current stored in Inductor = 0 & Inductor doesn't permit instantaneous change. $i_L(0) = 0$

ii) Initial Voltage on Capacitor = 0. Same at 0^+ .

$$V = L \frac{di_L}{dt} \rightarrow \frac{di_L}{dt}(0^+) = 0$$

iii) $\omega_0^2 = \frac{1}{LC} = \frac{10^8}{(25)(25)} = 16 \times 10^8$

$$\alpha = \frac{1}{2RC} = \frac{10^9}{(2)(400)(25)} = 5 \times 10^4 \text{ rad/s} ; \alpha^2 = 25 \times 10^8$$

$\omega_0^2 < \alpha^2 \therefore$ real & distinct roots.

iv) Inductor Current Response = overdamped.

$$i_L = I_f + A_1' e^{s_1 t} + A_2' e^{s_2 t}$$

$$i_L(0) = I_f + A_1' + A_2' = 0$$

$$\frac{di_L(0)}{dt} = s_1 A_1' + s_2 A_2' = 0 \quad \left[\begin{array}{l} \text{solve} \\ \text{simultaneously} \end{array} \right] \Rightarrow \begin{array}{l} A_1' = -32 \text{ mA} \\ A_2' = 8 \text{ mA} \end{array}$$

$$i_L(t) = 24 - 32e^{-20,000t} + 8e^{-80,000t} \text{ mA for } t \geq 0$$

$$\begin{aligned} s_1 &= (-5 \times 10^4) + (3 \times 10^4) \\ &= -20,000 \text{ rad/s} \\ s_2 &= (-5 \times 10^4) - (3 \times 10^4) \\ &= -80,000 \text{ rad/s} \end{aligned}$$

b) L & C same $\therefore \omega_0^2$ same = 16×10^8
 $R \uparrow$, so $\alpha \downarrow$. $\alpha = 3.2 \times 10^4 \text{ rad/s}$ } $\omega_0^2 > \alpha^2$ = complex roots. (underdamped)

$$s_1 = -3.2 \times 10^4 + j 2.4 \times 10^4 \text{ rad/s}$$

$$s_2 = -3.2 \times 10^4 - j 2.4 \times 10^4 \text{ rad/s}$$

$$i_L(t) = I_f + B_1' e^{-\alpha t} \cos(\omega_d t) + B_2' e^{-\alpha t} \sin(\omega_d t)$$

$$\alpha = 32 \text{ K rad/s}, \omega_d = 24 \text{ K rad/s}, I_f = 24 \text{ mA}$$

$$i_L(0) = I_f + B_1' = 0$$

$$\frac{di_L(0)}{dt} = \omega_d B_2' - \alpha B_1' = 0 \quad \left[\begin{array}{l} B_1' = -24 \text{ mA} \\ B_2' = -32 \text{ mA} \end{array} \right] \Rightarrow$$

$$i_L(t) = 24 - 24e^{-32,000t} \cos(24,000t) - 32e^{-32,000t} \sin(24,000t) \text{ mA for } t \geq 0$$

c) L & C same $\therefore \omega_0^2$ same = 16×10^8
 $R = 800 \Omega$, $\alpha = 4 \times 10^4 / s$ (critical damping)

$$i_L(t) = I_f + C_1' t e^{-\alpha t} + C_2' e^{-\alpha t}$$

$$i_L(0) = I_f + C_2' = 0$$

$$\frac{di_L(0)}{dt} = C_1' - \alpha C_2' = 0 \quad \left[\begin{array}{l} C_1' = -960,000 \text{ mA/s} \\ C_2' = -24 \text{ mA} \end{array} \right]$$

$$i_L(t) = 24 - 960,000 t e^{-40,000t} - 24 e^{-40,000t} \text{ mA for } t \geq 0$$

d) Final Value $i_L = 24 \text{ mA}$, 90% = 21.6 mA
 $R = 625 \Omega$ (under damped) $\rightarrow t = 74 \mu s$
 $R = 800 \Omega$ (critically damped) $\rightarrow t = 97 \mu s$
 $R = 400 \Omega$ (over damped) $\rightarrow t = 130 \mu s$
 underdamped response at $R = 625 \Omega$ reaches 90% output fastest.

Q7.

$$a) \frac{di^2}{dt^2} + 6 \frac{di}{dt} + 8i = 5 \cos(7t)$$

$$1) i_c(t) = ?$$

$$\text{Characteristic eq: } s^2 + 6s + 8 = 0$$

$$\text{Solving: } (s+2)(s+4) = 0$$

$$s = -2, -4$$

$$i_c(t) = K_1 e^{-2t} + K_2 e^{-4t}$$

$$2) i_p(t) = A \cos(7t) + B \sin(7t)$$

$$\frac{di_p}{dt} = -7A \sin(7t) + 7B \cos(7t)$$

Plugging into original equation:

$$\begin{aligned} -49A \cos(7t) - 49B \sin(7t) - 42A \sin(7t) + 42B \cos(7t) \\ + 8A \cos(7t) + 8B \sin(7t) = 5 \cos(7t) \end{aligned}$$

By comparison:

$$-49A + 42B + 8A = 5$$

$$-49B - 42A + 8B = 0$$

$$-41A + 42B = 5 \quad \text{--- (1)}$$

$$-42A - 41B = 0 \quad \text{--- (2)}$$

$$\Rightarrow A = -0.0595, B = 0.0610$$

$$\Rightarrow i(t) = K_1 e^{-2t} + K_2 e^{-4t} - 0.0595 \cos(7t) + 0.0610 \sin(7t)$$



Using conditions for K_1 and K_2 :

$$1) i(0^+) = K_1 + K_2 - 0.0595 = 3.94$$

$$\Rightarrow K_1 + K_2 = 4 \quad \text{--- (3)}$$

$$2) \frac{di(0^+)}{dt} = -2K_1 - 4K_2 + 0.427 = -9.57$$

$$\Rightarrow 2K_1 + 4K_2 = 10 \quad \text{--- (4)}$$

$$\Rightarrow K_1 = 3, K_2 = 1$$

$$i(t) = 3e^{-2t} + e^{-4t} - 0.0595 \cos(7t) + 0.0610 \sin(7t)$$

$$b) \frac{d^3 i}{dt^3} + 10 \frac{d^2 i}{dt^2} + 31 \frac{di}{dt} - 30i = 0$$

This is a homogenous equation, hence only the complementary solution exists for this equation.

Char. eq:

$$s^3 + 10s^2 + 31s - 30 = 0$$

Solving:

$$s = -5, -2, -3$$

$$\Rightarrow i(t) = K_1 e^{-5t} + K_2 e^{-2t} + K_3 e^{-3t}$$

Using conditions to find K_1, K_2, K_3 :

$$1) i(0^+) = K_1 + K_2 + K_3 = 5 \quad \text{--- (1)}$$

$$2) \frac{di}{dt}(0^+) = -5K_1 - 2K_2 - 3K_3 = -6 \quad \text{--- (2)}$$


$$3) \frac{d^2 i}{dt^2}(0^+) = 25K_1 + 4K_2 + 9K_3 = 30 \quad \text{--- (3)}$$

Solving simultaneously:

$$\Rightarrow K_1 = 5, K_2 = 19, K_3 = -19$$

$$\Rightarrow \boxed{i(t) = 5e^{-5t} + 19e^{-2t} - 19e^{-3t}}$$

QUESTION # 8

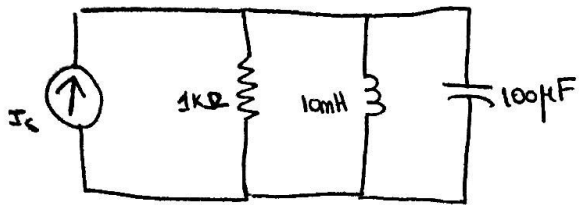

- a) Resonant Frequency
- b) Bandwidth
- c) Quality Factor


$$a) \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(10^{-2})(10^{-4})}} = 10^3 \text{ rad/s}$$

$$b) BW = \frac{1}{RC} = \frac{1}{(10^3)(100 \times 10^{-6})} = \frac{1}{0.1} = 10 \text{ rad/s}$$

$$c) QF = \frac{\omega_0}{BW} = \frac{\left(\frac{1}{\sqrt{LC}}\right)}{\left(\frac{1}{RC}\right)} = \frac{RC}{\sqrt{LC}} = R\sqrt{\frac{C}{L}} = 10^3 \sqrt{\frac{(10^{-4})}{(10^{-2})}} = 100$$

9. a) roots are $s_1 = -4, s_2 = -6$

char eq. $s^2 + 10s + 24$

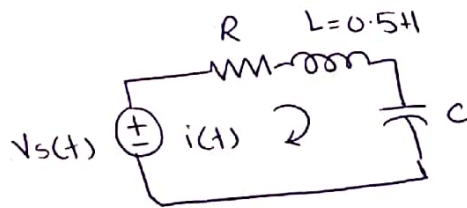

$$Ri(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt = v_s(t)$$

$$\frac{d^2 i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{1}{LC} i(t) = \frac{v_s'(t)}{L}$$

$$\frac{d^2 i(t)}{dt^2} + \frac{2R}{L} \frac{di(t)}{dt} + \frac{2}{C} i(t) = 2 \frac{v_s'(t)}{L}$$

$$2R = 10$$

$$R = 5 \Omega$$

$$\frac{2}{C} = 24$$

$$C = \frac{1}{12} F$$

b) $i(0) = 0 A$

$$\frac{di(0)}{dt} = \frac{v_s(0)}{L} = 2 \times 8 = 16 A s^{-1}$$

$$i(t) = K_1 e^{-4t} + K_2 e^{-6t} \rightarrow -25.5$$

$$i(t) = K_1 e^{-4t} + K_2 e^{-6t} + -2.5e^{-2t} + 30e^{-5t}$$

$$i(0) = K_1 - 25.5 - 2.5 + 30 = 0$$

$$K_1 = -2$$

$$X = -2$$

c) $v_L(t) = L \frac{di(t)}{dt}$

$$v_L(t) = 4e^{-4t} + 76.5e^{-6t} + 2.5e^{-2t} - 75e^{-5t}$$

$$v_L(1) = 0.0959 V$$