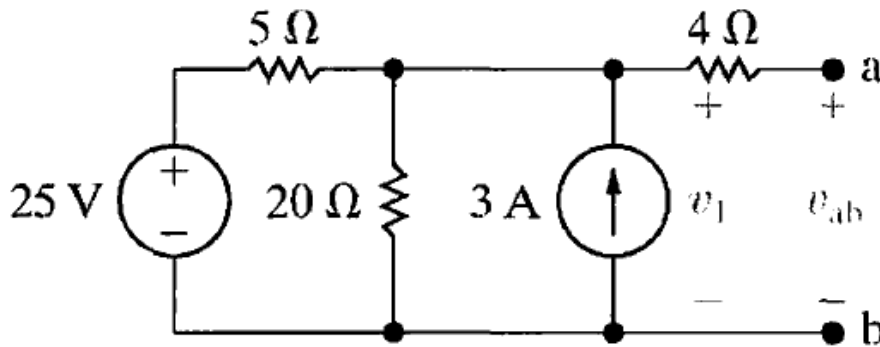


Thevenin's and Norton's Theorems

Problems – In class

Problem 1: Find the Thevenin's equivalent circuit for the following circuit.




V_{th} :

$$* V_{oc} = V_{ab} = v_1$$

$$* \frac{v_1 - 25}{5} + \frac{v_1}{20} = 3$$

$$\frac{v_1}{5} + \frac{v_1}{20} = 8 \Rightarrow \boxed{v_1 = 32V}$$


R_{th} : Find I_{sc} :

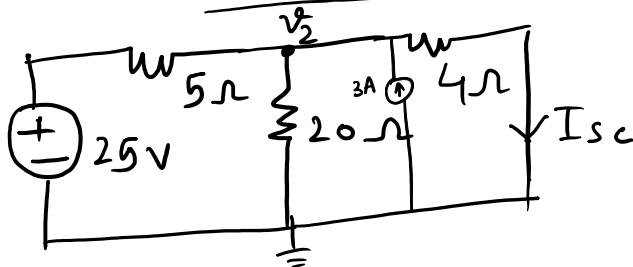

$$\frac{v_2 - 25}{5} + \frac{v_2}{20} + \frac{v_2}{4} = 3$$

$$v_2 = 16V \Rightarrow \boxed{I_{sc} = 4A}$$

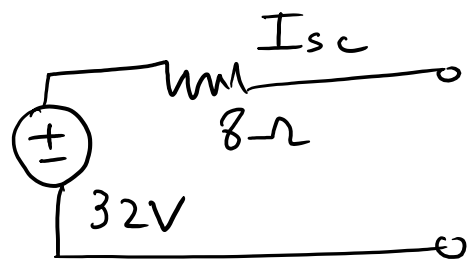
$$R_{th} = \frac{V_{th}}{I_{sc}} = 8\Omega$$





Thevenin's and Norton's Theorems

Problems – In class

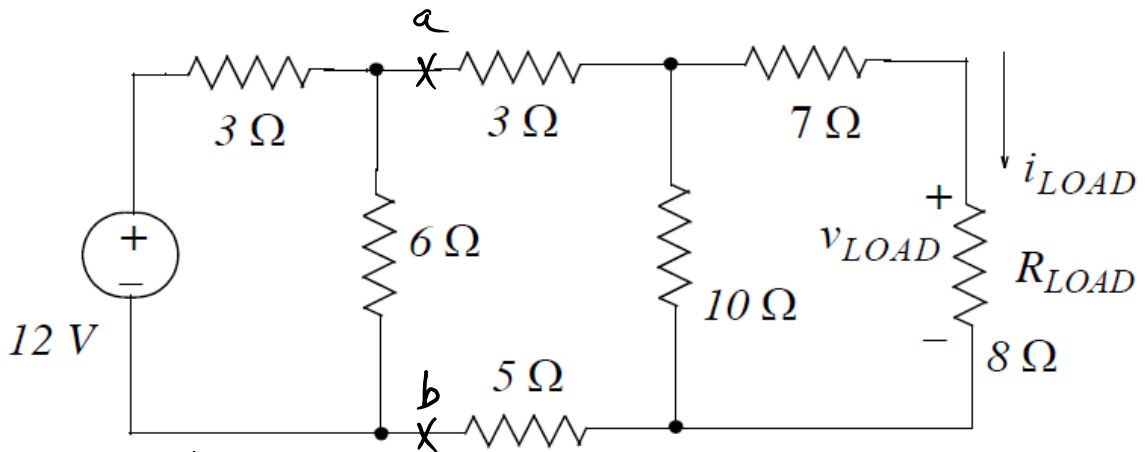
Problem 2: Find i_{LOAD} through R_{LOAD} using Thevenin's theorem



Thevenin at ab

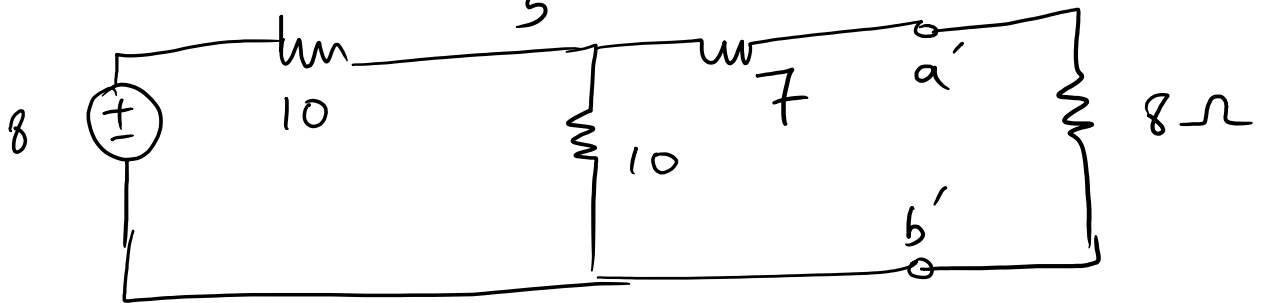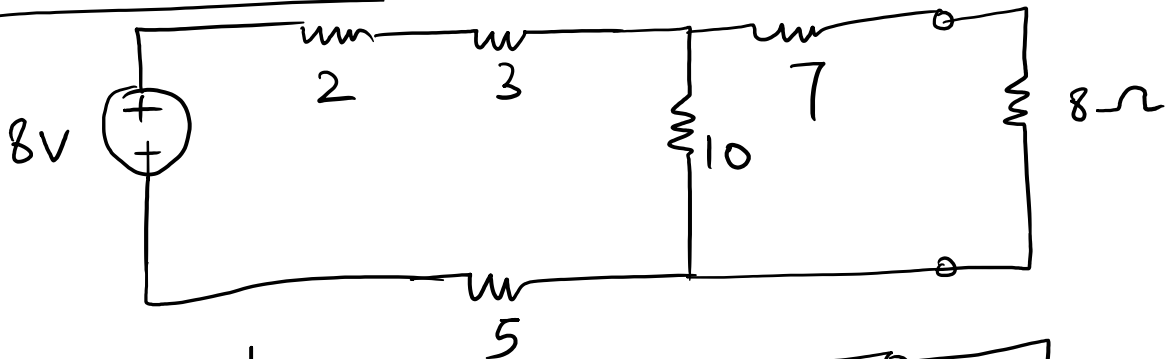

Thevenin at a' - b'



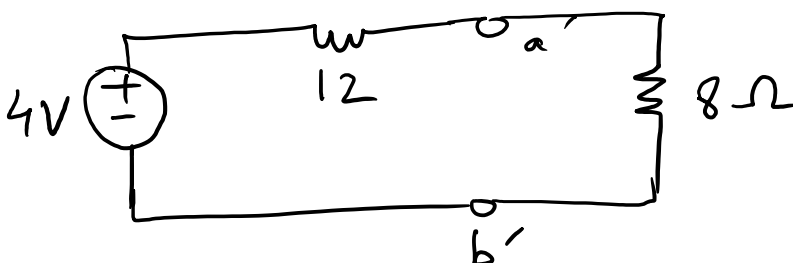


$$i_{LOAD} = \frac{4}{20} = 0.2A$$

Thevenin's and Norton's Theorems

Problems – In class

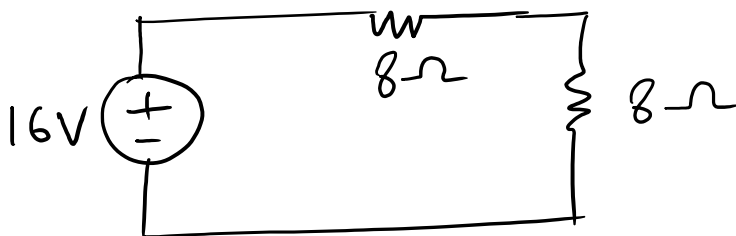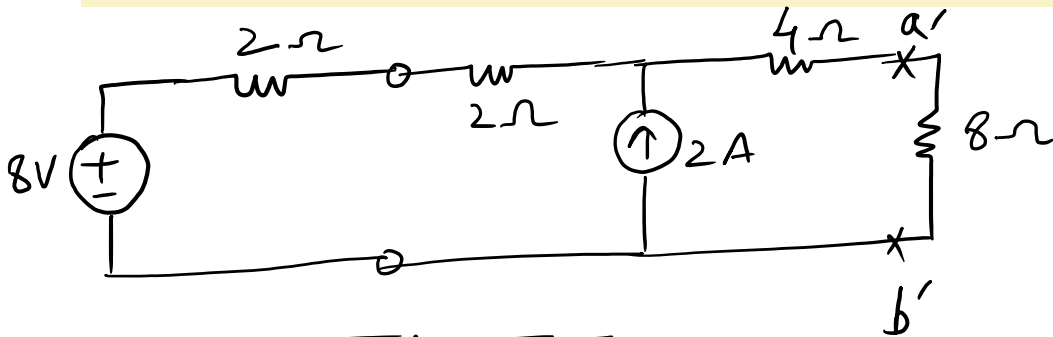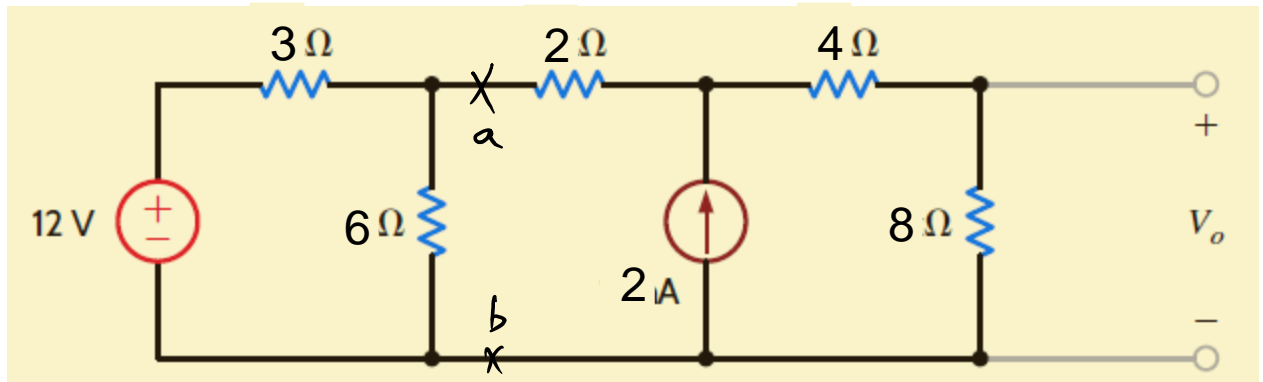Problem 3: Find V_o using Thevenin's theorem




$$V_o = 16 \times \frac{8}{16} = \boxed{8V}$$


Thevenin's and Norton's Theorems

Problems – In class

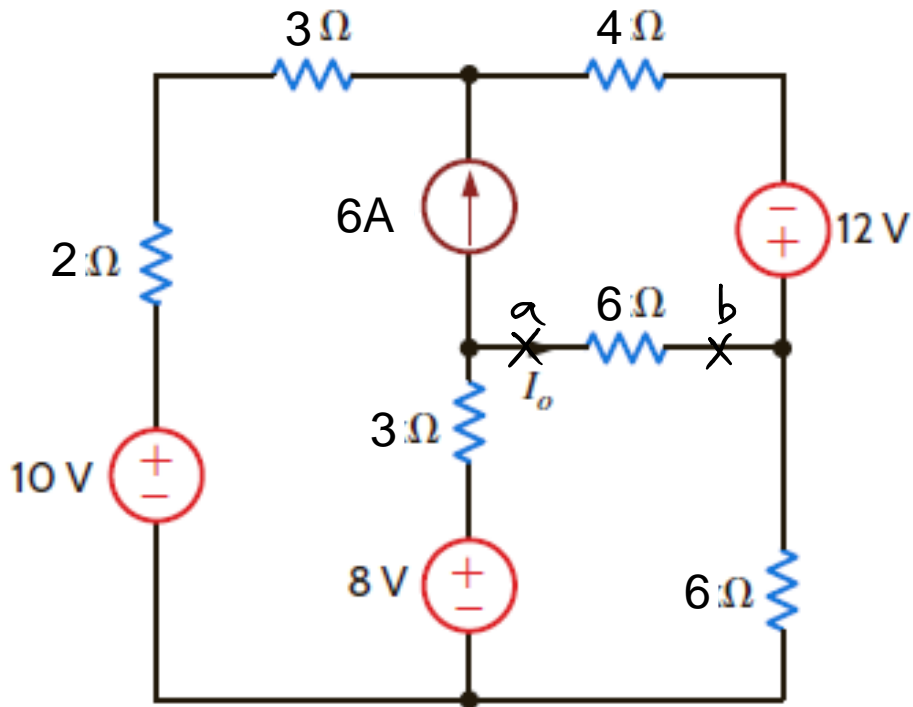Problem 4: Find I_o using Thevenin's or Norton's theorem




Equivalent^t : (computed on next page)

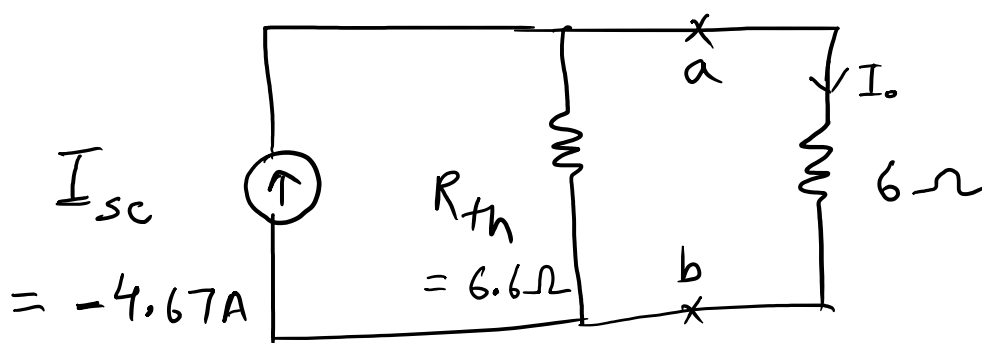

$$I_o = \frac{6.6}{12.6} \times (-4.67) = \underline{\underline{-2.44A}}$$

Thevenin's and Norton's Theorems

Problems – In class

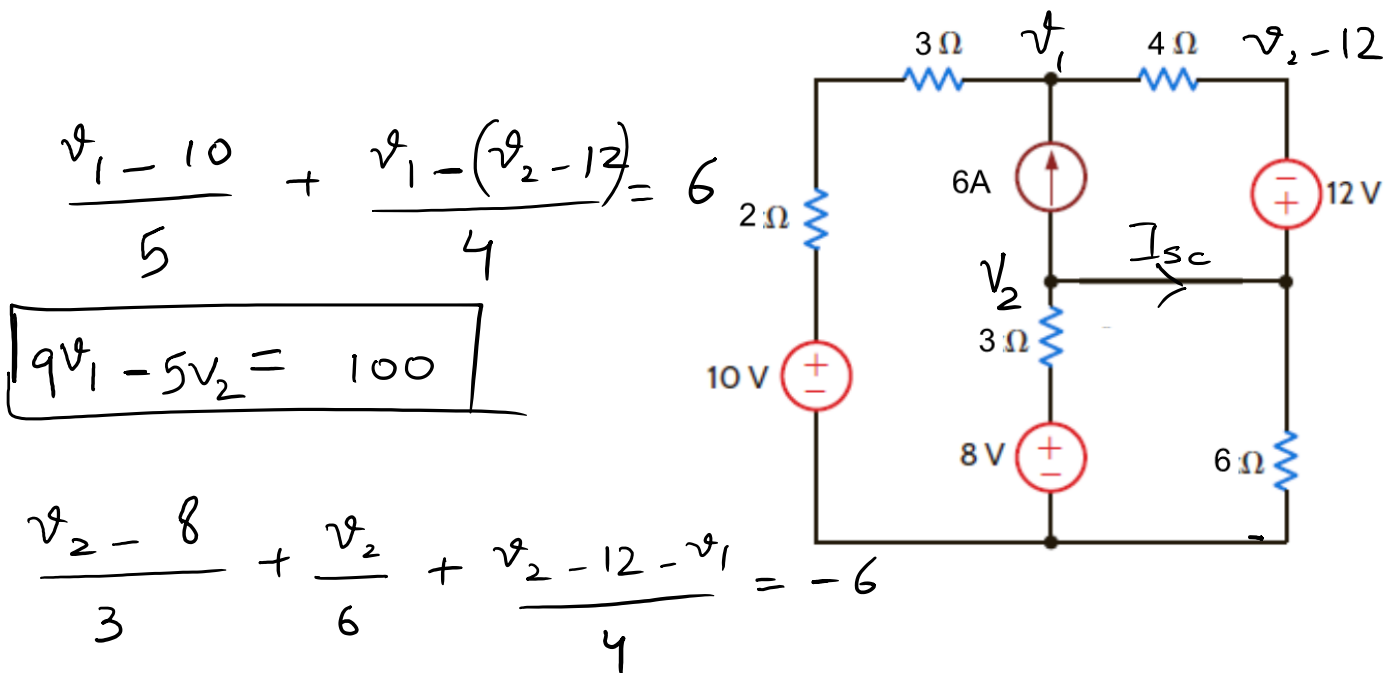


$$\Rightarrow \frac{4v_2 - 24 + 2v_2 + 3v_2 - 36 - 3v_1}{12} = -6$$

$-3v_1 + 9v_2 = -4$

 $\Rightarrow -9v_1 + 27v_2 = -12$
 $\Rightarrow 22v_2 = 88 \Rightarrow v_2 = 4V$


$$\frac{v_2 - 8}{3} + 6 + I_{sc} = 0 \Rightarrow I_{sc} = -4.667A$$

R_{tn}:

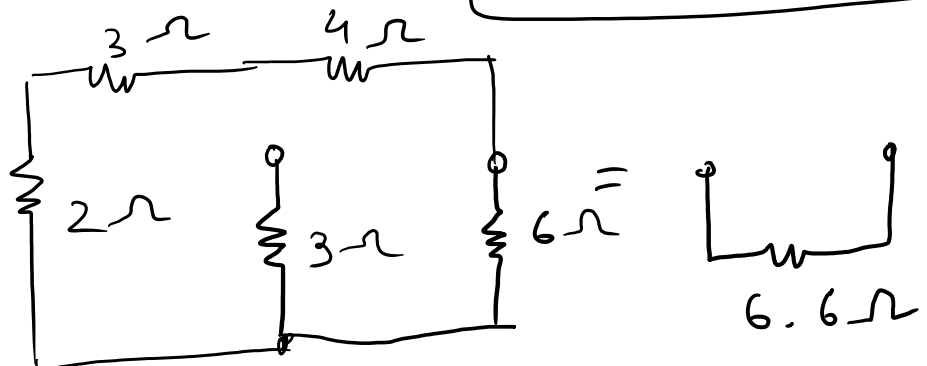


Thevenin's and Norton's Theorems

Problems – In class

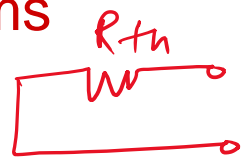

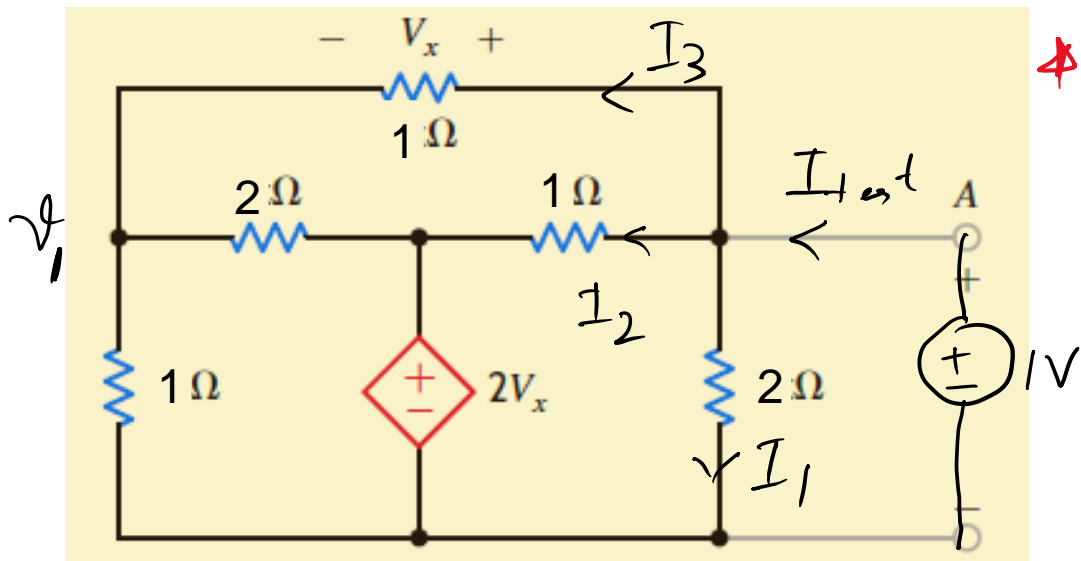Problem 5: Find the Thevenin equivalent circuit for the following circuit with respect to the terminals AB (Irwin – Example 5.8)



$V_{th} = 0V$

We have

$$V_x + V_1 = 1V \Rightarrow V_1 = 1 - V_x$$

KCL ; $\frac{V_1}{1} + \frac{V_1 - 2V_x}{2} + \frac{V_1 - 1}{1} = 0$

$$\Rightarrow 1 - V_x + \frac{1 - 3V_x}{2} - V_x = 0$$

$$\Rightarrow 3 = 7V_x \Rightarrow V_x = \frac{3}{7}V$$

$$I_1 = \frac{1}{2}A, I_2 = \frac{1 - 2(3/7)}{1} = \frac{1}{7}A$$

$$I_3 = \frac{3}{7}A$$

$$I_{ext} = I_1 + I_2 + I_3 = \frac{15}{14}A$$


EE240 Circuits I

$$\Rightarrow R_{th} = \frac{1}{I_{ext}} = \frac{14}{15}\Omega$$

Thevenin's and Norton's Theorems

Problems – In class

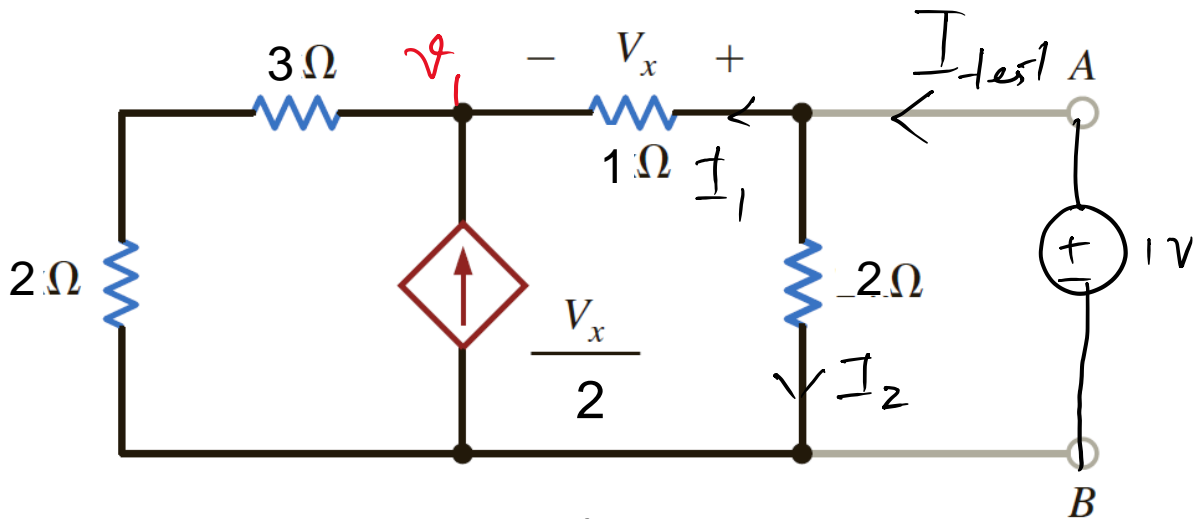Problem 6: Find the Thevenin equivalent circuit for the following circuit with respect to the terminals AB (Irwin – E 5.13)




$$\frac{V_1}{5} + \frac{V_1 - 1}{1} = \frac{V_x}{2} \quad \left\{ \begin{array}{l} V_x + V_1 = 1 \\ \Rightarrow V_x = 1 - V_1 \end{array} \right.$$

$$\Rightarrow \boxed{V_1 = \frac{15}{17} \text{ V}}$$

$$I_{\text{test}} = I_1 + I_2 = \frac{1}{2} + \frac{2}{17} = \frac{21}{34} \text{ A}$$

$$\left. \begin{array}{l} I_1 = \frac{1 - V_1}{1} = \frac{2}{17} \text{ A} \\ I_2 = \frac{1}{2} \end{array} \right\} \Rightarrow R_{\text{th}} = \frac{1}{I_{\text{test}}} = \frac{34}{21} \Omega$$


Equivalent :-

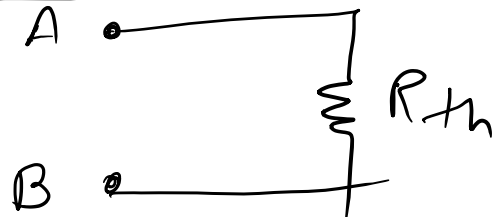

Thevenin's and Norton's Theorems

Problems – In class

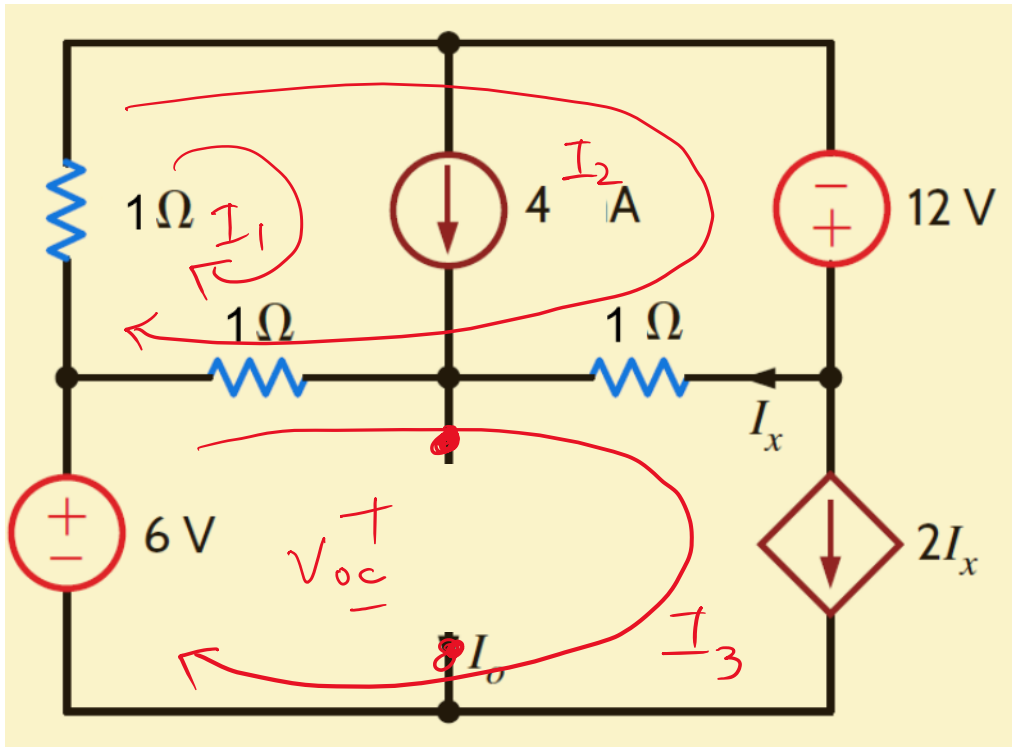Problem 7: Find I_o using Thevenin's theorem (See problem sheet for problems)



$$I_1 = 4A, \quad I_3 = 2I_x$$

$$\begin{aligned} \text{Loop 2} \quad & -12 + 1(I_2 - I_3) + 1(I_1 + I_2 - I_3) \\ & + (I_1 + I_2)1 = 0 \end{aligned}$$

$$I_x = I_2 - I_3 \Rightarrow \boxed{3I_x = I_2}$$

Solving


$$I_3 = \frac{8A}{5}, \quad I_2 = \frac{12A}{5}, \quad I_x = \frac{4}{5}A$$

$$V_{oc} = 6 + (I_1 + I_2 - I_3)1 = \frac{54}{5}V$$

Thevenin's and Norton's Theorems

Problems – In class

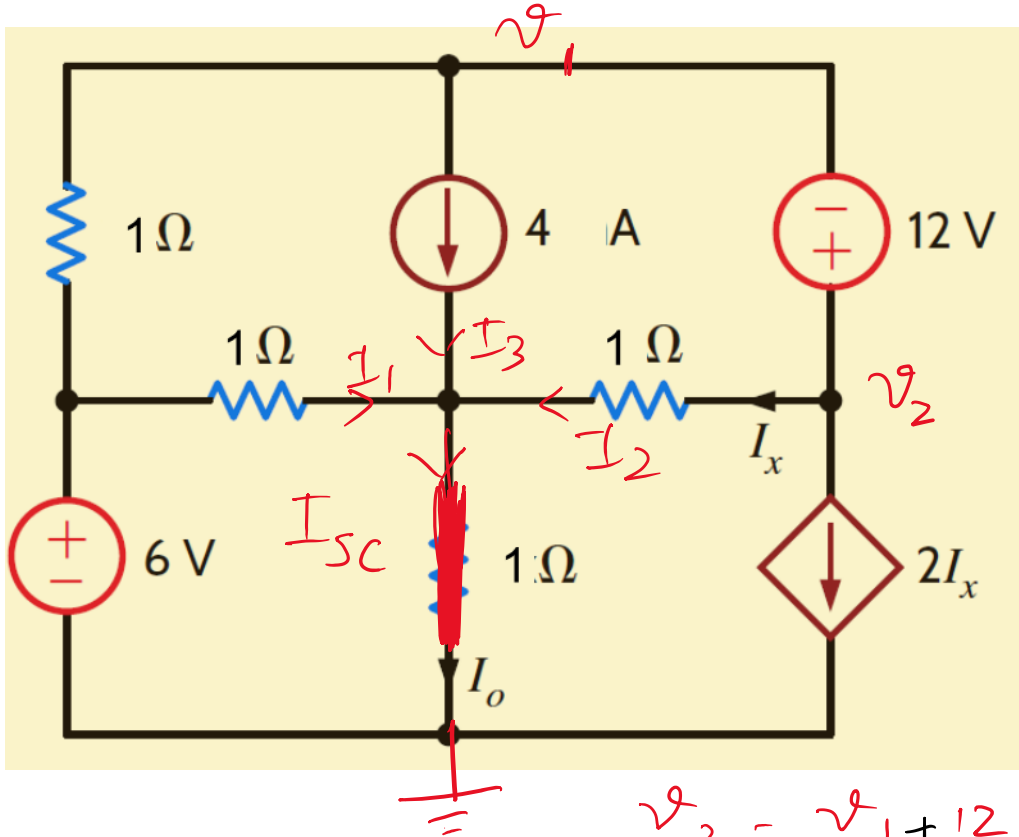Problem 7: Find I_o using Thevenin's theorem



$$v_2 = v_1 + 12 \quad (\text{Super Node})$$

$$\left. \begin{aligned} \frac{v_1 - 6}{1} + 4 + \frac{v_2}{1} + 2I_x &= 0 \end{aligned} \right\} I_x = \frac{v_2}{1}$$

$$\Rightarrow v_1 - 6 + 4 + 3v_1 + 36 = 0$$

$$\Rightarrow v_1 = -\frac{17}{2} \text{ V}, \quad v_2 = 7/2$$

$$I_{sc} = \frac{6}{1} + \frac{7}{2} + 4 = \frac{27}{2} \text{ A}$$


$$\Rightarrow R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{54/5}{27/2} = \frac{4}{5} \Omega$$

Thevenin's and Norton's Theorems


Problems – In class

Problem 7: Find I_o using Thevenin's theorem

Thevenin Equivalent

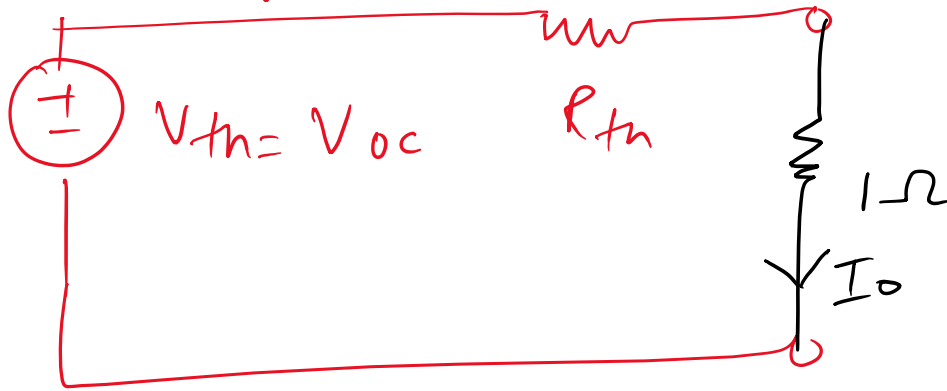

Norton Equivalent

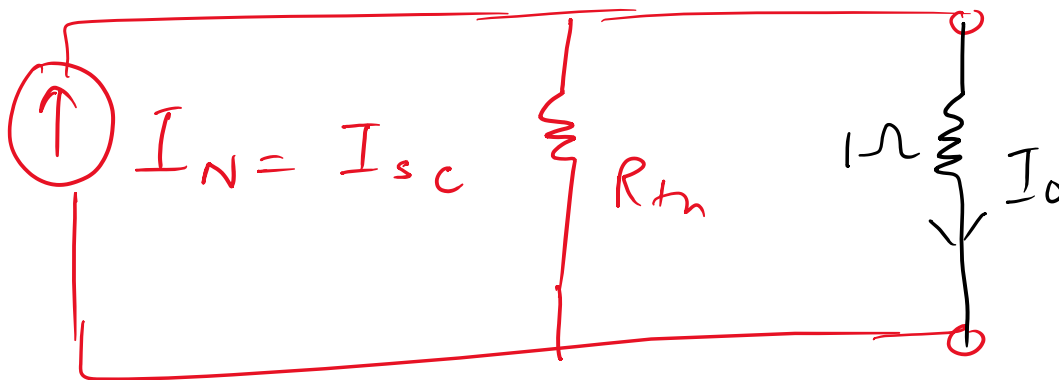


$$I_o = \frac{54/5}{1 + \frac{4}{5}} = \boxed{6 \text{ A}}$$

Thevenin's and Norton's Theorems

Problems – In class

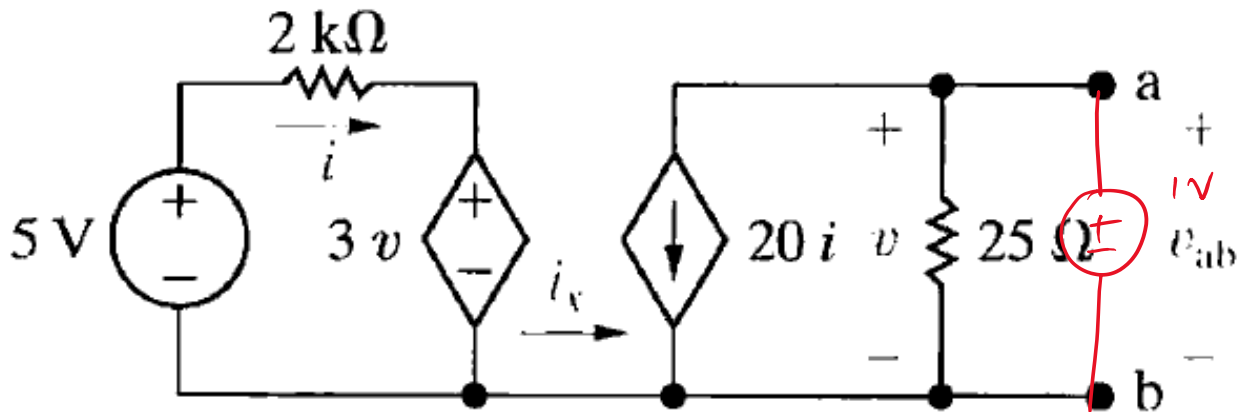Problem 8: Find the Thevenin equivalent circuit for the following circuit with respect to the terminals a,b




First find R_{th} :-

Switch off sources and connect 1V test source

$$v = 1V$$

$$3v = 3V$$

$$i = -3/2k$$

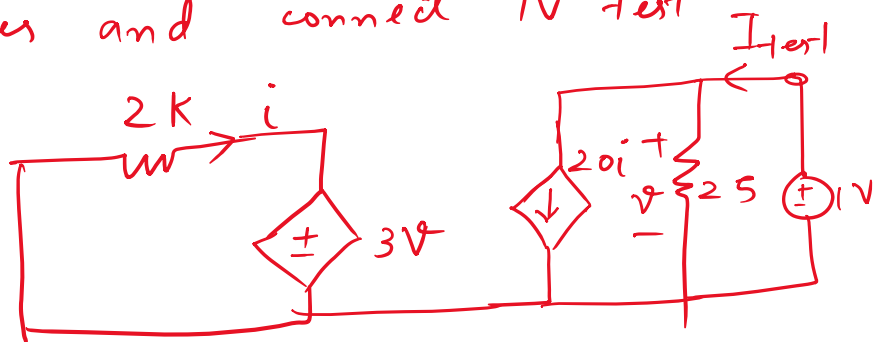

$$\Rightarrow I_{test} = \frac{1}{25} - (20)(i) = 0.04 - 0.03 = 0.01A$$

$$\Rightarrow \boxed{R_{th} = 100\Omega} \leftarrow \frac{1}{I_{sc}}$$

$$\underline{V_{th}}:- \quad \underline{v_{ab} = v = v_{th}}$$

$$V_{th} = -20i \times 25 - \textcircled{1}$$


$$i = \frac{25 - v_{th}}{2k} - \textcircled{2}$$

$$\textcircled{1} + \textcircled{2} \Rightarrow \boxed{V_{th} = -5V}$$

Thevenin's and Norton's Theorems

Problems – In class

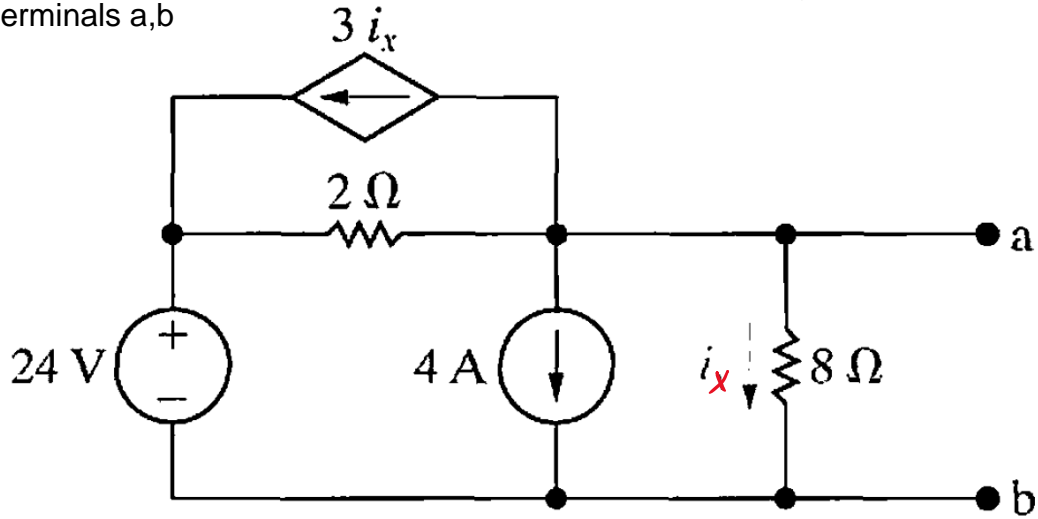Problem 9: Find the Thevenin equivalent circuit for the following circuit with respect to the terminals a,b



* Circuit contains both dependent and Independent sources; we can use either of the following techniques

- 1) Determine V_{ab} and I_{sc}
- 2) Determine V_{ab} ; Determine R_{th} by switching off **independent** sources and applying test current (or voltage) source at a-b.

Let's apply 2)

Using KCL;

V_{ab} :

$$\frac{V_{ab}}{8} + \frac{V_{ab} - 24}{2} + 3i_x + 4 = 0$$


where

$$i_x = \frac{V_{ab}}{8} \Rightarrow \boxed{V_{ab} = 8i_x}$$

Solving $\boxed{V_{ab} = 8V}$


R_{th} : Apply 1V voltage source :

Switch off
Sources

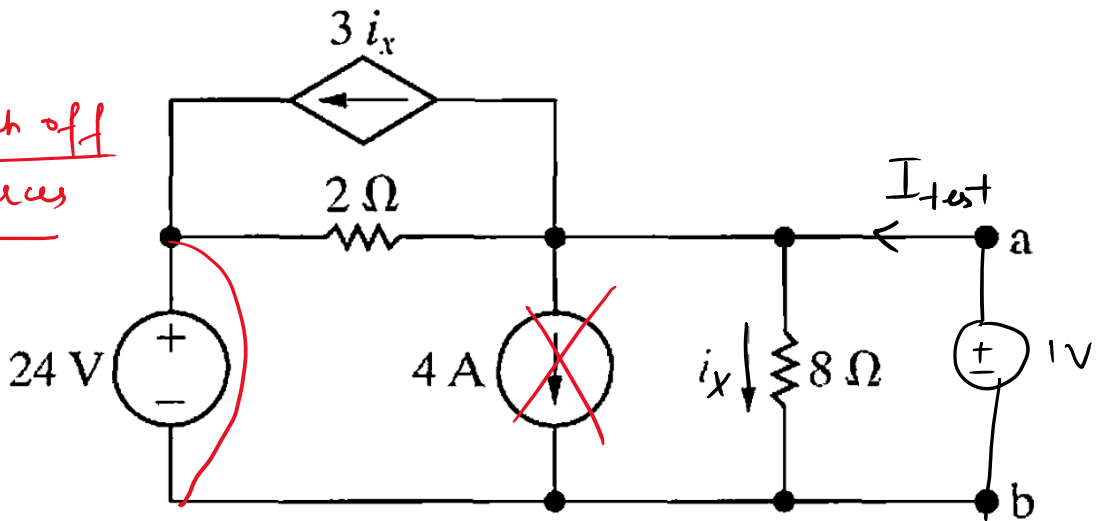

$$i_x = \frac{1}{8} \text{ A}$$
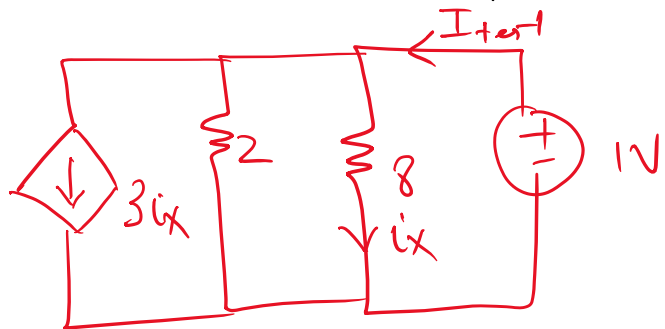
$$\begin{aligned} I_{test} &= \frac{1}{8} + \frac{1}{2} + \frac{3}{8} \\ &= \frac{8}{8} = 1 \text{ A} \end{aligned}$$



$$\Rightarrow R_{th} = \frac{1 \text{ V}}{I_{test}} = \underline{\underline{1 \Omega}}$$