

LAHORE UNIVERSITY OF MANAGEMENT SCIENCES  
Department of Electrical Engineering

EE240 Circuits I  
Quiz 01 - Section 1 - Solutions

Name: \_\_\_\_\_

Campus ID: \_\_\_\_\_

Total Marks: 10

Time Duration: 15 minutes

Question 1 (10 marks)

- (a) [8 marks] The current  $i_c(t)$  through the capacitor of capacitance  $\frac{1}{2}F$  is shown in Figure 1 below. Determine the voltage across the capacitor. Also plot the voltage for  $-2 \leq t \leq 5$ .

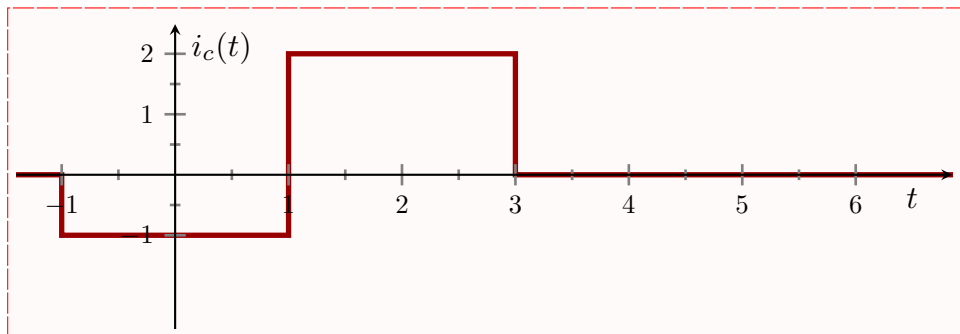


Figure 1: Current through the Capacitor.

**Solution:** Voltage across capacitor is given by

$$v_c = \frac{1}{C} \int_{-\infty}^t i_c(t) dt = 2 \int_{-\infty}^t i_c(t) dt$$
$$v_c = \begin{cases} 0 & t \leq -1 \\ 2 \int_{-1}^t (-1) dt = -2(t+1) = -2t - 2 & -1 < t \leq 1 \\ 2 \int_{-1}^1 (-1) dt + 2 \int_1^t (2) dt = 4t - 8 & 1 < t \leq 3 \\ 2 \int_{-1}^1 (-1) dt + 2 \int_1^3 (2) dt = 4 & 3 < t \end{cases}$$

The plot is given below:

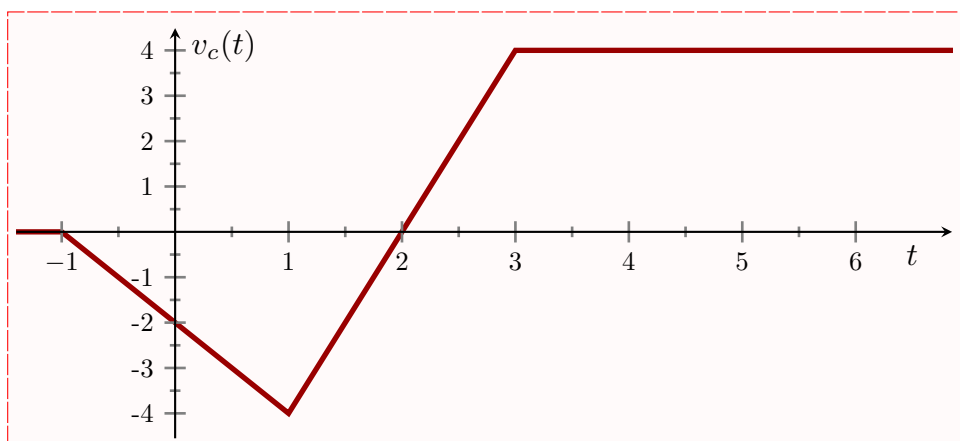


Figure 2: Voltage across the Capacitor.

(b) [1 mark] Draw the  $i - v$  characteristics of an ideal DC voltage source.

**Solution:** Line parallel to the current ( $i$ ) axis on the  $i - v$  plot.

(c) [1 mark] Write an expression to relate the voltage and current for the capacitor.

**Solution:**

$$i_c(t) = C \frac{dv_c(t)}{dt}, \quad \text{or} \quad v_c = \frac{1}{C} \int_{-\infty}^t i_c(t) dt$$