

**LAHORE UNIVERSITY OF MANAGEMENT SCIENCES**  
**Department of Electrical Engineering**

**EE240 Circuits I**  
**Quiz 02 - Section 2**

---

**Name:** \_\_\_\_\_

**Campus ID:** \_\_\_\_\_

**Total Marks:** 10

**Time Duration:** 15 minutes

---

**Question 1** (5 marks)

Consider a circuit where the DC current source of  $4A$  is connected with a parallel combination of a  $2\ \Omega$  resistor and  $1F$  capacitor through the switch. Assume that the switch is initially open and is closed at  $t = 0$  and the capacitor is not carrying any charge before the switch is closed, that is, the voltage across capacitor  $v(t) = 0$  for all  $t < 0$ .

- (a) [1 mark] Draw the circuit and indicate the voltage  $v(t)$  across the capacitor and the currents  $i_R(t)$  and  $i_C(t)$  through the resistor and capacitor respectively.
- (b) [4 marks] Plot the waveforms of the currents  $i_R(t)$  and  $i_C(t)$ .

**Question 2** (3 marks)

The current through the  $0.5H$  inductor is given by

$$i(t) = \begin{cases} 1 - e^{-2t}, & t \geq 0, \\ 0, & t < 0. \end{cases}$$

Determine the total energy consumed by the inductor.

**Question 3** (2 marks)

Do you agree with the following statements (support your answer with the justification)?

- (a) [1 mark] Ideal voltage sources can be connected in series.
- (b) [1 mark] Ideal voltage source and ideal current source in series is equivalent to the voltage source only.