

**LAHORE UNIVERSITY OF MANAGEMENT SCIENCES**  
**Department of Electrical Engineering**

**EE240 Circuits I**  
**Quiz 08 - Section 1 (Solutions)**

Name: \_\_\_\_\_

Campus ID: \_\_\_\_\_


Total Marks: 10

Time Duration: 20 minutes

**Question 1 (10 marks)**

In the following circuit, the switch is *opened* at  $t = 0$ .

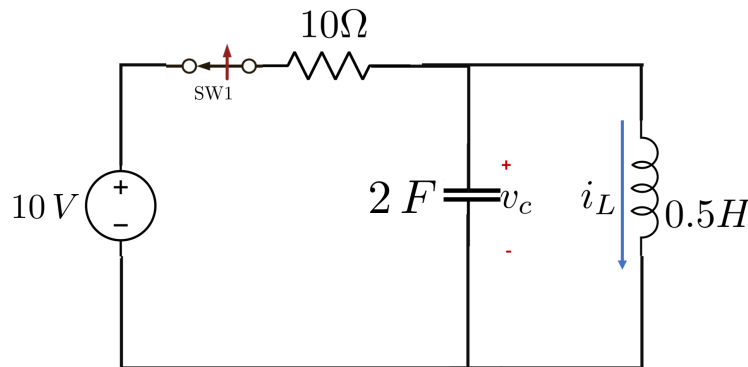- (a) [5 marks] Determine the current  $i_L(t)$  for all times.
- (b) [2 marks] Determine the voltage  $v_c(t)$  for all times
- (c) [2 marks] Plot the current  $i_L(t)$ .
- (d) [1 mark] What is the nature (over-damped, under-damped, critically damped or undamped) of the response?



**Solution:**

(a) **Initial Conditions:**

- Inductor short-circuited, which implies:  $i_L(0^-) = 1 \text{ A}$ ,  $v_c(0^-) = 0$ .
- Voltage across inductor is  $L di_L/dt$ .
- $i_L(0^+) = 1 \text{ A}$ ,  $\frac{di_L(0^+)}{dt} = 0$  (Since voltage across capacitor is zero at  $t = 0^+$ ).

**Network Equation for  $t \geq 0$**

Using KCL, we have

$$LC \frac{d^2 i_L}{dt^2} + i_L = \frac{d^2 i_L}{dt^2} + i_L = 0.$$

The roots of the characteristic equation  $s^2 + 1$  are  $s_1, s_2 = \pm j$ . Therefore the solution is

$$i_L(t) = K_1 \cos(t) + K_2 \sin(t) = \cos(t).$$

Since we have  $K_1 = 1$  and  $K_2 = 0$  using initial conditions.

(b)

$$v_c(t) = L \frac{di_L}{dt} = 0.5 \frac{di_L}{dt} = -\sin(t).$$

(d) Undamped