

EE240 – Circuits I  
**Final Examination (Fall 2018)**

December 19, 2018

06:30 pm–09:00 pm

Student ID .....

Name .....

Signature .....


**INSTRUCTIONS:**

- Do not flip this page over until told to do so.
- The exam consists of 6 problems worth a total of 85 points.
- **The exam needs to be solved on this book and not on blue book.**
- If you need the blue book for rough work, please ask the exam staff.
- The exam is closed book and notes. You are allowed to bring calculator and two A4 sheet with you with *hand-written* notes on both sides.
- Read all the questions before you start working on the exam.
- You cannot keep your mobile phone(s) with you (even on silent mode or switched off).

<b>Problem</b>	<b>Total Points</b>	<b>Obtained Points</b>
Problem 1	20	
Problem 2	10	
Problem 3	10	
Problem 4	10	
Problem 5	15	
Problem 6	20	
Total	85	

## Part 1: First Order Circuits

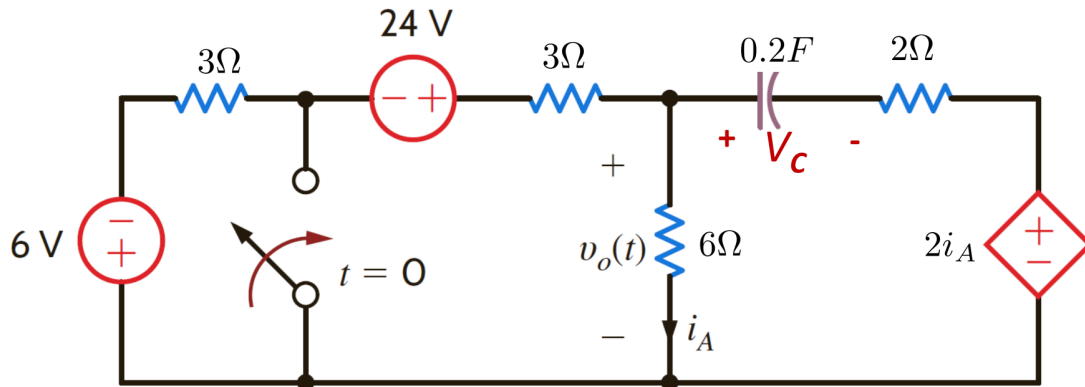**Problem 1. (20 pts)** The circuit given below is in steady state with switch open. The switch is closed at  $t = 0$ .




- (a) (4 pts) Determine the voltage  $V_c(t)$  at  $t = 0^-$ , that is, just before the switch is operated.
- (b) (1 pts) Determine the voltage  $V_c(t)$  at  $t = 0^+$ , that is, just after the switch is operated.
- (c) (4 pts) Determine the current  $i_A(t)$  at  $t = 0^+$ , that is, just after the switch is operated.

- (d) (**5 pts**) Find the  $R_{\text{th}}$  across the capacitor terminals for the circuit obtained after the switch is operated. (Hint: Use test voltage or current source to find  $R_{\text{th}}$ )
- (e) (**4 pts**) Using the results of the parts (c) and (d), or otherwise, determine the current  $i_A(t)$  for all times  $t > 0$ .
- (f) (**2 pts**) Plot the current  $i_A(t)$  for  $-\tau \leq t \leq 6\tau$  (where  $\tau$  denotes the time constant of the circuit).

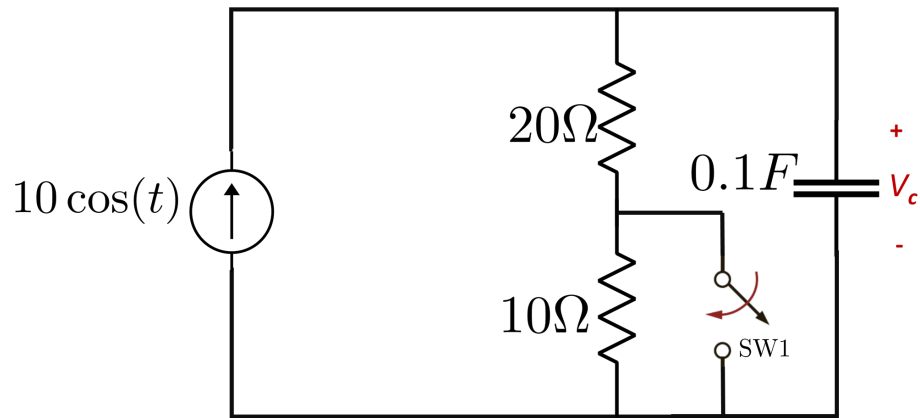
**Problem 2. (10 pts)** The circuit given below is operating in the steady state with the switch SW1 open. At  $t = 0$ , the switch is closed. Find an expression for the voltage  $V_c(t)$  for  $t \geq 0$ .

**(Hint:** Analyse the circuit for  $V_c(t)$  at  $t = 0^-$ , that is determine  $V_c(t)$  before operating the switch. Use the fact that the circuit is in steady state.)




## Part 2: Evaluation of Initial Conditions

**Problem 3. (10 pts)** In the circuit given below, assume that the switch SW1 is initially open and is closed at  $t = 0$ . Determine  $v_1(t)$ ,  $v_2(t)$ ,  $dv_1(t)/dt$ ,  $dv_2(t)/dt$  and  $dv_1^2(t)/dt^2$  at  $t = 0^+$ .

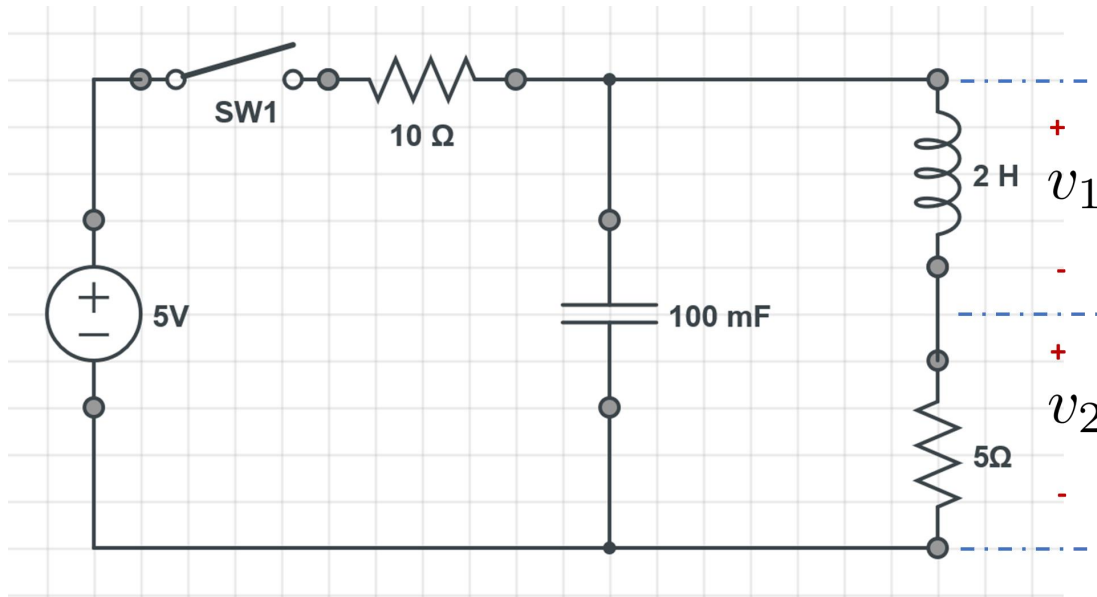

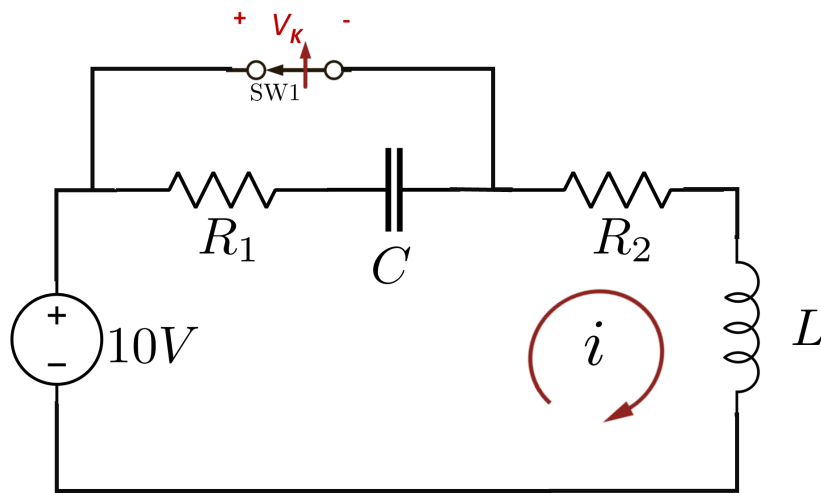**Problem 4. (10 pts)**


Consider the circuit shown below with  $C = 1F$ . The switch SW1 is initially closed for long time and is opened at  $t = 0$ . Given  $i(0^+) = 1 A$ ,  $di/dt(0^+) = -10A/s$  and  $v_k(0^+) = 20V$ , determine  $R_1$ ,  $R_2$  and  $L$ .



### Part 3: Second-Order Circuits

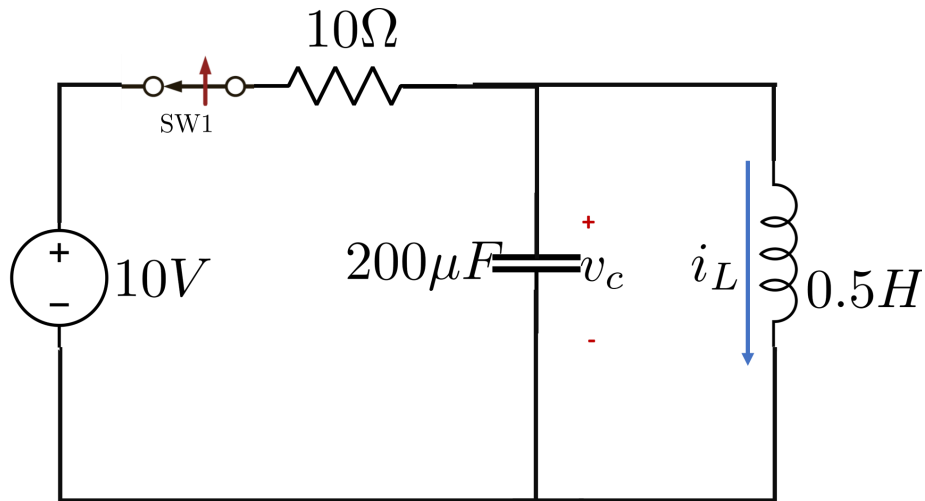**Problem 5. (15 pts)**

Consider the circuit shown below. The circuit is in steady state before the switch is opened at  $t = 0$ .



- (a) (1 pts) Determine  $i_L(t)$  at  $t = 0^-$ .
- (b) (7 pts) Determine  $i_L(t)$  for all times  $t \geq 0$ .


(c) (**3 pts**) Determine  $v_c(t)$  for  $t \geq 0$ .

(d) (**2 pts**) Plot  $i_L(t)$  and  $v_c(t)$  for  $t \geq -1$  s.

(e) (**2 pts**) Determine the damping ratio  $\zeta$  and the natural frequency  $\omega_n$  of the circuit (after operating the switch).



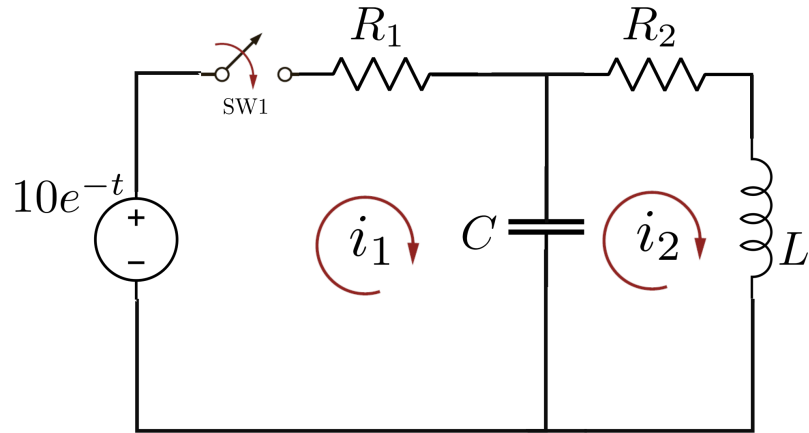**Problem 6. (20 pts)** In the circuit given below, assume that the switch SW1 is initially open and is closed at  $t = 0$ . Assume  $L = 0.5H$ ,  $C = 0.1F$ ,  $R_1 = 10\Omega$  and  $R_2 = 5\Omega$ .



(a) **(8 pts)** Formulate the loop equations and eliminate  $i_1(t)$  to obtain a second-order differential equation for  $i_2(t)$ .

(b) **(4 pts)** Determine  $i_1(0^-)$ ,  $i_2(0^-)$ ,  $i_2(0^+)$  and  $di_2/dt(0^+)$ .

(c) (**8 pts**) Determine  $i_2(t)$  for all times  $t \geq 0$