

EE240 – Circuits I
Mid Examination (Fall 2019)
Solutions

October 31, 2019

06:00 pm–08:45 pm

Student ID _____

Name _____

Signature _____

INSTRUCTIONS:


- Reading time: 15 minutes
- Writing time: 2 hours and 30 minutes
- Do not flip this page over until told to do so.
- **The exam needs to be solved on this book and not on blue book.**
- If you need the blue book for rough work, please ask the exam staff.
- The exam is closed book and notes. You are allowed to bring calculator and two A4 sheet with you with *hand-written* notes on both sides.
- Read all the questions before you start working on the exam.
- You cannot keep your mobile phone(s) with you (even on silent mode or switched off).

Mapping between exam parts and course learning outcomes (CLOs)

- Part 1: Sources and I-V Characteristics of R, L, C (CLO1)
- Part 2: Network Topology, Network Equations and Equivalent Circuits (CLO2)
- Part 3: Additional Analysis Techniques (CLO3)

Part 1: Sources and I-V Characteristics of R, L, C

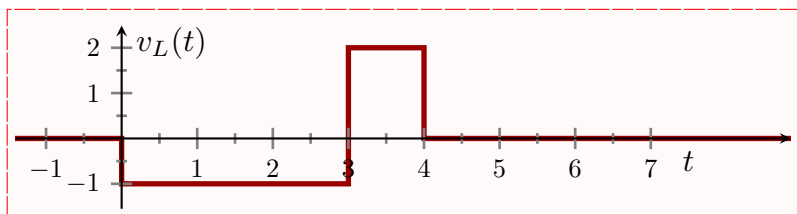Problem 1. (8 pts) The voltage $v_L(t)$ through the inductor of inductance $2H$ is shown in Figure 1 below.



(a) (1 pts) Express $v_L(t)$ as piecewise function of time.


$$v_L(t) = \begin{cases} 0 & t < 0 \\ -1 & 0 \leq t < 3 \\ 2 & 3 \leq t < 4 \\ 0 & 6 \leq t \end{cases}$$

(b) (6 pts) Assuming that the current is zero for times $t \leq -1$ seconds, determine the current through the inductor and **plot** for $0 \leq t \leq 7$ seconds.

Let $i_L(t)$ be the current through inductor.

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L(t) dt$$
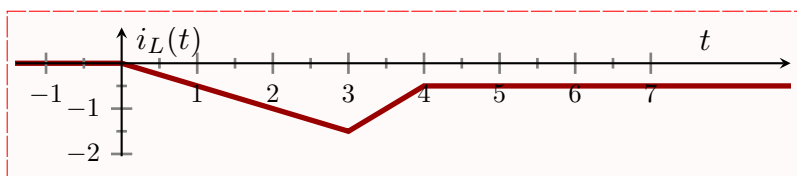
$$i_L(t) = \frac{1}{2} \begin{cases} 0 & t < 0 \\ -t & 0 \leq t < 3 \\ 2t - 9 & 3 \leq t < 4 \\ -1 & 6 \leq t \end{cases}$$




(c) (1 pts) Determine the energy stored in an inductor at $t = 3$ seconds.

$$w_L(t) = \frac{1}{2} L (i_L(t))^2 \Rightarrow w_L(3) = (i_L(3))^2 = 2.25 \text{ J.}$$


Problem 2. (5 pts)

Consider a circuit where the DC current source of $2A$ is connected with a parallel combination of a 2Ω resistor and $1F$ capacitor through the switch. Assume that the switch is initially open and is closed at $t = 0$ and the capacitor is not carrying any charge before the switch is closed, that is, the voltage across capacitor $v(t) = 0$ for all $t < 0$.

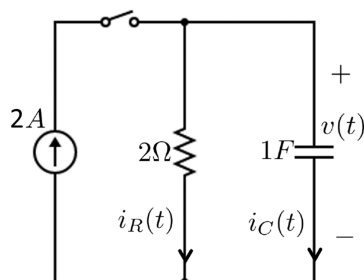
- (a) (1 pts) Draw the circuit and indicate the voltage $v(t)$ across the capacitor and the currents $i_R(t)$ and $i_C(t)$ through the resistor and capacitor respectively.



- (b) (5 pts) Plot the waveforms of the currents $i_R(t)$ and $i_C(t)$.

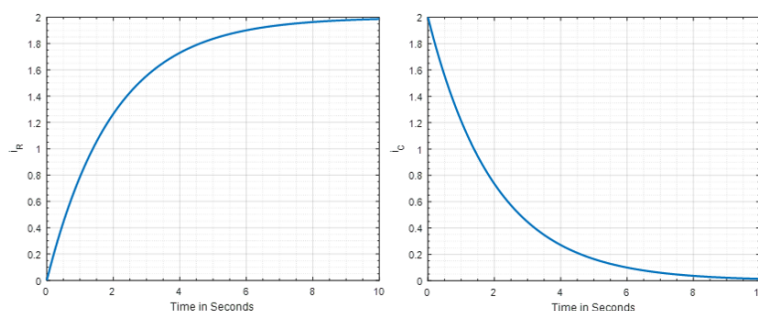

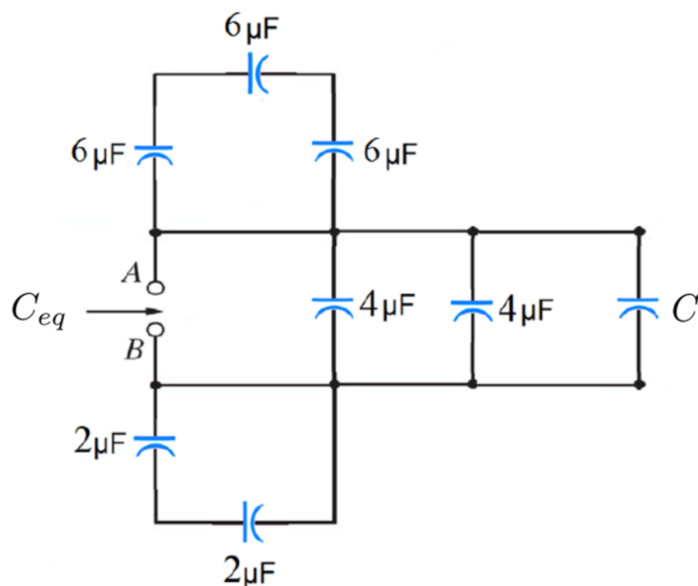
Problem 3. (3 pts) For the network of capacitors shown below, determine the capacitance C if the equivalent capacitance C_{eq} across terminals $A-B$ is $16\mu F$.




$$C_{eq} = 16 = 4 + 4 + C \Rightarrow C = 8\mu F$$

Problem 4. (4 pts) We consider a practical 12V voltage source of $0.1\ \Omega$ internal resistance and practical 2A current source with internal resistance of $1\ k\Omega$.

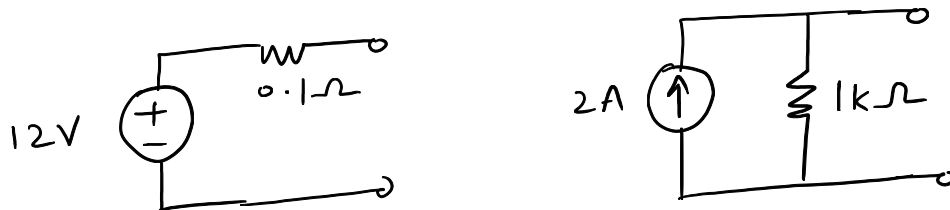(a) (2 pts) Draw the circuit models of the practical sources.



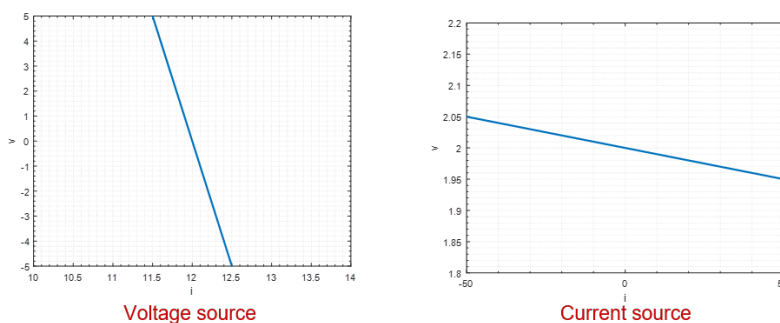(b) (2 pts) Plot the $i - v$ characteristics of the practical sources.



Problem 5. (4 pts) Consider a practical voltage source with rated voltage of V_o and internal resistance r_s . When no current is drawn from the circuit, the voltage across terminals of the voltage source is V_o . When 2W load is connected to the circuit, the voltage across the load is 12 V. When the terminals of the source are short circuited, the source supplies the current of 8 A. Determine the rated voltage V_o and internal resistance r_s .

When terminals are short-circuited, the current is $8A = \frac{V_o}{r_s} \Rightarrow V_o = 8r_s$.


When 2W resistor is connected, the voltage is 12 V, the current is

$$\frac{1}{12} = \frac{1}{6} = \frac{V_o - 12}{r_s} \Rightarrow 6V_o - 72 = r_s$$

. Solving these two equation yields

$$r_s = \frac{72}{47} = 1.532\ \Omega, \quad V_o = 12.25\ V.$$


Problem 6. (6 pts) The figure (right) shows windings marked on a magnetic flux-conducting core. Mark the dots on the windings to establish the mutual coupling using the dot convention.

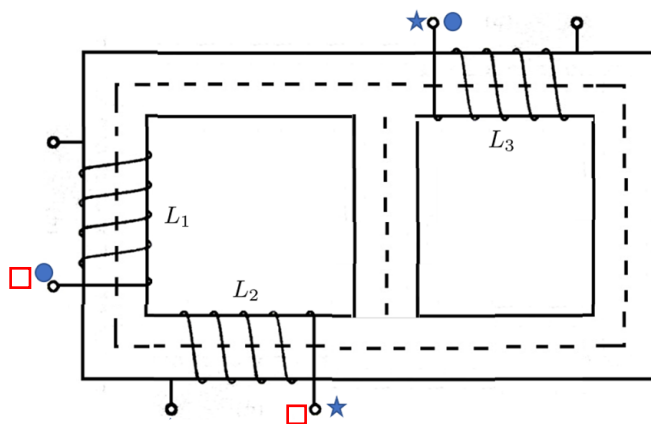

Part 2: Network Topology, Network Equations and Equivalent Circuits


Problem 7. (18 pts)

Consider the circuit given below.

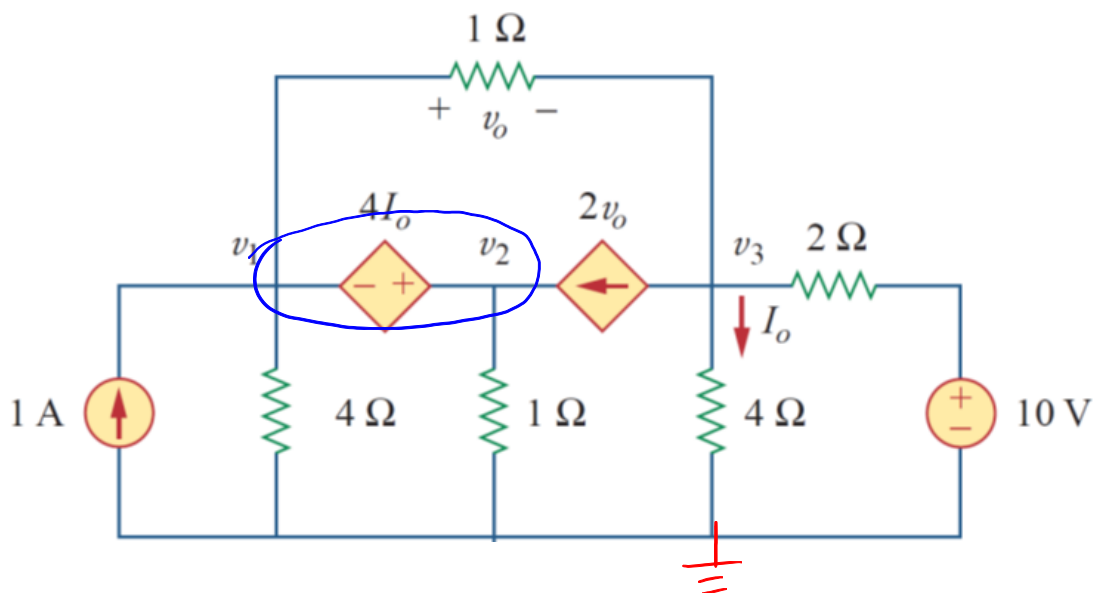

- (a) (4 pts) Draw the graph and one tree of the circuit. Determine the number of nodes and number of branches in a circuit.


Graph

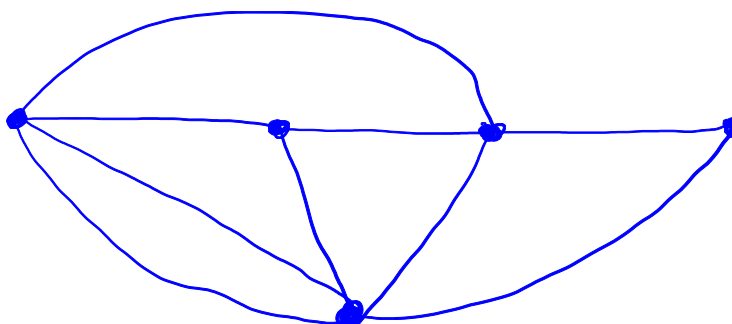

$$n = 5$$

$$b = 9$$

Tree

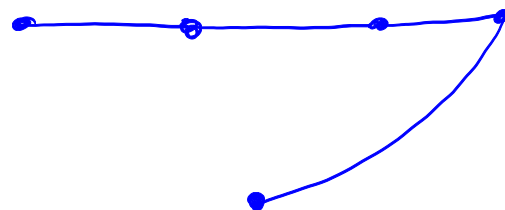

- (b) (2 pts) Determine the number of network equations required for carrying out i) nodal analysis and ii) loop analysis.

Nodal Analysis ; $n - 1 = 4$

Loop Analysis ; $b - n + 1 = 5$

(c) (8 pts) Use Kirchhoff current law to determine the nodal voltages.

Nodes ① and ② form a supernode

$$\frac{v_1}{4} + \frac{v_2}{1} + \frac{v_1 - v_3}{1} - 1 - 2v_0 = 0$$

$$\Rightarrow \frac{v_1}{4} + v_2 + v_1 - v_3 - 2v_1 - 2v_3 = 1$$

$$\boxed{-3v_1 + 4v_2 - 12v_3 = 4}$$

Node 3 : $\frac{v_3}{4} + \frac{v_3 - 10}{2} + v_3 - v_1 + 2v_0 = 0$

$$\Rightarrow \frac{v_3}{4} + \frac{v_3}{2} + v_3 - v_1 + 2v_1 - 2v_3 = 5$$

$$\boxed{-v_3 + 4v_1 = 20}$$

$$\begin{bmatrix} -3 & 4 & -12 \\ 4 & 0 & -1 \\ -1 & 1 & -1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 4 \\ 20 \\ 0 \end{bmatrix} \Rightarrow$$

$$v_1 = \frac{164}{33} = 4.97V$$

$$v_2 = \frac{160}{33} = 4.85V$$

$$v_3 = \frac{-4}{33} = -0.12V$$

Controlled Source

$$v_1 - v_3 = v_0$$

$$I_0 = \frac{v_3}{4}$$

$$v_2 - v_1 = 4I_0 = v_3$$

$$\Rightarrow \boxed{-v_1 + v_2 - v_3 = 0}$$

(d) (4 pts) Determine the power supplied by (i) voltage source and (ii) current source.

Power supplied by current source


$$(1A)(v_1) = 4.97W$$

Power supplied by voltage source

$$(10)\left(\frac{10 - v_3}{2}\right) = (10)(5.06) = 50.6W$$

current supplied by voltage source

Problem 8. (7 pts) For the circuit given below, formulate the network equations using Kirchhoff voltage law.

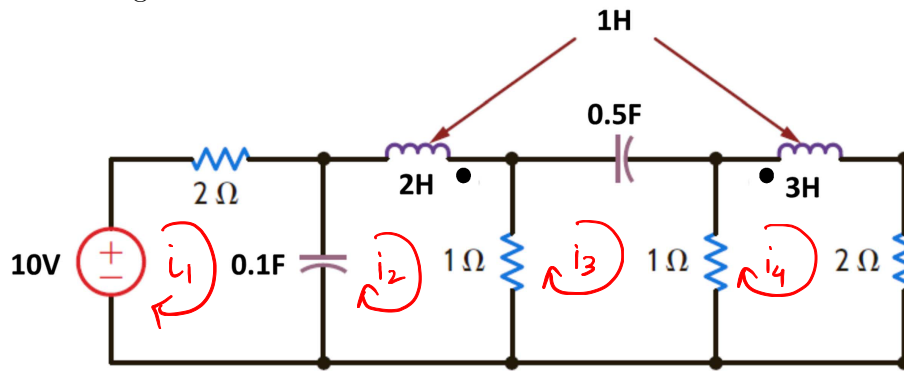

Loop 1

$$2i_1 + 10 \int (i_1 - i_2) dt = 10$$

Loop 2

$$10 \int (i_2 - i_1) dt + (i_2 - i_3) + 2 \frac{di_2}{dt} - \frac{di_4}{dt} = 0$$


$$(i_3 - i_2) + (i_3 - i_4) + 2 \int i_3 dt = 0$$

$$(i_4 - i_3) + 2i_4 + 3 \frac{di_4}{dt} - \frac{di_2}{dt} = 0$$

~~~~ terms due to mutual inductance.

### Part 3: Additional Analysis Techniques

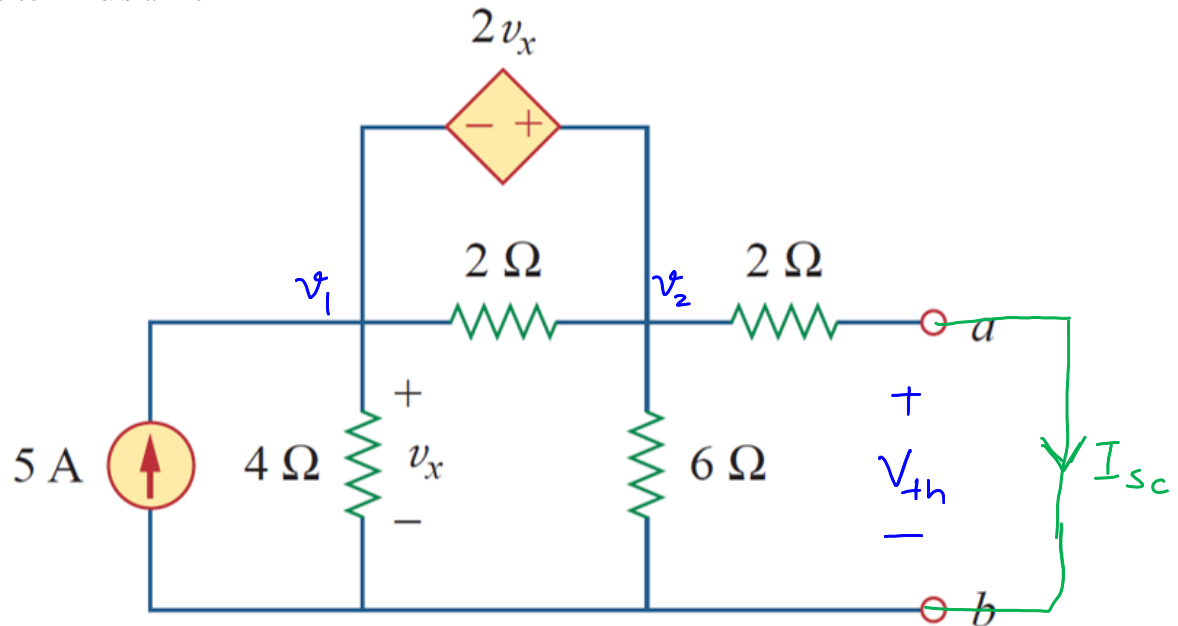**Problem 9.** (12 pts) For the circuit given below, determine the Thevenin equivalent circuit at terminals  $a - b$ .



$$V_{th} : \quad \frac{v_1 - v_2}{2} + \frac{v_1}{4} - 5 + \frac{v_2}{6} + \frac{v_2 - v_1}{2} = 0$$

Super Node:

$$\Rightarrow \frac{v_1}{4} + \frac{v_2}{6} = 5$$

Controlled Source:  $v_2 - v_1 = 2v_x$   
 $v_1 = v_x$

$$v_2 = 3v_1$$

$$\Rightarrow \frac{v_1}{2} + \frac{v_1}{2} = 5 \Rightarrow v_1 = \frac{20}{3} \text{ V}$$

$$v_2 = 20 \text{ V} = V_{th}$$

$I_{sc}$ : Again:  $v_2 = 3v_1$

Super-node:

$$\frac{v_1}{4} + \frac{v_2}{6} + \frac{v_2}{2} = 5$$

This term added when  $a-b$  are short-circuited


$$v_1 = \frac{20}{9} \text{ V}$$

$$v_2 = \frac{10}{9} \text{ V}$$

$$I_{sc} = \frac{v_2}{2}$$

$$\Rightarrow I_{sc} = \frac{10}{3} \text{ A}$$




Equivalent circuit

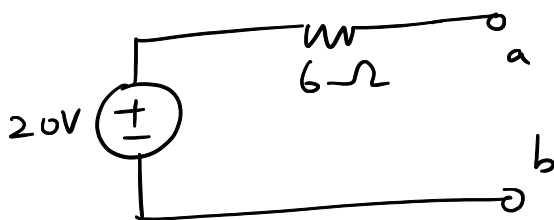

$$R_{th} = \frac{V_{th}}{I_{sc}}$$

$$R_{th} = 6 \Omega$$

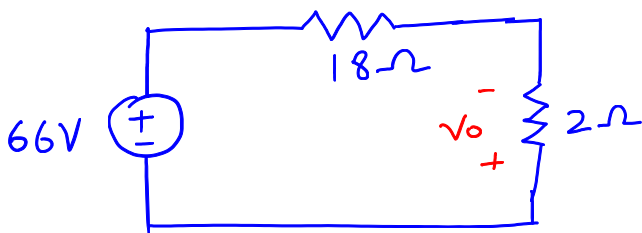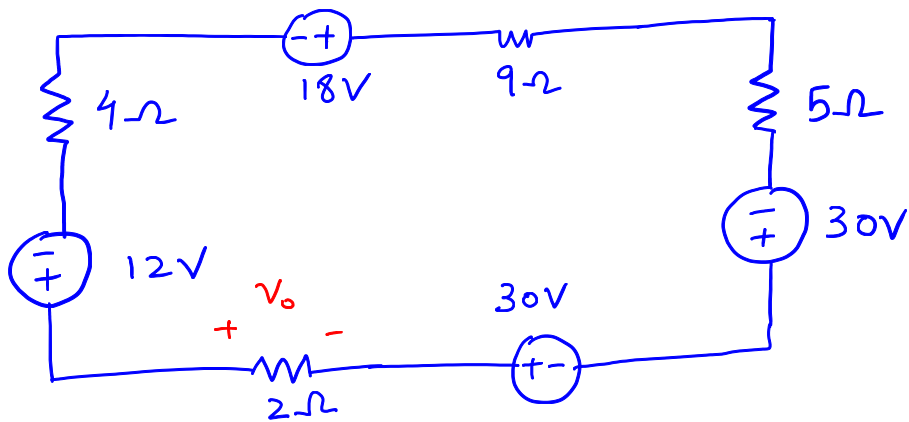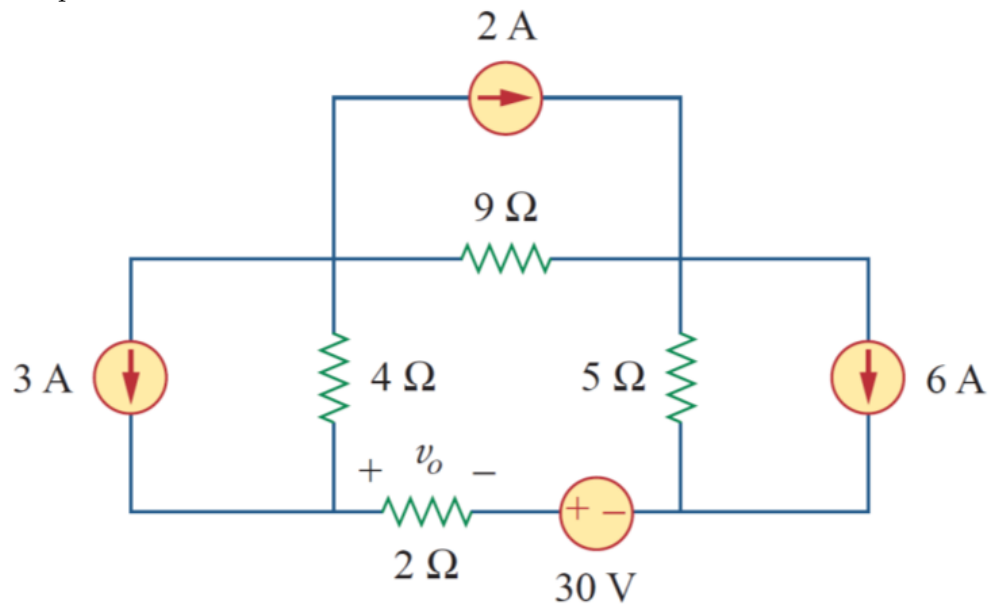
**Problem 10.** (7 pts) Determine  $v_o$  in the following circuit using the source transformation technique.



$$v_o = -\frac{2}{20} \times 66$$


$$v_o = -6.6V$$

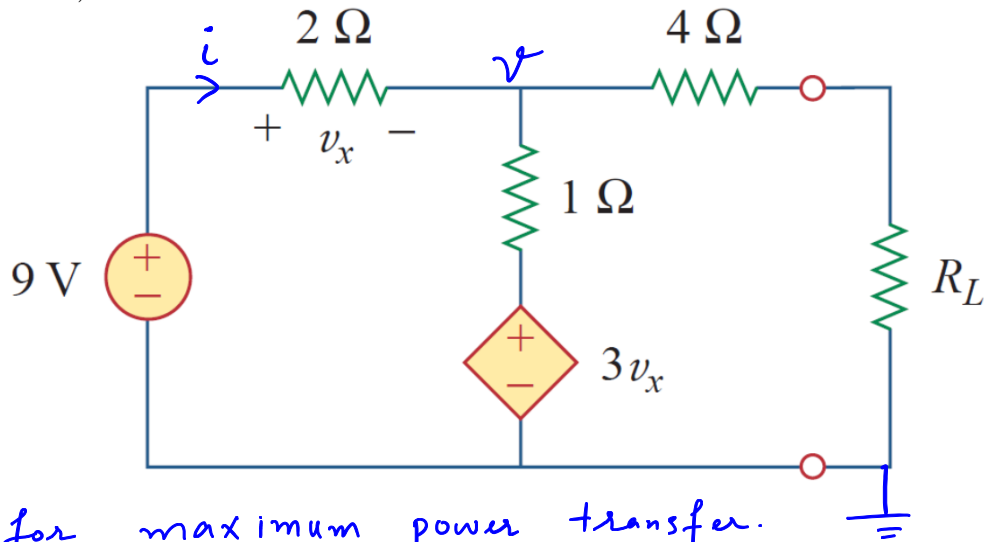**Problem 11. (8 pts)** Consider the circuit given below. For the value of the load resistance  $R_L$  that draws maximum power from the circuit, determine the power supplied by the voltage source.  
(Hint: Determine the value of load resistance  $R_L$  first using the maximum power transfer theorem.)



\*  $R_L = R_{th}$  for maximum power transfer.

\*  $R_{th}$

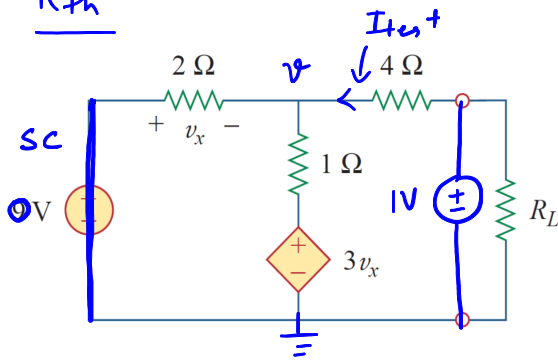

\*  $v = -v_x$

\*  $\frac{v}{2} + \frac{v+3v}{1} + \frac{v-1}{4} = 0 \Rightarrow \boxed{v = \frac{1}{19} \text{ V}}$

$I_{test} = \frac{1 - \frac{1}{19}}{4} = \frac{18}{76} \Rightarrow R_{th} = \frac{1}{I_{test}} = \frac{76}{18} = 4.22 \Omega$

When  $R_L = R_{th}$  connected;

$v_x = 9 - v$

Node Equation:  $\frac{v-9}{2} + \frac{v}{8.22} + v - 3(9-v) = 0$


$\frac{v}{2} + \frac{v}{8.22} + 4v = 31.5 \Rightarrow v = \frac{31.5}{4.62} = \boxed{6.818 \text{ V}}$

$i$  - indicated in the circuit:

$i = \frac{9 - 6.818}{2} = \boxed{1.091 \text{ A}}$

Power,  $P = i \times 9 = \boxed{9.818 \text{ W}}$  qed!  
↓  
supplied by source

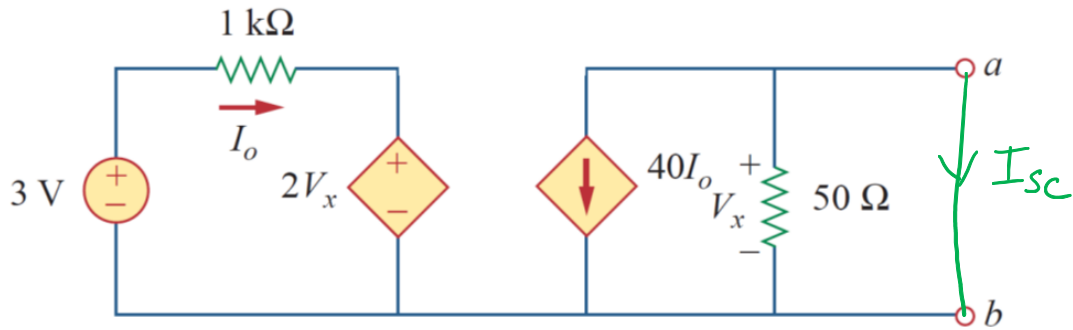**Problem 12.** (8 pts) Find the Norton equivalent of the following circuit at terminals  $a-b$ .



Determine  $V_{oc}$ :  $V_{oc} = V_x = -(50)(40I_o) = -2000I_o$

$$I_o = \frac{3 - 2V_x}{1k} \Rightarrow 3 - 2V_x = 1000I_o$$

$$\Rightarrow 3 + 4000I_o = 1000I_o \Rightarrow \boxed{I_o = -1mA} \Rightarrow \boxed{V_x = V_{oc} = 2V}$$

$I_{sc}$ : \* When terminals are short-circuited,  $V_x = 0$

$$\text{and } I_{sc} = -40I_o$$

$$* 2V_x = 0; (\text{controlled source}) \therefore I_o = \frac{3}{1k} = \boxed{3mA}$$

$$I_N = I_{sc} = -(40)(3mA) = \boxed{0.12A}$$

$$\underline{R_{th}}; \quad R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{50}{3} \Omega$$

Norton Equivalent:

