

LAHORE UNIVERSITY OF MANAGEMENT SCIENCES
Department of Electrical Engineering

EE240 Circuits I
Quiz 04

Total Marks: 10

Time Duration: 20 minutes

Question 1 (10 marks)

For a circuit below, find Thevenin equivalent circuit across the terminals A and B.

