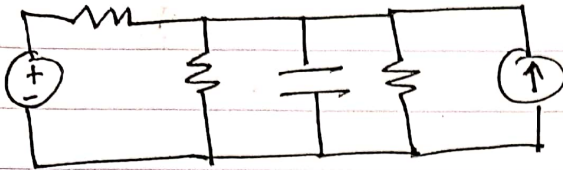


Date: \_\_\_\_\_

a) Analyze circuit at  $t=0^-$


0.5 Mark

(circuit is ~~not~~ considered with switch closed)




2 marks on method used.

S.T

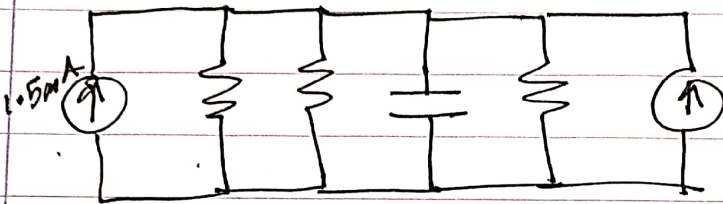

Simplify parallel Resistors & C, source

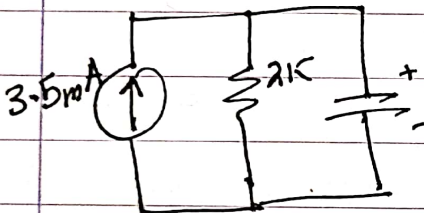

$$V = IR$$

$$= 3.5 \text{ mA} \times 2 \text{ K}$$

$$= 7 \text{ V}$$

0.5 Mark


(Ohms law & final Answer)

b)  $V_0(0^+) = V_0(0^-)$  Cap does not allow inst-change in voltage.

1 MARK (ECF if part A is incorrect).

c) circuit at  $t=0^+$

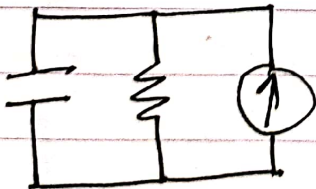0.5 Mark (circuit considered with switch open).



Nodal Analysis.

$$\frac{V(t)}{6 \text{ K}} + 2.5 \text{ m} \frac{dV(t)}{dt} = 2 \text{ m}$$

1 Mark

(Correct Eq)

$$\frac{dV(t)}{dt} + \frac{200}{3} V(t) = 800$$

0.5 Mark


(Eq in standard form)

d)

Equivalent Model of energized capacitor used 0-5 Marks

$$\begin{aligned}
 V &= IR \\
 &= 6000 \times 2 \times 10^{-3} \\
 &= 12V
 \end{aligned}$$

0.5 Mark for Ohms law. & Ans.

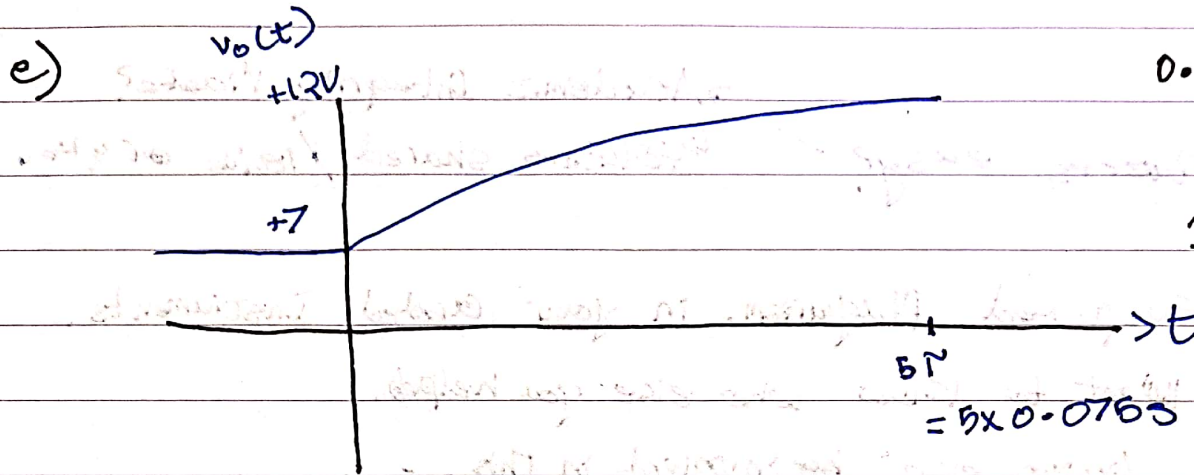

0.5 Mark for Imp points Marked.

1 Mark for correct shape.

$$K_1 = v(\infty) = 12V$$

$$\begin{aligned}
 K_2 &= v(0^+) - K_1 \\
 &= -5V
 \end{aligned}$$

$$\tau = RC \quad 0.5 \text{ Mark.}$$

$$\begin{aligned}
 &= 6000 \times 2.5 \times 10^{-6} \\
 &= 0.015
 \end{aligned}$$

$$v_o(t) = \begin{cases} 7V & t < 0 \\ 12 - 5e^{-\frac{200}{3}t} & t \geq 0 \end{cases}$$

1 Mark for overall correct Expression