

EE240 – Circuits I
Final Examination (Fall 2020)


December 21, 2020

12:30 pm–03:30 pm

INSTRUCTIONS:

- We require you to solve the exam in a single time-slot of two hours and thirty minutes without any external or electronic assistance.
- We encourage you to solve the exam on A4 paper, use new sheet for each question and write sheet number on every sheet.
- The exam is closed book and notes. You are allowed to have two A4 sheet with you with hand-written notes on both sides. Calculators can be used.
- For the sake of completeness, we require you to write the following statement on your first page of submission: *I commit myself to uphold the highest standards of (academic) integrity.*
- Reading time: 10 minutes
- Writing time: 2 hours and 30 minutes
- Submission time: 20 minutes
- The exam consists of 6 problems worth a total of 90 points.

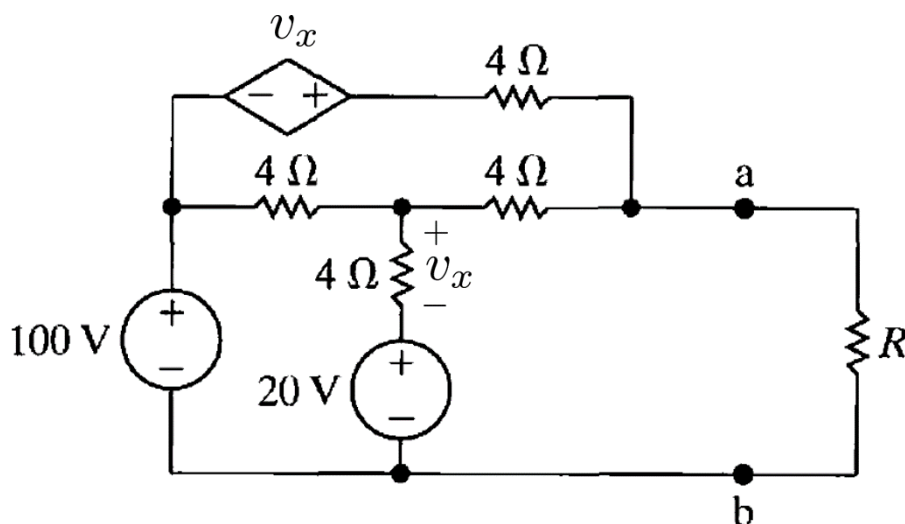Problem 1. (15 pts) The variable resistor R in the circuit given below is adjusted until it absorbs the maximum power from the circuit.



(a) (6 pts) Calculate the value of R for maximum power.


solution:

For maximum power, $R = R_{th}$. Switching off sources, connecting 1V voltage source across terminals a-b and applying KCL at node 1 yields

$$\frac{v_x}{4} + \frac{v_x}{4} + \frac{v_x - 1}{4} \Rightarrow v_x = \frac{1}{3} V$$


$$I_{test} = 2 \frac{1 - \frac{1}{3}}{4} = \frac{1}{3}$$
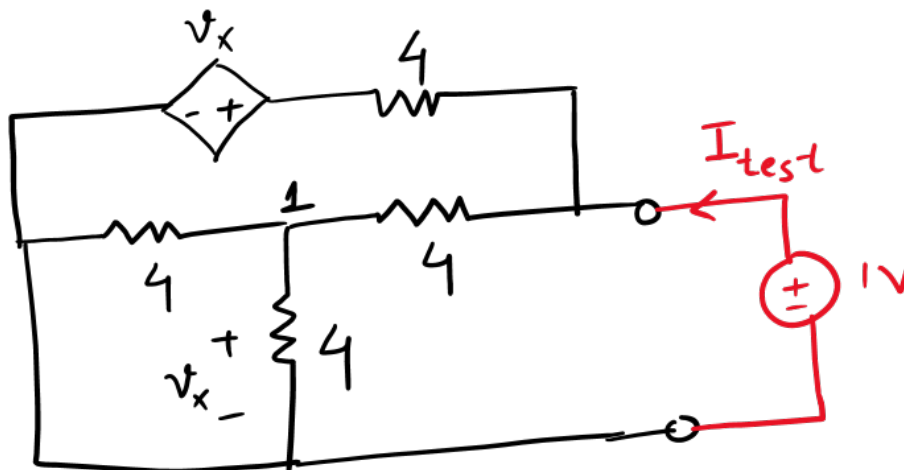
$$R_{th} = \frac{1}{I_{test}} = 3 \Omega.$$



(b) (6 pts) Determine the maximum power absorbed by R .

solution:

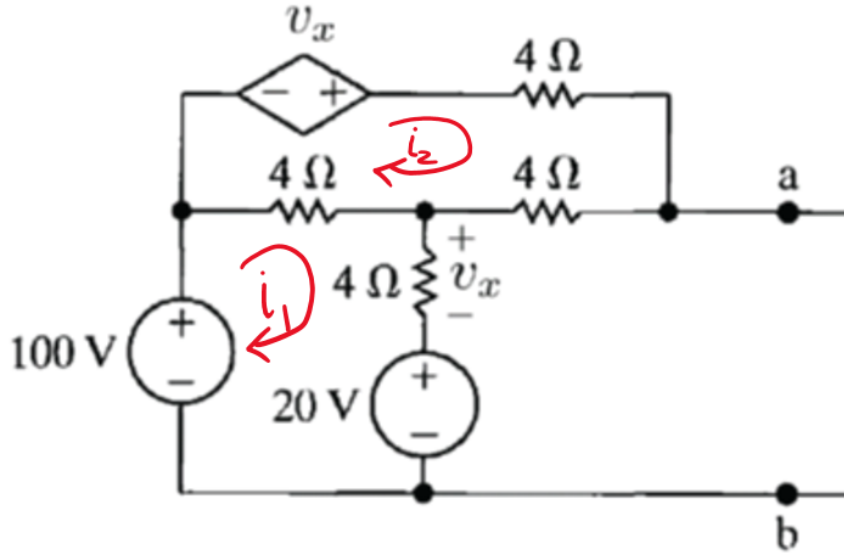

We determine V_{th} in order to find the power. Considering the loop currents indicated, we have $v_x = 4i_1$ Using KVL

Loop 1 equation:

$$8i_1 - 4i_2 = 80$$

Loop 2 equation:

$$-4i_1 + 12i_2 - v_x = 0 \Rightarrow 12i_2 = 8i_1$$

These two equations yield

$$i_1 = 15 A, \quad i_2 = 10 A$$

Using these currents, we determine V_{th} as

$$V_{th} = 4i_1 + 4i_2 + 20 = 120 V$$


Now we have Thevenin equivalent circuit across terminals $a - b$. Power across R_{th} can be determine as: $P = \frac{60^2}{R_{th}} = 1200 W$

(c) (**3 pts**) Determine the Norton equivalent of the circuit at terminals a-b.

solution:

Source transformation of Thevenin equivalent yields Norton equivalent.

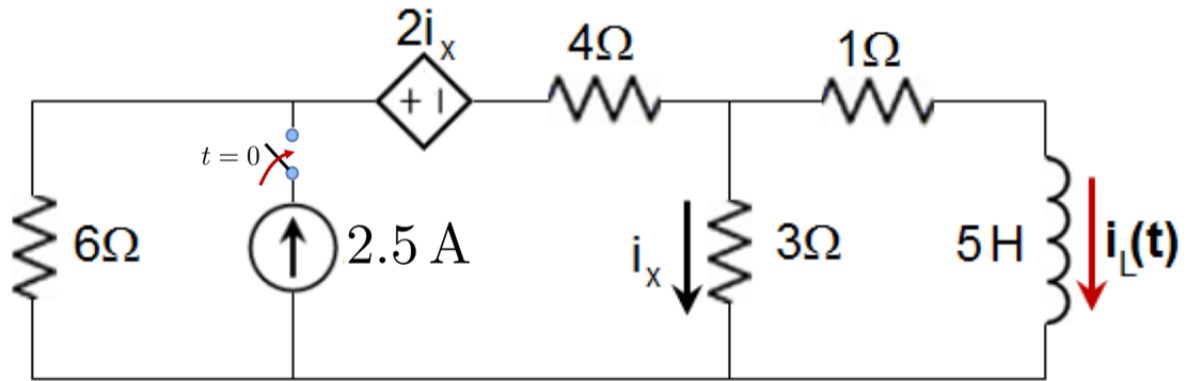Problem 2. (15 pts) The circuit given below is in steady state with switch in open state. The switch is closed at $t = 0$.



(a) (2 pts) Determine the current $i_L(t)$ at $t = 0^-$.

solution: $i_L(t) = 0$ at $t = 0^-$


(b) (1 pts) Determine the current $i_L(t)$ at $t = 0^+$.

solution: $i_L(t) = 0$ at $t = 0^+$

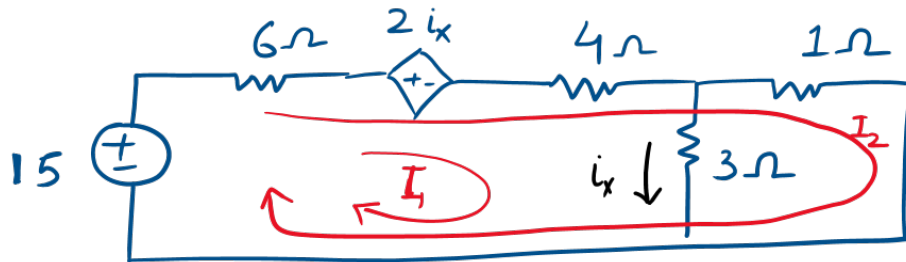(c) (5 pts) Determine the current $i_L(t)$ at $t = \infty$

solution:

Switch is closed and inductor is short-circuit, we have the following circuit:



Applying KVL yields

$$15I_1 + 10I_2 = 15 \Rightarrow 3I_1 + 2I_2 = 3$$


$$12I_1 + 11I_2 = 15$$

Solving for I_2 , we get $i_L(\infty) = I_2 = 1$ A.

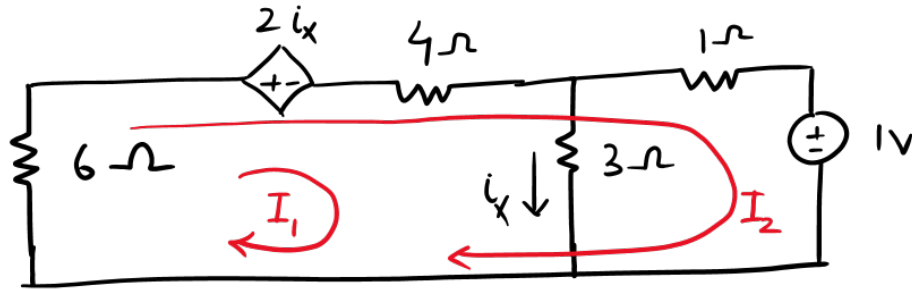(d) (7 pts) Using the results of the previous parts, or otherwise, determine the current $i_L(t)$ for all times and plot it.

solution:

We need to find time-constant or equivalent resistance across inductor using Thevenin theorem approach. By switching off sources and replacing inductor with 1V test source, we obtain the following circuit:



Applying KVL yields

$$15I_1 + 10I_2 = 0 \Rightarrow 3I_1 + 2I_2 = 0$$

$$12I_1 + 11I_2 = -1$$

Solving for I_2 , we get $I_2 = -\frac{1}{3} A$. R_{eq} across inductor is given by $R_{eq} = \frac{1}{I_{test}} = -\frac{1}{I_2} = 3\Omega$.


Now, $i_L(t)$ for $t \geq 0$ is given by

$$i_L(t) = K_1 + K_2 e^{-t/\tau}, \quad t \geq 0$$

$K_1 = i_L(\infty) = 1$, $K_2 = i_L(0) - i_L(\infty) = -1$, $\tau = L/R_{eq} = 5/3$ s.

$$i_L(t) = 1 - 1e^{-3t/5}, \quad t \geq 0.$$

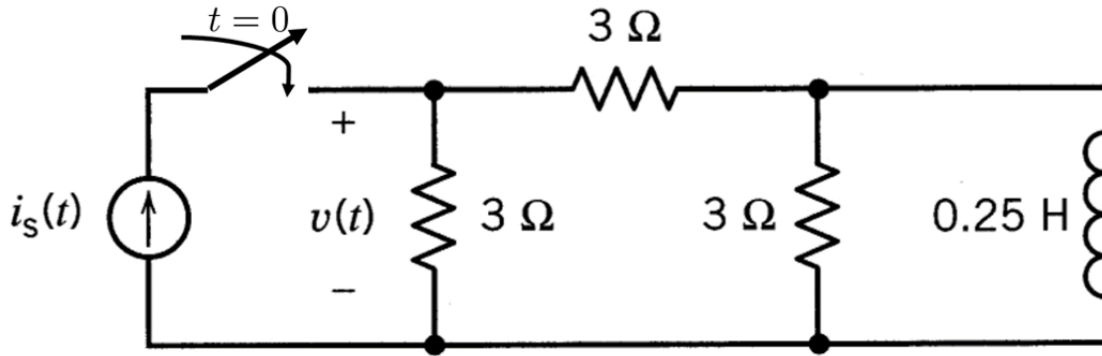
Problem 3. (15 pts) Consider the circuit given below. The circuit is in steady state and the the switch is closed at $t = 0$.



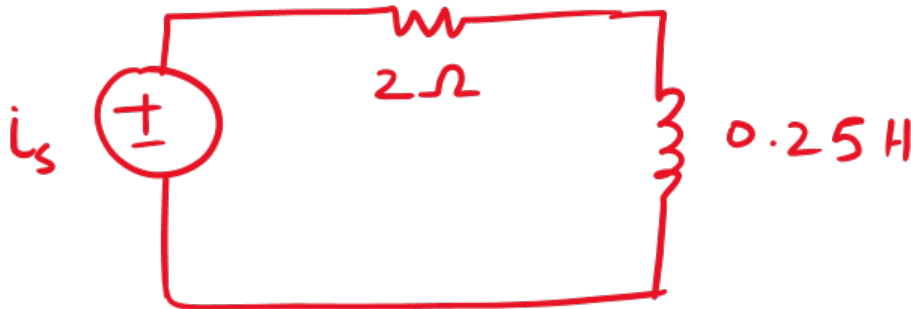- (a) (4 pts) For a circuit for $t > 0$, form an equivalent series RL circuit containing one source, one resistor and one inductor. Ignore $v(t)$ indicated in the circuit. (Hint: You may use source transformation or Thevenin equivalent approach.)

solution:

Using source transformation, we obtain a circuit with voltage source $i_s(t)$, resistor of resistance 2Ω and inductor.



- (b) (8 pts) For $i_s(t) = e^{-t} \cos t$, determine the current through the inductor for $t \geq 0$. Ignore $v(t)$ indicated in the circuit.

solution:

Let $i(t)$ be the current through inductor. We first note that $i(0^+) = 0$. We have a series RL circuit. Applying KVL yields

$$\frac{di}{dt} + 8i = 4e^{-t} \cos t.$$

The solution is a sum of following two solution

$$i_c(t) = K_1 e^{-8t}$$

$$i_p(t) = Ae^{-t} \cos t + Be^{-t} \sin t$$

Solving for A and B , we get $A = 0.56$ and $B = 0.08$.

$$i(t) = K_1 e^{-8t} + 0.56e^{-t} \cos t + 0.08e^{-t} \sin t, \quad t \geq 0$$

Using initial conditions, $K_1 = -0.56$.


- (c) (**3 pts**) Using the result of previous part or otherwise, determine the voltage $v(t)$ indicated in the circuit for $t \geq 0$.

solution:

$$v(t) = (0.25) \frac{di}{dt} + 3 \left(i(t) + \frac{1}{3} (0.25) \frac{di}{dt} \right) = 3i(t) + \frac{1}{3} \frac{di}{dt} \text{ V.}$$

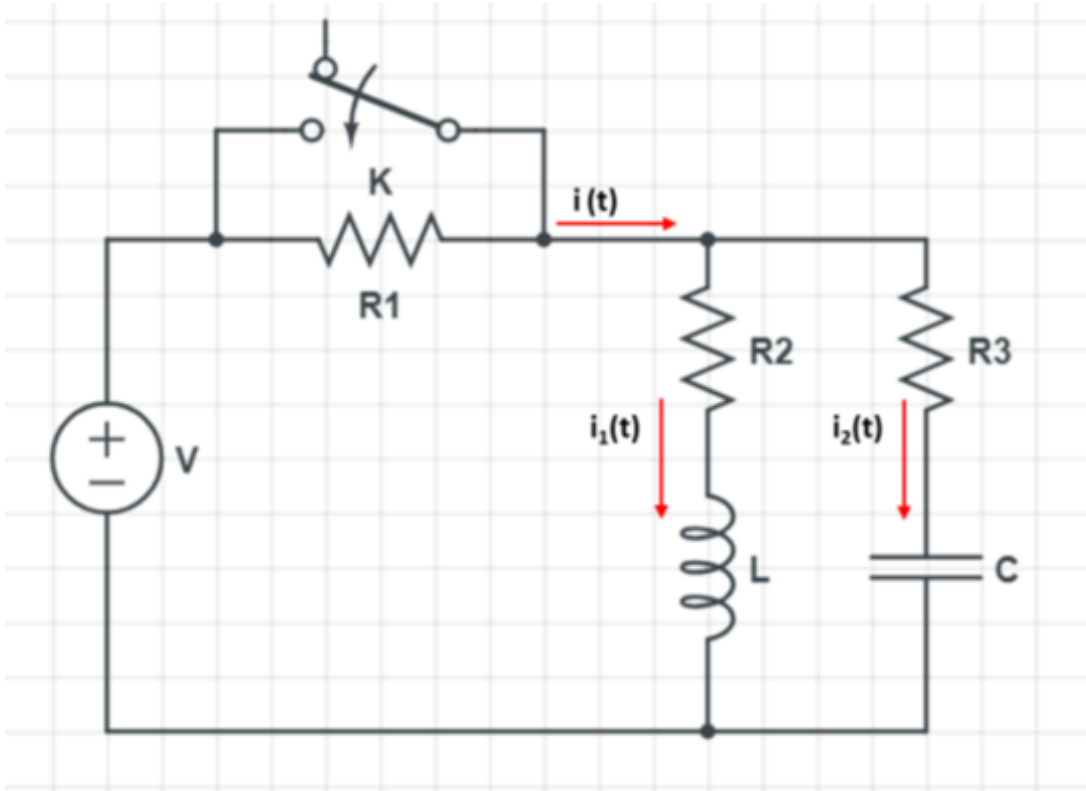Problem 4. (10 pts) In the circuit below, we have $R_2 = R_3 = 20\Omega$. We assume that the steady state is reached with switch K open. At time $t = 0$, the switch is closed. Determine values of resistance R_1 , inductance L , capacitance C and voltage V of the voltage source using the following information.

- $i_1(0^+) = 2 \text{ A}$
- $i_2(0^+) = 1 \text{ A}$
- $\frac{di_1}{dt}(0^+) = 40 \text{ A/s}$
- $\frac{di_2}{dt}(0^+) = -\frac{1}{2} \text{ A/s}$



solution:

Noting

$$2 = i_1(0^+) = i_1(0^-) = \frac{V}{R_1 + R_2}, \quad (1)$$

$$1 = i_2(0^+) = \frac{V - v_c}{R_3} = \frac{VR_1}{R_3(R_1 + R_2)}, \quad (2)$$

$$40 = \frac{di_1}{dt}(0^+) = \frac{VR_1}{L(R_1 + R_2)}, \quad (3)$$

$$-\frac{1}{2} = \frac{di_2}{dt}(0^+) = -\frac{i_2(0^+)}{R_3 C}. \quad (4)$$

First two equations yield


$$R_1 = 2R_3 = 10\Omega, \quad V = 60 \text{ Volts}$$

Using (3) and (4), we obtain

$$L = 0.5 \text{ H}, \quad C = 0.1 \text{ F}$$

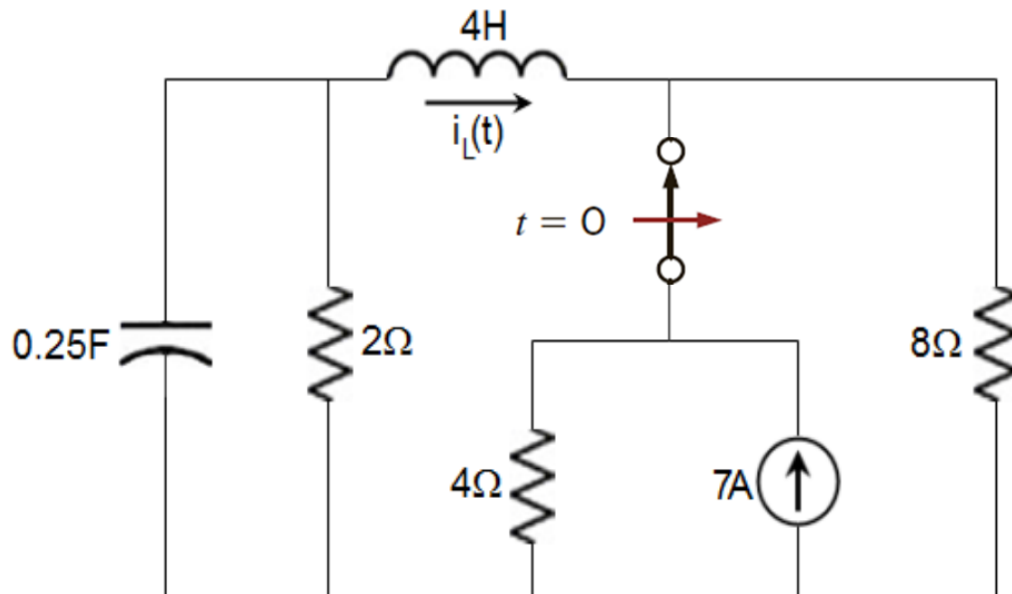Problem 5. (20 pts)


Consider the circuit shown below. The circuit is in steady state with switch in closed state. The switch is opened at $t = 0$.



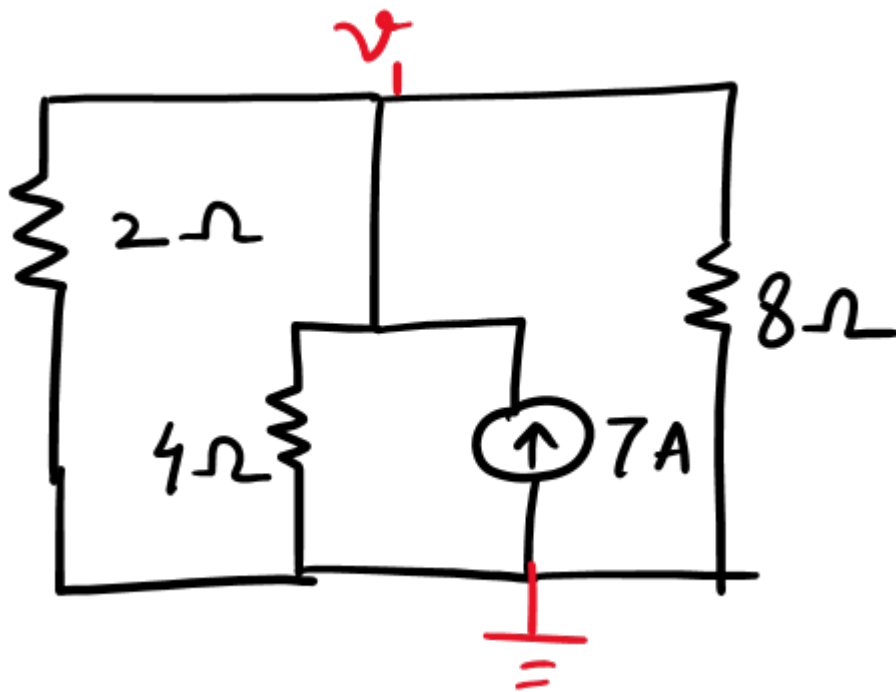- (a) (6 pts) Determine $i_L(t)$ and $\frac{di_L}{dt}$ at $t = 0^+$.

solution:

We have the following circuit at $t = 0^-$.



KCL yields

$$\frac{v_1}{2} + \frac{v_1}{4} + \frac{v_1}{8} = 7 \Rightarrow v_1 = 8V$$

At $t = 0^-$, we have

$$i_L(0^-) = -\frac{v_1}{2} = -4A, \quad v_c(0^-) = v_1 = 8V$$

At $t = 0^+$, we have

$$i_L(0^+) = i_L(0^-) = -4A$$

In order to find $\frac{di_L}{dt}(0^+)$, we note that we have

$$4\frac{di_L}{dt} + 8i_L(t) = v_c(t) \Rightarrow \frac{di_L}{dt}(0^+) = 10 \text{ A/s}$$

- (b) (**5 pts**) Formulate the second-order differential equation describing the current $i_L(t)$ for $t \geq 0$.

solution:

We first note

$$4\frac{di_L}{dt} + 8i_L(t) = v_c(t)$$

KCL yields

$$i_L + \frac{v_c}{2} + 0.25\frac{dv_c}{dt} = 0$$

Manipulation of these two equations yield

$$i_L + 2\frac{di_L}{dt} + 4i_L(t) + \frac{d^2i_L}{dt^2} + 2\frac{di_L}{dt} = 0 \Rightarrow \frac{d^2i_L}{dt^2} + 4\frac{di_L}{dt} + 5i_L(t) = 0$$

- (c) (**2 pts**) Determine the damping ratio ζ and natural frequency ω_n of the circuit after the switch is closed.

solution:

Comparing the characteristic equation of the differential equation given by

$$s^2 + 4s + 5 = 0$$

with the standard form

$$s^2 + 2\zeta\omega_n s + \omega_n^2 = 0,$$

we obtain $\omega_n = \sqrt{5}$ and $\zeta = \frac{2}{\sqrt{5}}$.

- (d) (**7 pts**) Determine and plot (with labels) $i_L(t)$ for all times.

solution:

The roots of the characteristic equation associated with the differential equation has the roots

$$s = -2 \pm j,$$

and therefore the solution is underdamped and has the form

$$i_L(t) = e^{-2t}(K_1 \cos t + K_2 \sin t)$$


Using the initial conditions evaluated in part (a), $K_1 = -4$, and $K_2 - 2K_1 = 10$, $\Rightarrow K_2 = 2$.

Overall

$$i_L(t) = \begin{cases} e^{-2t}(-4 \cos t + 2 \sin t) & t \geq 0 \\ -4 & t < 0 \end{cases}$$

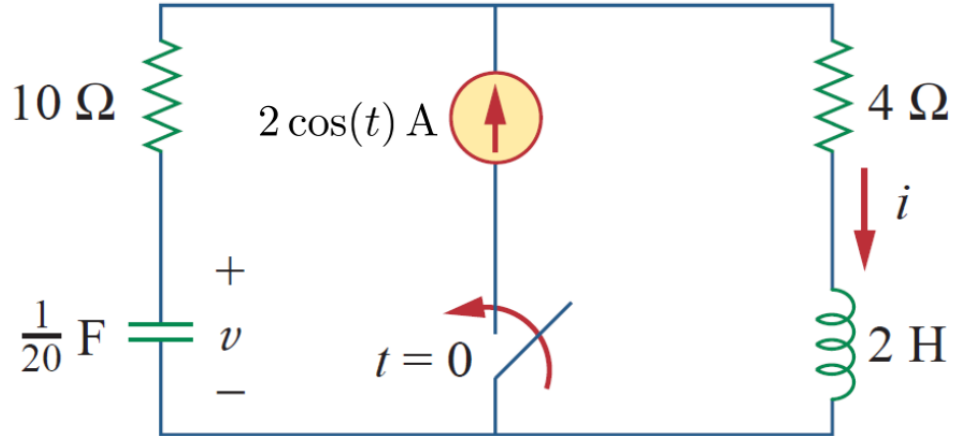Problem 6. (15 pts)

The switch in the following circuit is closed at $t = 0$.



- (a) (5 pts) Formulate the second order differential equation describing the voltage $v(t)$ after the switch is closed.

solution:

We first note

$$v + 12 \frac{dv}{dt} = 4i + 2 \frac{di}{dt}$$

KCL yields

$$i = 2 \cos t - \frac{1}{20} \frac{dv}{dt}$$

Manipulation yields

$$v + 12 \frac{dv}{dt} = 8 \cos t - \frac{1}{5} \frac{dv}{dt} - 4 \sin t - 110 \frac{d^2v}{dt^2}$$

$$\frac{1}{10} \frac{d^2v}{dt^2} + \frac{1}{5} \frac{dv}{dt} + v + \frac{1}{2} \frac{dv}{dt} = 8 \cos t - 4 \sin t$$

$$\frac{d^2v}{dt^2} + 7 \frac{dv}{dt} + 10v = 80 \cos t - 40 \sin t$$

- (b) (8 pts) Determine $v(t)$ for all times.

solution:

For the differential equation, we have the following characteristic equation

$$s^2 + 7s + 10 = 0, \Rightarrow s_1 = -2, s_2 = -5$$

We have

$$v(t) = v_c(t) + v_p(t),$$

where

$$v_c(t) = K_1 e^{-2t} + K_2 e^{-5t}$$

and

$$v_p(t) = A \cos t + B \sin t$$

Substituting $v_p(t)$ in the differential equation yields

$$-A \cos t - B \sin t - 7A \sin t + 7B \cos t + 10A \cos t + 10B \sin t = (9A - 7B) \cos t + (9B - 7A) \sin t$$

$$= 80 \cos t - 40 \sin t$$

$$9A + 7B = 80, \quad 63A + 49B = 560$$

$$9B - 7A = -40, \quad 81B - 63A = -360$$

$$B = 20/13,$$

$$A = 100/13$$

Overall,

$$v(t) = K_1 e^{-2t} + K_2 e^{-5t} + \frac{100}{13} \cos t + \frac{20}{13} \sin t$$

We also note the following initial conditions

$$v(0^+) = 0, \quad i(0^+) = 0$$

Noting $i = 2 \cos t - \frac{1}{20} \frac{dv}{dt}$, we have

$$\frac{dv}{dt}(0^+) = 40 \text{ Volts/second}$$

Using these initial conditions, we obtain

$$K_1 + K_2 = -\frac{100}{13}, \quad 2K_1 + 2K_2 = -\frac{200}{26}$$

$$-2K_1 - 5K_2 = 40 - \frac{20}{13}$$

Manipulation yields

$$-3K_2 = 40 - \frac{240}{26}, \quad K_2 = -\frac{400}{39}, \quad K_1 = \frac{100}{39}$$

Finally, we have

$$v(t) = \frac{100}{39} e^{-2t} - \frac{400}{39} e^{-5t} + \frac{100}{13} \cos t + \frac{20}{13} \sin t, \text{ V}$$

(c) (**2 pts**) Using the result of previous part or otherwise, determine $i(t)$ for all times.

solution:

$$i = 2 \cos t - \frac{1}{20} \frac{dv}{dt}$$