

# EE 240 Circuits I



Dr. Zubair Khalid

Department of Electrical Engineering  
School of Science and Engineering  
Lahore University of Management Sciences

[https://www.zubairkhalid.org/ee240\\_2020.html](https://www.zubairkhalid.org/ee240_2020.html)
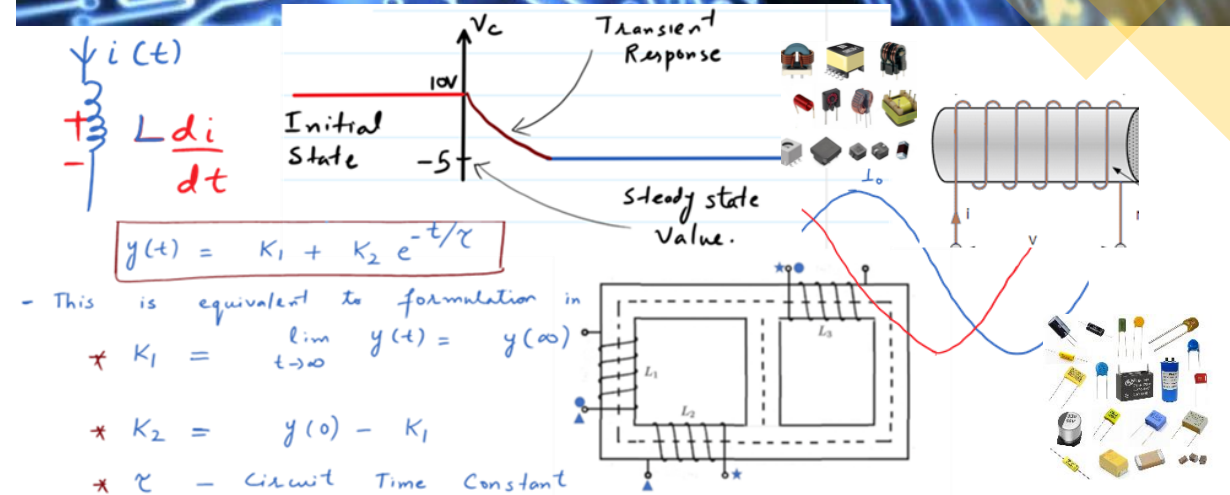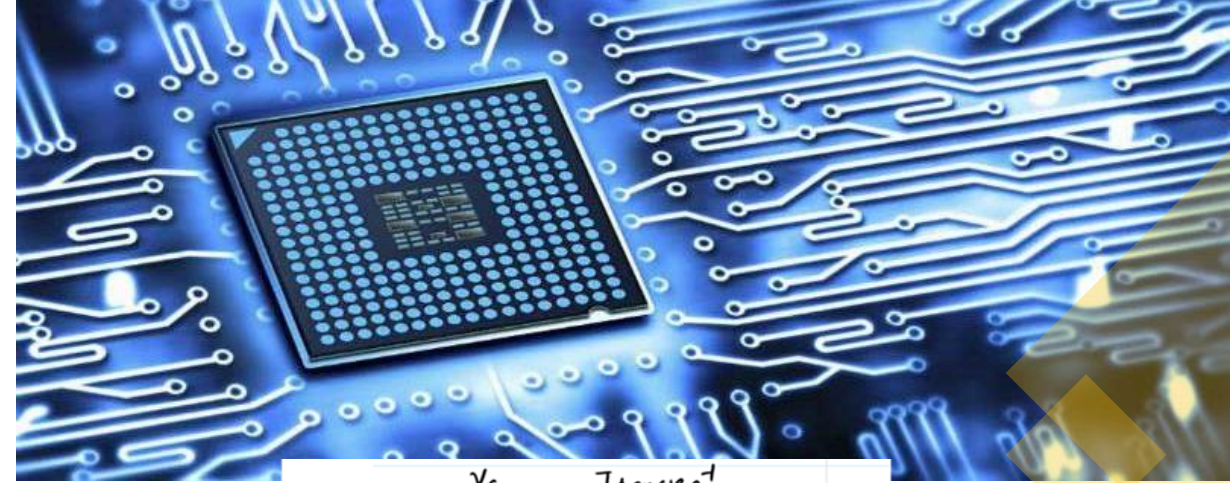
## Topics:


- R,L,C summary
- Series, parallel connection




# Resistor, Capacitor, Inductor (R,C,L)

## Summary:

R,C and L are passive elements

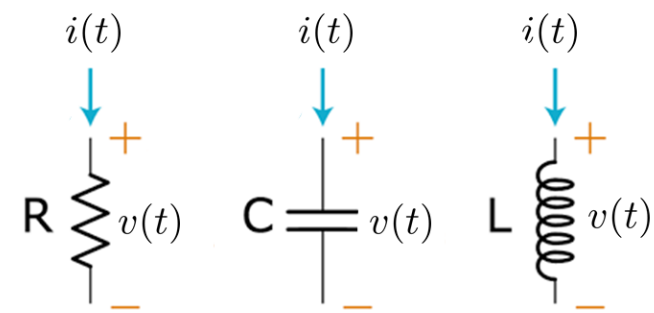

## Resistor, $R$

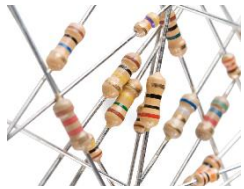


$$v = iR$$

$$i = \frac{v}{R}$$

$$w(t) = \int_{\tau=-\infty}^t p(\tau) d\tau \quad p = vi = i^2 R = \frac{v^2}{R}$$

## Capacitor, $C$

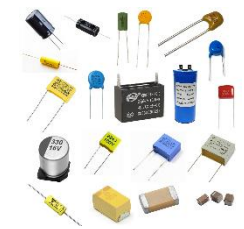


$$v(t) = \frac{1}{C} \int_{\tau=-\infty}^t i(\tau) d\tau$$

$$i = C \frac{dv}{dt}$$

$$w = \frac{1}{2} C v^2$$

$$q = Cv$$

## Inductor, $L$

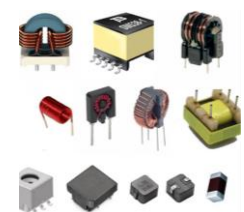

$$v = L \frac{di}{dt}$$


$$i(t) = \frac{1}{L} \int_{\tau=-\infty}^t v(\tau) d\tau$$

$$w = \frac{1}{2} L i^2$$

$$\Psi = Li$$

# Resistor, Capacitor, Inductor (R,C,L)


Encapsulated:

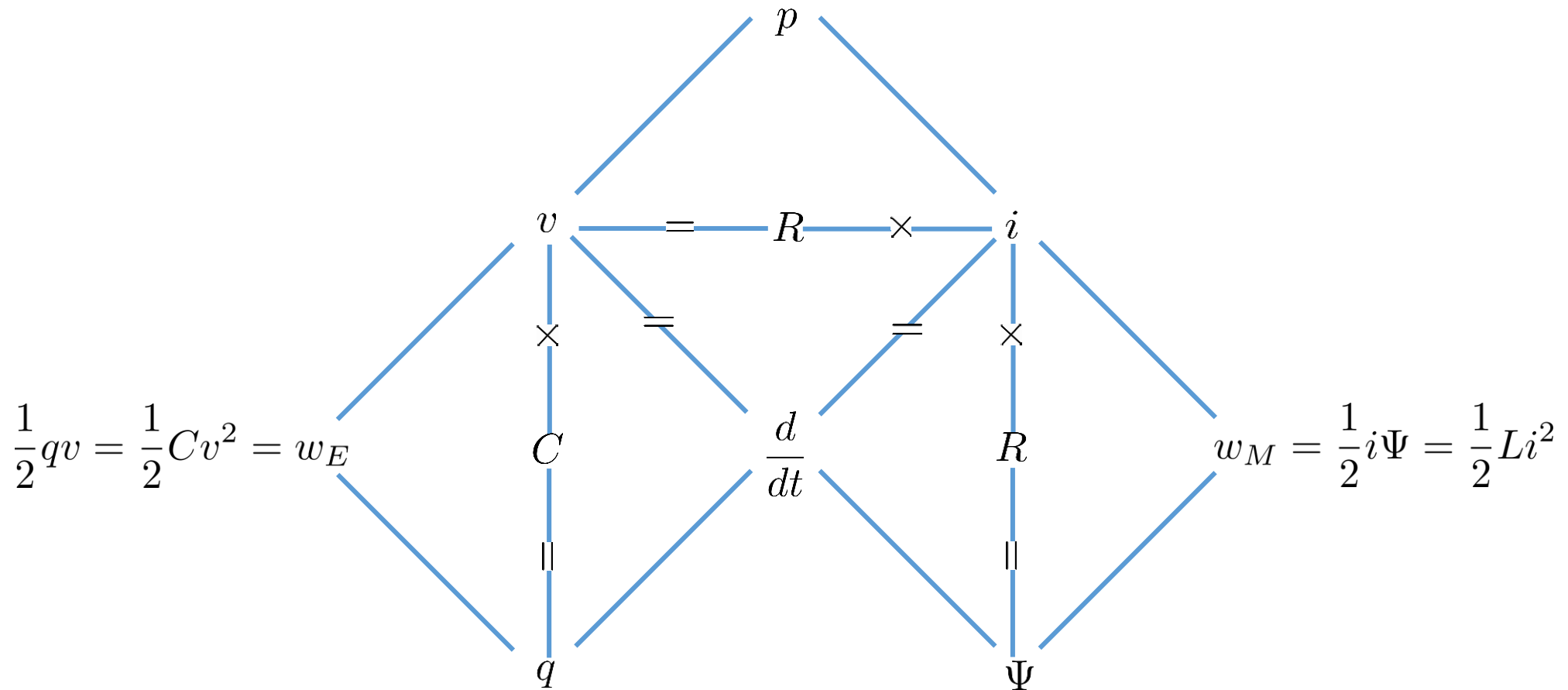

# Elements and Sources in Series/Parallel


## Series Connection:

Idea: same current, voltage is divided


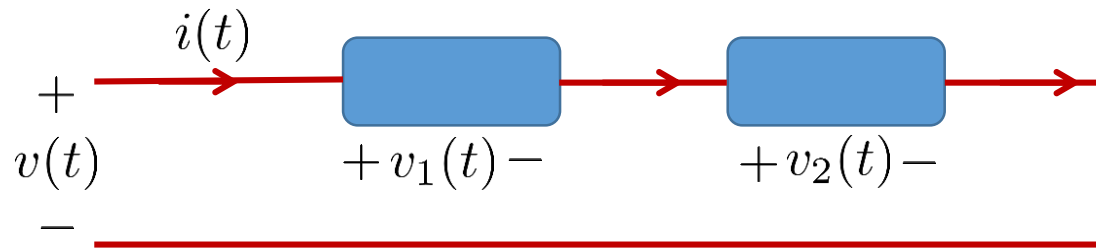


## Parallel Connection:

Idea: same voltage, current is divided

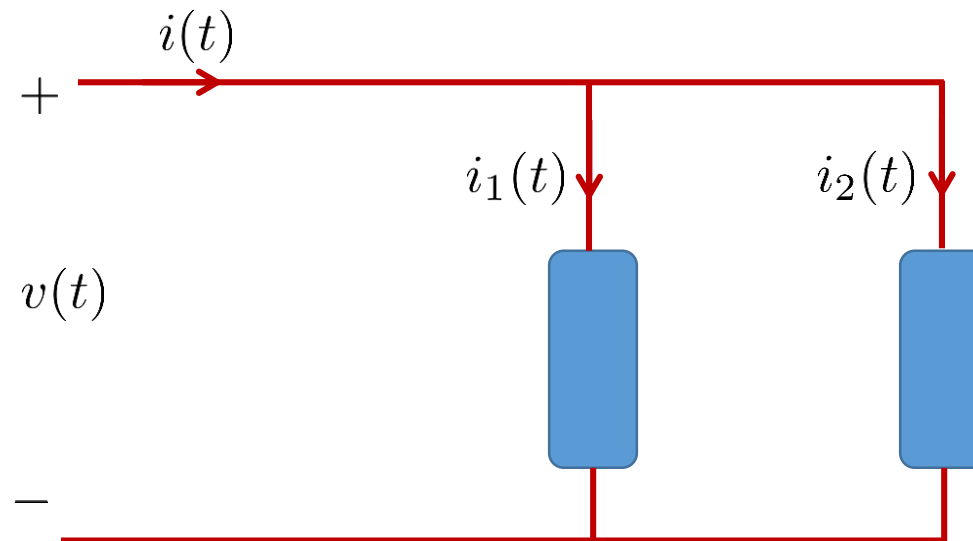

# Resistors in Series or Parallel

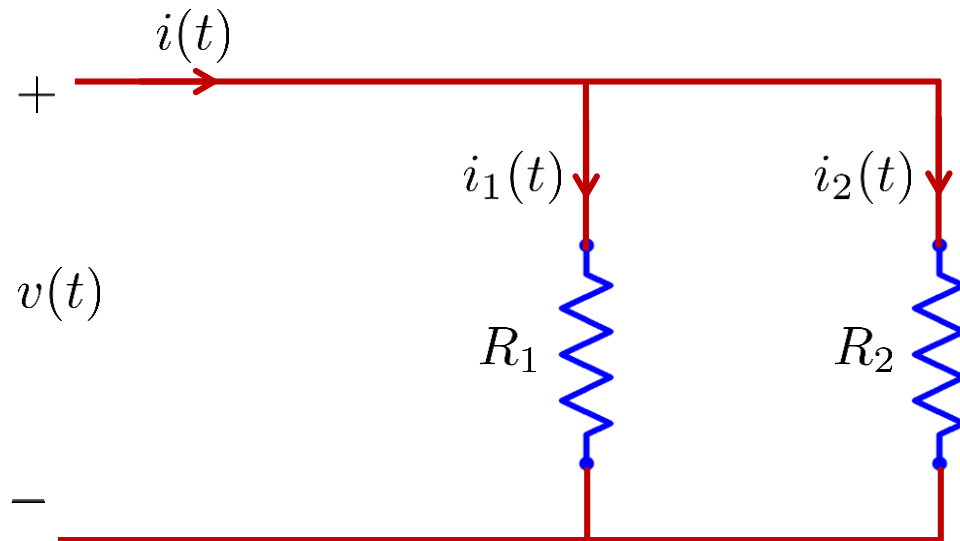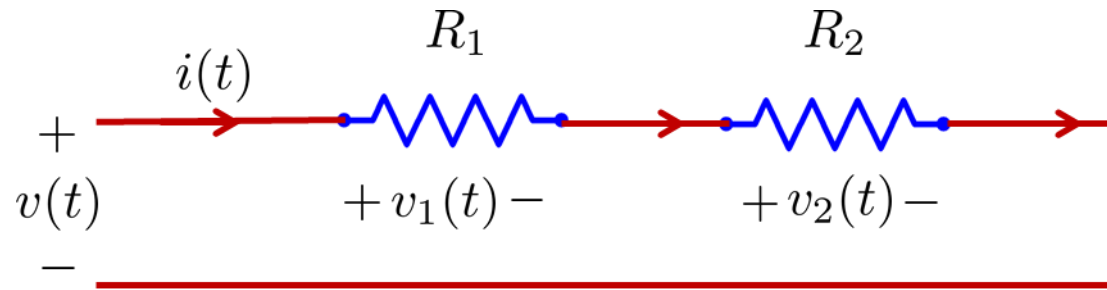

$$v_1(t) = i(t) R_1$$

$$v_2(t) = i(t) R_2$$

$$v(t) = v_1 + v_2 = i(t) (R_1 + R_2)$$

$$v(t) = i(t) R_{eq}$$

$$\Rightarrow R_{eq} = R_1 + R_2$$

$$i_1(t) = \frac{v(t)}{R_1}, \quad i_2 = \frac{v(t)}{R_2}$$


$$i(t) = i_1 + i_2 = v(t) \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$i(t) = \frac{v(t)}{R_{eq}}$$

$$\Rightarrow \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

# Capacitors in Series or Parallel

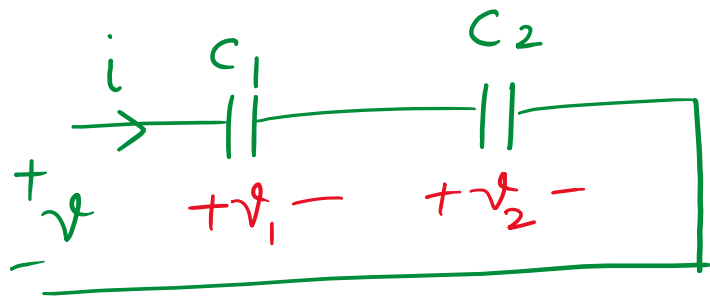

Same current  $\leftrightarrow$  same charge  $\Rightarrow i \leftrightarrow q$

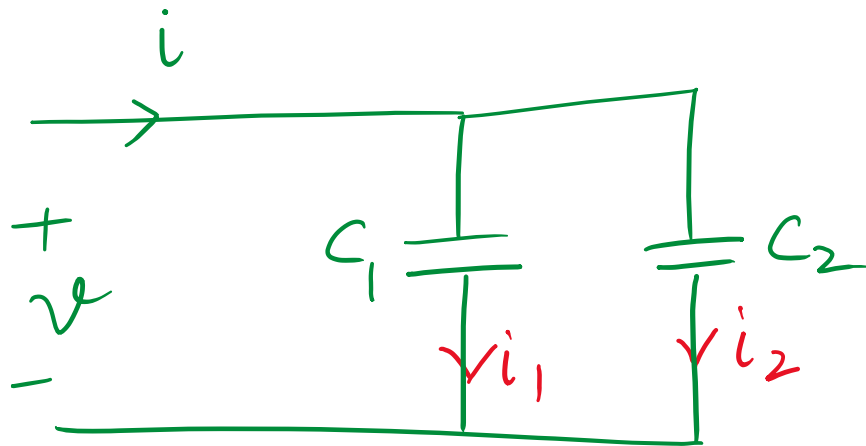
$$v_1 = \frac{q}{C_1}, \quad v_2 = \frac{q}{C_2} \Rightarrow v = q \left( \frac{1}{C_1} + \frac{1}{C_2} \right)$$
$$v = \frac{q}{C_{eq}} \Rightarrow \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} \Rightarrow \boxed{C_{eq} = \frac{C_1 C_2}{C_1 + C_2}}$$



Similarly

$$C_{eq} = C_1 + C_2$$

# Inductors in Series or Parallel

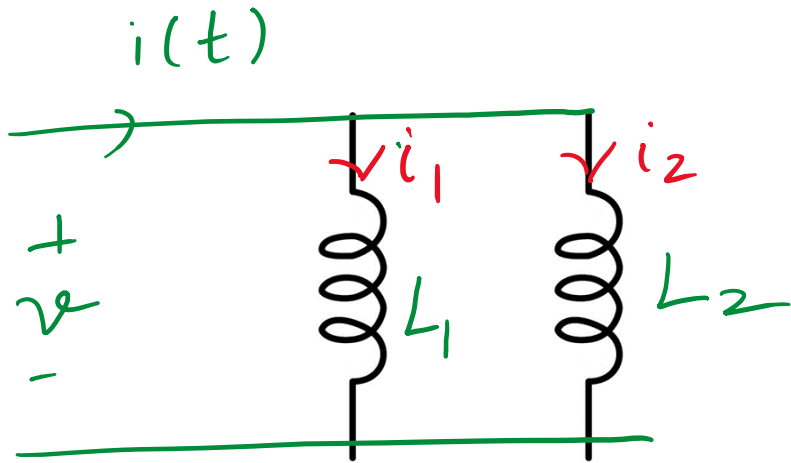

\* Since flux  $\propto$  current in inductor, we can use flux to determine equivalent inductance ( $L_{eq}$ ).

\* Let's determine  $L_{eq}$  using

$$v = L_{eq} \frac{di}{dt}$$


Since  $i = i_1 + i_2 \Rightarrow v = L_{eq} \left( \frac{di_1}{dt} + \frac{di_2}{dt} \right)$

$$\frac{di_1}{dt} = \frac{v}{L_1}, \quad \frac{di_2}{dt} = \frac{v}{L_2} \Rightarrow v = L_{eq} \left( \frac{1}{L_1} + \frac{1}{L_2} \right) v$$

$$\Rightarrow \boxed{\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}}$$

$$\text{OR } \boxed{L_{eq} = \frac{L_1 L_2}{L_1 + L_2}}$$

# Inductors in Series or Parallel

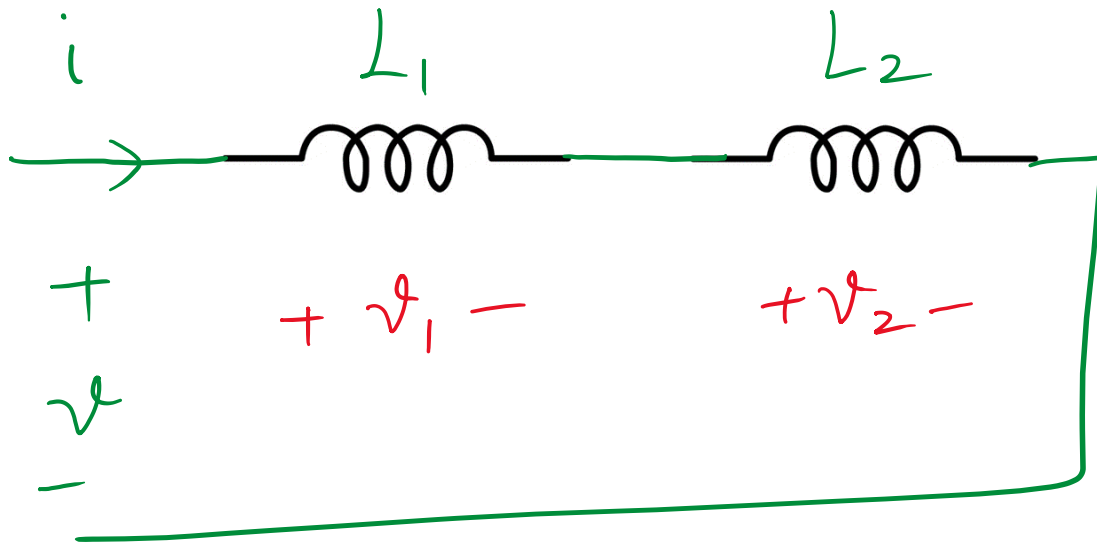

$$v = v_1 + v_2$$

$$v = L_1 \frac{di}{dt} + L_2 \frac{di}{dt}$$

$$\Rightarrow v = \underbrace{(L_1 + L_2)}_{L_{eq}} \frac{di}{dt}$$

$$\Rightarrow L_{eq} = L_1 + L_2$$

# Example: Equivalent Capacitance

Determine Equivalent Capacitance:


$$* C_7 - C_8 - C_9 = 2 \mu F$$

series

$$* C_6 \parallel C_7 C_8 C_9$$
$$= 2 \mu + 4 \mu = 6 \mu F$$

$$* C_4 C_5 (C_6 \parallel C_7 C_8 C_9) = 2 \mu F$$


$$* C_3 \parallel ( \quad ) = 6 \mu F$$

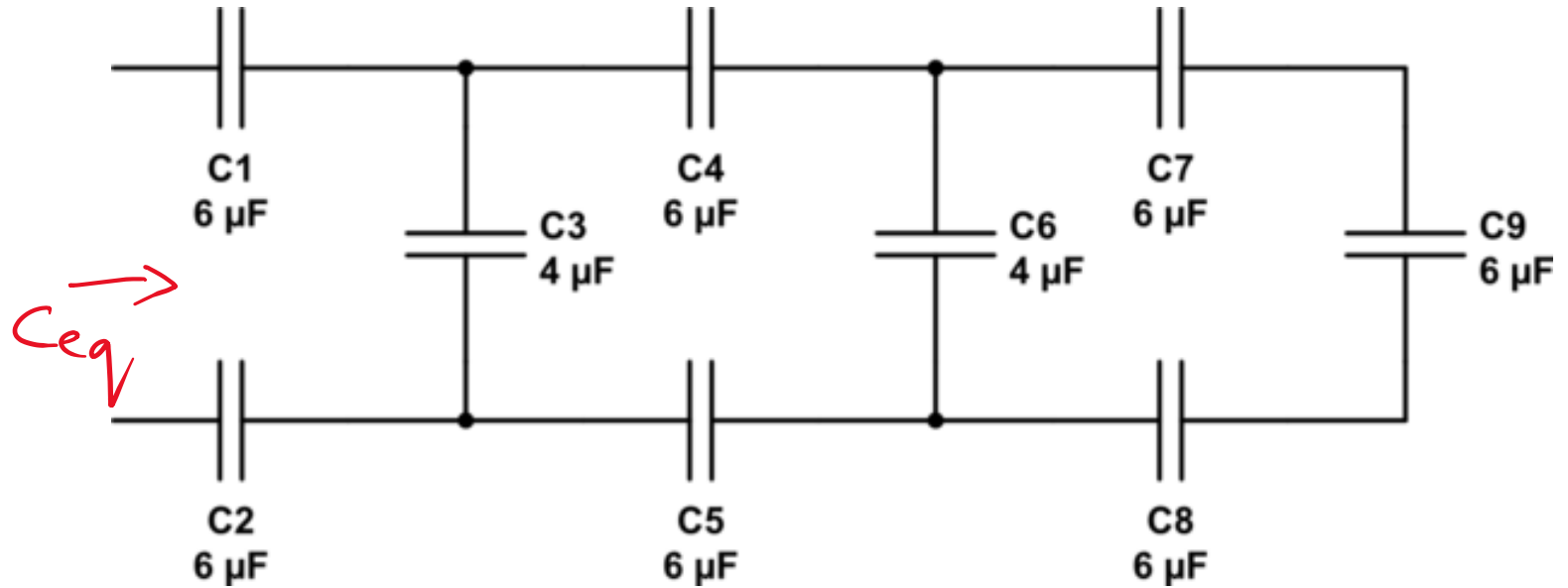

$$C_{eq} = 2 \mu F$$

# Example: Voltage and Current Divider Rules


## Voltage Divider:

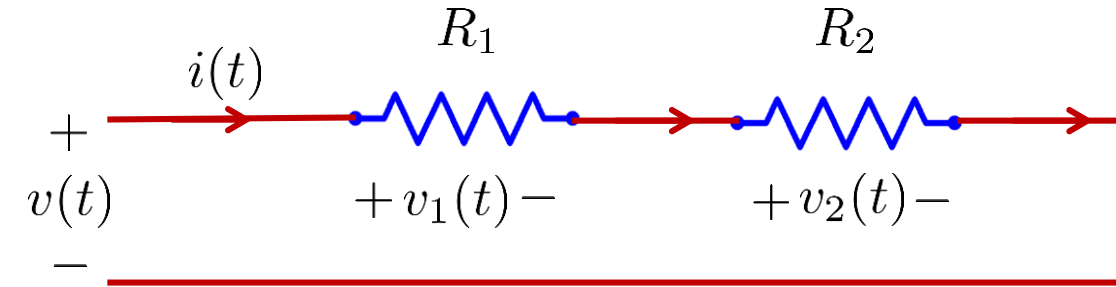

$$v_1(t) = \frac{R_1}{R_1 + R_2} v(t)$$

$$v_2(t) = \frac{R_2}{R_1 + R_2} v(t)$$

## Current Divider:

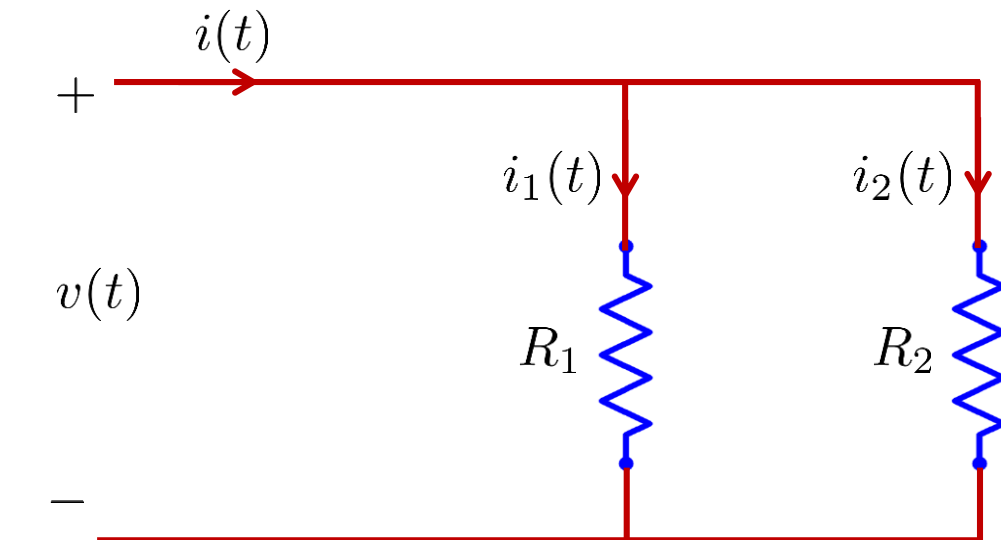

$$i_1(t) = \frac{R_2}{R_1 + R_2} i(t)$$

$$i_2(t) = \frac{R_1}{R_1 + R_2} i(t)$$