



# EE 240 Circuits I

Dr. Zubair Khalid

Department of Electrical Engineering  
School of Science and Engineering  
Lahore University of Management Sciences

[https://www.zubairkhalid.org/ee240\\_2020.html](https://www.zubairkhalid.org/ee240_2020.html)

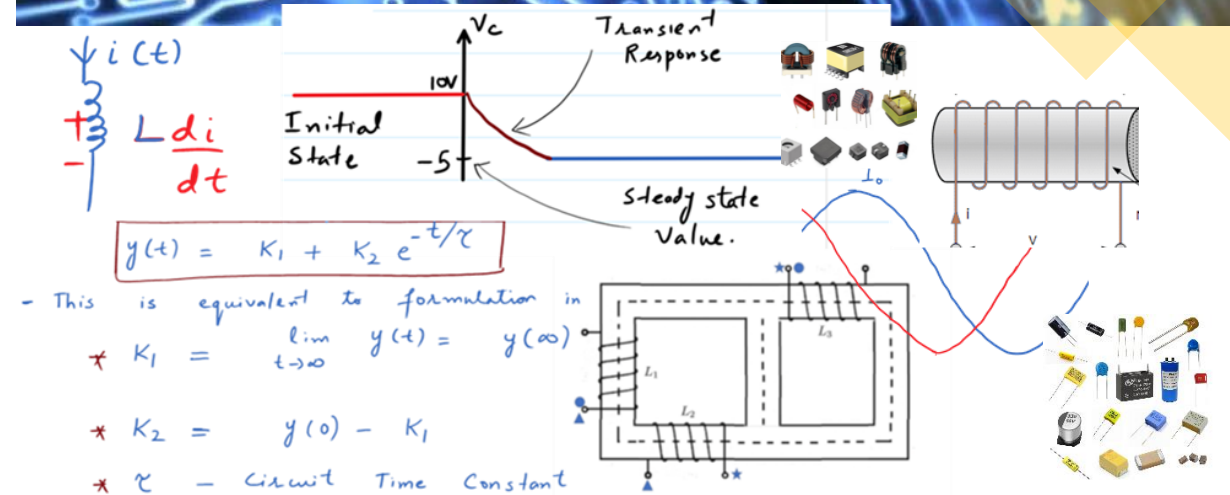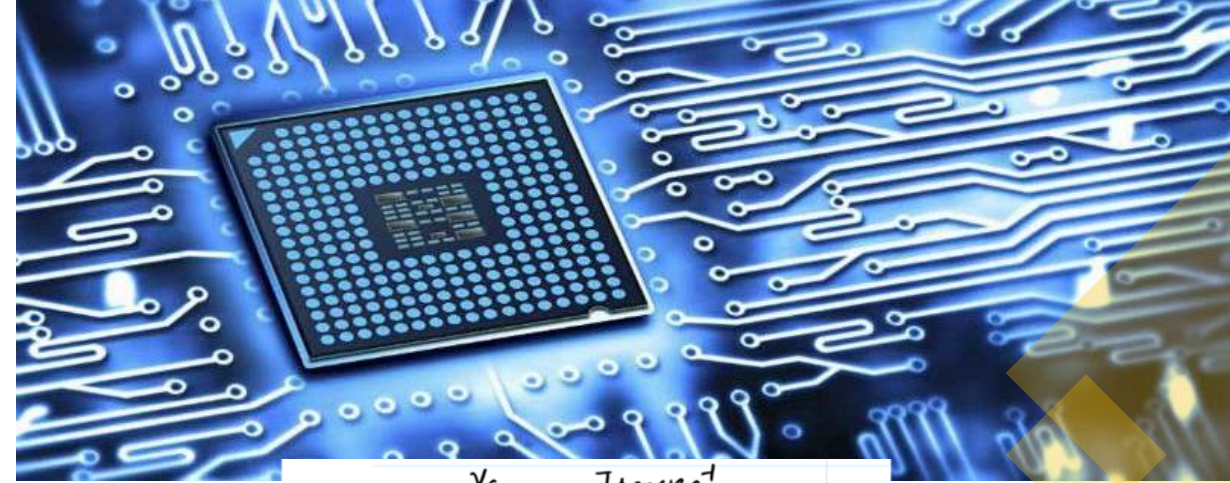- Thevenin's Theorem and Norton's Theorem
- Equivalent Circuit




# Thevenin's Theorem

## Overview

Thevenin theorem is used to change a complicated circuit into a simple equivalent circuit consisting of *a single voltage source*, referred to as Thevenin voltage  $V_{th}$  in series with *a single resistance*, referred to as Thevenin Resistance  $R_{th}$ .
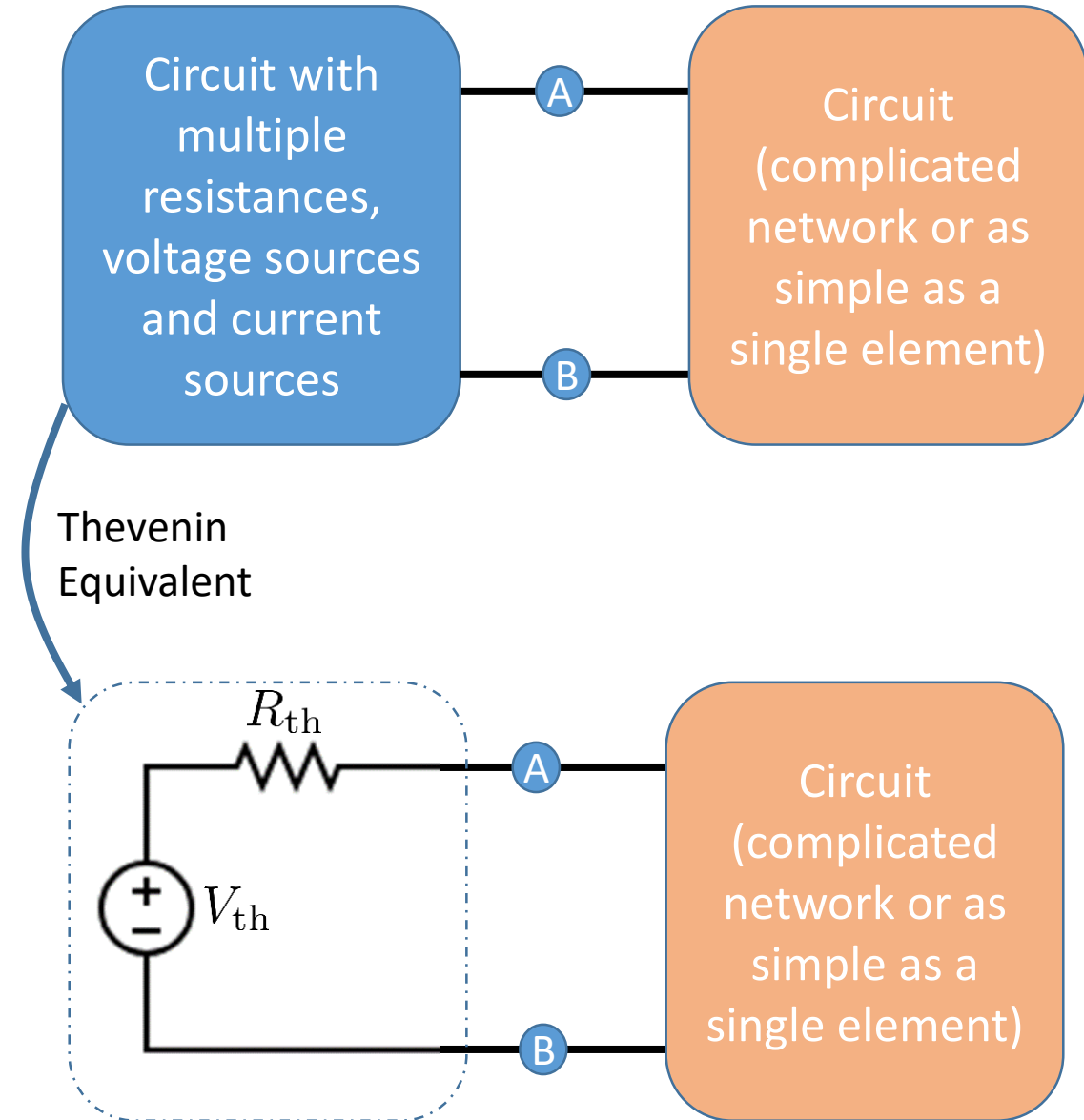
## Thevenin Theorem Statement:

Any circuit containing only resistances, voltage sources, and current sources be replaced at the terminals A-B by an equivalent combination of a voltage source  $V_{th}$  in a series connection with a resistance  $R_{th}$ .



# Thevenin's Theorem

## How to Obtain Thevenin Equivalent

**Key Idea:** Use the concept of equivalence: same current and voltage characteristics across terminals A-B.


*Only keep the circuit for which we want to find the equivalent circuit; disconnect the rest of the circuit.*

Determine  $V_{th}$ :

As no current is flowing from A to B,  $V_{th}$  is simply a voltage across terminals A-B.

We can determine  $V_{th}$  by analysing the circuit inside blue box and determine the voltage across terminals A-B.

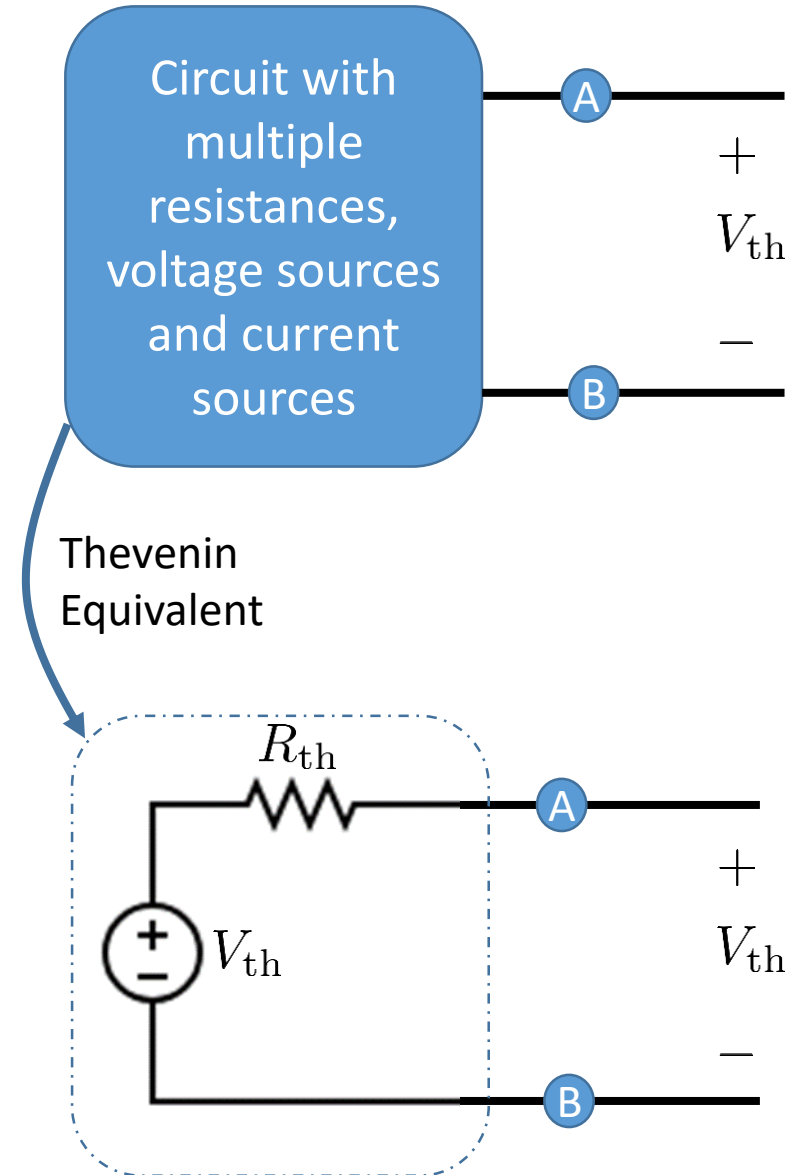*We will learn different methods to obtain Thevenin Resistance*



# Thevenin's Theorem

## How to Obtain Thevenin Equivalent

Determine  $R_{th}$ :


### Method 1:

- Switch off the independent sources and determine the equivalent resistance across terminals A and B.

### Method 2:

- Short-circuit terminals A and B and determine the current flowing from A to B, referred to as  $I_{sc}$ .
- Using this current, we can determine  $R_{th}$  as

$$R_{th} = \frac{V_{th}}{I_{sc}}$$

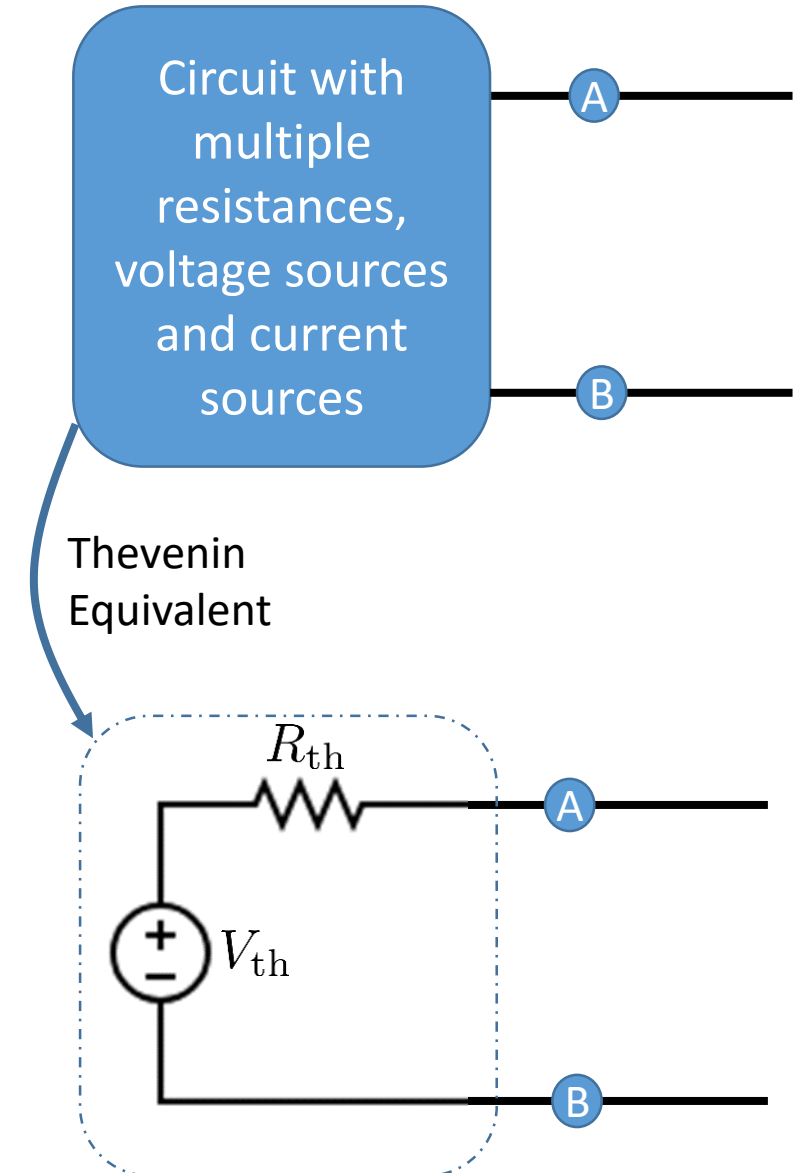

# Thevenin's Theorem

## How to Obtain Thevenin Equivalent

Determine  $R_{th}$ :

### Method 3:

- Switch off the independent sources
- Connect a test source across terminals A-B
- If 1V (known) voltage test-source is connected:

Determine the current  $I_{test}$  supplied by voltage source.

We can determine  $R_{th}$  as follows:



$$R_{th} = \frac{1}{I_{test}}.$$

- If 1A (known) current test-source is connected:

Determine the voltage  $V_{test}$  developed across the current source.

We can determine  $R_{th}$  as follows:

$$R_{th} = \frac{V_{test}}{1}.$$

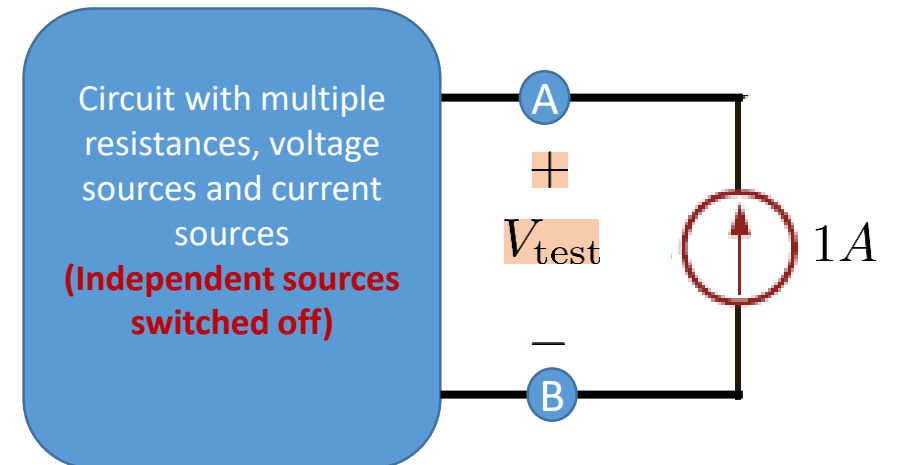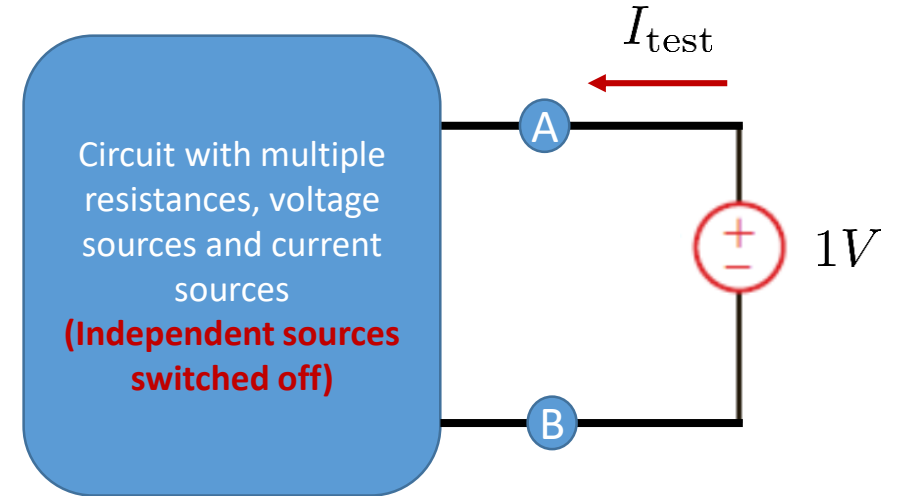



# Thevenin's Theorem

## How to Obtain Thevenin Equivalent

Determine  $R_{th}$ :

Which method to use?

Independent sources	Dependent sources	Method - can be used	Justification
✓	✗	Methods 1, 2 and 3	
✓	✓	Methods 2 and 3	Method 1 cannot be used due to the presence of dependent sources
✗	✓	Method 3	No independent source driving $V_{th}$ or $I_{sc}$
✗	✗	Methods 1 and 3	No independent source driving $V_{th}$ or $I_{sc}$

**Note:** Equivalent circuit does not have the voltage source if there is no independent source in the circuit.


# Norton's Theorem

Norton theorem is used to change a complicated circuit into a simple equivalent circuit consisting of **a single current source**, referred to as Norton current voltage  $I_N$  in parallel with **a single resistance** (the same as Thevenin Resistance  $R_{th}$ , explained below).

- The value of the Norton current is one that flows from terminal A to B when the two terminals are shorted together. This is in fact  $I_{sc}$ , that is short-circuit current.
- The resistance represents the resistance looking back into the terminals when source is switched off. This is in fact Thevenin Resistance.


## Connection with the Thevenin's Theorem

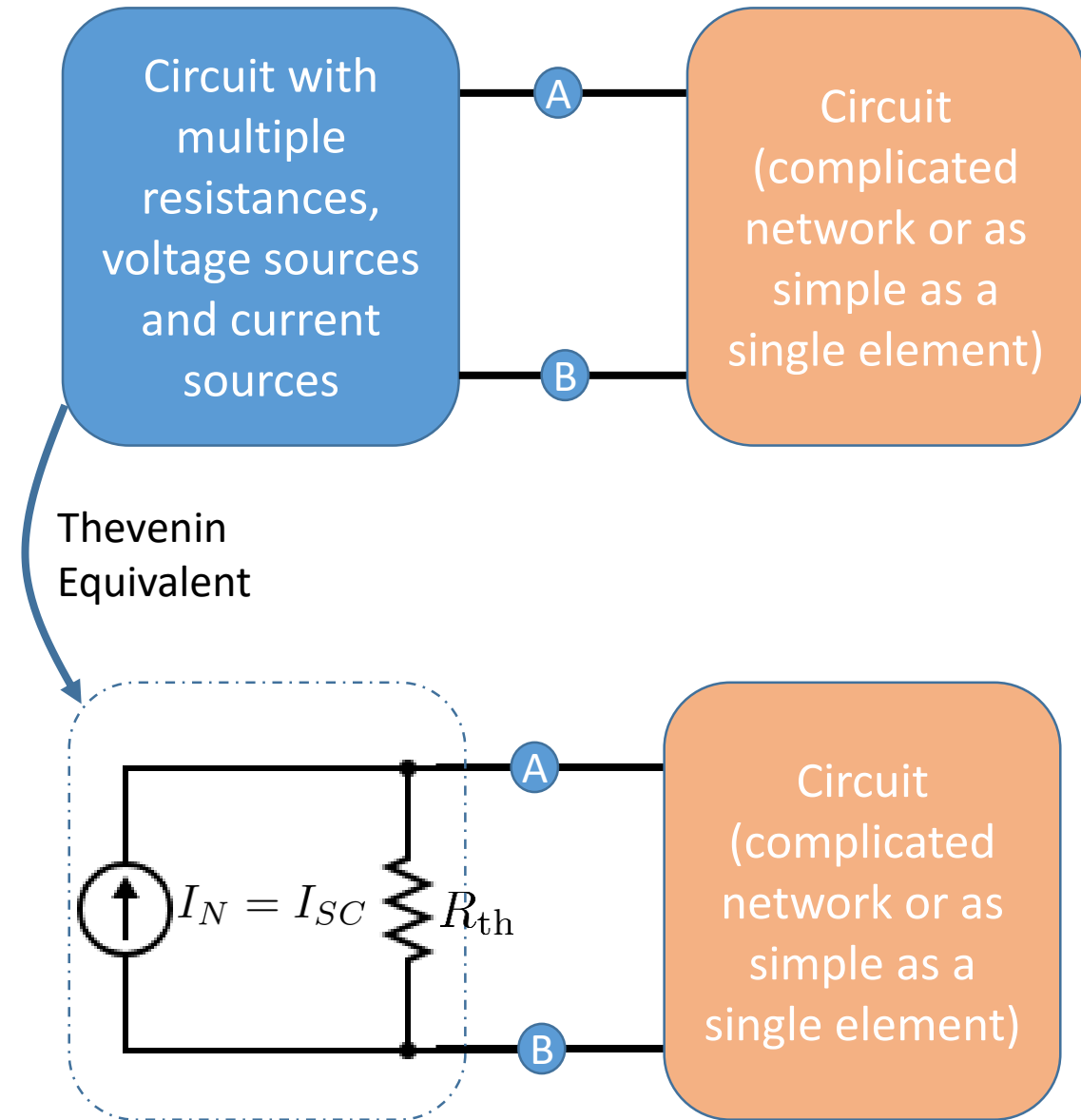**The source transformation of Thevenin's equivalent yields Norton's equivalent and vice versa.**



# Thevenin's Theorem

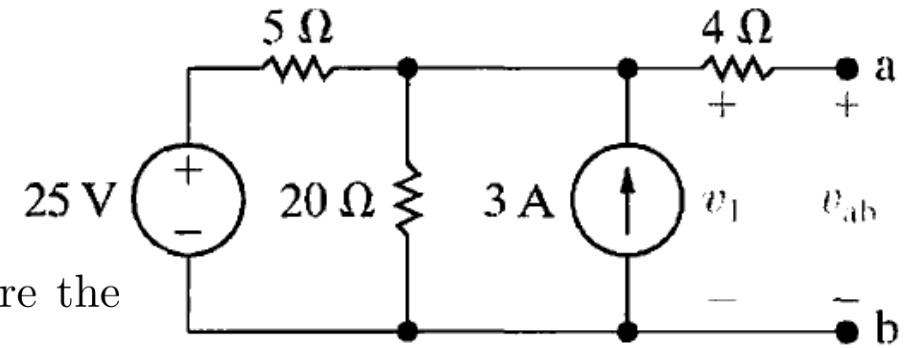**Example 1:** Find the Thevenin's equivalent circuit for the following circuit across terminals a-b.




Taking bottom node as ground node and applying KCL at a node where the voltage is  $v_1$

$$\star \frac{v_1 - 25}{5} + \frac{v_1}{20} = 3$$

$$\frac{v_1}{5} + \frac{v_1}{20} = 8 \Rightarrow \boxed{v_1 = 32\text{V}}$$


$R_{th}$  : Find  $I_{sc}$ :

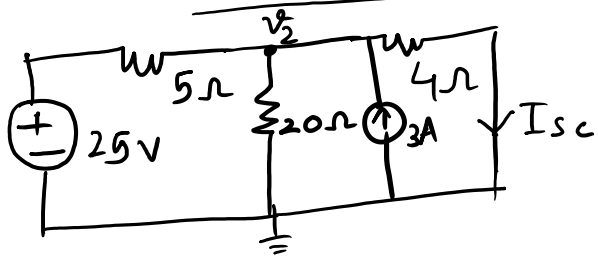

$$-3 + \frac{v_2 - 25}{5} + \frac{v_2}{20} + \frac{v_2}{4} = 0$$

$$v_2 = 16\text{V} \Rightarrow \boxed{I_{sc} = 4\text{A}}$$
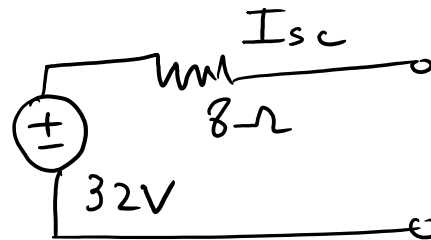
$$R_{th} = \frac{v_{th}}{I_{sc}} = 8\Omega$$






# Thevenin's Theorem

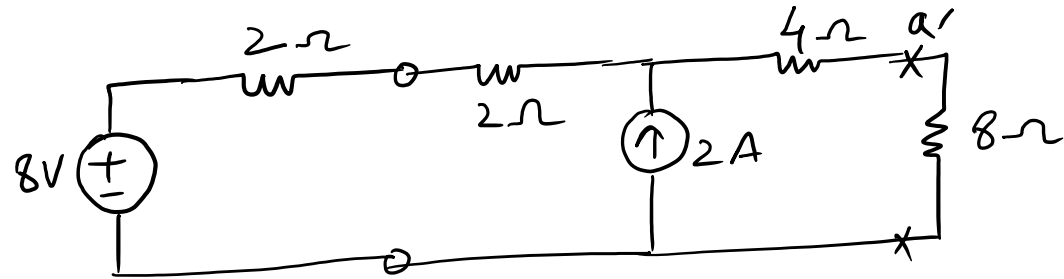
**Example 2:** Find  $V_o$  using Thevenin's theorem.

We will use Thevenin's theorem twice here.


Obtaining Thevenin equivalent across terminals a-b:



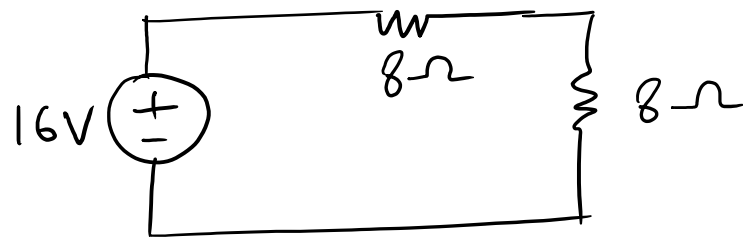Obtaining Thevenin equivalent across terminals a'-b':



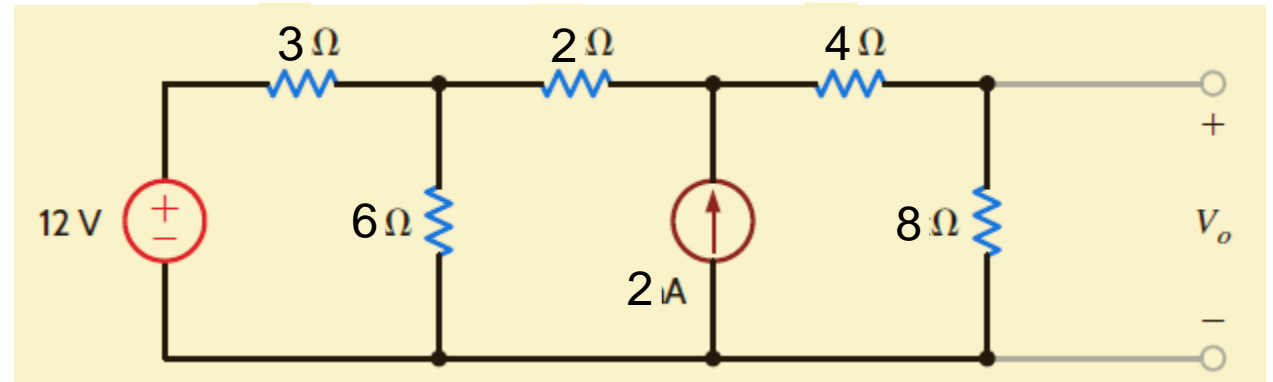
$$V_o = 16 \times \frac{8}{16} = \boxed{8V}$$




# Thevenin's and Norton's Theorems

## Problems – In class

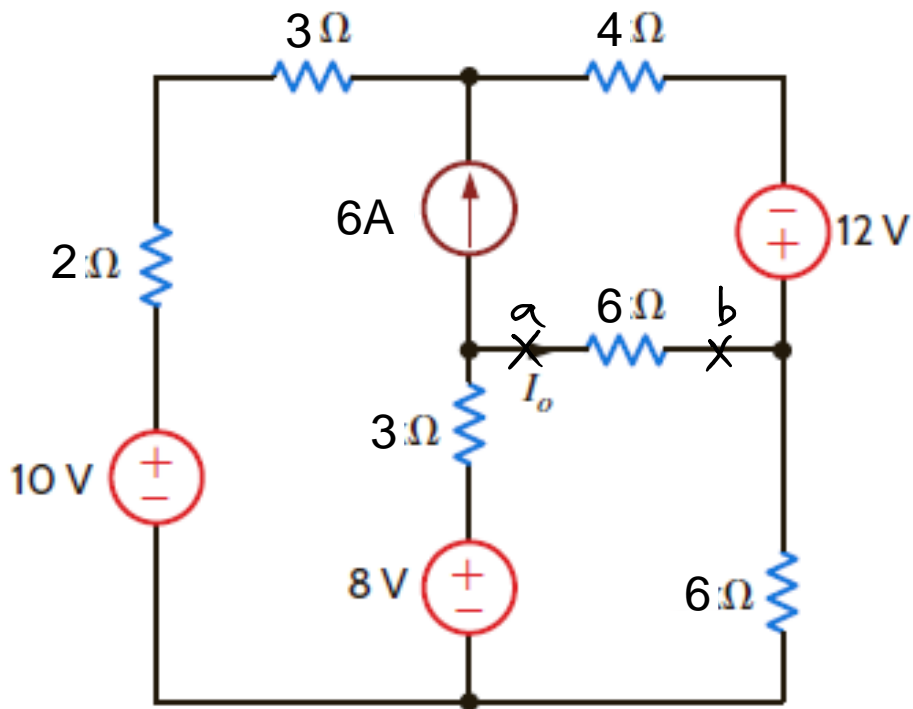**Example 3:** Find  $I_o$  using Thevenin's or Norton's theorem



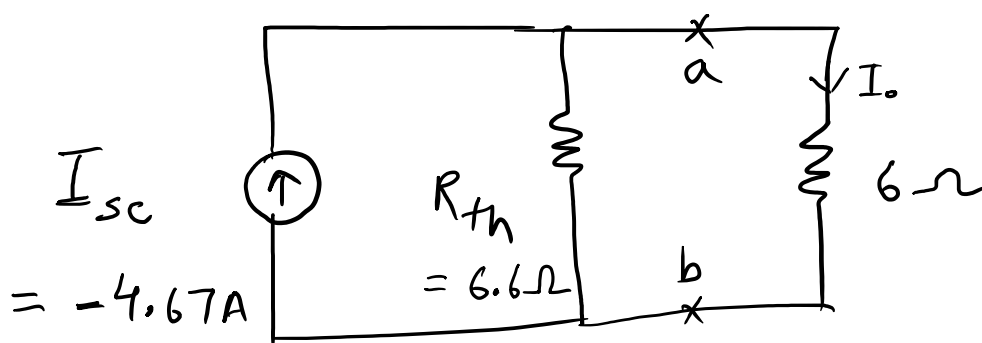
Equivalent<sup>t</sup> : (computed on next page)



$$I_o = \frac{6.6}{12.6} \times (-4.67) = \underline{\underline{-2.44A}}$$

# Thevenin's and Norton's Theorems

## Problems – In class

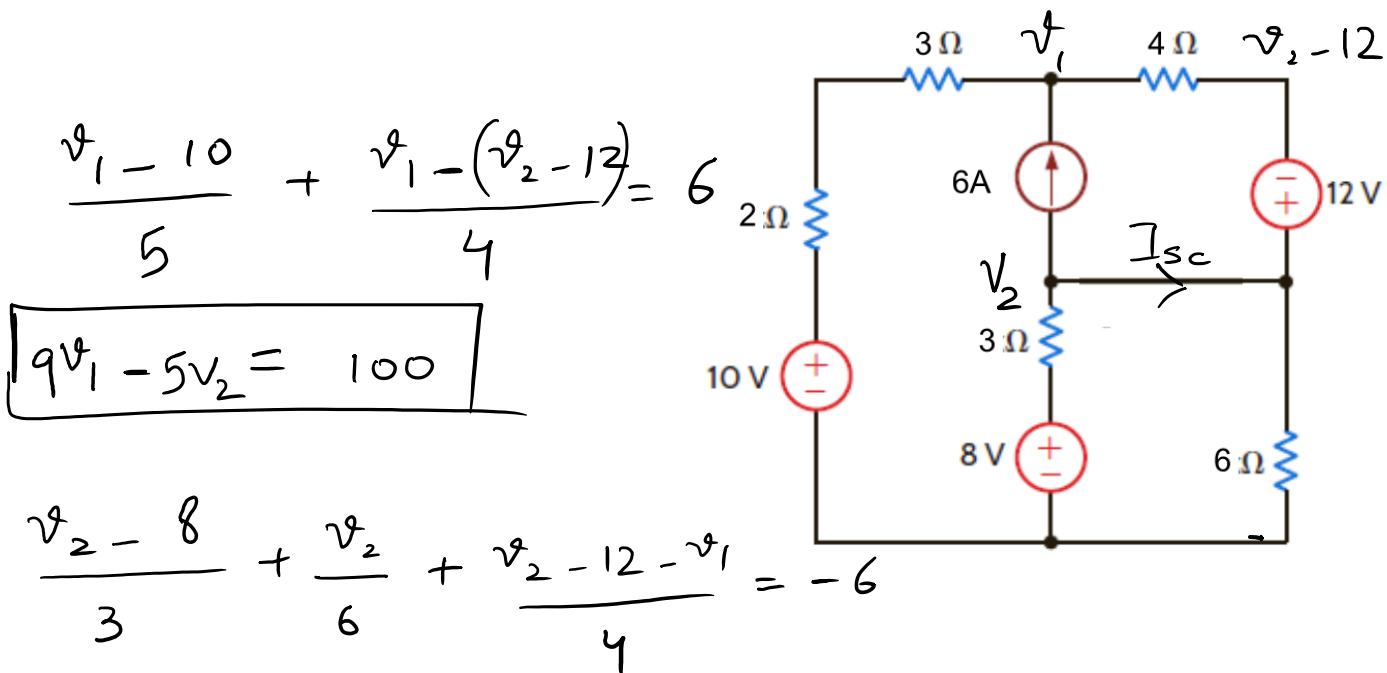


$$\Rightarrow \frac{4v_2 - 24 + 2v_2 + 3v_2 - 36 - 3v_1}{12} = -6$$

$$\boxed{-3v_1 + 9v_2 = -4} \Rightarrow -9v_1 + 27v_2 = -12$$

$$\Rightarrow 22v_2 = 88 \Rightarrow \boxed{v_2 = 4V}$$


$$\frac{v_2 - 8}{3} + 6 + I_{sc} = 0 \Rightarrow \boxed{I_{sc} = -4.667A}$$

R<sub>th</sub>:

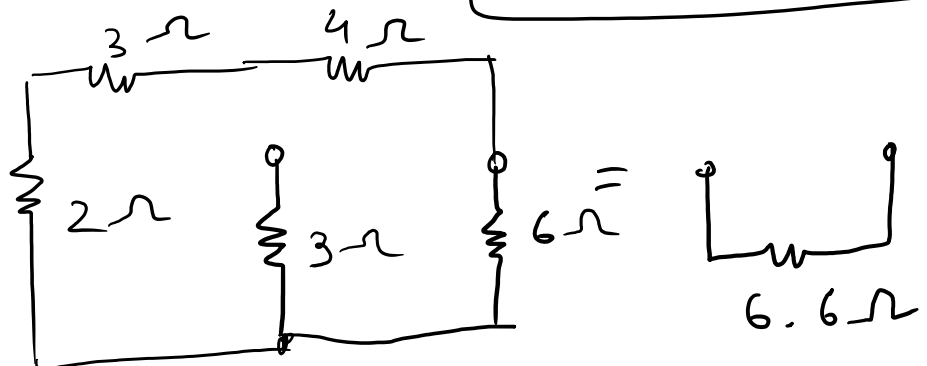


# Thevenin's and Norton's Theorems

## Problems – In class

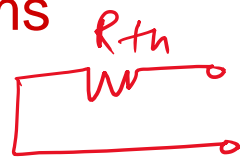

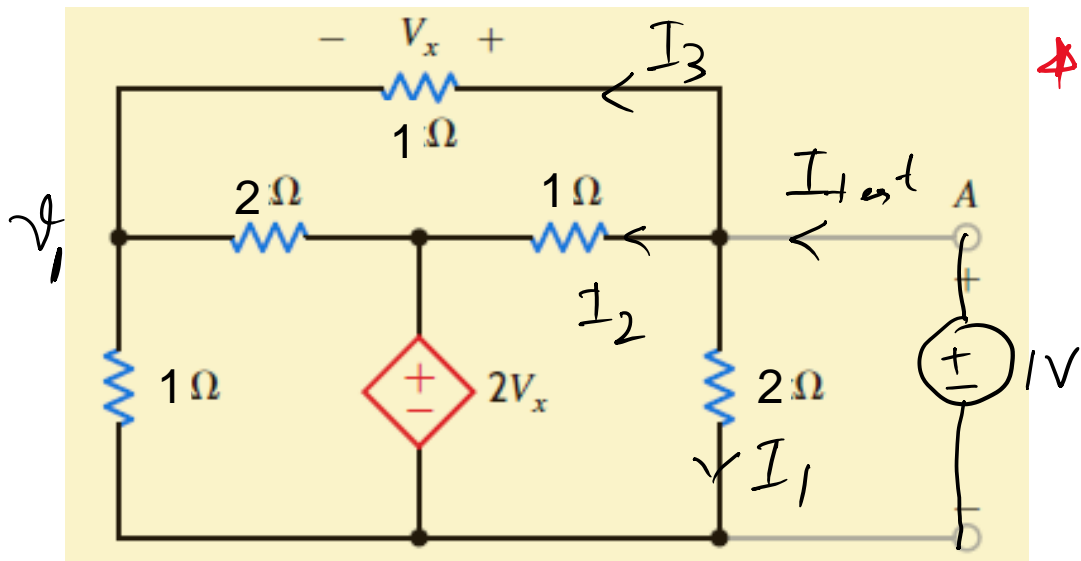**Example 4:** Find the Thevenin equivalent circuit for the following circuit with respect to the terminals AB (Irwin – Example 5.8)



$$V_{th} = 0V$$

We have

$$V_x + V_1 = 1V \Rightarrow V_1 = 1 - V_x$$

$$\text{KCL ; } \frac{V_1}{1} + \frac{V_1 - 2V_x}{2} + \frac{V_1 - 1}{1} = 0$$

$$\Rightarrow 1 - V_x + \frac{1 - 3V_x}{2} - V_x = 0$$

$$\Rightarrow 3 = 7V_x \Rightarrow V_x = \frac{3}{7}V$$

$$I_1 = \frac{1}{2}A, \quad I_2 = \frac{1 - 2(3/7)}{1} = \frac{1}{7}A$$

$$I_3 = \frac{3}{7}A$$

$$I_{ext} = I_1 + I_2 + I_3 = \frac{15}{14}A$$


EE240 Circuits I

$$\Rightarrow R_{th} = \frac{1}{I_{ext}} = \frac{14}{15}\Omega$$

# Thevenin's and Norton's Theorems

## Problems – In class

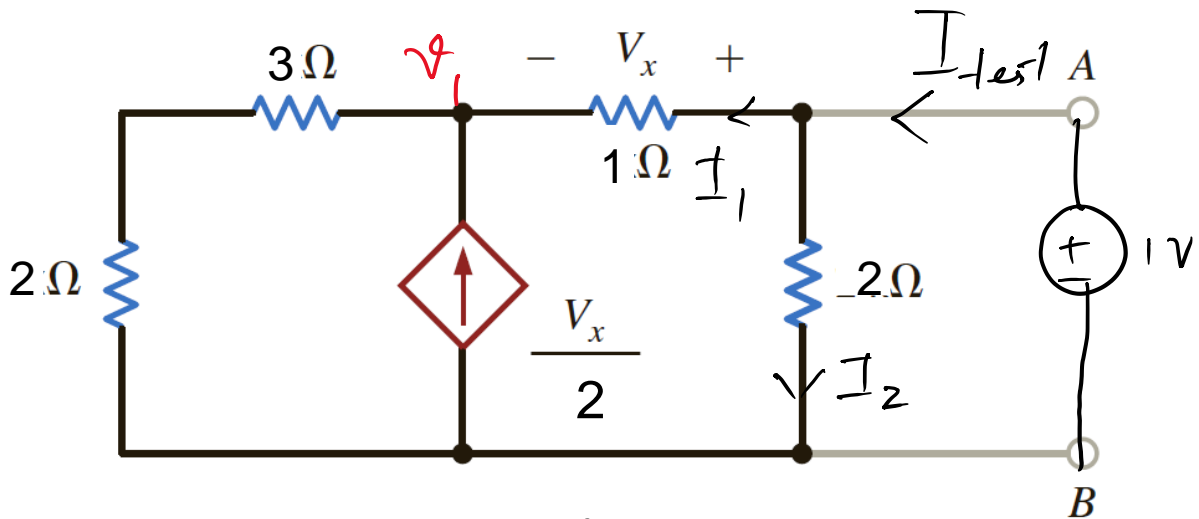**Example 5:** Find the Thevenin equivalent circuit for the following circuit with respect to the terminals AB (Irwin – E 5.13)




$$\frac{V_1}{5} + \frac{V_1 - 1}{1} = \frac{V_x}{2} \quad \left\{ \begin{array}{l} V_x + V_1 = 1 \\ \Rightarrow V_x = 1 - V_1 \end{array} \right.$$

$$\Rightarrow \boxed{V_1 = \frac{15}{17} \text{ V}}$$

$$I_{\text{test}} = I_1 + I_2 = \frac{1}{2} + \frac{2}{17} = \frac{21}{34} \text{ A}$$

$$\left. \begin{array}{l} I_1 = \frac{1 - V_1}{1} = \frac{2}{17} \text{ A} \\ I_2 = \frac{1}{2} \end{array} \right\} \Rightarrow R_{\text{th}} = \frac{1}{I_{\text{test}}} = \frac{34}{21} \Omega$$


Equivalent :-

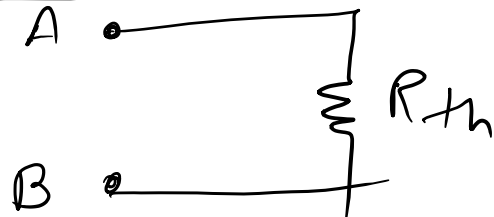

# Thevenin's and Norton's Theorems

## Problems – In class

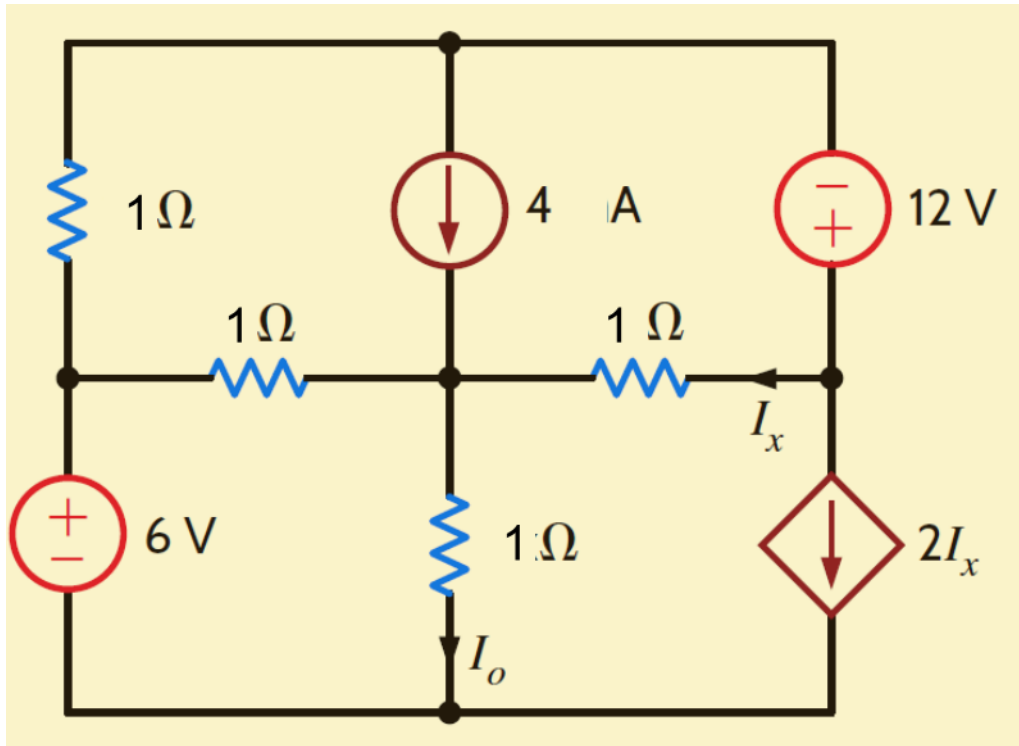**Example 6:** Find  $I_o$  using Thevenin's theorem or Norton's theorem






# Thevenin's and Norton's Theorems

## Problems – In class

Determine  $V_{oc}$  first:

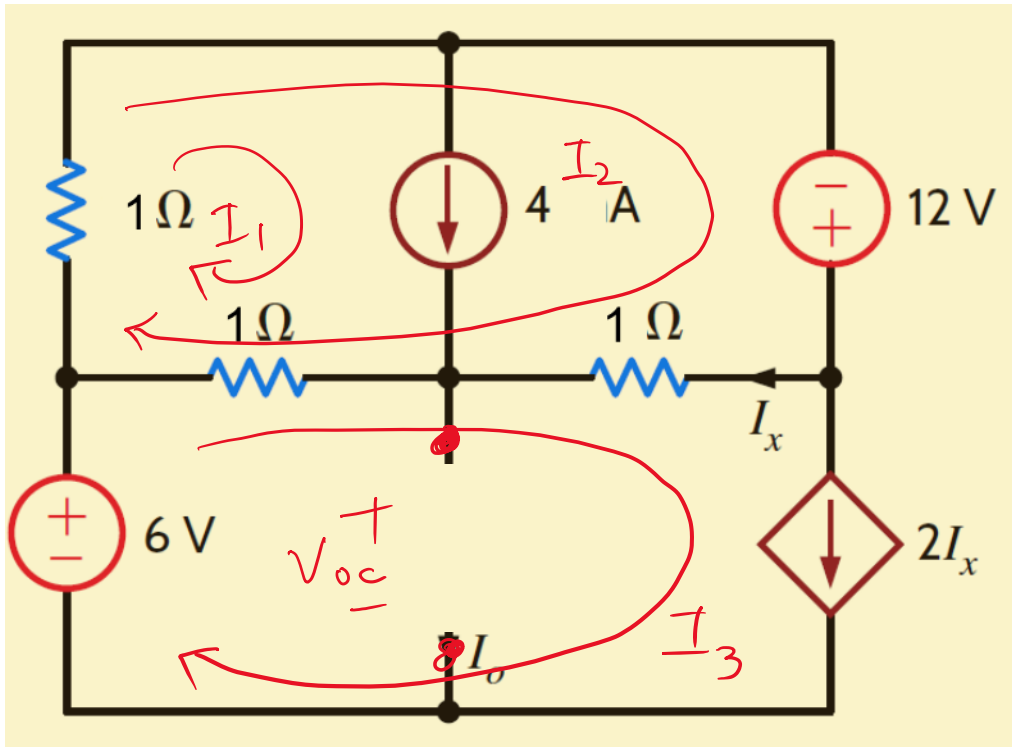

$$I_1 = 4A, \quad I_3 = 2I_x$$

$$\begin{aligned} \text{Loop 2} \quad & -12 + 1(I_2 - I_3) + 1(I_1 + I_2 - I_3) \\ & + (I_1 + I_2)1 = 0 \end{aligned}$$

$$I_x = I_2 - I_3 \Rightarrow \boxed{3I_x = I_2}$$

Solving


$$I_3 = \frac{8A}{5}, \quad I_2 = \frac{12A}{5}, \quad I_x = \frac{4}{5}A$$

$$V_{oc} = 6 + (I_1 + I_2 - I_3)1 = \frac{54}{5}V$$

# Thevenin's and Norton's Theorems

## Problems – In class

Determine  $I_{sc}$

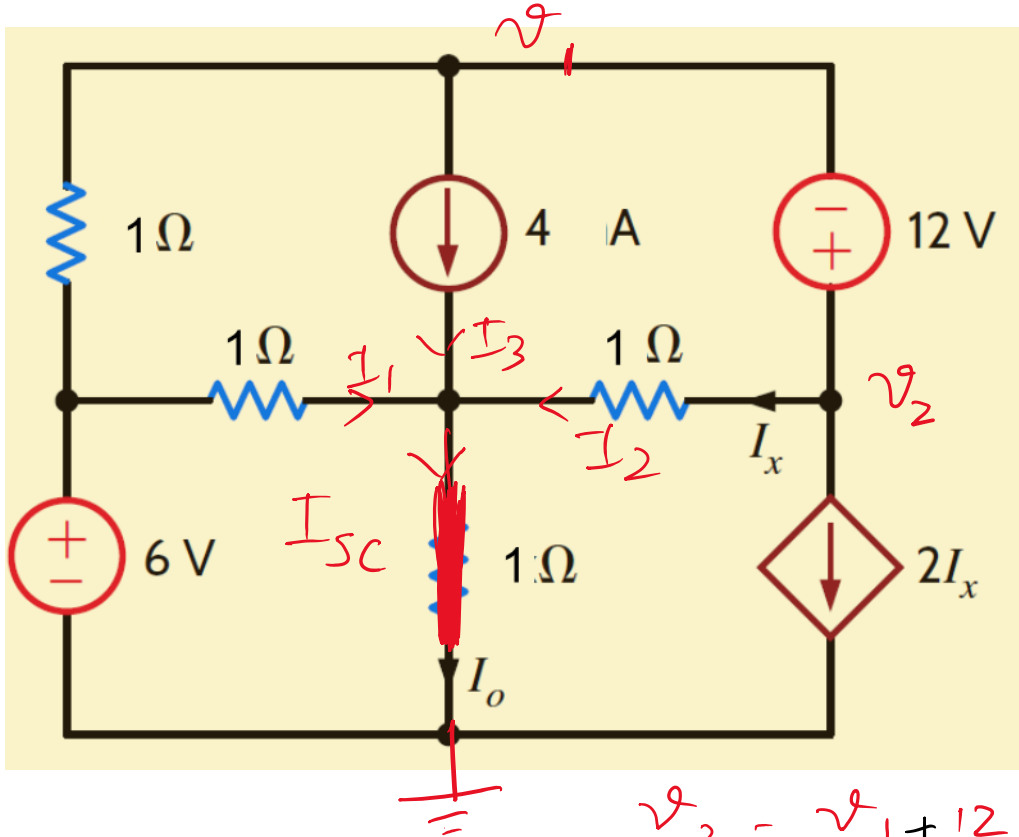

$$v_2 = v_1 + 12 \quad (\text{Super Node})$$

$$\left. \begin{aligned} \frac{v_1 - 6}{1} + 4 + \frac{v_2}{1} + 2I_x &= 0 \end{aligned} \right\} I_x = \frac{v_2}{1}$$

$$\Rightarrow v_1 - 6 + 4 + 3v_1 + 36 = 0$$

$$\Rightarrow v_1 = -\frac{17}{2} \text{ V}, \quad v_2 = 7/2$$

$$I_{sc} = \frac{6}{1} + \frac{7}{2} + 4 = \frac{27}{2} \text{ A}$$


$$\Rightarrow R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{54/5}{27/2} = \frac{4}{5} \Omega$$

# Thevenin's and Norton's Theorems


## Problems – In class

Using equivalent circuits to determine  $I_o$

Thevenin Equivalent

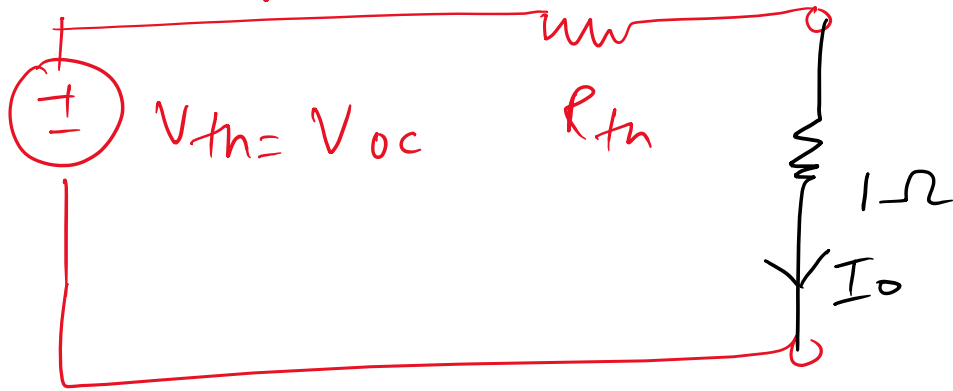

Norton Equivalent

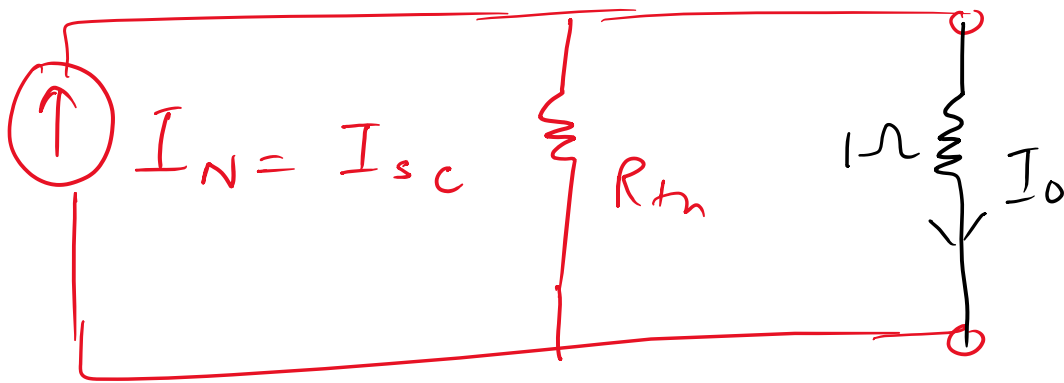


$$I_o = \frac{54/5}{1 + \frac{4}{5}} = \boxed{6 \text{ A}}$$

# Thevenin's and Norton's Theorems

## Problems – In class

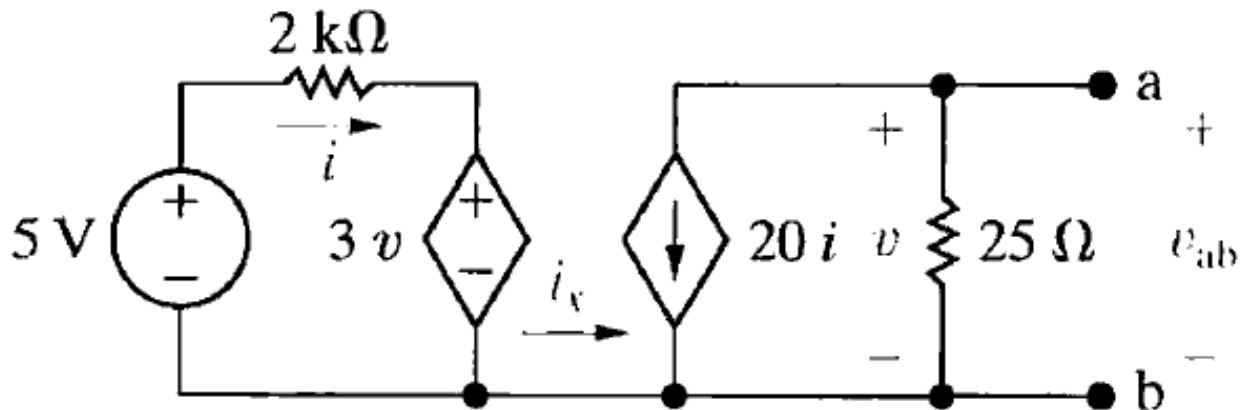**Example 7:** Find the Thevenin equivalent circuit for the following circuit with respect to the terminals a,b




First find  $R_{th}$ :-

Switch off sources and connect 1V test source

$$v = 1V$$

$$3v = 3V$$

$$i = -3/2k$$

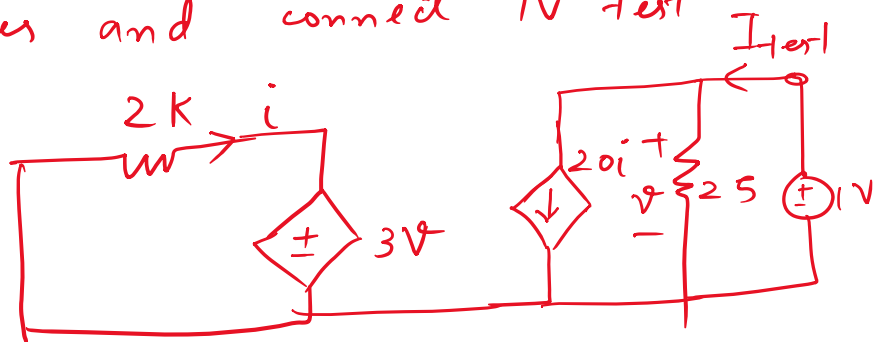

$$\Rightarrow I_{test} = \frac{1}{25} - (20)(i) = 0.04 - 0.03 = 0.01A$$

$$\Rightarrow \boxed{R_{th} = 100\Omega} \leftarrow \frac{1}{I_{sc}}$$

$$\underline{V_{th}}:- \quad \underline{v_{ab} = v = v_{th}}$$

$$V_{th} = -20i \times 25 - \textcircled{1}$$


$$i = \frac{5 - 3V_{th}}{2k} - \textcircled{2}$$

$$\textcircled{1} + \textcircled{2} \Rightarrow \boxed{V_{th} = -5V}$$

# Thevenin's and Norton's Theorems

## Problems – In class

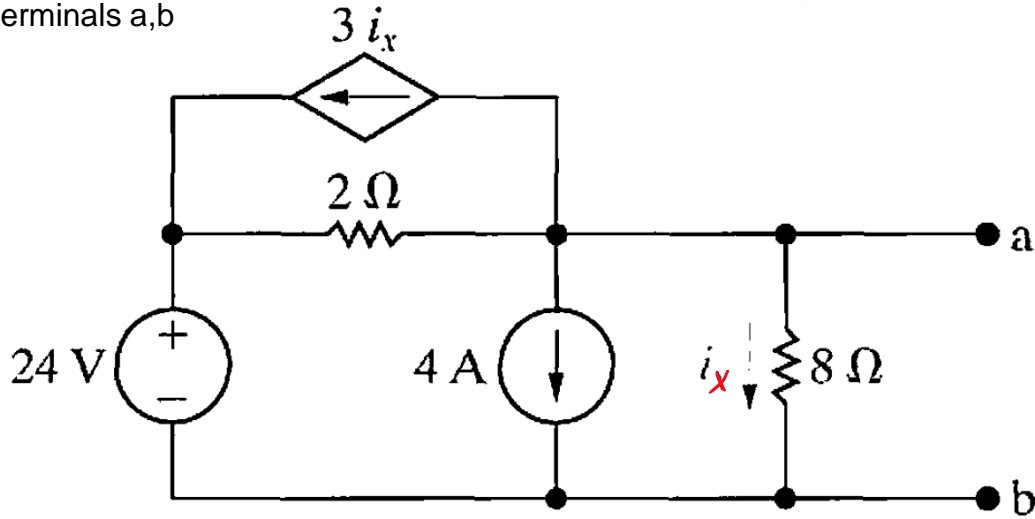**Example 8:** Find the Thevenin equivalent circuit for the following circuit with respect to the terminals a,b



\* Circuit contains both dependent and Independent sources; we can use either of the following techniques

- 1) Determine  $V_{ab}$  and  $I_{sc}$
- 2) Determine  $V_{ab}$ ; Determine  $R_{th}$  by switching off **independent** sources and applying test current (or voltage) source at a-b.

Let's apply 2)

Using KCL;

$V_{ab}$  :

$$\frac{V_{ab}}{8} + \frac{V_{ab} - 24}{2} + 3i_x + 4 = 0$$


where

$$i_x = \frac{V_{ab}}{8} \Rightarrow \boxed{V_{ab} = 8i_x}$$

Solving  $\boxed{V_{ab} = 8V}$


$R_{th}$  : Apply 1V voltage source :

Switch off  
Sources

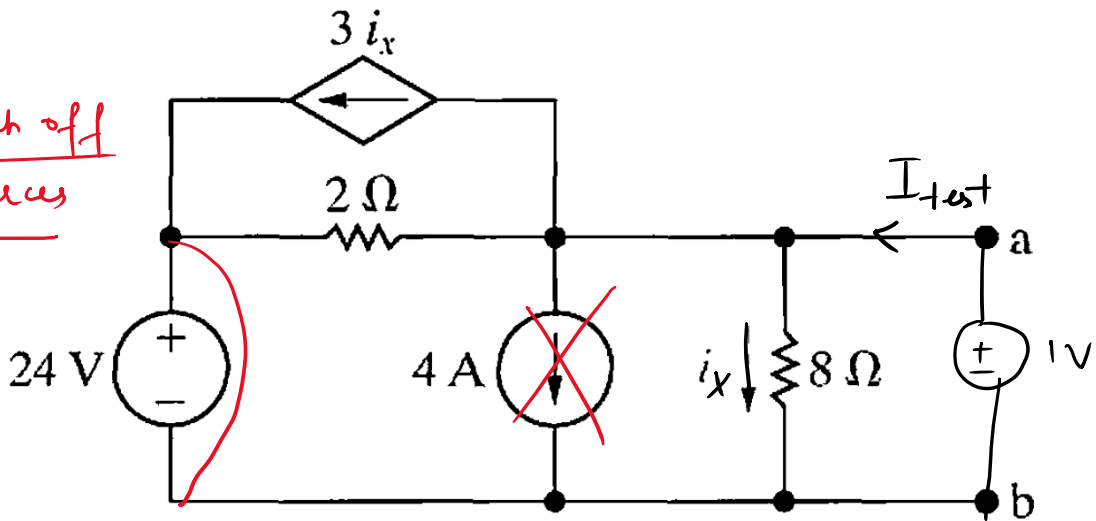

$$i_x = \frac{1}{8} \text{ A}$$
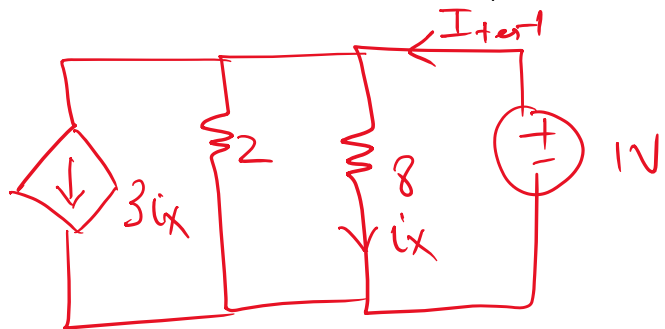
$$\begin{aligned} I_{test} &= \frac{1}{8} + \frac{1}{2} + \frac{3}{8} \\ &= \frac{8}{8} = 1 \text{ A} \end{aligned}$$



$$\Rightarrow R_{th} = \frac{1 \text{ V}}{I_{test}} = \boxed{1 \Omega}$$