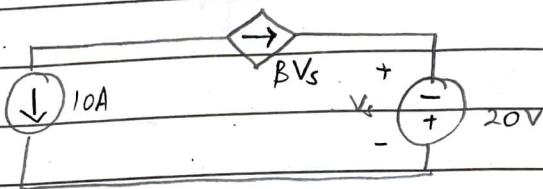


Assignment 2.

Q1:



$$V_s = -20V$$

We know, a ^{DC} current source maintains constant current in a branch.


$$\therefore \beta V_s = -10A \quad \text{direction}$$

$$\beta(-20) = -10$$

$$\therefore \boxed{\beta = \frac{1}{2} \text{ or } 0.5}$$

Thus, interconnection is valid for just 1 value of β i.e. 0.5.

Q2:

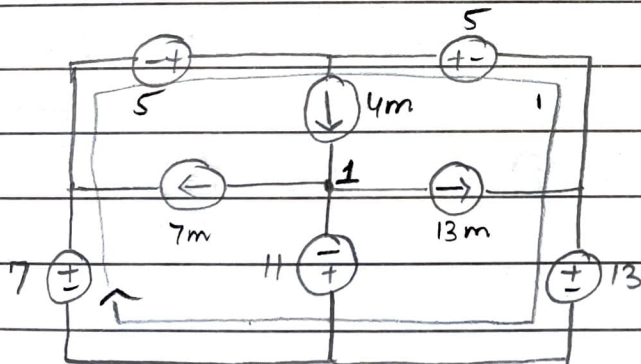


that interconnection is not valid
Many ways to show! Here is one way:

apply KVL on the bigger loop.

$$-5 + 5 + 13 - 7 = 6 \neq 0 \text{ (violates KVL)}$$

Thus, interconnection is not valid!

Q3:

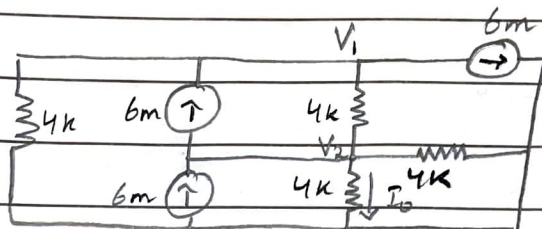

Applying KCL on node labelled V_1 :-

$$\frac{V_1}{4} + \frac{(V_1 - V_2)}{4} + 6 = 6$$

or $V_1 + V_1 = V_2$

$$\therefore 2V_1 = V_2 \quad \text{--- (1)}$$

Applying KCL on node labelled V_2 :-

$$\frac{V_2}{4} + \frac{V_2 - V_1}{4} + \frac{V_2}{4} + 6 = 6$$

$$\Rightarrow 3V_2 - V_1 = 0$$

$$\therefore V_1 = 3V_2 \quad \text{--- (2)}$$

(1) & (2) :-

$$2V_1 - V_2 = 0$$

$$V_1 - 3V_2 = 0$$

This system of equations can have infinite solutions.


Also, $I_0 = \frac{V_2}{4k}$

Let $V_1 = 0 \Rightarrow V_2 = 0$

$$\therefore \boxed{I_0 = 0}$$

note: dropping kilo & milli during mathematical analysis. Do not forget them in final ans!

Q5:

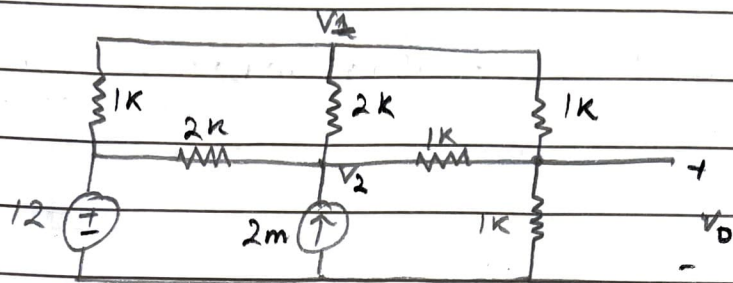

Applying KCL on node 1:-

$$\frac{V_1 - 12}{1} + \frac{V_1 - V_2}{2} + \frac{V_1 - V_0}{1} = 0$$

$$2V_1 + \frac{V_1}{2} - \frac{V_2}{2} - V_0 = 12$$

$$\frac{5}{2}V_1 - \frac{1}{2}V_2 - V_0 = 12 \quad \text{--- (1)}$$

Applying KCL on node 2:-

$$\frac{V_2 - 12}{2} + \frac{V_2 - V_1}{2} + \frac{V_2 - V_0}{1} = 2$$

$$-\frac{1}{2}V_1 + 2V_2 - V_0 = 8 \quad \text{--- (2)}$$

Applying KCL on node 0:-

$$\frac{V_0}{1} + \frac{V_0 - V_2}{1} + \frac{V_0 - V_1}{1} = 0$$

$$-V_1 - V_2 + 3V_0 = 0 \quad \text{--- (3)}$$

In Matrix form:- (from (1), (2), (3))

$$\begin{bmatrix} 5/2 & -1/2 & -1 \\ -1/2 & 2 & -1 \\ -1 & -1 & 3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_0 \end{bmatrix} = \begin{bmatrix} 12 \\ 8 \\ 0 \end{bmatrix}$$

A
X
B


* Remember, A matrix formed should always be symmetric i.e. $A = A^T$; in case of independent sources.

Solve for $\begin{bmatrix} v_1 \\ v_2 \\ v_o \end{bmatrix}$ using calculator or find inverse by reduce-echelon and then $\rightarrow X = A^{-1}B$.


$$\therefore \begin{bmatrix} v_1 \\ v_2 \\ v_o \end{bmatrix} = \begin{bmatrix} 64/7 \\ 328/35 \\ 216/35 \end{bmatrix}$$

$$\Rightarrow \boxed{V_o = \frac{216}{35} \approx 6.17 \text{ V}}$$

Q6:

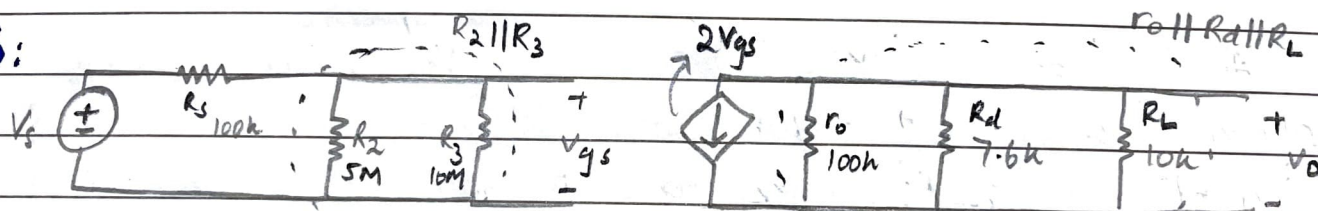

We can redraw the circuit as -

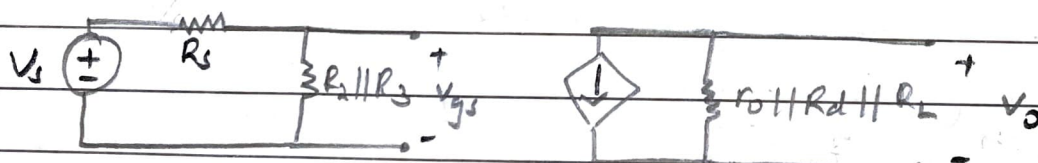

(a) $\frac{V_{gs}}{V_s}$

simple voltage divider

$$\Rightarrow V_{gs} = \frac{R_2 || R_3}{(R_2 || R_3) + R_s} V_s$$

$$\therefore \frac{V_{gs}}{V_s} = \frac{R_2 || R_3}{(R_2 || R_3) + R_s}$$

$$\frac{V_{gs}}{V_s} = \frac{3.33 \text{ M}}{3.33 \text{ M} + 100 \text{ k}} = 0.971$$

$$R_2 || R_3 = \frac{1}{\frac{1}{R_2} + \frac{1}{R_3}}$$

$$R_2 || R_3 = \frac{1}{0.2 + 0.1} = \frac{10 \text{ M}\Omega}{3} \approx 3.33 \text{ M}\Omega$$

$$r_o || R_d || R_L = \frac{1}{\frac{1}{r_o} + \frac{1}{R_d} + \frac{1}{R_L}}$$

$$= \frac{1}{0.01 + \frac{5}{38} + 0.1} \approx 4.139 \text{ k}\Omega$$

$$(b) \quad V_o$$

$$V_{gs}$$

$$V_o = (-2V_{gs})(r_o \parallel R_d \parallel R_L) \quad (\text{from } V = IR)$$

$$\Rightarrow \frac{V_o}{V_{gs}} = (-2)(r_o \parallel R_d \parallel R_L)$$

$$\therefore \frac{V_o}{V_{gs}} = -8.278$$

$$\frac{V_o}{V_s} = \frac{V_o}{V_{gs}} \times \frac{V_{gs}}{V_s}$$


$$\frac{V_o}{V_s} = -8.278 \times 0.971$$

$$\frac{V_o}{V_s} \approx -8.038$$

Note: As you can observe, if we apply V_s , it will appear ~ 8 times larger at output & inverted.

Thus, what we just solved was the gain of a simplified amplifier.

Q7:

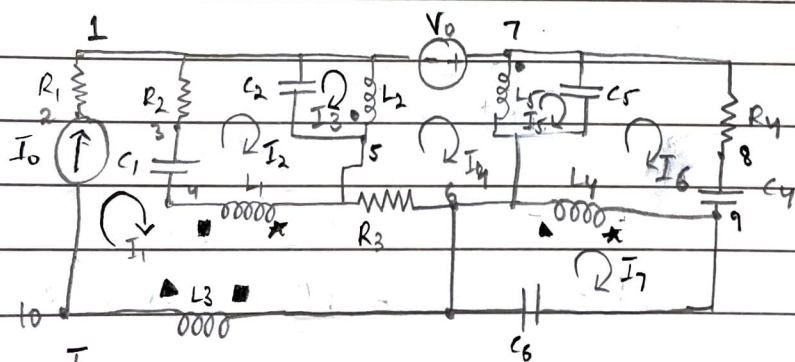

$$L_1 \text{ } C_1 \text{ } L_3 = M_a$$

$$L_1 \text{ } C_1 \text{ } L_4 = M_b$$

$$L_2 \text{ } C_1 \text{ } L_5 = M_c$$

$$L_3 \text{ } C_1 \text{ } L_4 = M_d$$

$$I_1 = I_o$$

Loop 1 :-

$$R_1 I_o + R_2 (I_o - I_2) + \frac{1}{C_1} \int (I_o - I_2) dt + L_1 \frac{d(I_o - I_2)}{dt}$$

$$+ R_3 (I_o - I_4) + L_3 \frac{dI_o}{dt} + M_a \frac{d(I_o - I_2)}{dt} + M_a \frac{dI_o}{dt} + M_b \frac{d(I_7 - I_6)}{dt}$$

$$- M_d \frac{d(I_7 - I_6)}{dt} = 0$$

Loop 2 :-

$$R_2 (I_2 - I_0) + \frac{1}{C_2} \int (I_2 - I_3) dt + L_1 \frac{d(I_2 - I_0)}{dt} + \frac{1}{C_1} \int (I_2 - I_0) dt$$

$$- M_a \frac{dI_0}{dt} - M_b \frac{d(I_7 - I_6)}{dt} = 0.$$

Loop 3 :-

$$\frac{1}{C_2} \int (I_3 - I_2) dt + L_2 \frac{d(I_3 - I_4)}{dt} + M_c \frac{d(I_5 - I_4)}{dt} = 0.$$

Loop 4 :-

$$L_5 \frac{d(I_4 - I_5)}{dt} + R_3 (I_4 - I_1) + L_2 \frac{d(I_4 - I_3)}{dt} = V_0$$
$$+ M_c \frac{d(I_4 - I_2)}{dt} - M_c \frac{d(I_5 - I_4)}{dt}$$

Loop 5 :-

$$\frac{1}{C_5} \int (I_5 - I_6) dt + L_5 \frac{d(I_5 - I_4)}{dt} - M_c \frac{d(I_4 - I_3)}{dt} = 0.$$

Loop 6 :-

$$R_4 I_6 + \frac{1}{C_4} \int I_6 dt + L_4 \frac{d(I_6 - I_7)}{dt} + \frac{1}{C_5} \int (I_6 - I_5) dt + M_d \frac{dI_0}{dt}$$
$$- M_b \frac{d(I_0 - I_2)}{dt} = 0.$$

Loop 7 :-

$$L_4 \frac{d(I_7 - I_6)}{dt} + \frac{1}{C_6} \int I_7 dt - M_d \frac{dI_0}{dt} + M_b \frac{d(I_0 - I_2)}{dt} = 0.$$

Q8:

(a) No. of nodes = 10 = n (labelled as #s in prev. Q's diag)

(b) No. of nodal equations required $= n - 1$
 $= 9$


(c) No. of branches $b = 16$ (simply count the no. of elements).

(d) & (e)

Any graph having 10 nodes and proper interconnection in accordance with the original circuit would suffice.

Similarly, construct any tree from the graph obtained.

Q9:

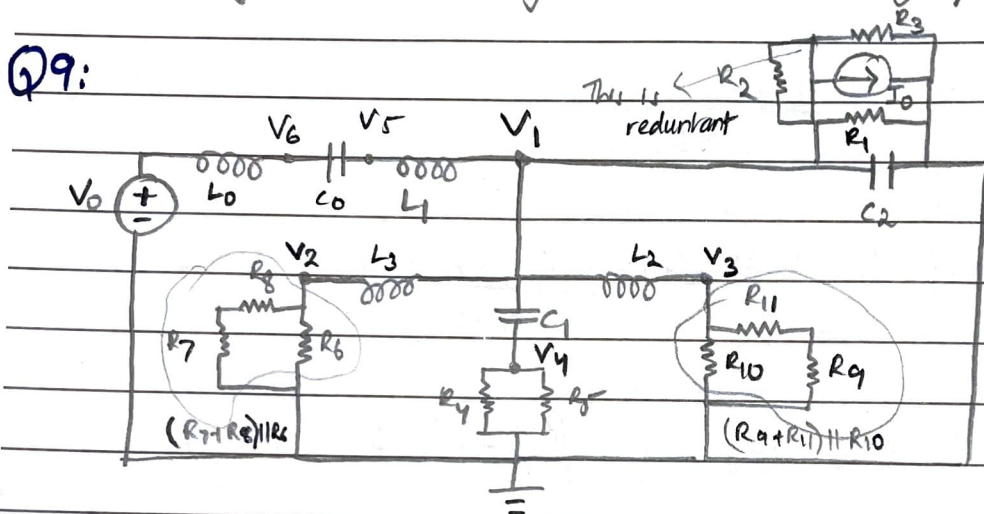

Node 1 :-

$$\frac{1}{L_1} \int (V_1 - V_5) dt + \frac{1}{L_2} \int (V_1 - V_3) dt + \frac{1}{L_3} \int (V_1 - V_2) dt + C_1 \frac{d(V_1 - V_4)}{dt} + C_2 \frac{dV_1}{dt} + \frac{V_1}{R_1} + \frac{V_1}{R_3} = -I_0$$

Node 2:-

$$\frac{V_2}{(R_7 + R_8) \parallel R_6} + \frac{1}{L_3} \int (V_2 - V_1) dt = 0$$

Node 3 :-

$$\frac{V_3}{(R_9 + R_{11}) \parallel R_{10}} + \frac{1}{L_2} \int (V_3 - V_1) dt = 0$$

Node 4 :-

$$\frac{V_4}{(R_4 || R_5)} + C_1 \frac{d(V_4 - V_1)}{dt} = 0$$

Node 5 :-

$$\frac{1}{L_1} \int (V_5 - V_1) dt + C_0 \frac{d(V_5 - V_6)}{dt} = 0.$$

Node 6 :-

$$\frac{1}{L_0} \int (V_6 - V_0) dt + C_0 \frac{d(V_6 - V_5)}{dt} = 0.$$