

EE240 – Circuits I
Final Examination (Fall 2021)

December 21, 2021

8:00 am–10:30 am

Student ID

Name

Signature

INSTRUCTIONS:


- Do not flip this page over until told to do so.
- Reading time: 10 minutes
- Writing time: 2 hours and 20 minutes
- The exam consists of 6 problems worth a total of 75 points.
- **The exam needs to be solved on this book and not on blue book.**
- You may use back-side of each paper to show your working.
- The exam is closed book and notes. You are allowed to bring calculator and two A4 sheets with *hand-written* notes on both sides.

Problem	Total Points	Obtained Points
Problem 1	10	
Problem 2	15	
Problem 3	10	
Problem 4	10	
Problem 5	15	
Problem 6	15	
Total	75	


Problem 1. (10 pts) Provide brief justification or working for each of the questions in this problem.

- (1) (1 pts) For an RL circuit with $R = 2\Omega$ and $L = 0.5H$, determine the time constant of the circuit.
- (2) (1 pts) In an RC circuit with $R = 2\Omega$ and $C = 4\text{ F}$, a capacitor is being charged. How much time does v_c (capacitor voltage) take to reach 63.2 percent of its steady state value?

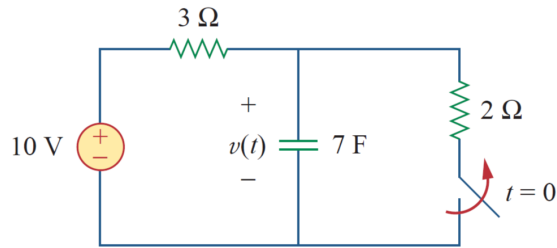- (3) (2 pts) In the circuit given below, the switch is opened at $t = 0$. Determine $v(t)$ at $t = 0^+$ and $t = \infty$.



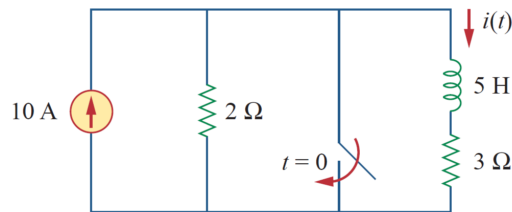
- (4) (2 pts) In the circuit given below, the switch is closed at $t = 0$. Determine $i(t)$ at $t = 0^+$ and $t = \infty$.



- (5) (1 pts) If the roots of the characteristic equation are -1 and -3 , the response is
- $K_1 e^{-t} + K_2 e^{-3t}$
 - $e^{-t}(K_1 \cos(3t) + K_2 \sin(3t))$
 - $K_1 e^{-t} + K_2 t e^{-3t}$
 - $K_1 t e^{-t} + K_2 t e^{-3t}$
- (6) (1 pts) In a series RLC circuit with $R = 0$, the response is
- overdamped
 - undamped
 - underdamped
 - critically damped
- (7) (3 pts) Consider a series RLC circuit driven by voltage source $V_o \sin(\omega t)$. Draw a circuit and formulate a second order differential equation in terms of voltage across capacitor (denoted by $v_c(t)$).

Part 1: First Order Circuits

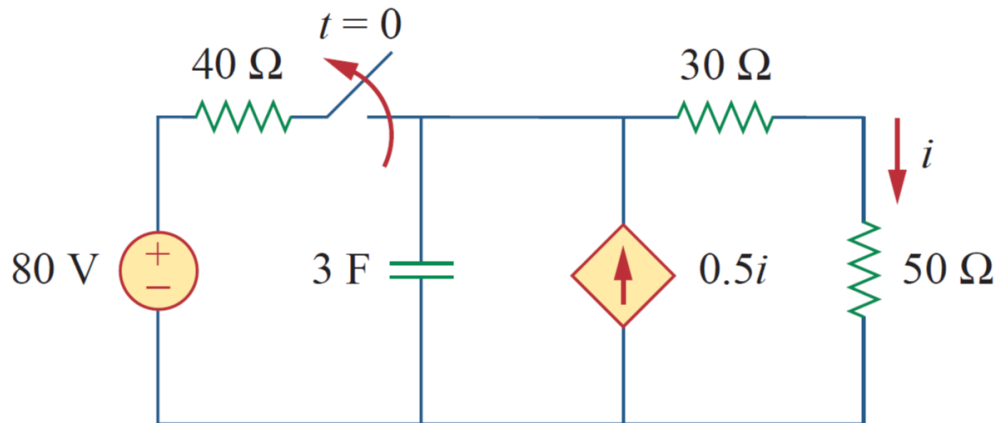Problem 2. (15 pts) The circuit given below is in steady state with switch closed. The switch is opened at $t = 0$.




- (a) (4 pts) Determine the current $i(t)$ at $t = 0^-$, that is, just before the switch is operated. Also determine the current through the inductor.
- (b) (2 pts) Determine the current $i(t)$ at $t = 0^+$, that is, just after the switch is operated.
- (c) (1 pts) Determine the current $i(t)$ at $t = \infty$.

(d) (**6 pts**) Using the results of the previous parts, or otherwise, determine the current $i(t)$ for all times $t > 0$.

(e) (**2 pts**) Plot the current $i(t)$ for $-\tau \leq t \leq 6\tau$ (where τ denotes the time constant of the circuit).

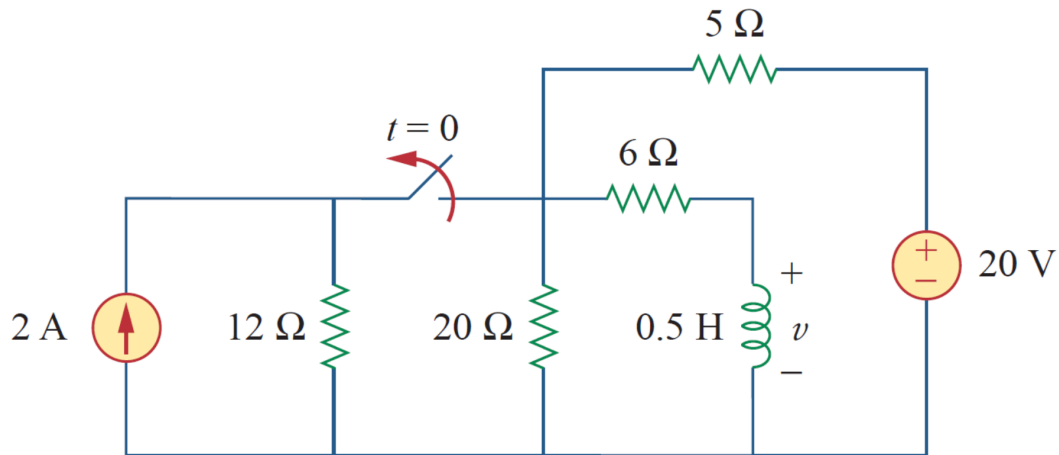Problem 3. (10 pts) The circuit given below is in steady state with **switch in closed state**. The switch is opened at $t = 0$.




(a) (3 pts) Determine the current through inductor at $t = 0^-$.

(b) (4 pts) Determine the the voltage $v(t)$ at $t = 0^+$.

(c) (3 pts) Determine the voltage $v(t)$ for all times.

Part 2: Evaluation of Initial Conditions


Problem 4. (10 pts) In the circuit given below, assume that the switch SW1 is initially open and is closed at $t = 0$. If $i_1(0^+) = 1 \text{ A}$ and $\frac{d^2 i_2}{dt^2}(0^+) = 40 \text{ A/s}^2$, find values of resistance R_1 and inductance L .

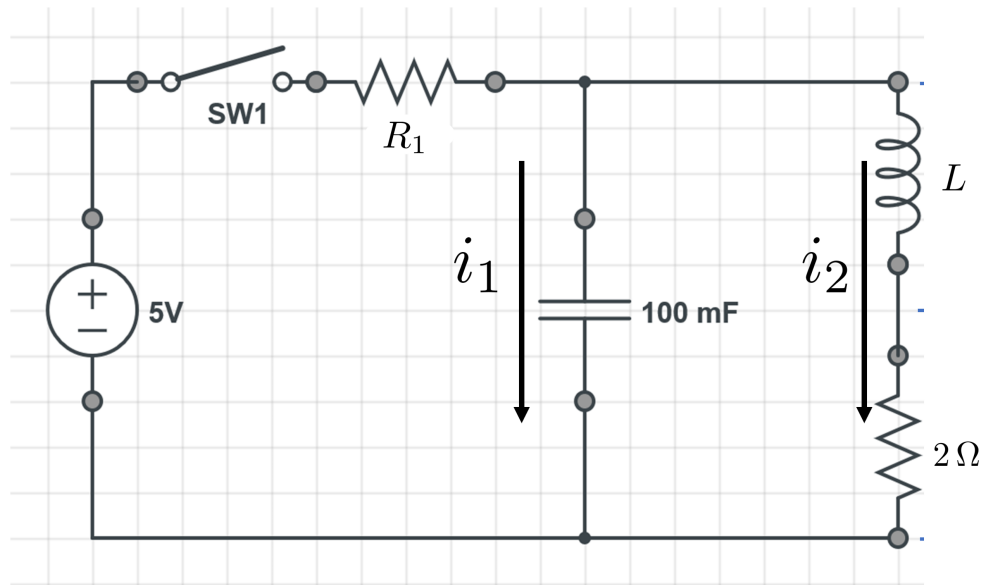

Part 3: Second-Order Circuits

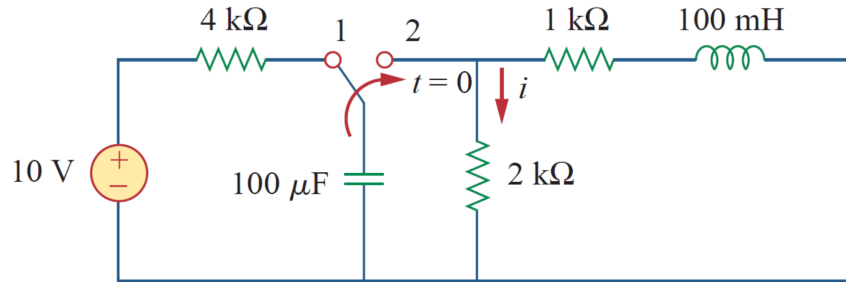Problem 5. (15 pts)

Consider the circuit shown below. The circuit is in steady state with switch at position 1. At $t = 0$, the switch is moved from position 1 to position 2.



- (a) (1 pts) Draw the snapshot of the circuit at $t = 0^+$.

- (b) (1 pts) Determine $i(t)$ at $t = 0^+$.


- (c) (3 pts) Formulate a second-order differential equation in terms of i describing circuit for $t \geq 0$.

- (d) (2 pts) Determine the damping ratio ζ and undamped natural frequency ω_n for the circuit after the switch is operated.

- (e) (2 pts) Determine $\frac{di}{dt}$ at $t = 0^+$.

- (f) (6 pts) Determine $i(t)$ for all times $t \geq 0$.

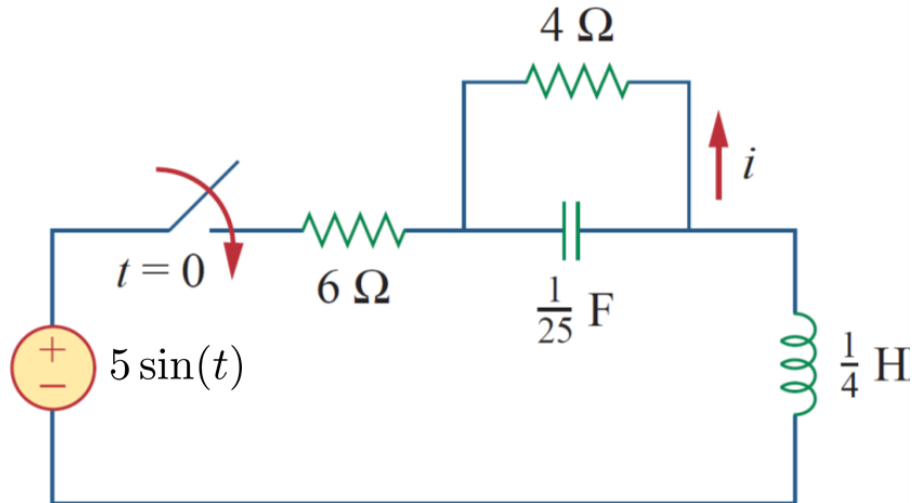Problem 6. (15 pts) In the circuit given below, assume that the switch is initially in open state and is closed at $t = 0$.



- (a) (1 pts) Draw the snapshot of the circuit at $t = 0^+$.
- (b) (5 pts) Formulate a second-order differential equation in $i(t)$ describing circuit for $t \geq 0$.
- (c) (9 pts) Determine $i(t)$ for all times $t \geq 0$.