## EE240 – Circuits I

## Mid Examination (Fall 2021)

## November 13, 2021

12:30 pm–02:45 pm

### **INSTRUCTIONS:**

- Reading time: 15 minutes
- Writing time: 2 hours
- We require you to solve the exam in a single time-slot of two hours without any external or electronic assistance.
- We encourage you to solve the exam on A4 paper, use new sheet for each question and write sheet number on every sheet.
- Clearly outline all your steps in order to obtain any partial credit.
- The exam is closed book and notes. You are allowed to have one A4 sheet with you with hand-written notes on both sides. Calculators can be used.
- If you are ready, please proceed to the next page.

#### Mapping between exam parts and course learning outcomes (CLOs)

- Part 1: R, L, C Basics, Sources and I-V Characteristics (CLO1)
- Part 2: Network Topology, Network Equations and Kirchhoff's Laws (CLO2)
- Part 3: Additional Analysis Techniques (CLO3)

## Part 1: R, L, C Basics, Sources and I-V Characteristics

**Problem 1.** (10 pts) The current  $i_c(t)$  through the capacitor of capacitance 1F is shown in Figure 1 below.



(a) (1 pts) Express  $i_c(t)$  as piecewise function of time.

(b) (7 pts) Assuming that the current is zero for times  $t \leq -1$  seconds, determine the voltage across the capacitor and plot for  $-2 \leq t \leq 7$  seconds.

(c) (2 pts) Determine the energy stored in the capacitor at t = 3 seconds.

- **Problem 2.** (8 pts) Consider a circuit where the DC current source of 2A is connected to a parallel combination of 2  $\Omega$  resistor and 0.5H inductor through the switch. Assume that the switch is initially closed and is opened at t = 0.
  - (a) (2 pts) Draw the circuit and indicate the voltage v(t) across the resistor and the current  $i_R(t)$  and  $i_L(t)$  through the resistor and the inductor respectively.

(b) (6 pts) Plot the waveforms (not to the scale but label the axes and indicate intercepts) of the currents  $i_R(t)$  and  $i_L(t)$ .

Problem 3. (4 pts) Calculate the power supplied by each element in the circuit given below.



**Problem 4.** (4 pts) For a network of resistors, calculate the equivalent resistance  $R_eq$  across terminals a and b.



## Part 2: Network Topology, Network Equations and Kirchhoff's Laws

Problem 5. (18 pts) Consider the circuit given below.



(a) (4 pts) Draw the graph and one tree of the circuit. Determine the number of nodes and number of branches in the circuit (or graph).

(b) (2 pts) Determine the number of network equations required for carrying out i) nodal analysis and ii) loop analysis.

(c) (9 pts) Carry out the nodal analysis, that is, identify and determine the nodal voltages.

(d) (3 pts) Determine the power delivered by the 10 V voltage source.

**Problem 6.** (06 pts) Formulate the network equations in terms of loop currents indicated in the circuit given below.



# Part 3: Additional Analysis Techniques

**Problem 7.** (06 pts) Use source transformation to find  $v_o$  in the circuit given below.



Problem 8. (06 pts) Obtain a dual circuit for the circuit given below.



Problem 9. (10 pts) Consider a circuit given below.



- (a) (4 pts) Determine the value of  $R_L$  for maximum power transfer to  $R_L$  using Thevenin's Theorem.
- (b) (4 pts) Obtain Thevenin equivalent of the circuit across terminals a and b.
- (c) (2 pts) Determine the power absorbed by  $R_L$



