

EE240 – Circuits I

Mid Examination (Fall 2021)

November 13, 2021

12:30 pm–02:45 pm

INSTRUCTIONS:


- Reading time: 15 minutes
- Writing time: 2 hours
- We require you to solve the exam in a single time-slot of two hours without any external or electronic assistance.
- We encourage you to solve the exam on A4 paper, use new sheet for each question and write sheet number on every sheet.
- Clearly outline all your steps in order to obtain any partial credit.
- The exam is closed book and notes. You are allowed to have one A4 sheet with you with hand-written notes on both sides. Calculators can be used.
- If you are ready, please proceed to the next page.

Mapping between exam parts and course learning outcomes (CLOs)

- Part 1: R, L, C Basics, Sources and I-V Characteristics (CLO1)
- Part 2: Network Topology, Network Equations and Kirchhoff's Laws (CLO2)
- Part 3: Additional Analysis Techniques (CLO3)

Part 1: R, L, C Basics, Sources and I-V Characteristics

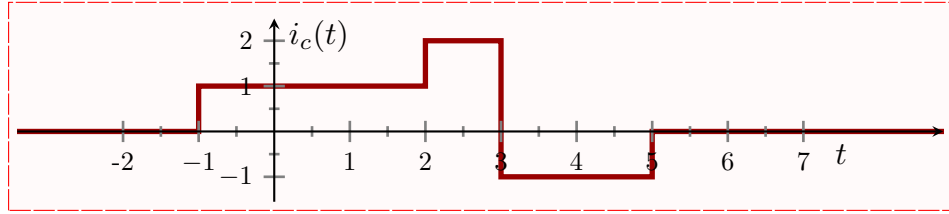Problem 1. (10 pts) The current $i_c(t)$ through the capacitor of capacitance $1F$ is shown in Figure 1 below.



(a) (1 pts) Express $i_c(t)$ as piecewise function of time.


$$i_c(t) = \begin{cases} 0 & t < -1 \\ 1 & -1 \leq t < 2 \\ 2 & 2 \leq t < 3 \\ -1 & 3 \leq t < 5 \\ 0 & t \geq 5 \end{cases}$$

(b) (7 pts) Assuming that the current is zero for times $t \leq -1$ seconds, determine the voltage across the capacitor and **plot** for $-2 \leq t \leq 7$ seconds.

Let $v_c(t)$ be the voltage across capacitor.

$$v_c(t) = \frac{1}{C} \int_{-\infty}^t i_c(t) dt$$
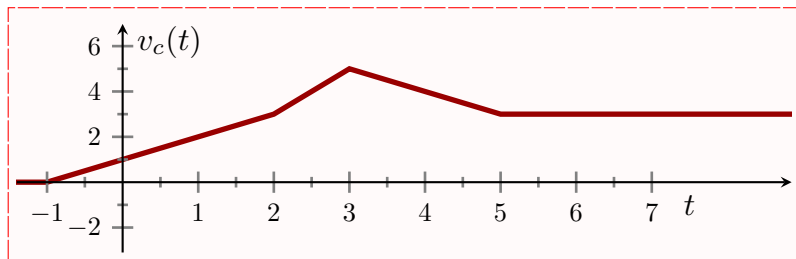
$$v_c(t) = \begin{cases} 0 & t < -1 \\ t + 1 & -1 \leq t < 2 \\ 2t - 1 & 2 \leq t < 3 \\ -t + 8 & 3 \leq t < 5 \\ 3 & t \geq 5 \end{cases}$$




(c) (2 pts) Determine the energy stored in the capacitor at $t = 3$ seconds.


$$w_c(t) = \frac{1}{2} C (v_c(t))^2 \Rightarrow w_c(3) = \frac{1}{2} (v_c(3))^2 = 12.5 \text{ J.}$$

Problem 2. (8 pts) Consider a circuit where the DC current source of $2A$ is connected to a parallel combination of 2Ω resistor and $0.5H$ inductor through the switch. **Assume that the switch is initially closed and is opened at $t = 0$.**

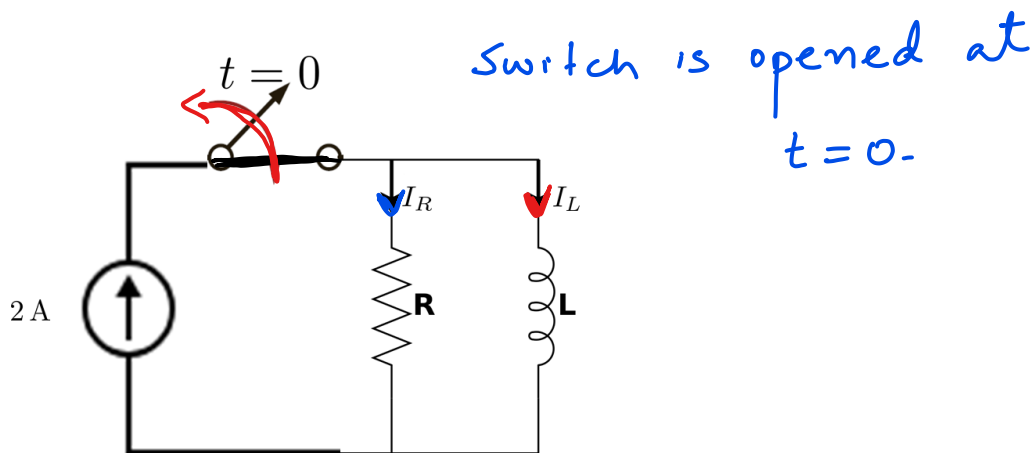- (a) (2 pts) Draw the circuit and indicate the voltage $v(t)$ across the resistor and the current $i_R(t)$ and $i_L(t)$ through the resistor and the inductor respectively.




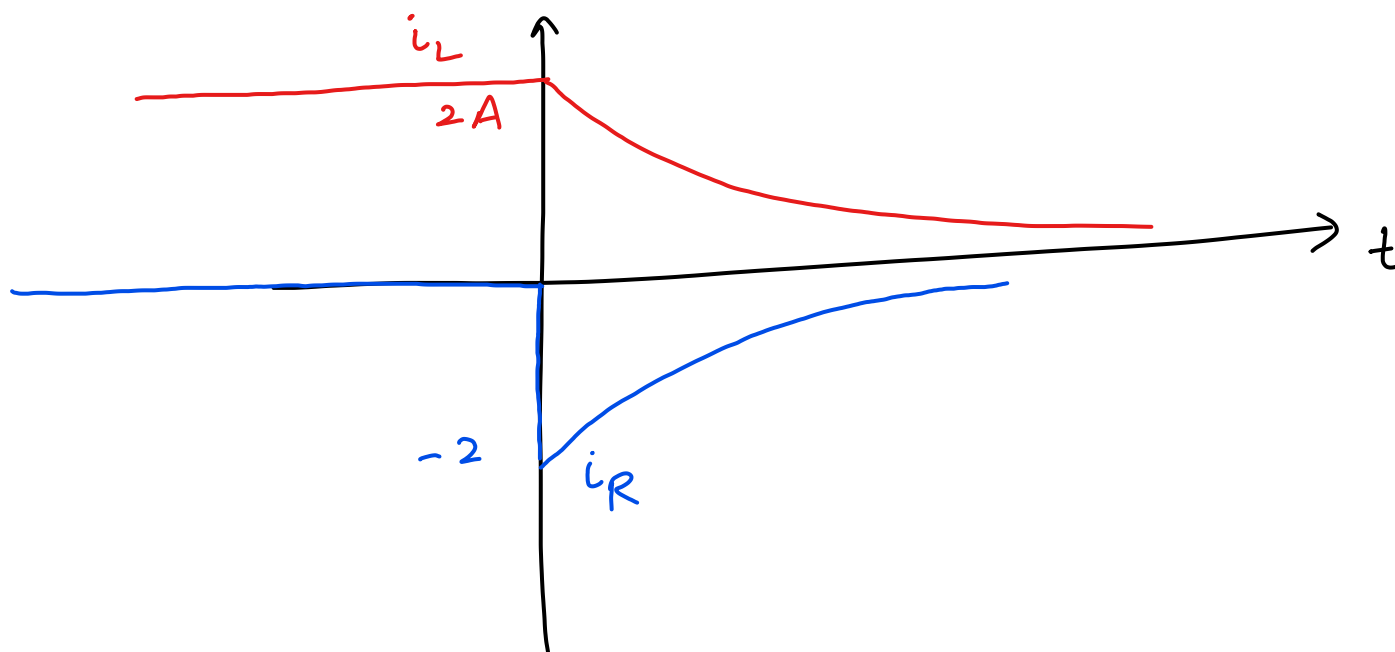- (b) (6 pts) Plot the waveforms (not to the scale but label the axes and indicate intercepts) of the currents $i_R(t)$ and $i_L(t)$.



$$\begin{aligned}
 i_R &= 0 & t < 0 \\
 i_R &= -i_L & t \geq 0
 \end{aligned}$$

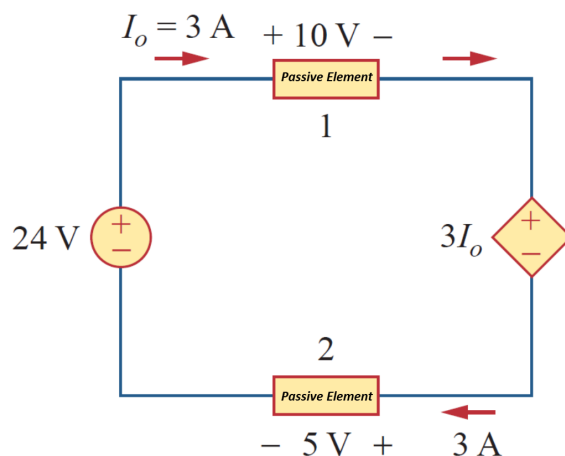Problem 3. (4 pts) Calculate the power **supplied** by each element in the circuit given below.



Solutions:


Power supplied by 24V voltage source: $24 \times 3 = 72 \text{ W}$

Power supplied by Passive element 1: $-10 \times 3 = -30 \text{ W}$

Power supplied by controlled voltage source: $-3I_o \times I_o = -27 \text{ W}$

Power supplied by Passive element 2: $-5 \times 3 = -15 \text{ W}$

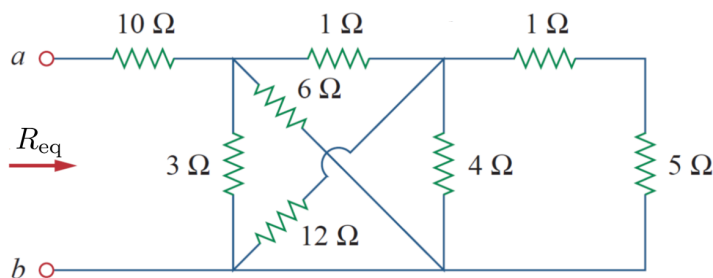Problem 4. (4 pts) For a network of resistors, calculate the equivalent resistance R_{eq} across terminals a and b .




Solutions:

$$((5 + 1) \parallel 4 \parallel 12 + 1) \parallel 6 \parallel 3 + 10 = 3 \parallel 6 \parallel 3 + 10 = \frac{6}{5} + 10 = \frac{56}{5} = 11.2 \Omega$$


Part 2: Network Topology, Network Equations and Kirchhoff's Laws

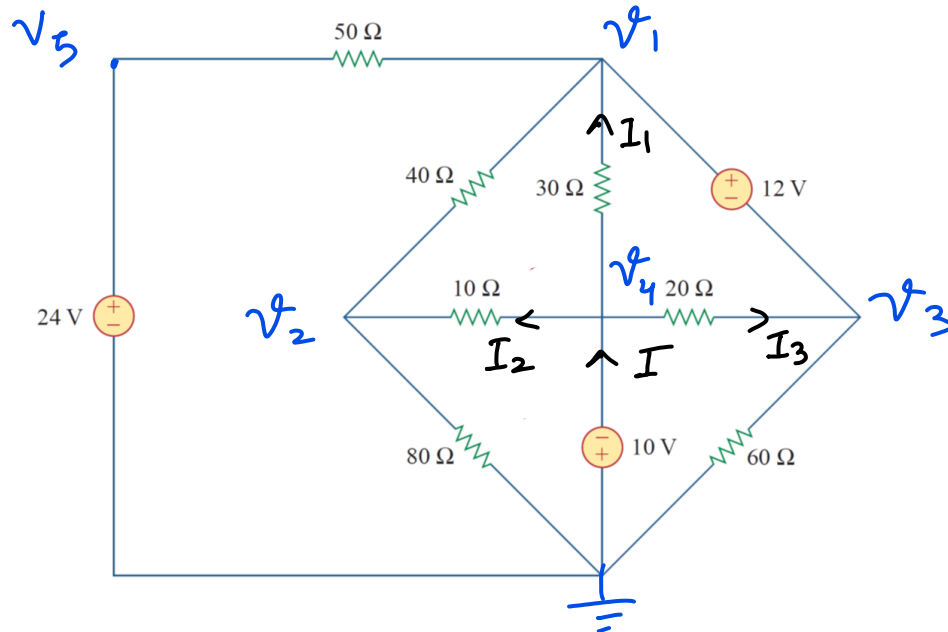Problem 5. (18 pts) Consider the circuit given below.



- (a) (4 pts) Draw the graph and one tree of the circuit. Determine the number of nodes and number of branches in the circuit (or graph).

Solutions:

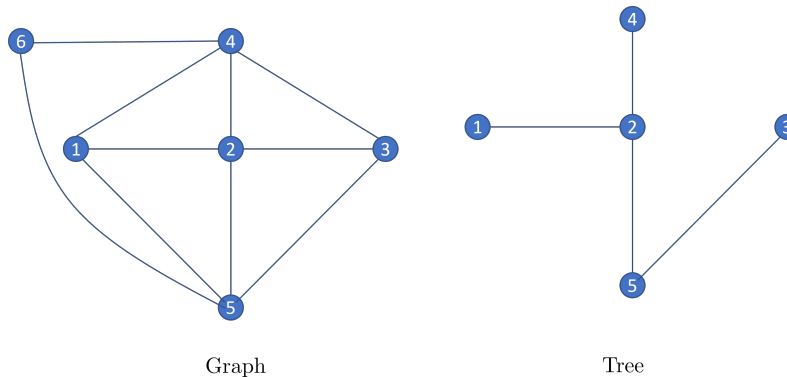

Number of branches = $b = 10$

Number of nodes = $n = 6$

- (b) (2 pts) Determine the number of network equations required for carrying out i) nodal analysis and ii) loop analysis.

Solutions:

For loop analysis, we need $n - 1 = 5$ equations. For nodal analysis, we need $b - n + 1 = 5$ equations.

- (c) (9 pts) Carry out the nodal analysis, that is, identify and determine the nodal voltages.

Node voltages indicated on circuit

$$v_4 = -10V, \quad v_5 = 24V$$

* Equation for node 2: $11V_2 - 2V_1 = -80$

* Equation for (node 1 and node 3) supernode:

$$47V_1 - 15V_2 + 40V_3 = -212$$

* Super node equation: $V_1 - V_3 = 12$

Solving for V_1 , V_2 and V_3 :

$$V_1 = 6.9169V$$

$$V_2 = -6.0151V$$

$$V_3 = -5.0831V$$

- (d) (3 pts) Determine the power delivered by the 10 V voltage source.


* In order to find power, we determine the current I (indicated on the circuit)

$$I = I_1 + I_2 + I_3 = \frac{-10 - V_1}{30} + \frac{-10 - V_2}{10} + \frac{-10 - V_3}{20}$$

* Since I is leaving -ve terminal

$$\text{Power delivered} = (10)(-I)$$

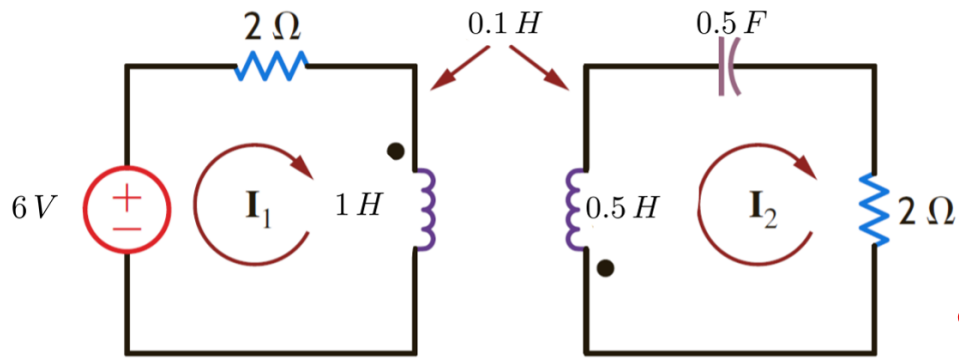Problem 6. (06 pts) Formulate the network equations in terms of loop currents indicated in the circuit given below.




coupling terms

$$* \quad 2I_1 + L \frac{dI_1}{dt} + \underbrace{0.1 \frac{dI_2}{dt}} = 6$$


$$* \quad 2 \int I_2 dt + 2I_2 + \frac{1}{2} \frac{dI_2}{dt} + \underbrace{0.1 \frac{dI_1}{dt}} = 0$$

Part 3: Additional Analysis Techniques

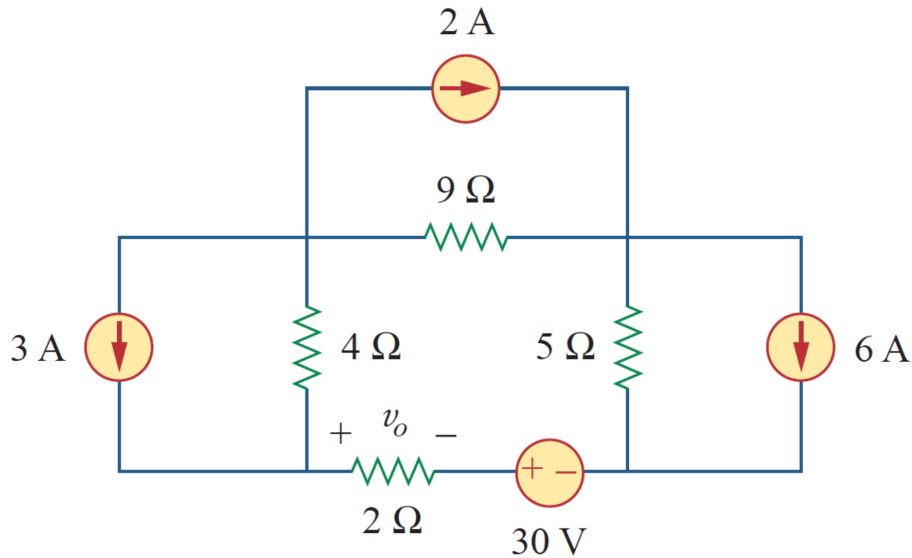Problem 7. (06 pts) Use source transformation to find v_o in the circuit given below.





Source transformation yields

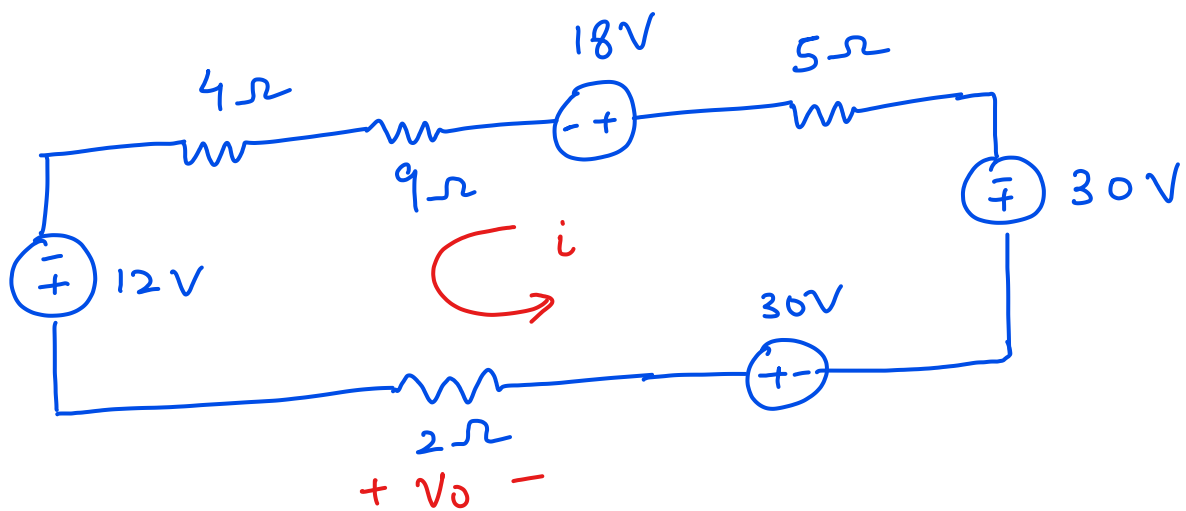


$$20i + 18 + 30 + 30 - 12 = 0 \Rightarrow i = -\frac{66}{20} = -3.3 \text{ A}$$

$$v_o = (-3.3)(2) = \boxed{-6.6 \text{ V}}$$

Problem 8. (06 pts) Obtain a dual circuit for the circuit given below.

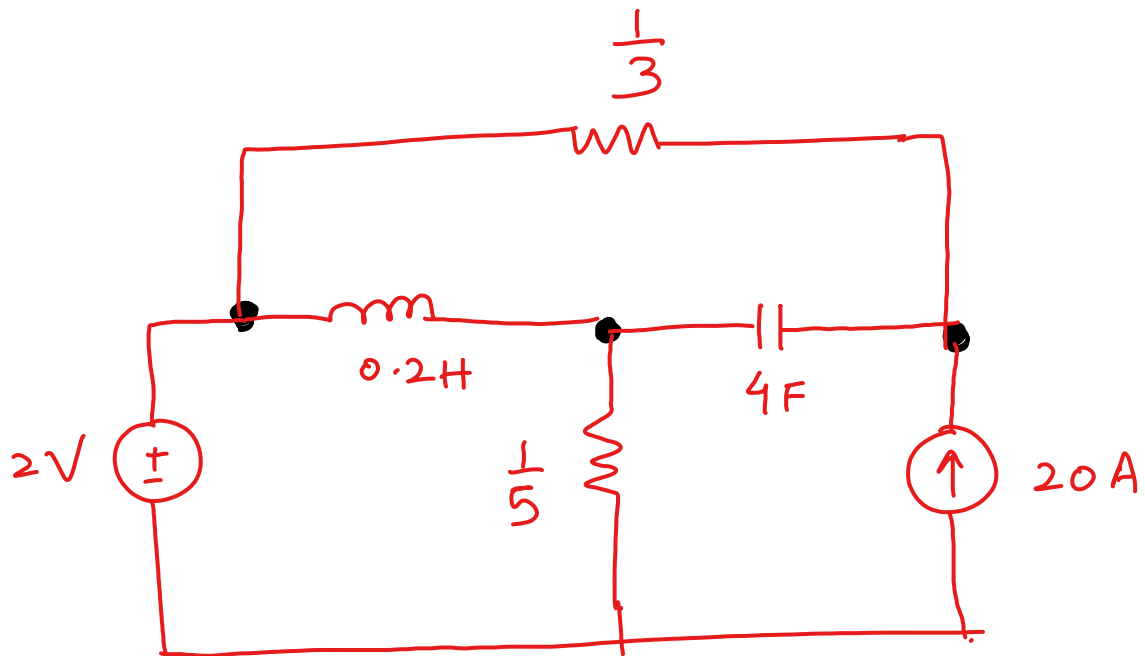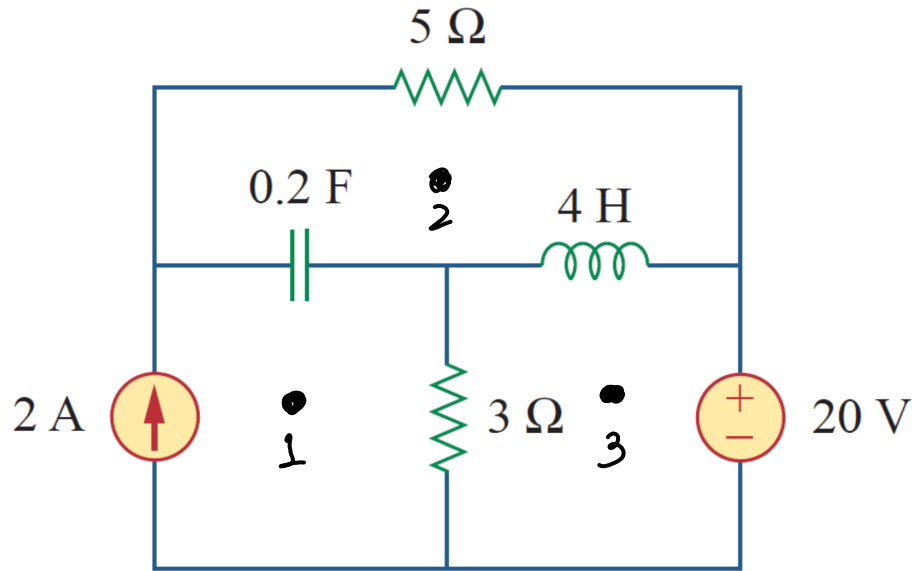


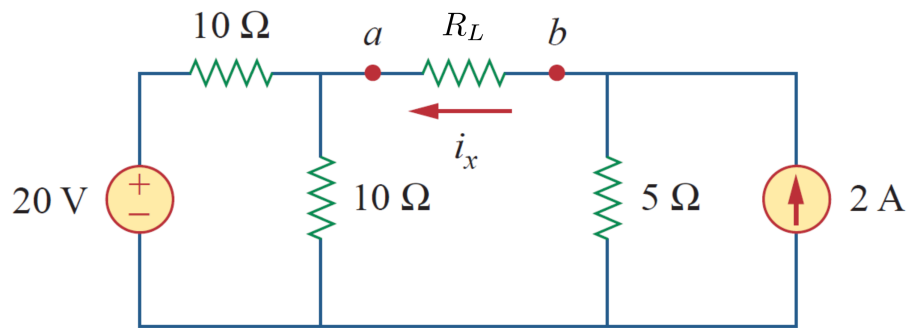Problem 9. (10 pts) Consider a circuit given below.




- (4 pts) Determine the value of R_L for maximum power transfer to R_L using Thevenin's Theorem.
- (4 pts) Obtain Thevenin equivalent of the circuit across terminals a and b .
- (2 pts) Determine the power absorbed by R_L

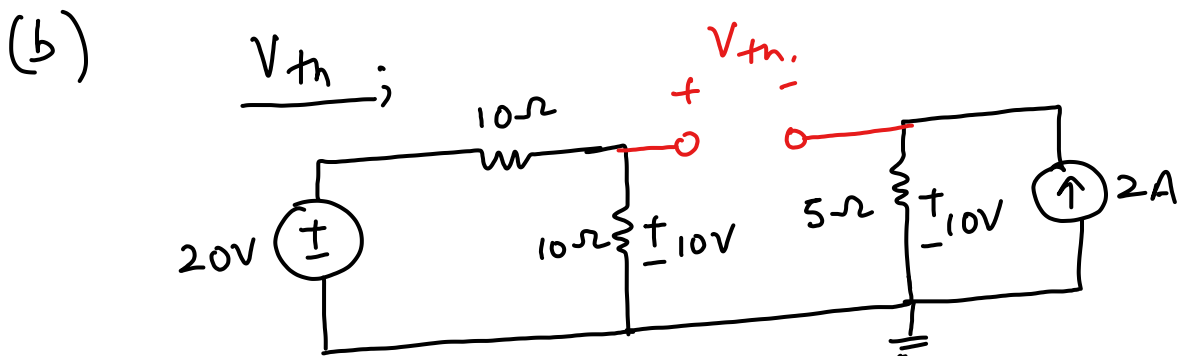(a) $R_{th} = 10 \parallel 10 + 5 = 10\Omega, \quad R_L = R_{th}$




$V_{th} = 0$

Thevenin Equivalent Circuit:

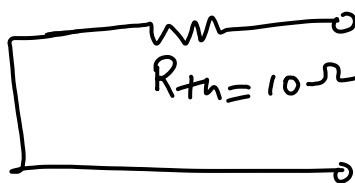

(c) $P = 0$ since $V_{th} = 0$.

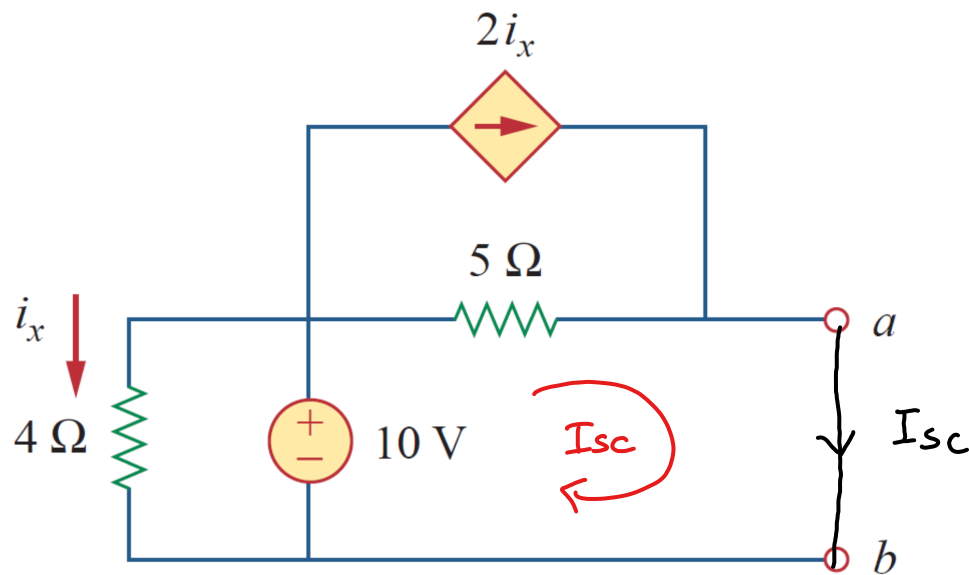Problem 10. (08 pts) Find the Norton equivalent circuit of the circuit given below



I_{sc} :

$$\ast i_x = \frac{10}{4} = 2.5 \text{ A}$$

$$5 (I_{sc} - 2i_x) - 10 = 0$$

$$I_{sc} = \frac{10 + 10i_x}{5} = \frac{35}{5} = 7 \text{ A}$$

V_{oc} :- (V_{th}) \ast open circuit voltage across a and b
 $i_x = 2.5 \text{ A}$

$$V_{oc} = (5)(2i_x) + 10 = 35 \text{ V}$$

$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{35}{7} = \boxed{5 \Omega}$$

Norton Equivalent:

