



EE 240 Circuits I

Dr. Zubair Khalid

Department of Electrical Engineering
School of Science and Engineering
Lahore University of Management Sciences

https://www.zubairkhalid.org/ee240_2021.html

- Duality

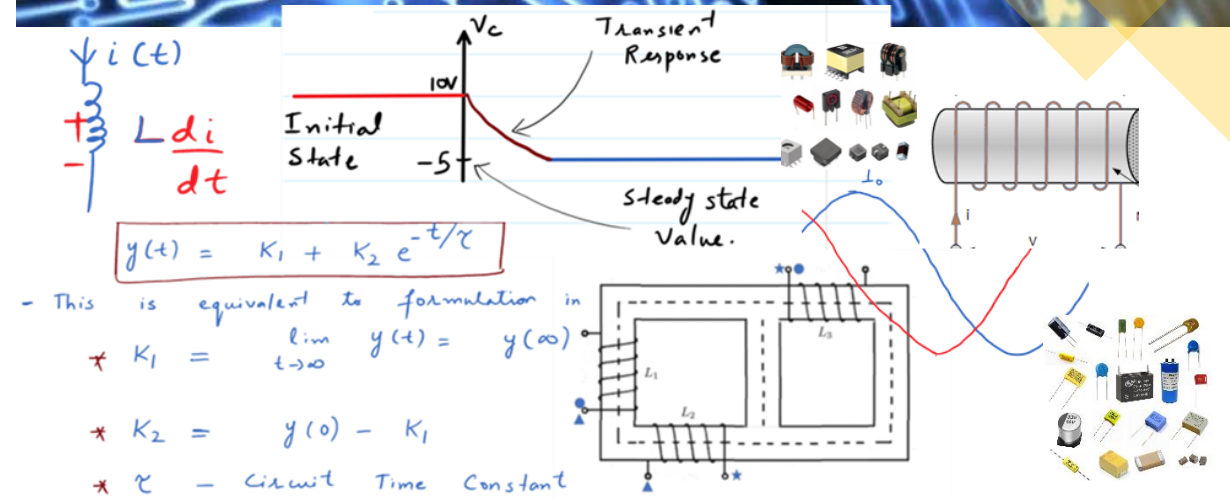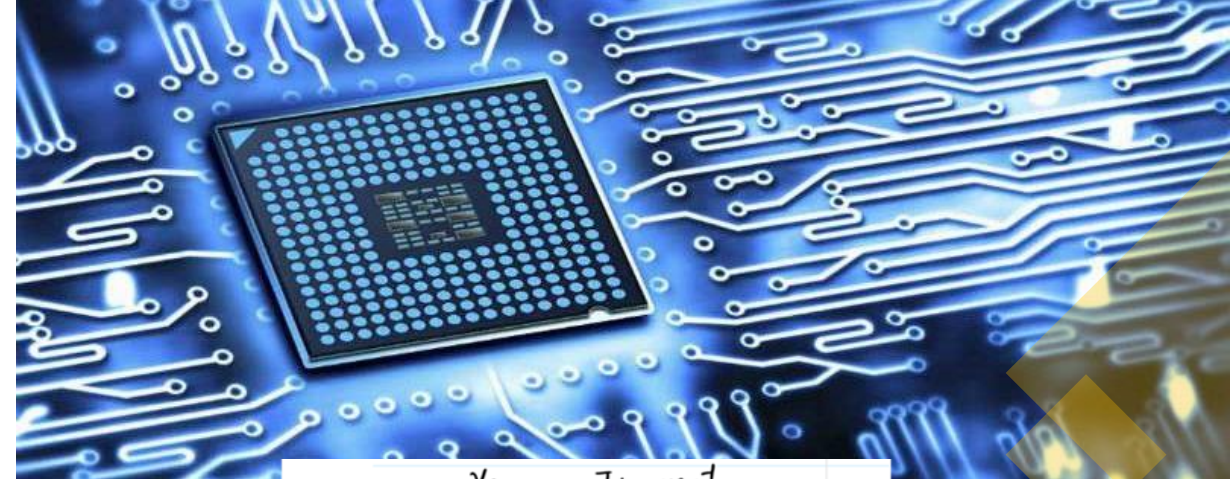

Duality in Circuits

Overview


The concept is that the **voltage** or **current** in a circuit behaves in **analogous** manner as the **current** or **voltage** in a dual circuit.

- Ohm's law is a simple example, that is, we have $v = iR$. This is equivalent to $i = v(1/R)$. If we current and voltage are swapped in the first equation and R is replaced with $(1/R)$, we obtain a second equation. We refer to this as 1) voltage and current are dual of each other and 2) $(1/R)$ is a dual of (R) .
- Similarly KCL and KVL are analogous.
- This similarity is part of large pattern of identical behaviour patterns between voltage and current in the network.
- Let's analyse series RLC and parallel RLC networks.


Duality in Circuits

Example:

Parallel RLC Circuit

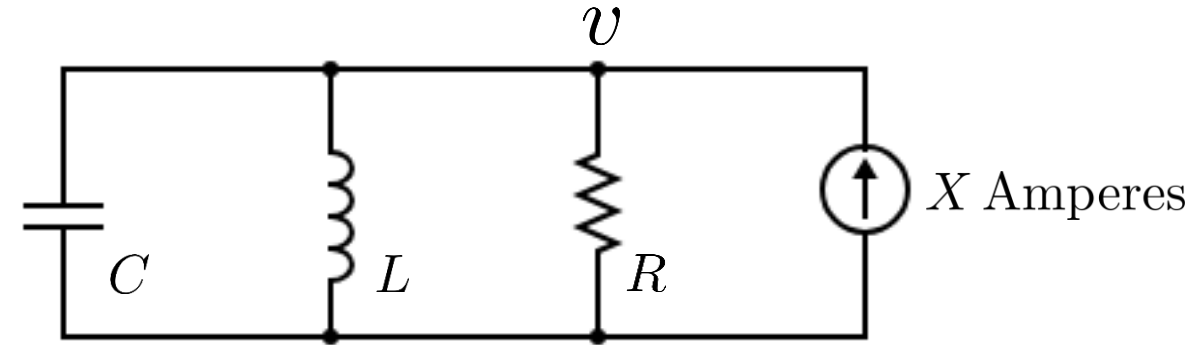

Series RLC Circuit

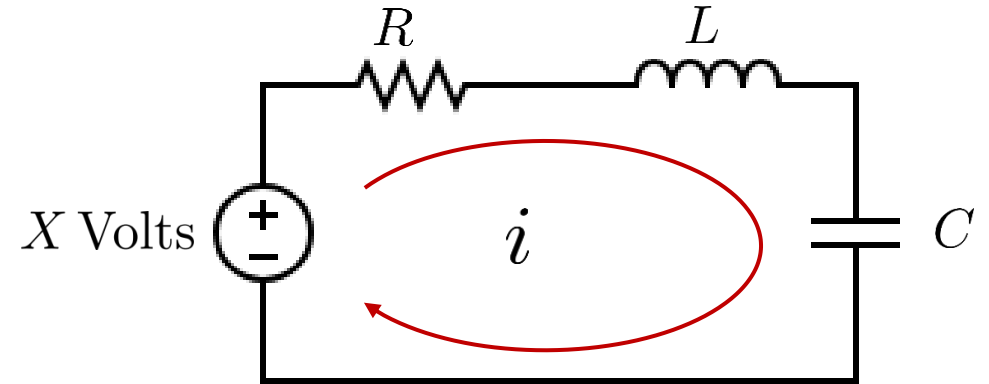

Apply KCL:

$$\frac{v}{R} + C \frac{dv}{dt} + \frac{1}{L} \int v dt - X = 0 \quad (1)$$

Apply KVL:

$$iR + L \frac{di}{dt} + \frac{1}{C} \int i dt - X = 0 \quad (2)$$

- Note the similarity between the resulting integro-differential equation.
- If we know the solution of one circuit, it can be utilized to readily obtain the solution of the other circuit.
- The solution of (1) yields $v(t)$ in terms of R, L, C and X .
- The solution of (2) yields $i(t)$ in terms of R, L, C and X .
- If we replace $v(t)$ with $i(t)$, C with L , L with C , R with $(1/R)$ in equation (1), we obtain equation (2).
- Noting this, we can make these substitutions in the solution $v(t)$ to determine the solution $i(t)$.

Duality in Circuits

Dual Quantities or Elements:

$$v \longleftrightarrow i$$

$$\text{Open circuit} \longleftrightarrow \text{Short circuit}$$

$$R \longleftrightarrow \frac{1}{R}$$

$$\text{Node pair} \longleftrightarrow \text{Loop}$$

$$L \longleftrightarrow C$$

$$\text{Voltage source and element in series} \longleftrightarrow \text{Current source and element in parallel} \quad (\text{Source Transformation})$$

$$\int v dt \longleftrightarrow \int i dt$$

$$\text{KVL} \longleftrightarrow \text{KCL}$$

- The two circuits are dual of each other if they have the same network equations with dual quantities replaced. For a given circuit, we can determine the dual circuit. Let's learn the graphical construction of the dual circuit.

Graphical Construction of a Dual Circuit

Step 01:




- In a given circuit, place a node inside each loop and place and add an additional node (a datum node) outside the circuit.
- On a separate space, arrange the same numbered nodes on a separate sheet.

Step 02:

- Draw lines from node to node through elements in the original network only traversing one element at one time.
- For each element traversed from one node to the other in the original network, connect the dual element from the list between a pair of nodes in the dual network.
- Continue this process until the number of possible paths through single element is exhausted.

Graphical Construction of a Dual Circuit



Example:

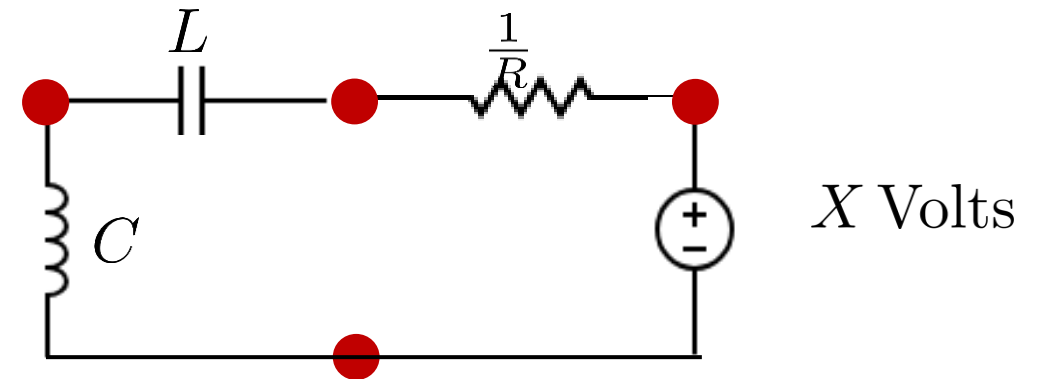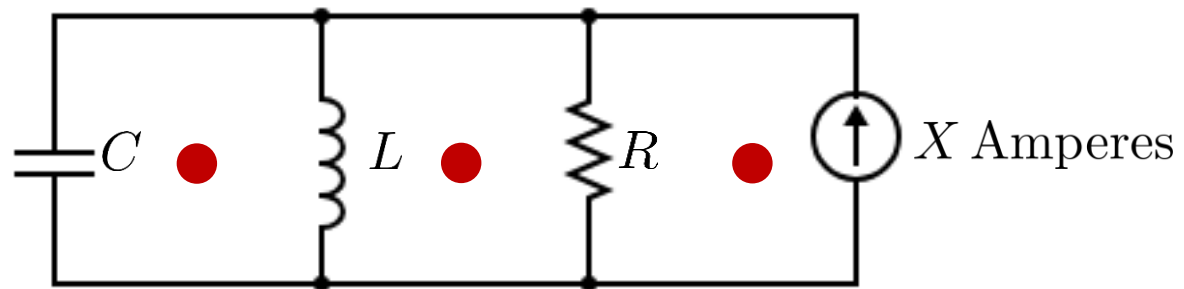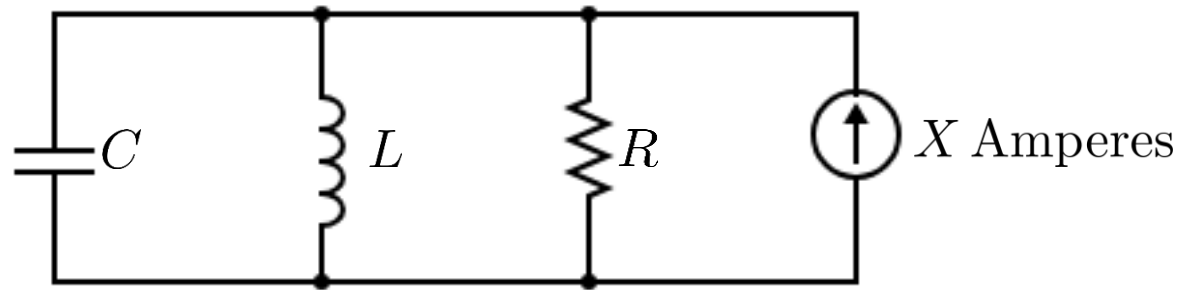

Dual Circuit

Graphical Construction of a Dual Circuit

Example:

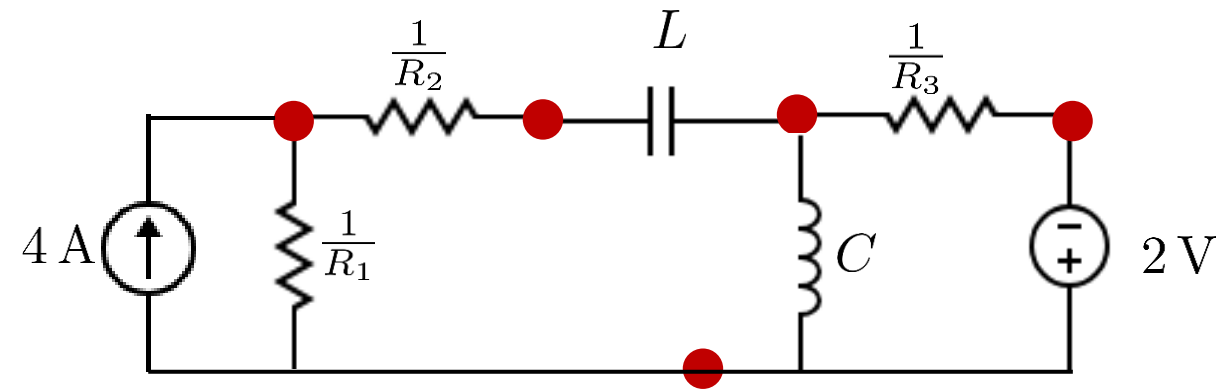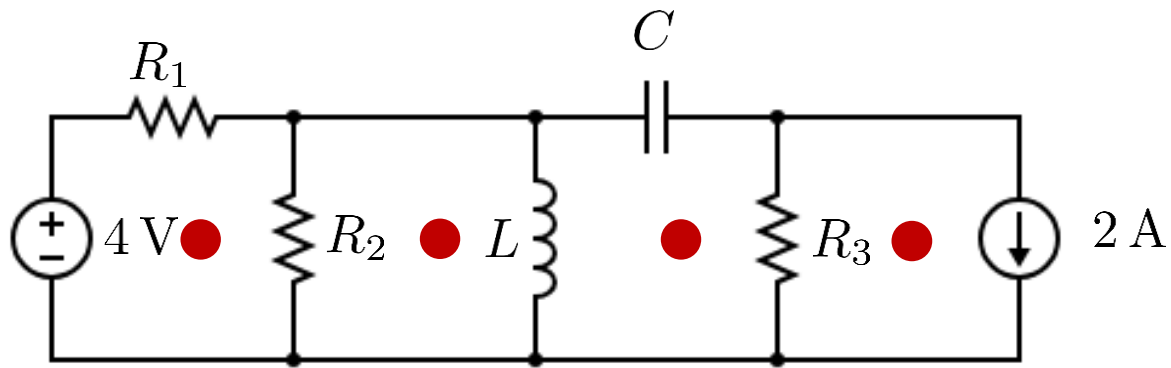

Dual Circuit