

# EE240 HW1-Solution

Problem 1:

(a):

Circuit fig.(a):  $V = -20 \text{ V}$ ,  $I = -4 \text{ A}$ .

Circuit fig.(b):  $V = -20 \text{ V}$ ,  $I = 4 \text{ A}$ .

Circuit fig.(c):  $V = 20 \text{ V}$ ,  $I = -4 \text{ A}$ .

Circuit fig.(d):  $V = 20 \text{ V}$ ,  $I = 4 \text{ A}$ .

Compare each figure and the statement given to identify the correct polarities of voltage and current.

(b):

Absorbing because the terminal 2 is at higher potential and the current enters the same terminal as described by the statement.

(c):

$$P = V \cdot I = 80 \text{ W}.$$

Problem 2:

(a):

$$0 \text{ s} \leq t < 1 \text{ s:}$$

$$v = 5 \text{ V}; \quad i = 20t \text{ A}; \quad p = 100t \text{ W}$$

$$1 \text{ s} < t \leq 3 \text{ s:}$$

$$v = 0 \text{ V}; \quad i = 20 \text{ A}; \quad p = 0 \text{ W}$$

$$3 \text{ s} \leq t < 5 \text{ s:}$$


$$v = -5 \text{ V}; \quad i = 80 - 20t \text{ A}; \quad p = 100t - 400 \text{ W}$$

$$5 \text{ s} < t \leq 7 \text{ s:}$$

$$v = 5 \text{ V}; \quad i = 20t - 120 \text{ A}; \quad p = 100t - 600 \text{ W}$$

$$t > 7 \text{ s:}$$
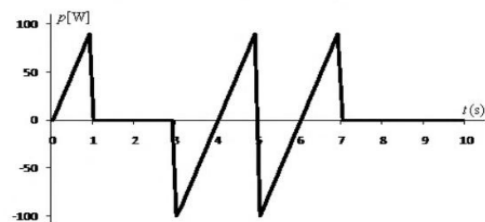
$$v = 0 \text{ V}; \quad i = 20 \text{ A}; \quad p = 0 \text{ W}$$



(b):

Calculate the area under the curve from zero up to the desired time:

$$w(1) = \frac{1}{2}(1)(100) = 50 \text{ J}$$

$$w(6) = \frac{1}{2}(1)(100) - \frac{1}{2}(1)(100) + \frac{1}{2}(1)(100) - \frac{1}{2}(1)(100) = 0 \text{ J}$$

$$w(10) = w(6) + \frac{1}{2}(1)(100) = 50 \text{ J}$$

Problem 3:

(a):

(i):

$$\frac{1}{2} * C * V^2 = 46$$

Putting  $V = 200$ ,

$$C = 2.3mF$$

(ii):

$$C = \frac{\epsilon A}{d}$$

Making A the subject,

$$A = \frac{[(2.3 * 10^{-3}) * (1 * 10^{-2})]}{\epsilon}$$

(iii):

Lets call the new capacitance due to quartering the distance as,

$$C_{\frac{d}{4}} = \frac{\epsilon A}{0.25 * 10^{-2}}$$

Using area from previous part,

$$C_{\frac{d}{4}} = 9.2 * 10^{-3} F = 9.2mF$$

i.e. the capacitance is quadrupled.

Lets call the capacitance due to half the area as,

$$C_{A/2} = 1.15mF$$

i.e. the capacitance is halved.

(iv):

For quarter the distance:

$$q_{discharged} = (C_{\frac{d}{4}} * V) - (C * V)$$

$$q_{discharged} = (9.2 * 10^{-3} * 200) - (2.3 * 10^{-3} * 200) = 1.380 C$$

$$i_{discharged} = \frac{1.380}{t}$$

For half the area:


$$q_{discharged} = (C * V) - (C_{\frac{A}{2}} * V)$$

$$q_{discharged} = (2.3 * 10^{-3} * 200) - (1.15 * 10^{-3} * 200) = 0.230 C$$

$$i_{\text{discharged}} = \frac{0.230}{t}$$

(b):

$$C_T = 4 * 10^{-6} F$$

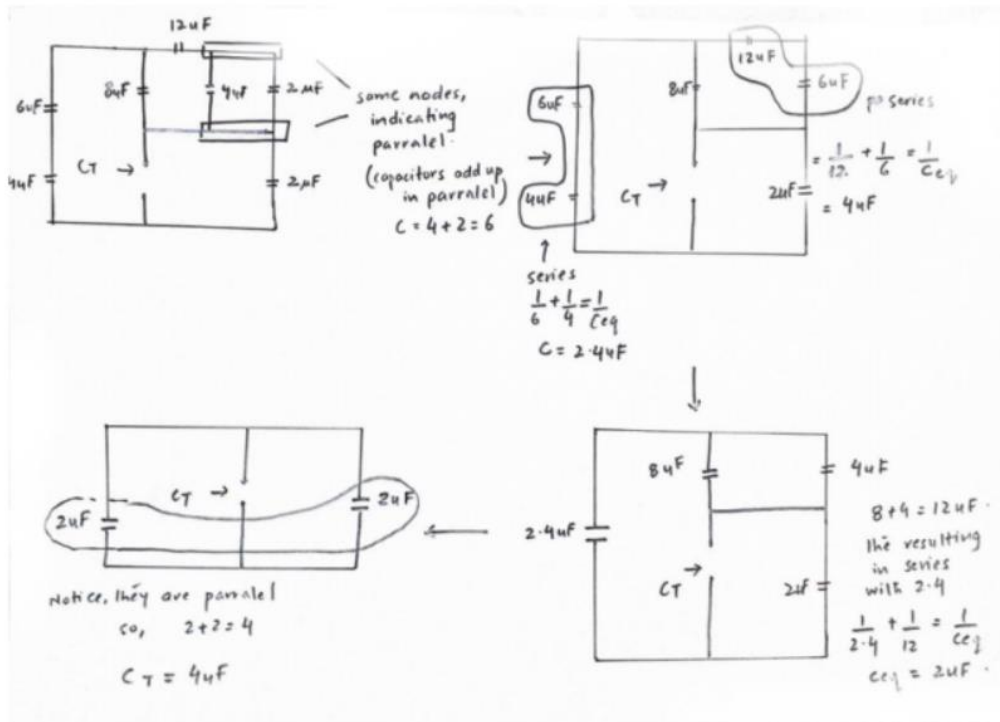

Problem 4:

(a):

$$60 \parallel 20 = 1200/80 = 15 \Omega \quad 12 \parallel 24 = 288/36 = 8 \Omega$$

$$15 + 8 + 7 = 30 \Omega \quad 30 \parallel 120 = 3600/150 = 24 \Omega$$

$$R_{ab} = 15 + 24 + 25 = 64 \Omega$$

(b):

$$35 + 40 = 75 \Omega \quad 75 \parallel 50 = 3750/125 = 30 \Omega$$

$$30 + 20 = 50 \Omega \quad 50 \parallel 75 = 3750/125 = 30 \Omega$$

$$30 + 10 = 40 \Omega \quad 40 \parallel 60 + 9 \parallel 18 = 24 + 6 = 30 \Omega$$

$$30 \parallel 30 = 15 \Omega \quad R_{ab} = 10 + 15 + 5 = 30 \Omega$$

(c):

$$50 + 30 = 80 \Omega \quad 80 \parallel 20 = 16 \Omega$$

$$16 + 14 = 30 \Omega \quad 30 + 24 = 54 \Omega$$

$$54 \parallel 27 = 18 \Omega \quad 18 + 12 = 30 \Omega$$

$$30 \parallel 30 = 15 \Omega \quad R_{ab} = 3 + 15 + 2 = 20 \Omega$$

Problem 5:

(a):

Since  $v = L di/dt$  and  $L = 0.1$  H,

$$v = 0.1 \frac{d}{dt}(10te^{-5t}) = e^{-5t} + t(-5)e^{-5t} = e^{-5t}(1 - 5t) \text{ V}$$

The energy stored is

$$w = \frac{1}{2}Li^2 = \frac{1}{2}(0.1)100t^2e^{-10t} = 5t^2e^{-10t} \text{ J}$$

(b):

The power  $p = vi = 60t^5$ , and the energy stored is then

$$w = \int p dt = \int_0^5 60t^5 dt = 60 \frac{t^6}{6} \Big|_0^5 = 156.25 \text{ kJ}$$

Alternatively, we can obtain the energy stored using Eq. (6.13), by writing

$$w \Big|_0^5 = \frac{1}{2}Li^2(5) - \frac{1}{2}Li^2(0) = \frac{1}{2}(5)(2 \times 5^3)^2 - 0 = 156.25 \text{ kJ}$$

as obtained before.

Since  $i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$  and  $L = 5$  H,

$$i = \frac{1}{5} \int_0^t 30t^2 dt + 0 = 6 \times \frac{t^3}{3} = 2t^3 \text{ A}$$

(c):

The 10-H, 12-H, and 20-H inductors are in series; thus, combining them gives a 42-H inductance. This 42-H inductor is in parallel with the 7-H inductor so that they are combined, to give

$$\frac{7 \times 42}{7 + 42} = 6 \text{ H}$$

This 6-H inductor is in series with the 4-H and 8-H inductors. Hence,

$$L_{\text{eq}} = 4 + 6 + 8 = 18 \text{ H}$$

(d):

$$\begin{aligned} w &= L \int_{-\infty}^t i dt = \frac{1}{2}Li^2(t) - \frac{1}{2}Li^2(-\infty) \\ &= \frac{1}{2} \times 80 \times 10^{-3} \times (60 \times 10^{-3})^2 - 0 \\ &= \underline{\underline{144 \mu\text{J}}} \end{aligned}$$

(e):

$$v = L \frac{di}{dt} = 12 \times 10^{-3} \times 4(100) \cos 100t$$

$$= \underline{4.8 \cos 100t \text{ V}}$$

$$p = vi = 4.8 \times 4 \sin 100t \cos 100t = 9.6 \sin 200t$$

$$w = \int_0^t p dt = \int_0^{11/200} 9.6 \sin 200t$$

$$= -\frac{9.6}{200} \cos 200t \Big|_0^{11/200} \text{ J}$$

$$= -48(\cos \pi - 1) \text{ mJ} = \underline{96 \text{ mJ}}$$

Problem 6:

Recall that current is related to charge by  $i(t) = \frac{dq(t)}{dt}$ . The current is equal to the slope of the charge waveform.

$i(t) = 0$	$0 \leq t \leq 1 \text{ ms}$
$i(t) = \frac{3 \times 10^{-3} - 1 \times 10^{-3}}{2 \times 10^{-3} - 1 \times 10^{-3}} = 2 \text{ A}$	$1 \leq t \leq 2 \text{ ms}$
$i(t) = 0$	$2 \leq t \leq 3 \text{ ms}$
$i(t) = \frac{-2 \times 10^{-3} - 3 \times 10^{-3}}{5 \times 10^{-3} - 3 \times 10^{-3}} = -2.5 \text{ A}$	$3 \leq t \leq 5 \text{ ms}$
$i(t) = 0$	$5 \leq t \leq 6 \text{ ms}$
$i(t) = \frac{2 \times 10^{-3} - (-2 \times 10^{-3})}{9 \times 10^{-3} - 6 \times 10^{-3}} = 1.33 \text{ A}$	$6 \leq t \leq 9 \text{ ms}$
$i(t) = 0$	$t \geq 9 \text{ ms}$


The current is plotted with the charge waveform in Fig. 1.21. Note that the current is zero during times when the charge is a constant value. When the charge is increasing, the current is positive, and when the charge is decreasing, the current is negative.

The power absorbed by the BOX is  $12 \times i(t)$ .

$p(t) = 12(0) = 0$	$0 \leq t \leq 1 \text{ ms}$
$p(t) = 12(2) = 24 \text{ W}$	$1 \leq t \leq 2 \text{ ms}$
$p(t) = 12(0) = 0$	$2 \leq t \leq 3 \text{ ms}$
$p(t) = 12(-2.5) = -30 \text{ W}$	$3 \leq t \leq 5 \text{ ms}$
$p(t) = 12(0) = 0$	$5 \leq t \leq 6 \text{ ms}$
$p(t) = 12(1.33) = 16 \text{ W}$	$6 \leq t \leq 9 \text{ ms}$
$p(t) = 12(0) = 0$	$t \geq 9 \text{ ms}$

The power absorbed by the BOX is plotted in Fig. 1.22. For the time intervals,  $1 \leq t \leq 2$  ms and  $6 \leq t \leq 9$  ms, the BOX is absorbing power. During the time interval  $3 \leq t \leq 5$  ms, the power absorbed by the BOX is negative, which indicates that the BOX is supplying power to the 12-V source.

(a):

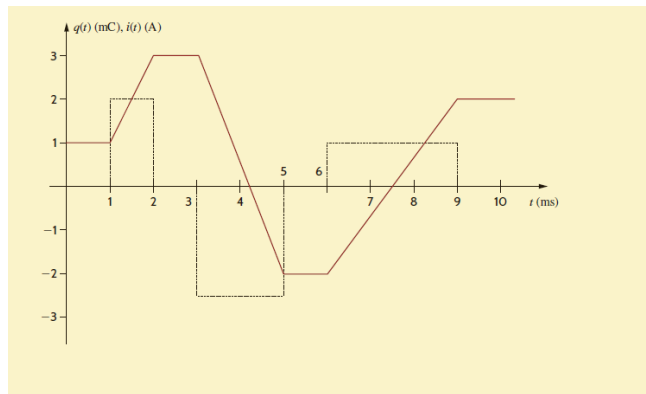

(b):

