

**LAHORE UNIVERSITY OF MANAGEMENT SCIENCES**  
**Department of Electrical Engineering**

**EE 240 Circuits I**  
**Quiz 6 Solution**

**Name:** \_\_\_\_\_

**Campus ID:** \_\_\_\_\_

**Total Marks:** 10

**Time Duration:** 15 minutes

**Question 1** (10 marks)

Study the figures below with ideal voltage and current sources. Given that an initially uncharged capacitor is connected to the configuration in figure a) at  $t = 0$  s.

- (a) [5 marks] Given that the capacitor is charged by a current source from  $t = 0$  s to  $t = 4$  s and  $v(4^-) = 80$  V, find the value of capacitance  $C_1$ .

$$i_1(t) = 2 \text{ A}$$

$$v(t) = \frac{1}{C_1} \int_{-\infty}^t i_c(\tau) d\tau$$


$$v(4^-) = \frac{1}{C_1} \int_0^4 2 d\tau$$

$$80 = 8 \times \frac{1}{C_1}$$


$$C_1 = 0.1 \text{ F}$$

- (b) [5 marks] The switch is now moved to the configuration in figure b) at  $t = 4$  s. Find a piecewise function for and sketch the current  $i_1(t)$  and  $i_2(t)$  for  $t \in (-\infty, \infty)$ .

$$i_1(t) = \begin{cases} 0 & t < 0 \\ 2 & 0 \leq t < 4 \\ 0 & 4 \leq t \end{cases}$$

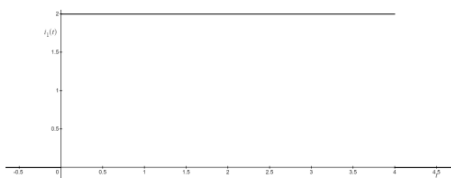

**Figure 1:** Waveform for  $i_1(t)$

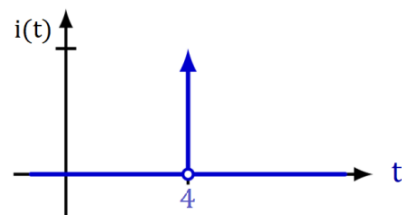

**Figure 2:** Waveform for  $i_2(t)$