

**LAHORE UNIVERSITY OF MANAGEMENT SCIENCES**  
**Department of Electrical Engineering**

**EE 240 Circuits I**  
**Quiz 7**

**Name:** \_\_\_\_\_


**Campus ID:** \_\_\_\_\_

**Total Marks:** 10

**Time Duration:** 15 minutes

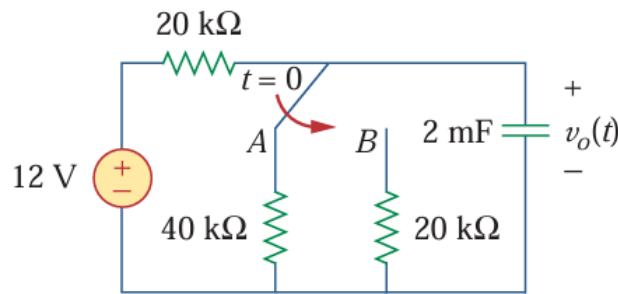**Question 1** (10 marks)

Assuming that the switch in the circuit given below has been in position A for a long time and is moved to position B at  $t = 0$ . Find  $v_o(t)$  at  $t \geq 0$



**Solution:**

When the switch has been at position A for a long time, the circuit reaches steady state. The voltage across the capacitor should be the same as the voltage across the  $40k\Omega$  resistor which is:

$$v_o(0^-) = \frac{40}{40+20}(12\text{ V}) = 8\text{ V}$$

$$v_o(0^-) = v_o(0^+) = 8\text{ V}$$

When the switch has been at position B for a long time, the circuit reaches steady state again. Now, the voltage across the capacitor should be the same as the voltage across the  $20k\Omega$  resistor in parallel with the capacitor which is:

$$v_o(\infty) = \frac{20}{20+20}(12\text{ V}) = 6\text{ V}$$

To find an expression for  $v_o(t)$  we need  $k_1$ ,  $k_2$  and  $\tau$  which we can find in the following way:

$$k_1 = v_o(\infty) = 6\text{ V}$$

$$k_2 = v_o(0^+) - v_o(\infty) = 8 - 6 = 2\text{ V}$$

Find  $R_{eq}$  across the capacitor terminals by shorting the voltage source. You will be left with the two  $20k\Omega$  resistors in parallel.

$$R_{eq} = 20||20 = 10k\Omega$$

$$\tau = R_{eq}C = 10k * 2m = 20s$$

Putting it all together:

$$v_o(t) = k_1 + k_2 e^{-t/\tau}$$

$$v_o(t) = 6 + 2e^{-t/20}\text{V}$$